
## UNIVERSITY OF UTAH ELECTRICAL & COMPUTER ENGINEERING DEPARTMENT


## ECE 1270


## HOMEWORK #5

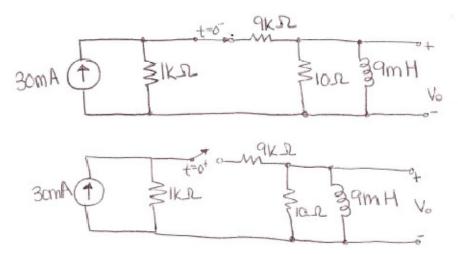- 1. After being closed(top circuit) for a long time, the switch is opened(bottom circuit) at t=0.
  - (a) Find an expression for  $V_0(t)$  for  $(t \ge 0)$ .
  - (b) Find the energy stored in the inductor at time  $t = 0^+$ .



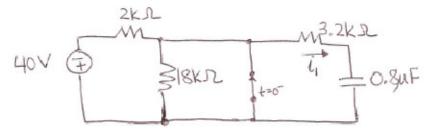
- 2. After being closed(top circuit) for a long time, the switch is opened(bottom circuit) at t=0.
  - (a) Find an expression for  $i_1(t)$  for  $(t \ge 0)$ .
  - (b) Find the energy stored in the capacitor at time  $t = 0^+$ .



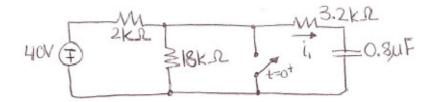


Use the circuits below for problems 3 and 4. After being in position 1 (top circuit) for a long time, the switch is moved to position 2(bottom circuit) at t=0.

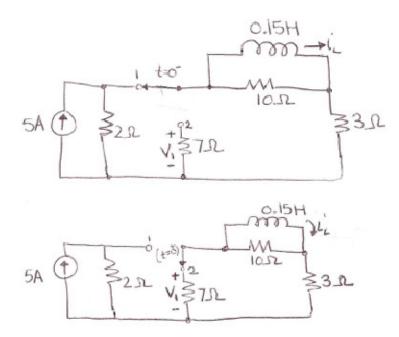- 3. (a) Find an expression for  $i_L(t)$  for  $(t \ge 0)$ .
  - (b) Make a sketch of the expression for  $i_L(t)$
- 4. (a) Find an expression for  $V_1(t)$  for  $(t \ge 0)$ .
  - (b) Make a sketch of the expression for  $V_1(t)$




Use the circuits below for problems 5 and 6. After being in position 1 (top circuit) for a long time, the switch is moved to position 2(bottom circuit) at t=0.

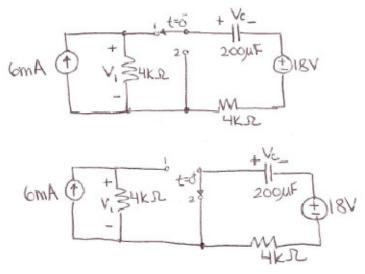
- 5. (a) Find an expression for  $V_C(t)$  for  $(t \ge 0)$ .
  - (b) Make a sketch of the expression for  $V_C(t)$
- 6. (a) Find an expression for  $V_1(t)$  for  $(t \ge 0)$ .
  - (b) Make a sketch of the expression for  $V_1(t)$



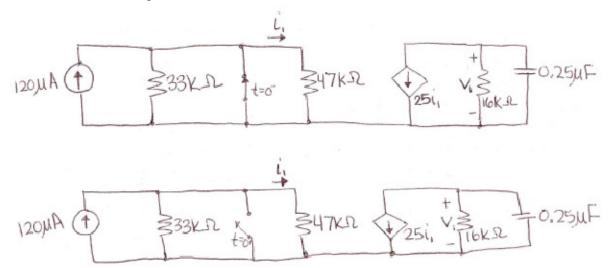
7. After being closed (top circuit) for a long time, the switch is opened (bottom circuit) at t=0. Find an expression for  $V_1(t)$  for (t  $\ge 0$ ).



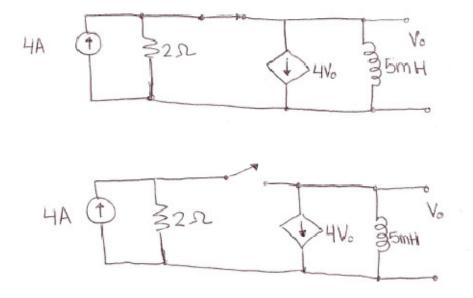8. After being closed (top circuit) for a long time, the switch is opened (bottom circuit) at t=0. Find an expression for  $V_0(t)$  for (t  $\geq 0$ ).



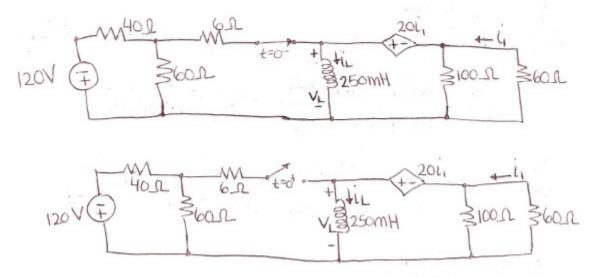9. After being closed (top circuit) for a long time, the switch is opened (bottom circuit) at t=0. Find an expression for  $V_L(t)$  and  $i_L(t)$  for (t≥0).



10. After being in position 1 (top circuit) for a long time, the switch is moved in position 2 (bottom circuit) at t=0. Find an expression for  $i_1(t)$  for  $(t \ge 0)$ .

