
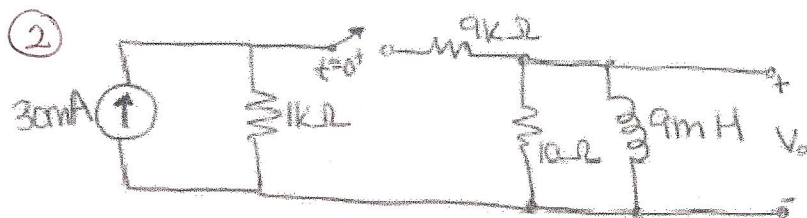



1. After being closed (top circuit) for a long time, the switch is opened (bottom circuit) at $t=0$.

(a) Find an expression for $V_o(t)$ for $(t \geq 0)$.

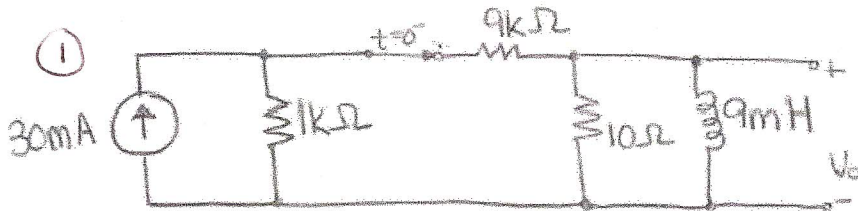(b) Find the energy stored in the inductor at time $t = 0^+$.




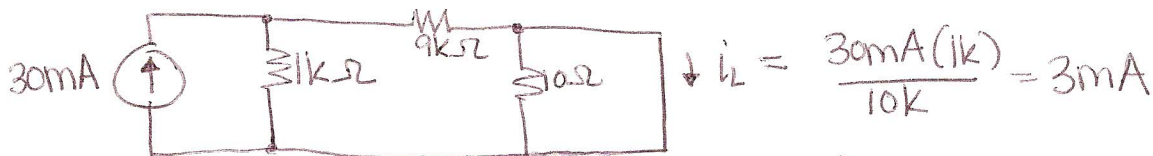circuit ①: ($t=0^-$), inductor becomes a wire, switch closed





$i_L(t=0^-) = i_L(t=0^+) = 3\text{mA}$ (current source)

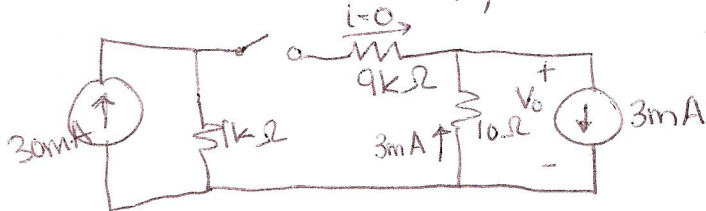circuit ②: ($t=0^+$), inductor acts as a current source, switch opened



$V_o = -3\text{mA}(10) = \underline{\underline{-30\text{mV}}}$
INITIAL VALUE

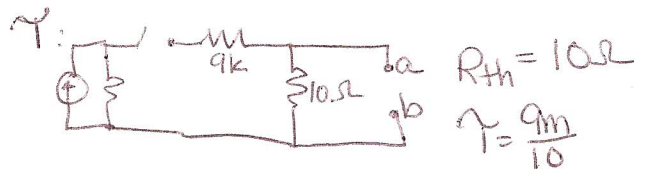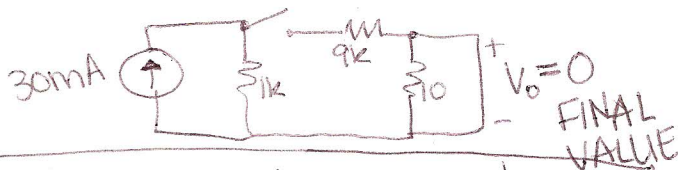circuit ②: ($t \rightarrow \infty$), inductor acts as a wire, switch opened





$t \geq 0, V_o(t) = 0 + (-30\text{mV} - 0)e^{-t/(9\text{m}/10)} \text{ V}$

b) energy at ($t=0^+$) = $\frac{1}{2}(9\text{m})(3\text{mA})^2$
= $\underline{\underline{40.5\text{nJ}}}$


2. After being closed (top circuit) for a long time, the switch is opened (bottom circuit) at $t=0$.

(a) Find an expression for $i_1(t)$ for $(t \geq 0)$.

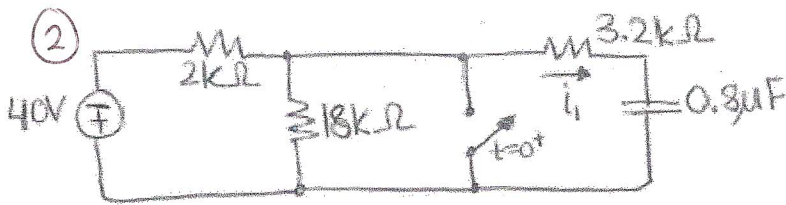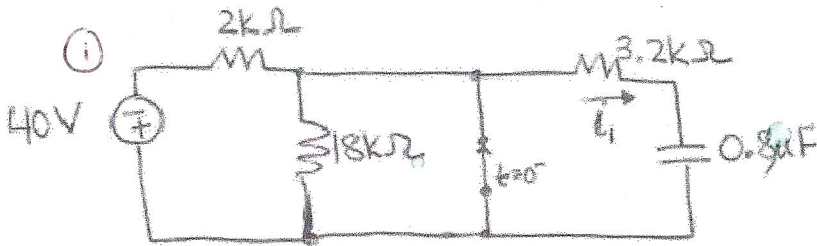(b) Find the energy stored in the capacitor at time $t = 0^+$.




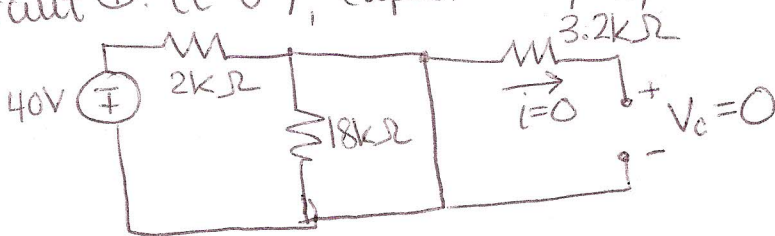circuit (1): ($t=0^-$), capacitor open, switch closed \Rightarrow



$$V_c(t=0^-) = V_c(t=0^+) = 0V$$

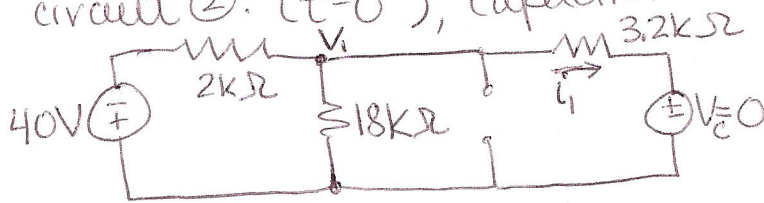circuit (2): ($t=0^+$), capacitor acts as a voltage source, switch open



$$i_1 = \frac{V_1}{3.2k}$$

node V_1 :


$$\frac{V_1 + 40}{2k} + \frac{V_1}{18k} + \frac{V_1}{3.2k} = 0$$

$$V_1 \left(\frac{1}{2k} + \frac{1}{18k} + \frac{1}{3.2k} \right) = \frac{-40}{2k}$$

$$V_1 (868\mu) = 20m \rightarrow V_1 = -23V$$

$$i_1 = -7.2mA \quad \text{INITIAL VALUE}$$

($t \rightarrow \infty$):

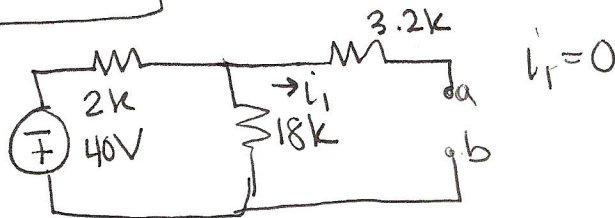

$$\tau = R_{th}C$$

$$R_{th} = 3.2k + 2k \parallel 18k$$

$$R_{th} = 5k$$

2. (cont.)

I.V.

$$i_1(t=0^+) = -7.2\text{mA}$$

$$\text{Final: } i_1(t \rightarrow \infty) = 0$$

$$R_{th} = 5\text{k}$$



$$(t \geq 0) i_1(t) = 0 + (-7.2\text{mA} - 0)e^{-t/5\text{k}(0.8\mu\text{F})} = \boxed{-7.2\text{mA}e^{-t/4\text{ms.}}}$$

b) at $t=0^+$: $v_c(t=0^+) = 0$

$$\therefore \boxed{w_c(t=0^+) = 0\text{J}}$$


Use the circuits below for problems 3 and 4. After being in position 1 (top circuit) for a long time, the switch is moved to position 2 (bottom circuit) at $t=0$.

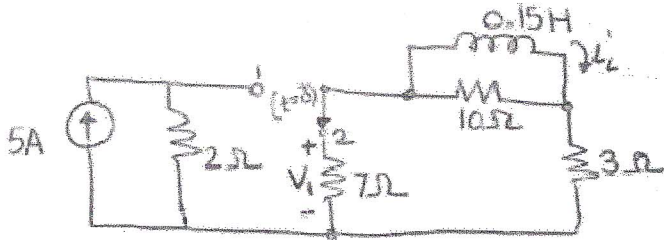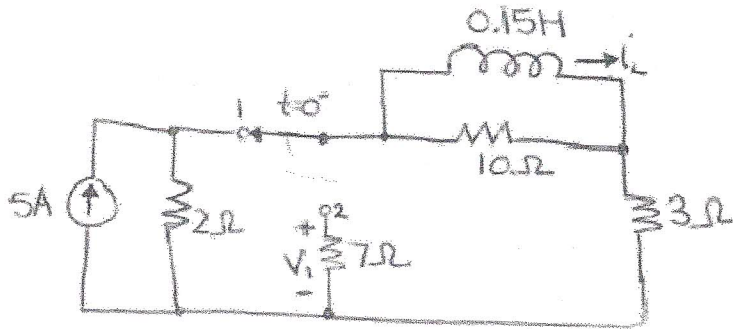3. (a) Find an expression for $i_L(t)$ for $(t \geq 0)$.
- (b) Make a sketch of the expression for $i_L(t)$
4. (a) Find an expression for $V_1(t)$ for $(t \geq 0)$.
- (b) Make a sketch of the expression for $V_1(t)$




circuit at $(t=0^-)$:

$$i_L = \frac{5(2)}{5} = 2A$$

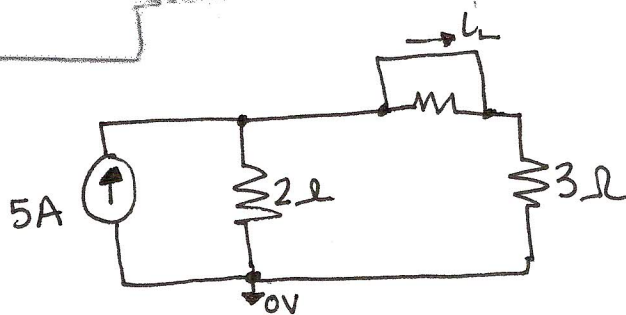

circuit at $(t=0^+)$:

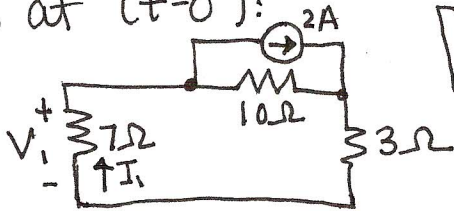


$$i_L(t=0^+) = 2A$$


$$I_1 = \frac{2(10)}{20} = 1A$$

$$\therefore V_1 = -1(7) = -7V$$

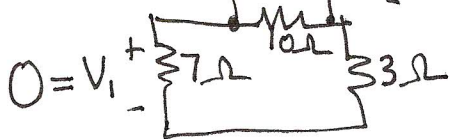circuit at $(t \rightarrow \infty)$: $i_L = 0$




$$0 = V_1$$

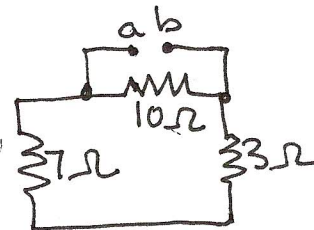


$$R_{th} = 10 \parallel 10$$

$$R_{th} = 5 \Omega$$

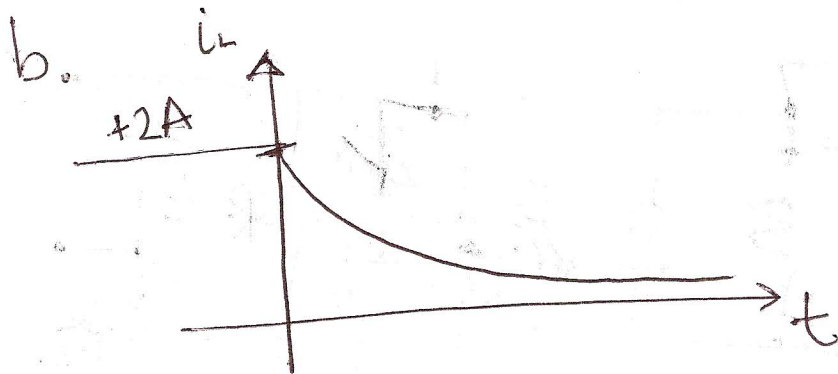3 a. $i_L(t) = 0 + (2-0)e^{-t/(0.15/5)}$ $= 2e^{-t/0.03s}$
(for $t \geq 0$)





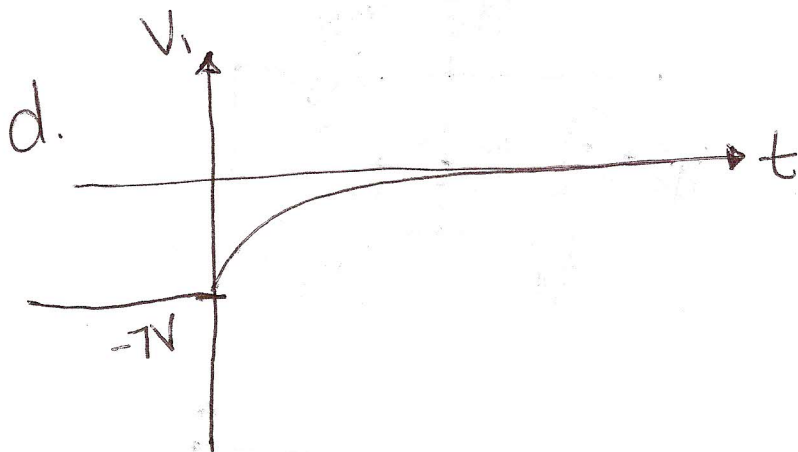c. $V_1(t \geq 0) = 0 + (-7-0)e^{-t/0.03}$ $= -7e^{-t/0.03s}$




Use the circuits below for problems 5 and 6. After being in position 1 (top circuit) for a long time, the switch is moved to position 2 (bottom circuit) at $t=0$.

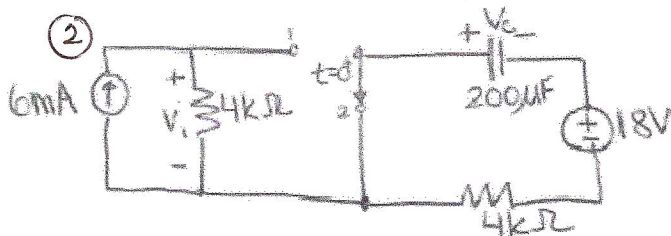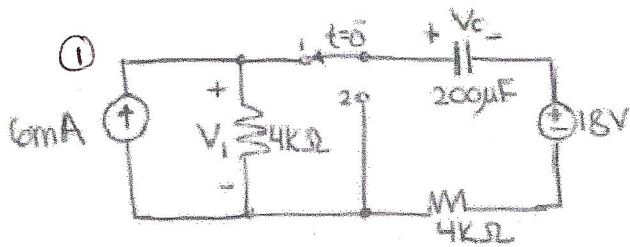5. (a) Find an expression for $V_C(t)$ for $(t \geq 0)$.
 (b) Make a sketch of the expression for $V_C(t)$
6. (a) Find an expression for $V_1(t)$ for $(t \geq 0)$.
 (b) Make a sketch of the expression for $V_1(t)$



circuit ① ($t=0^-$):

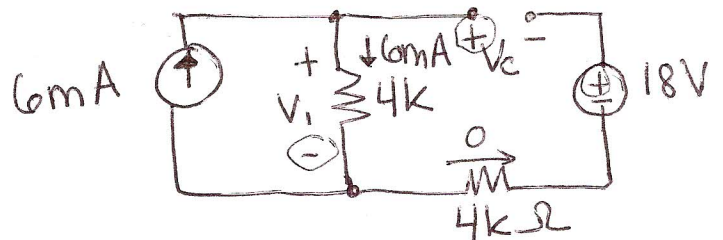

$$V_1 = 6m(4k) = 24V$$

$$+V_c - 24 - 0 + 18 = 0$$

$$V_c = 24 - 18 = +6V$$


circuit ② ($t=0^+$): INITIAL VALUE



$$V_c(t=0^+) = 6V$$

$$V_1(t=0^+) = +24V$$

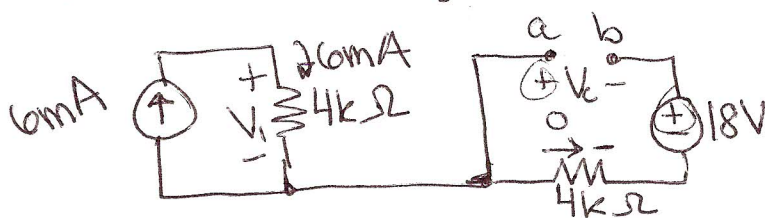circuit ② ($t \rightarrow \infty$): FINAL VALUE



$$+V_c - 0 + 18 = 0$$

$$V_c = -18V$$

$$V_1 = +24V$$

$$-t / (4k \times 800\mu)$$

τ :

$$R_{th} = 4k$$

$$\tau = 4k(200\mu)$$



$$\tau = 800ms$$

a. $V_c(t \geq 0) = -18 + (6 - (-18))e^{-t/800ms}$




$$V_c(t \geq 0) = -18 + 24e^{-t/800ms}$$

6. a. $V_1(t \geq 0) = +24 + (24 - 24)e^{-t/800msec}$

$$V_1(t \geq 0) = +24V$$

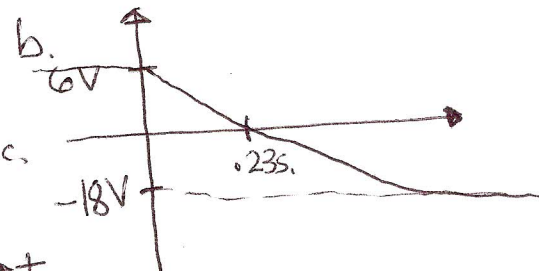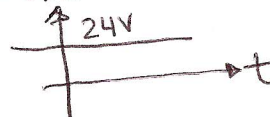

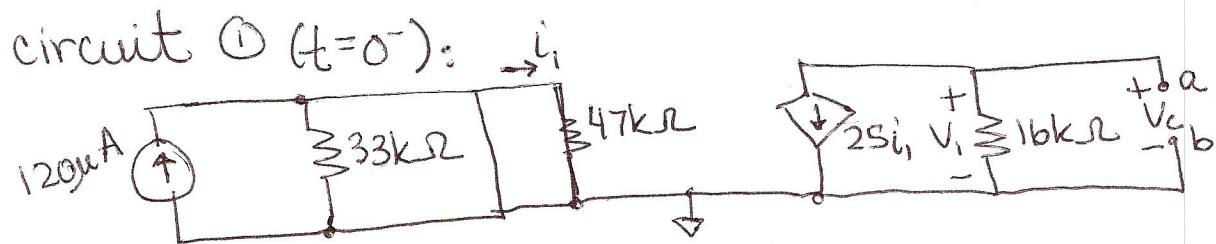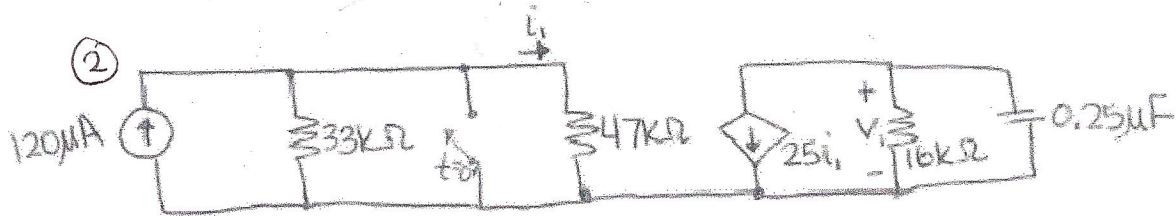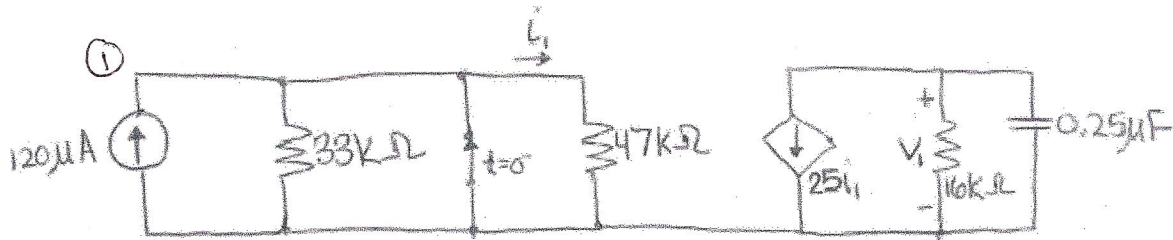7. After being closed (top circuit) for a long time, the switch is opened (bottom circuit) at $t=0$. Find an expression for $V_1(t)$ for ($t \geq 0$).



$$i_1 = 0A, V_1 = 0V$$


$$V_1 = V_c = 0V$$

circuit ② ($t=0^+$): INITIAL VALUE



$$V_1 = 0V$$

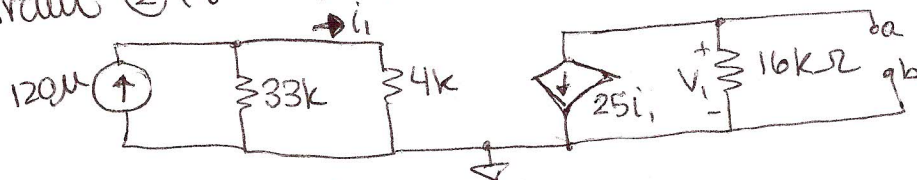
circuit ② ($t \rightarrow \infty$): FINAL VALUE



$$i_1 = \frac{120\mu(33k)}{37k} = 107\mu A$$

$$V_1 = -25i_1(16k) = -25(107\mu)(16k) = -42.8V$$

circuit at ② ($t \rightarrow \infty$): τ

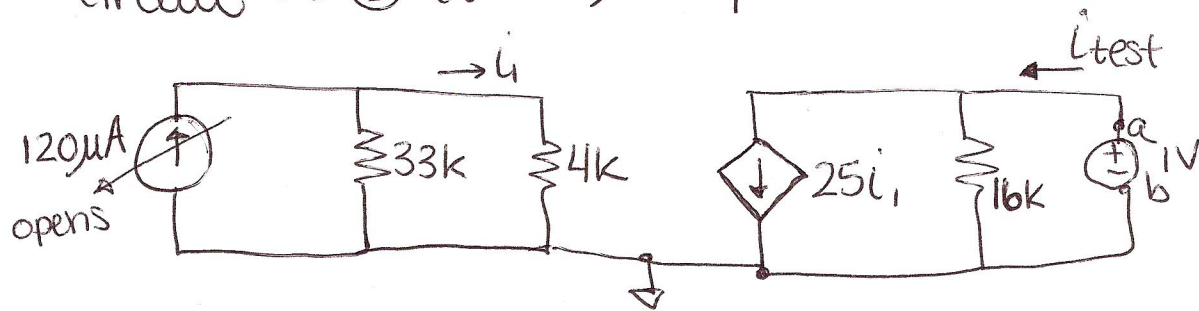

Note: The dependent source has resistance!

$$i_1 = 0, \quad 25i_1 = 0 \text{ (open)}$$



$$\therefore i_{\text{test}} = \frac{1}{16k}$$

$$R_{\text{th}} = \frac{1}{\frac{1}{16k}} = \underline{\underline{16k \Omega}}$$


$$\therefore \tau = 16k(0.25\mu) = 4\text{msec.}$$

$$V_1(t \geq 0) = -42.8 + (0 + 42.8)e^{-t/4\text{ms.}} = \boxed{[-42.8 + 42.8e^{-t/4\text{ms.}}] \text{ V}}$$

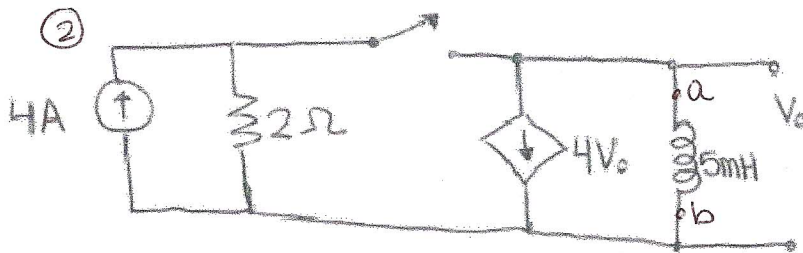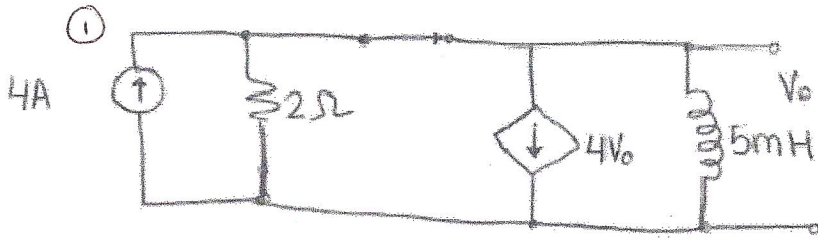8. After being closed (top circuit) for a long time, the switch is opened (bottom circuit) at $t=0$. Find an expression for $V_o(t)$ for ($t \geq 0$).




circuit ① ($t=0^-$):

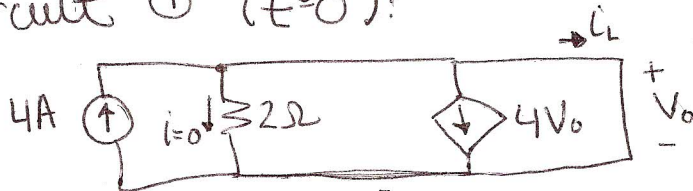


$$i_L = 4A$$

circuit ② ($t=0^+$): INITIAL VALUE

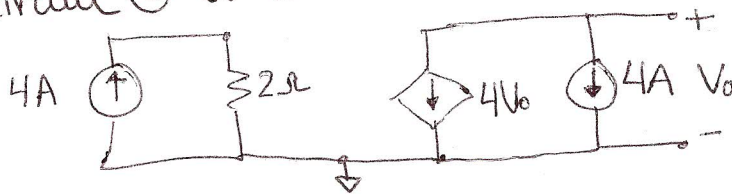

$$\begin{aligned} -4V_o &= 4A \\ \therefore V_o &= -1V \end{aligned}$$


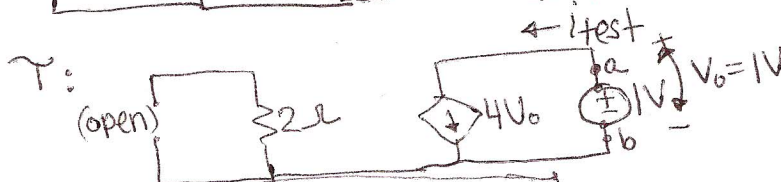
circuit ② ($t \rightarrow \infty$): FINAL VALUE




$$\begin{aligned} i_{test} &= 4(1) = 4A \\ R_{th} &= \frac{1}{4} = \frac{1}{4}\Omega \\ \tau &= \frac{5m}{\left(\frac{1}{4}\right)} = 20ms. \end{aligned}$$

$$V_o(t \geq 0) = 0 + (-1 + 0)e^{-t/20ms} \text{ V}$$

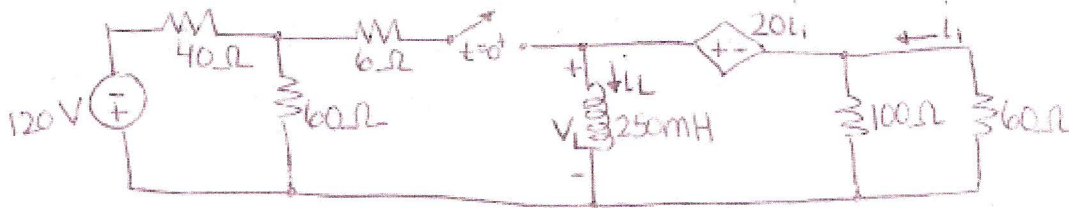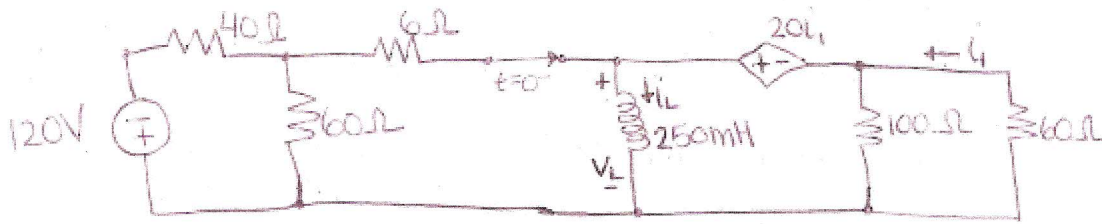9. After being closed (top circuit) for a long time, the switch is opened (bottom circuit) at $t=0$. Find an expression for $V_L(t)$ and $i_L(t)$ for $(t \geq 0)$.



#9. circuit at $(t=0^-)$:

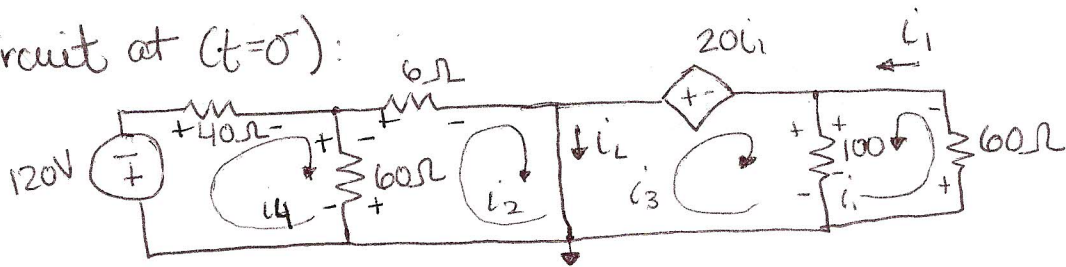

$$-i_2 + i_L + i_3 = 0 \rightarrow i_L = (i_2 - i_3)$$

$$\textcircled{1} -20i_4 - 100(i_3 + i_1) = 0$$

$$\textcircled{2} +100(i_3 + i_1) + i_1(60) = 0$$

$$\textcircled{3} -120 - i_4(40) + 60(i_2 - i_4) = 0$$

$$\textcircled{4} +60(i_4 - i_2) - i_2(6) = 0$$

$$\text{From } \textcircled{2} \quad 100i_3 = -\frac{160i_1}{100} = -\frac{8}{5}i_1$$

plug into $\textcircled{1}$:

$$-20i_1 - 100i_1 - (100)\left(-\frac{8}{5}i_1\right) = 0$$

$$\therefore i_1 = 0 \rightarrow i_3 = 0$$

From $\textcircled{4}$:

$$60i_4 = \frac{66i_2}{60} = \frac{11}{10}i_2$$

plug into $\textcircled{3}$:


$$-120 - \frac{11}{10}i_2(40) + 60i_2 - 60\left(\frac{11}{10}\right)i_2 = 0$$

$$120 = -44i_2 + 60i_2 - 66i_2 = +60i_2 - 110i_2$$

$$-120 = -50i_2$$

$$\therefore i_L = i_2 = -\frac{12}{5} \text{ A}$$

#9 circuit at $(t=0^+)$: INITIAL VALUE

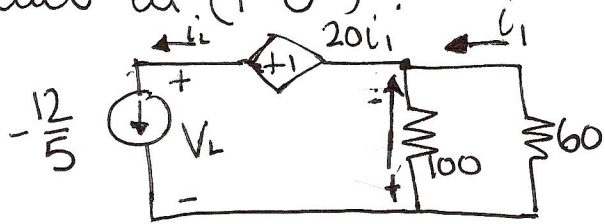

$$i_1 = \frac{+(-\frac{12}{5})100}{160} = \frac{-12(20)}{8 \cdot 160} = -\frac{3}{2} \text{ A} = 1.5 \text{ A}$$


$$100 \parallel 60 = \frac{50(3)}{4 \cdot 160} = \frac{150}{4} = 37.5$$

$$+V_L - 20i_1 + (-\frac{12}{5})(\frac{150}{4}) = 0$$

$$V_L = +20(-\frac{3}{2}) + 3(3) = -30 + 9 = \underline{\underline{-21 \text{ V}}}$$

$$i_L = -\frac{12}{5}$$

circuit at $(t \rightarrow \infty)$:

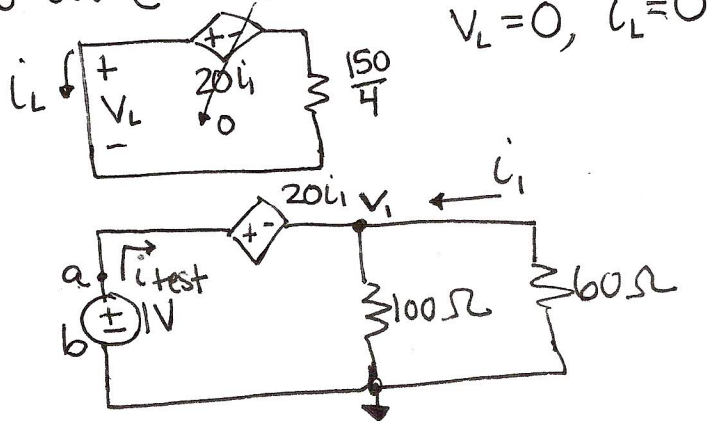

$$V_L = 0, i_L = 0$$

$$+1 - 20i_1 - V_1 = 0 \rightarrow V_1 = (+1 - 20i_1)$$

$$-i_{\text{test}} + \frac{(1 - 20i_1)}{100} + \frac{(1 - 20i_1)}{60} = 0$$

$$i_1 = \frac{-1 + 20i_1}{60} \rightarrow 60i_1 - 20i_1 = -1 \rightarrow i_1 = -\frac{1}{40}$$

$$i_{\text{test}} = \frac{1}{100} + \frac{1}{60} - \frac{20}{100}(-\frac{1}{40}) - \frac{20}{60}(-\frac{1}{40})$$

#9.

$$i_{\text{test}} = \frac{6}{600} + \frac{10}{600} + \frac{1}{200} + \frac{1}{120} = \frac{16}{600} + \frac{3}{600} + \frac{5}{600} = \frac{24}{600}$$

$$i_{\text{test}} = \frac{1}{25}$$



$$R_{\text{th}} = \frac{1}{\frac{1}{25}} = 25 \Omega$$

$$\tau = L/R_{\text{th}} = \frac{250\text{mH}}{25\Omega} = 10\text{ms.}$$


$$v_L(t \geq 0) = 0 + (-21 - 0)e^{-t/10\text{ms.}} = \boxed{-21Ve^{-t/10\text{ms.}}}$$

$$i_L(t \geq 0) = 0 + \left(-\frac{12}{5} - 0\right)e^{-t/10\text{ms.}} = \boxed{-\frac{12}{5}e^{-t/10\text{ms.}}}$$

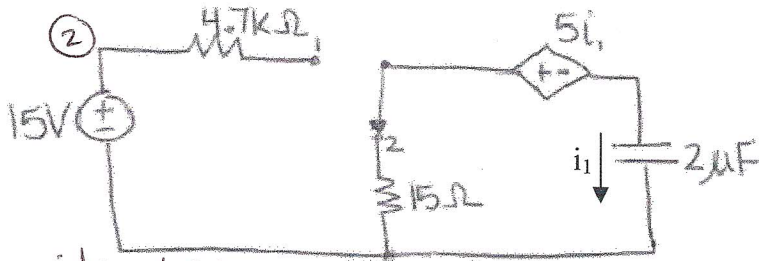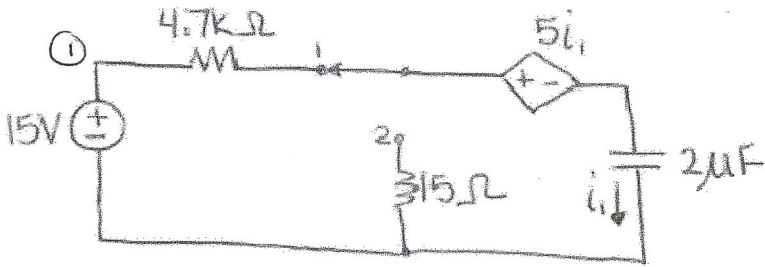
10. After being in position 1 (top circuit) for a long time, the switch is moved in position 2 (bottom circuit) at $t=0$. Find an expression for $i_1(t)$ for ($t \geq 0$).




circuit at ($t=0^-$):

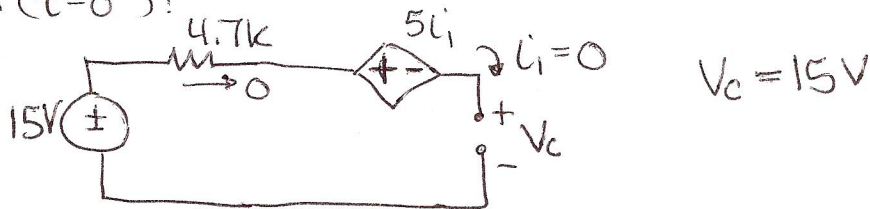

circuit at ($t=0^+$): INITIAL VALUE

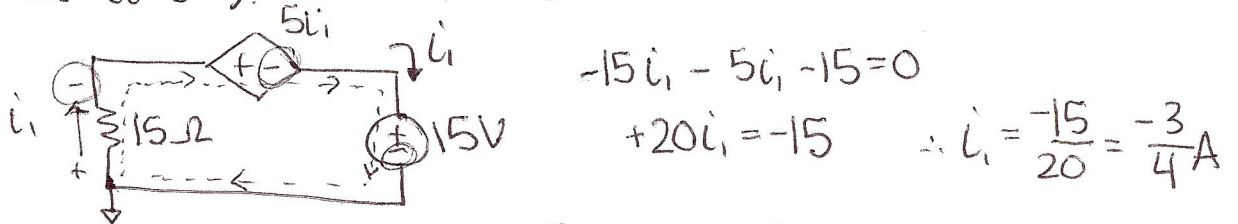

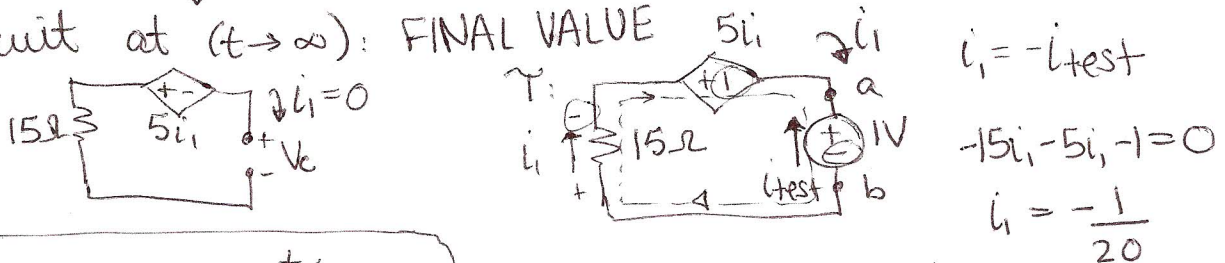circuit at ($t \rightarrow \infty$): FINAL VALUE



$$i_1(t \geq 0) = -\frac{3}{4} e^{-t/40\mu s} \text{ A}$$

$$\therefore R_{th} = \left(\frac{1}{20}\right) = 20\Omega$$

$$\tau = 20(2\mu) = 40\mu s$$