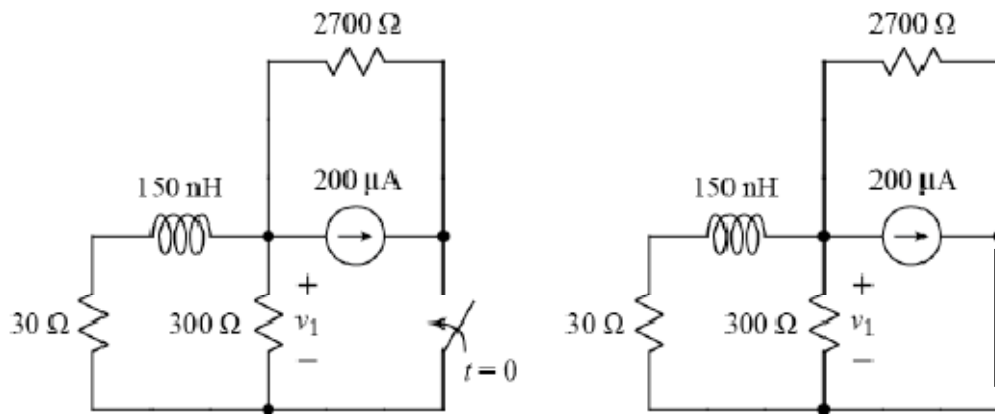



1.



After being open(left circuit) for a long time, the switch closes at $t = 0$ (right circuit).

- a) Calculate the energy stored on the inductor as $t \rightarrow \infty$.
- b) Write a numerical expression for $v_1(t)$ for $t > 0$.


2.

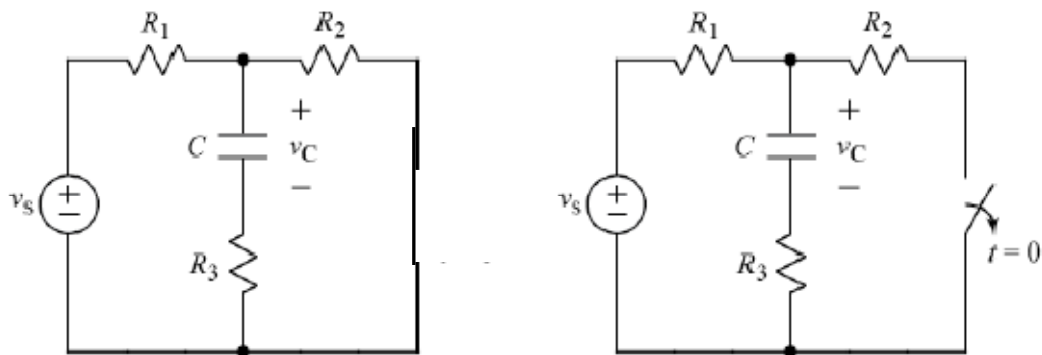

After being closed(left circuit) for a long time, the switch opens at $t = 0$ (right circuit).


- a) Write an expression for $v_C(t = 0^+)$.
- b) Write an expression for $v_C(t > 0)$ in terms of no more than $R_1, R_2, R_3, v_s,$ and C .

3.

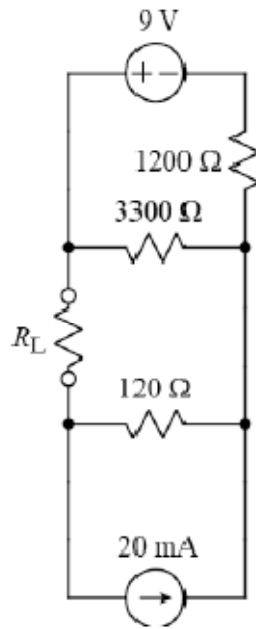


- a) Calculate the value of R_L that would absorb maximum power.
- b) Calculate that value of maximum power R_L could absorb.

4.

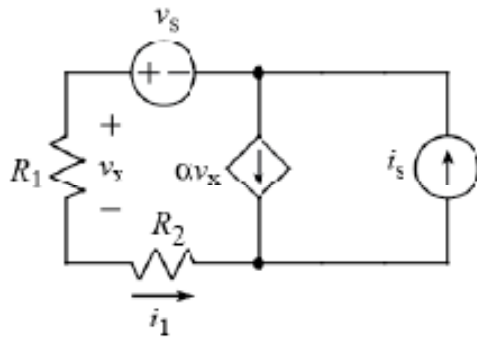

Using superposition, derive an expression for i_1 that contains no circuit quantities other than i_s , v_s , R_1 , R_2 , and α . Note: $\alpha > 0$.


5.

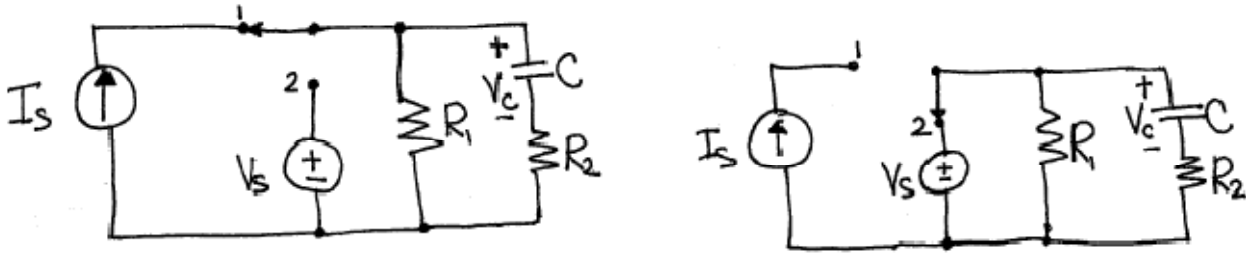

After being in position 1(left circuit) for a long time, the switch moves to position 2 at $t=0$ (right circuit).

- Write an expression for $v_C(t > 0)$ in terms of no more than $R_1, R_2, V_s, I_s,$ and C .
- Write an expression for the energy stored on the capacitor as $t \rightarrow \infty$ in terms of no more than $R_1, R_2, V_s, I_s,$ and C .


6.

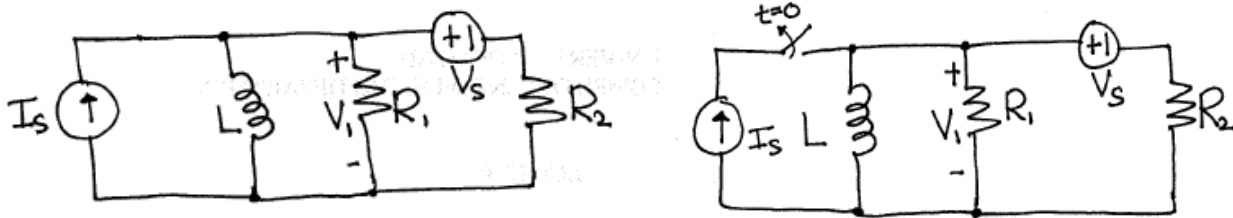

After being closed(left circuit) for a long time, the switch opens at $t = 0$ (right circuit).


- Write an expression for $v_1(t > 0)$ in terms of no more than $R_1, R_2, V_s, I_s,$ and L .
- Write an expression for the energy stored on the inductor as $t \rightarrow \infty$ in terms of no more than $R_1, R_2, V_s, I_s,$ and L .

7.

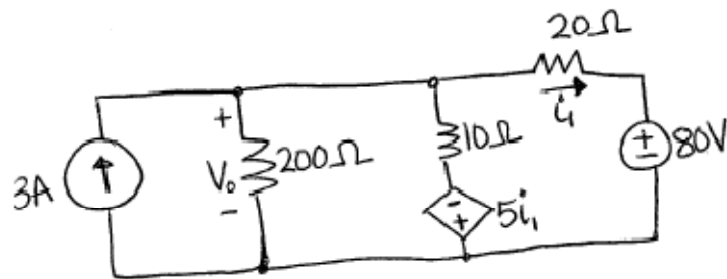


Using superposition, derive a value for i_1 .

8.

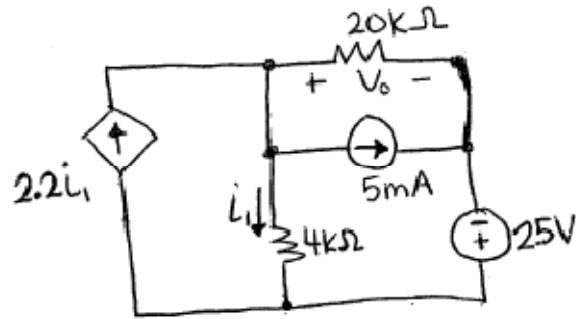


Using superposition, derive an expression for V_o .

9.

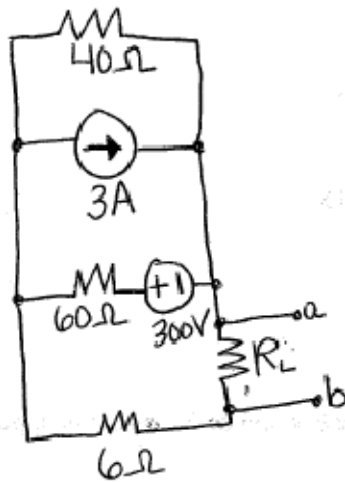

- a) Calculate the value of R_L that would absorb maximum power.
- b) Calculate that value of maximum power R_L could absorb.

10.

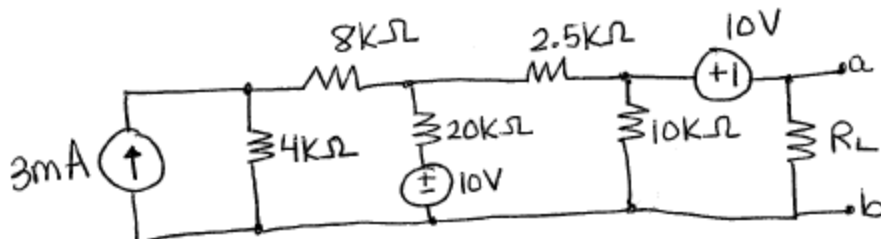

- a) Calculate the value of R_L that would absorb maximum power.
- b) Calculate that value of maximum power R_L could absorb.