
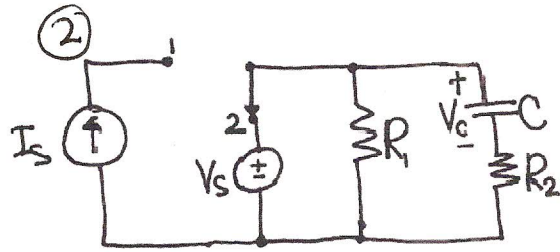



5.

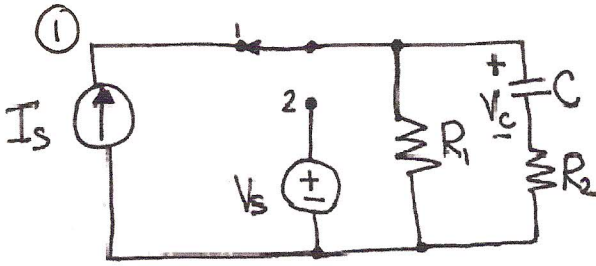

After being in position 1 (left circuit) for a long time, the switch moves to position 2 at $t=0$ (right circuit).


- Write an expression for $v_C(t > 0)$ in terms of no more than R_1 , R_2 , V_s , I_s , and C .
- Write an expression for the energy stored on the capacitor as $t \rightarrow \infty$ in terms of no more than R_1 , R_2 , V_s , I_s , and C .

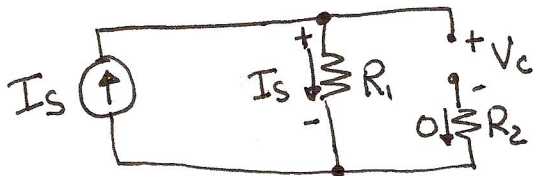circuit ① at $(t=0^-)$: cap open, find V_c




$$V_c = I_s \cdot R_1$$

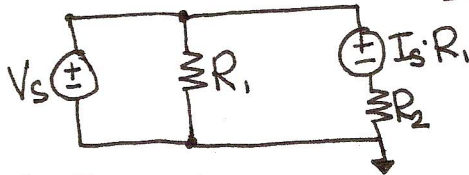circuit ② at $(t=0^+)$: cap keeps value at $(t=0^-)$ {V src.} INITIAL VALUE from this circuit



$$V_c = I_s R_1$$

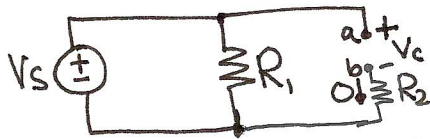circuit ② at $(t \rightarrow \infty)$: cap open, tau, γ , found for this circuit



$$V_c = V_s$$


$$R_{th} = R_2 \text{ (} V_s \text{ becomes short)}$$

$$\gamma = R_2 C$$

$$a) \quad v_C(t \geq 0) = [V_s + (I_s R_1 - V_s) e^{-t/R_2 C}] V$$

$$b) \quad w_C(t \rightarrow \infty) = \frac{1}{2} C V_s^2$$


6.

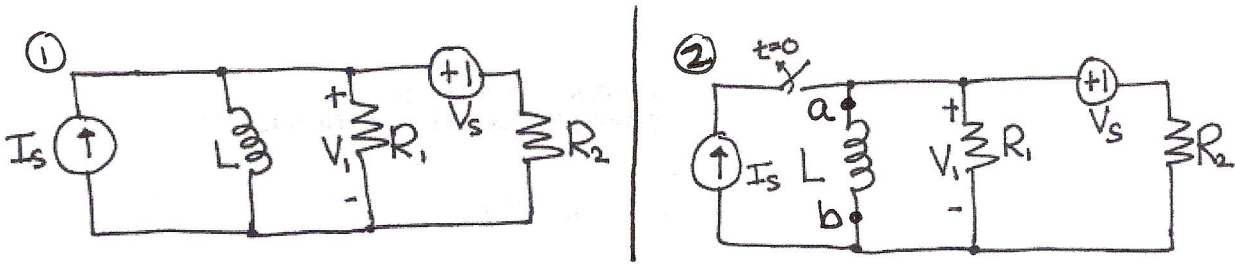


After being closed (left circuit) for a long time, the switch opens at $t = 0$ (right circuit).

- Write an expression for $v_1(t > 0)$ in terms of no more than R_1, R_2, V_s, I_s , and L .
- Write an expression for the energy stored on the inductor as $t \rightarrow \infty$ in terms of no more than R_1, R_2, V_s, I_s , and L .

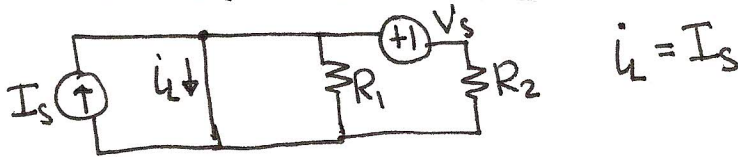circuit ① at ($t=0^-$): • inductor wire, find i_L



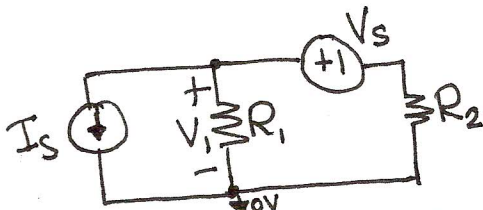
circuit ② at ($t=0^+$): • inductor currents, i_L , remains same
 { I src. }
 • find INITIAL VALUE at this time



$$+I_s + \frac{V_1}{R_1} + \frac{(V_1 - V_s)}{R_2} = 0 \rightarrow V_1 \left(\frac{1}{R_1} + \frac{1}{R_2} \right) = -I_s + \frac{V_s}{R_2}$$


$$\therefore V_1 = \left[-I_s + \frac{V_s}{R_2} \right] (R_1 \parallel R_2)$$

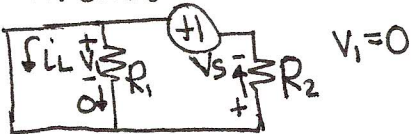circuit ② at ($t \rightarrow \infty$): • inductor becomes wire
 • find FINAL VALUE at this time
 • find " " " "



$$-i_L R_2 + V_s = 0$$


$$i_L = \frac{V_s}{R_2}$$

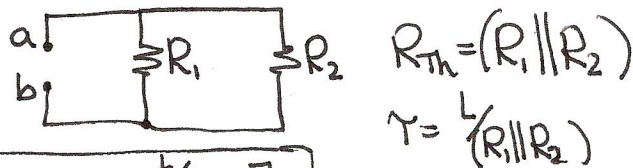

$$a) V_1(t \geq 0) = \left[-I_s + \frac{V_s}{R_2} \right] (R_1 \parallel R_2) e^{-\frac{t}{\tau}}$$


$$b) w_L(t \rightarrow \infty) = \frac{1}{2} L i_L^2(t \rightarrow \infty) = \frac{1}{2} L \cdot \frac{V_s^2}{R_2^2}$$

7.

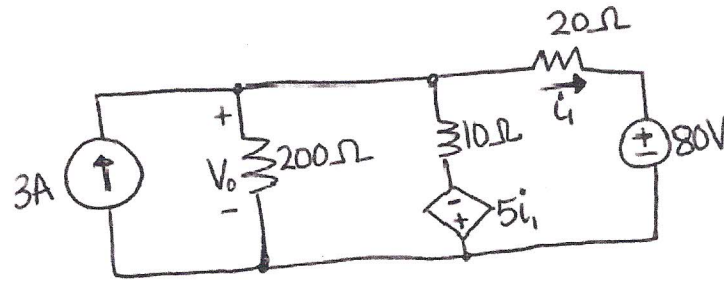

Using superposition, derive a value for i_1 .

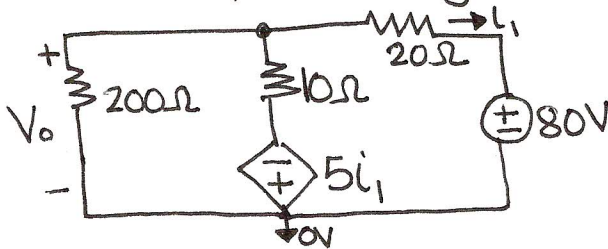Case I: Turn 3A off, 80V stays on. Dependent source ALWAYS stays.



$$i_1 = \frac{(V_o - 80)}{20}$$


$$\frac{V_o}{200} + \frac{(V_o + 5i_1)}{10} + \frac{(V_o - 80)}{20} = 0$$

$$\frac{V_o}{200} + \frac{V_o(20)}{200} + \frac{10V_o}{200} + \frac{1}{2} \left(\frac{V_o - 80}{20} \right) = +4 + 2$$

$$V_o \left(\frac{1}{200} + \frac{20}{200} + \frac{10}{200} + \frac{5}{200} \right) = +6 \left(\frac{200}{36} \right) \Rightarrow V_o = \frac{100}{3} \text{ V}$$

$$\textcircled{1} i_1 = \frac{100}{60} - \frac{80}{20} = \frac{5}{3} - \frac{12}{3} = -\frac{7}{3} \text{ A}$$

Case II: Turn 3A on, 80V off: v_1

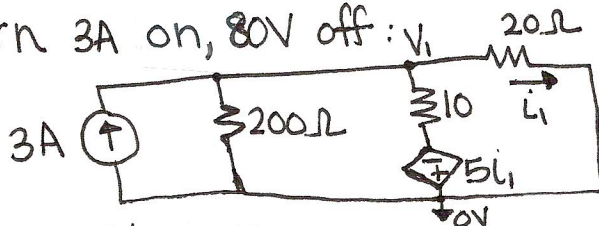

$$-3 + \frac{v_1}{200} + \frac{(v_1 + 5i_1)}{10} + \frac{v_1}{20} = 0$$

$$i_1 = \left[\frac{v_1}{20} \right]$$


$$-3 + \frac{v_1}{200} + \frac{v_1}{10} + \frac{1}{2} \left[\frac{v_1}{20} \right] + \frac{v_1}{20} = 0$$

$$v_1 \left[\frac{1}{200} + \frac{20}{200} + \frac{5}{200} + \frac{10}{200} \right] = 3 \left[\frac{200}{36} \right] = \frac{200}{12} = \frac{50}{3} \text{ V}$$

$$\textcircled{2} i_1 = \frac{v_1}{20} = \frac{5}{6} \text{ A}$$


$$\text{Total } \textcircled{1} + \textcircled{2} = -\frac{7}{3} + \frac{5}{6} = \frac{-14 + 5}{6} = \frac{-9}{6} = \boxed{-\frac{3}{2} \text{ A}}$$

8.

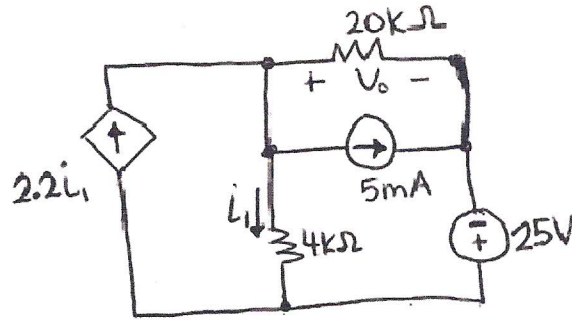

Case I: Using superposition, derive an expression for V_0 .

5mA on, 25V off:

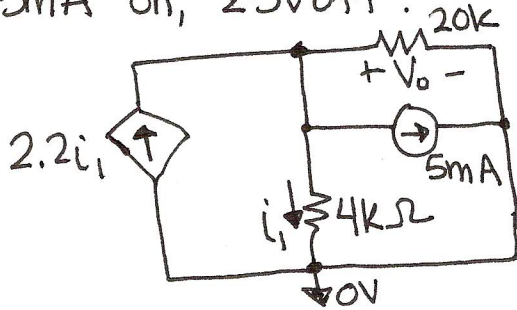

$$-2.2i_1 + i_1 + 5\text{m} + \frac{V_0}{20\text{k}} = 0$$


$$i_1 = \frac{V_0}{4\text{k}}$$

$$-1.2 \left(\frac{V_0}{4\text{k}} \right) + 5\text{m} + \frac{V_0}{20\text{k}} = 0$$

$$V_0 \left[\frac{-1.2}{4\text{k}} + \frac{1}{20\text{k}} \right] = -5\text{m} \left[\frac{20\text{k}}{1 - 1.2(5)} \right] = \underline{\underline{+20\text{V}}}$$

Case II:

5mA off, 25V on:

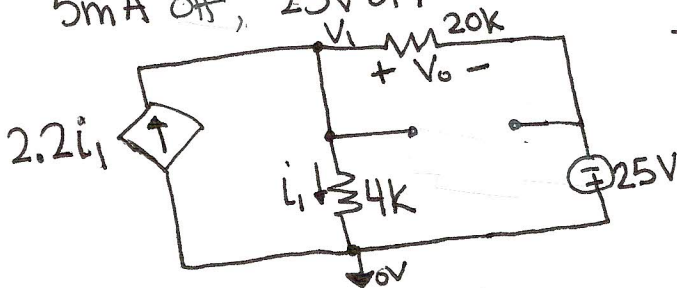

$$-2.2 \left[\frac{V_1}{4\text{k}} \right] + \left[\frac{V_1}{4\text{k}} \right] + \frac{(V_1 + 25)}{20\text{k}} = 0$$


$$V_1 \left[\frac{-2.2(5) + 5 + 1}{20\text{k}} \right] = \frac{-25}{20\text{k}}$$

$$\therefore V_1 = \frac{-25}{20\text{k}} \left[\frac{20\text{k}}{-5} \right] = \underline{\underline{+5\text{V}}}$$

$$V_0 = V_1 + 25 = 30\text{V}$$


$$\text{Total } V_0 = +20 + 30 = \boxed{+50\text{V}}$$

9.

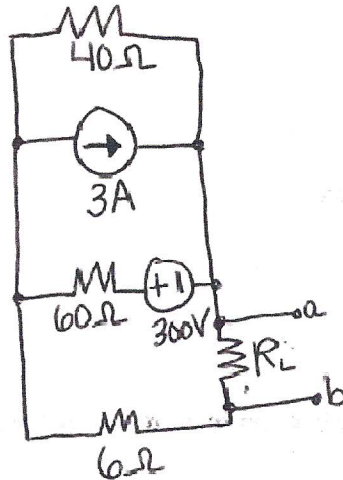


- a) Calculate the value of R_L that would absorb maximum power.
 b) Calculate that value of maximum power R_L could absorb.

$$R_L = R_{th}$$

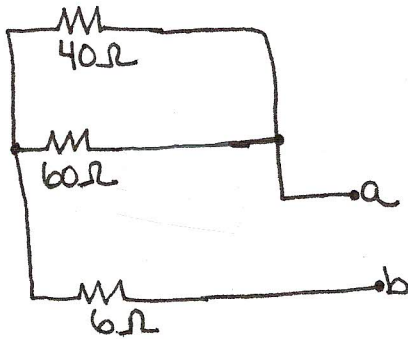

$$R_{th} = [60 \parallel 40] + 6 = 24 + 6 = 30 \Omega$$

$$R_L = 30 \Omega$$

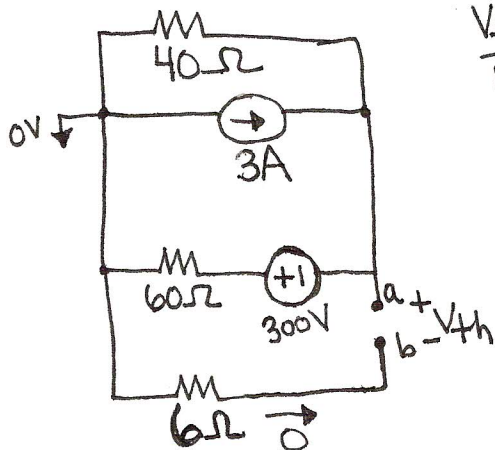


$$\frac{V_{th}}{40} - 3 + \frac{(V_{th} + 300)}{60} = 0$$

$$V_{th} \left[\frac{3+2}{120} \right] = \left[+3 - \frac{300}{60} \right]$$

$$V_{th} = \left[\frac{18-300}{6} \right] \left[\frac{120}{5} \right] = -\frac{240}{5} V$$

$$power = \frac{V_{th}^2}{4 \cdot R_{th}} = \left(\frac{-240}{5} \right)^2 \cdot \left(\frac{1}{4(30)} \right) = 19.2 W$$

9.

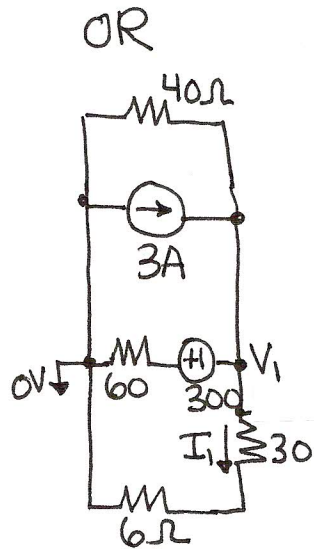

$$\text{Power} = [I_1^2 \cdot 30]$$

Using node-V:

$$\frac{V_1}{40} - 3 + \left[\frac{V_1 + 300}{60} \right] + \frac{V_1}{36} = 0$$

$$V_1 \left[\frac{1}{40} + \frac{1}{60} + \frac{1}{36} \right] = \left[+3 - \frac{30}{6} \right]$$


$$V_1 [69.4 \text{ m}] = \left[\frac{18 - 30}{6} \right]$$

$$V_1 = -28.8 \text{ V}$$


$$I_1 = \frac{V_1}{36} = -0.8 \text{ A}$$

$$\text{power} = (-.8)^2 \cdot 30 = \boxed{+19.2 \text{ W}}$$

10.

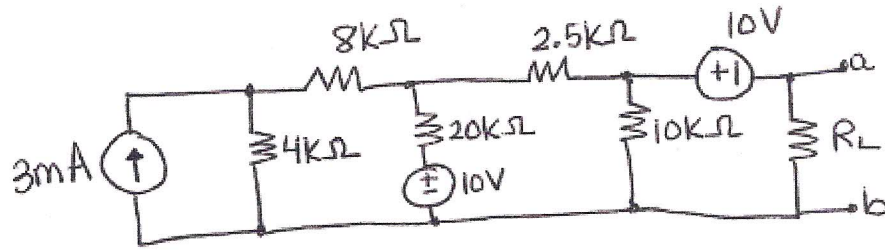


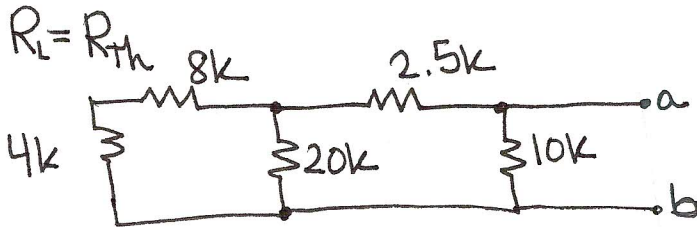- Calculate the value of R_L that would absorb maximum power.
- Calculate that value of maximum power R_L could absorb.



$$R_{Th} = 10k \parallel [2.5k + 12k \parallel 20k] = 10k \parallel \underbrace{(2.5k + 7.5k)}_{10k} = 5k \Omega$$

$$R_L = 5k \Omega$$

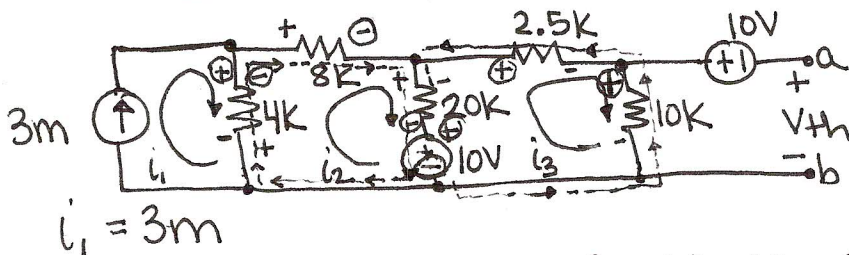

$$V_{Th} = i_3(10k) - 10$$

$$i_1 = 3m$$

$$\text{Eq. 1: } 4k(3m - i_2) - 8ki_2 + 20k(i_3 - i_2) - 10 = 0$$

$$i_2(-4k - 8k - 20k) + 12 - 10 + 20ki_3 = 0$$

$$i_2(32k) = (+2 + 20ki_3) / 32k$$

$$\text{Eq. 2: } +20k(-i_2 + i_3) - 10 + i_3(12.5k) = 0$$

$$+20ki_3 + 12.5ki_3 - 10 - 20k \left[\frac{2 + 20ki_3}{32k} \right] = 0$$


$$i_3 \left(32.5k - 20k \left(\frac{20k}{32k} \right) \right) = +10 + 20k \left(\frac{2}{32k} \right)$$

#10. $i_3(20K) = 11.25$

$i_3 = 562.5 \mu A$

$V_{th} = 562.5 \mu(10K) - 10V \cong -4.4$

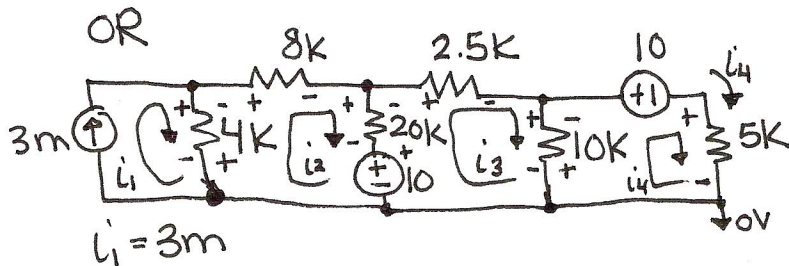power = $\frac{V_{th}^2}{4R_{th}} = \boxed{956 \mu W}$



power = $i_4^2 \cdot 5K$

Eq. 1: $4K(3m - i_2) - 8K i_2 + 20K(i_3 - i_2) - 10 = 0$

$i_2 = \left[\frac{2 + 20K i_3}{32K} \right]$

Eq. 2: $+20K(i_3 - i_2) - 10 + 2.5K i_3 + 10K(i_3 - i_4) = 0$

$-10K i_4 + i_3(20K + 2.5K + 10K) - 20K \left[\frac{2 + 20K i_3}{32K} \right] = +10$

$-10K i_4 + i_3 \left(32.5K - \frac{20K(20K)}{32K} \right) = \left[+10 + \frac{20K(2)}{32K} \right]$

$-10K i_4 + i_3(20K) - 11.25 = 0$

$10K i_4 = \frac{-11.25 + i_3(20K)}{10K}$

Eq. 3: $+10K(i_3 - i_4) - 10 - i_4(5K) = 0$

$10K i_3 - 10 - 15K \left[\frac{-11.25 + 20K i_3}{10K} \right] = 0$

$i_3 \left(10K - \frac{15K(20K)}{10K} \right) = +10 + 15K \left[\frac{-11.25}{10K} \right]$

#10.

$$i_3(-20K) = +10K - 16.875$$

$$i_3 = \frac{-6.875}{-20K} = +343.75\mu A$$

$$i_4 = \frac{-11.25 + i_3(20K)}{10K} = \frac{-11.25 + (343.75\mu)20K}{10K}$$

$$i_4 = -437.5\mu A$$

$$\text{power} = (-437.5\mu)^2 \cdot 5K = \boxed{957\mu W}$$