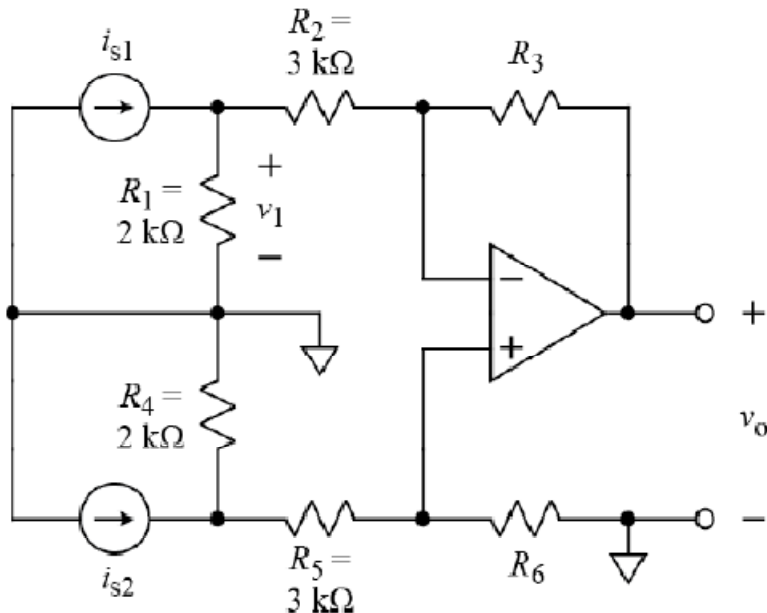


(Each problem is worth double points)

1.



The above circuit operates in linear mode. Derive a symbolic expression for v_o . The expression must contain not more than the parameters i_{s1} , i_{s2} , R_1 , R_2 , R_3 , R_4 , R_5 , and R_6 .

2. If $i_{s1} = 100 \mu\text{A}$ and $i_{s2} = 0 \text{ A}$, find the value of $R_3 = R_6$ that will yield an output voltage of $v_o = -6 \text{ V}$.

3. Assuming $R_1 = R_4$, $R_2 = R_5$, and $R_3 = R_6$ derive a symbolic expression for v_o in terms of common mode and differential input voltages:

$$i_{\text{cm}} \equiv \frac{(i_{s2} + i_{s1})}{2} \quad \text{and} \quad i_{\text{dm}} \equiv i_{s2} - i_{s1}$$

The expression must contain not more than the parameters i_{cm} , i_{dm} , R_1 , R_2 , and R_3 . Write the expression as i_{cm} times a term plus i_{dm} times a term. Hint: start by writing i_{s1} and i_{s2} in terms of i_{cm} and i_{dm} :



$$i_{s1} = i_{\text{cm}} - \frac{i_{\text{dm}}}{2} \quad \text{and} \quad i_{s2} = i_{\text{cm}} + \frac{i_{\text{dm}}}{2}$$

4. Assuming $i_{s2} = 0 \text{ A}$, find the numerical value of the circuit's input resistance, R_{in} , as seen by source i_{s1} . In other words, write a formula for voltage, v_1 , divided by i_{s1} :

$$R_{\text{in}} \equiv \frac{v_1}{i_{s1}}$$

Write R_{in} in terms of not more (and possibly less) than R_1 , R_2 , and R_3 .

5.

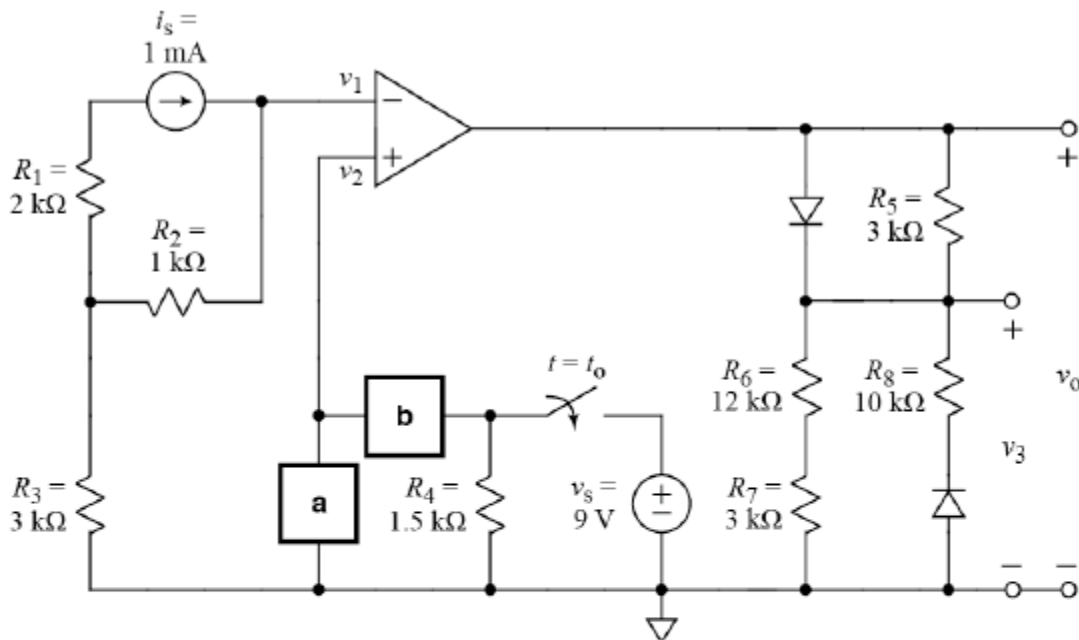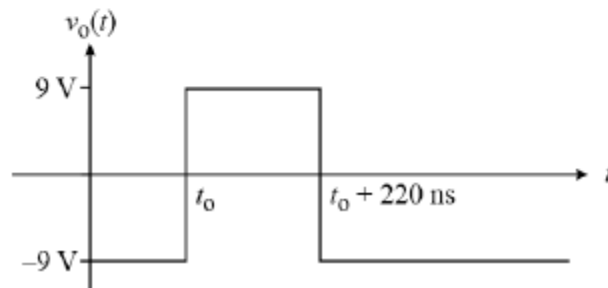
Rail voltages = $\pm 9 \text{ V}$ After being open for a long time, the switch closes at time $t = t_0$.

Choose either an R or L to go in box **a** and either an R or L to go in box **b** to produce the $v_o(t)$ shown above. Note that v_o stays low forever after $t_0 + 220 \text{ ns}$. Specify which element goes in each box and its value.

6. a) Sketch $v_1(t)$, showing numerical values appropriately.b) Sketch $v_2(t)$, showing numerical values appropriately.7. Sketch $v_3(t)$. Show numerical values for $t < t_0$, for $t_0 < t < t_0 + 220 \text{ ns}$, and for

$t > t_0 + 220 \text{ ns}$. Use the ideal model of the diode: when forward biased, its resistance is zero, (a wire); when reverse biased, its resistance is infinite, (an open).


8.

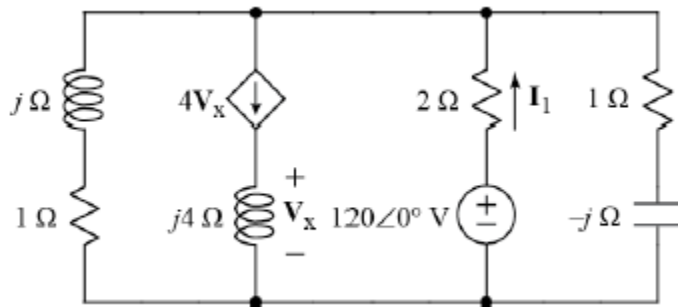

A frequency-domain circuit is shown above. Write the value of phasor current \mathbf{I}_1 in polar form.

9. Given $\omega = 377$ rad/s, write a numerical time-domain expression for $i_1(t)$, the inverse phasor of \mathbf{I}_1 .

10.

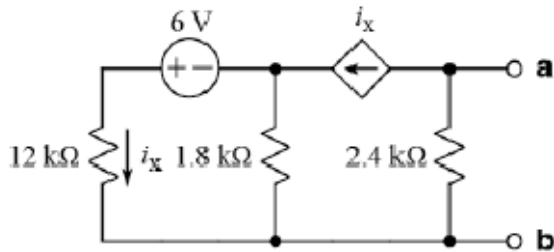

- Find the Thevenin equivalent of the above circuit relative to terminals **a** and **b**.
- If we attach R_L to terminals **a** and **b**, find the value of R_L that will absorb maximum power.
- Calculate the value of that maximum power absorbed by R_L .