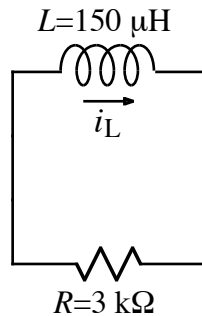


Ex: Find the current, i_L , through the inductor in the circuit below for $t > 0$ if $i_L(t = 0) = 100 \mu\text{A}$.



SOL'N: The same current flows in both the L and R, and the voltages are the same except for a minus sign:

$$v_L = L \frac{di_L}{dt} = -i_L R = -v_R$$

The inductor current, i_L , that solves this equation is an exponential:

$$i_L(t) = A e^{-t/(L/R)} = A e^{-t/50\text{ns}}$$

To satisfy the initial condition as given for $t = 0$, the value of the constant A must be $100 \mu\text{A}$ since the exponential has a value of unity: $e^0 = 1$.

$$i_L(t > 0) = 100 \mu\text{A} e^{-t/50\text{ns}}$$