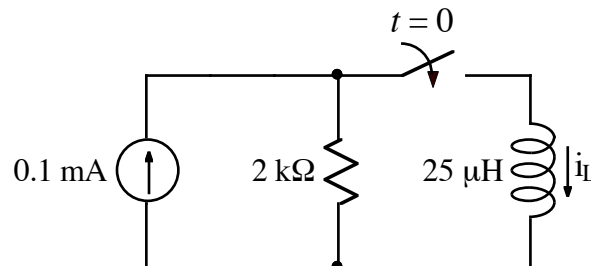


Ex:



After being open for a long time, the switch closes at  $t = 0$ .  $i_L(t = 0^-) = 0A$ . Find  $i_L(t)$  for  $t > 0$ .

sol'n: Since  $i_L$  is an energy variable, it cannot change instantly.

$$\therefore i_L(t=0^+) = i_L(t=0^-) = 0A$$

This is one of the values we need for the general solution that describes  $i_L(t)$ :

$$i_L(t) = i_L(t \rightarrow \infty) + [i_L(t=0^+) - i_L(t \rightarrow \infty)] e^{-t/\tau}$$

where  $\tau = L/R_{Th}$ .

Note:  $R_{Th}$  is the Thevenin equivalent resistance seen looking into the terminals where  $L$  is connected. Since the circuit seen looking into the terminals is a Norton equivalent, and  $R_N = R_{Th}$ , we have


$$R_{Th} = 2k\Omega \quad \text{and} \quad \tau = \frac{25\mu H}{2k\Omega} = 12.5 \text{ ns}$$

The value we lack for a complete sol'n is  $i_L(t \rightarrow \infty)$ . To find this value, we

employ the idea that, as  $t \rightarrow \infty$ , the currents and voltages become constant, we have  $v_L = L \frac{di}{dt} = L \cdot 0 = 0 \text{ V}$ .

Thus, the  $L$  acts like a wire.

$t \rightarrow \infty$  model:

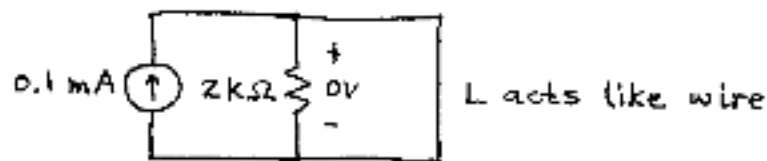

Since the  $2 \text{ k}\Omega$  resistor is shorted out, it has  $0 \text{ V}$  across, meaning that the current in the  $2 \text{ k}\Omega$  is  $0 \text{ V} / 2 \text{ k}\Omega = 0 \text{ A}$ .

$\therefore$  All the  $0.1 \text{ mA}$  from the source flows thru the  $L$ .

Thus,  $i_L(t \rightarrow \infty) = 0.1 \text{ mA}$ .

Plugging values into the general sol'n yields

$$i_L(t) = 0.1 \text{ mA} + [0 - 0.1 \text{ mA}] e^{-t/12.5 \text{ ns}}$$

$$\text{or } i_L(t) = 0.1 \text{ mA} [1 - e^{-t/12.5 \text{ ns}}]$$