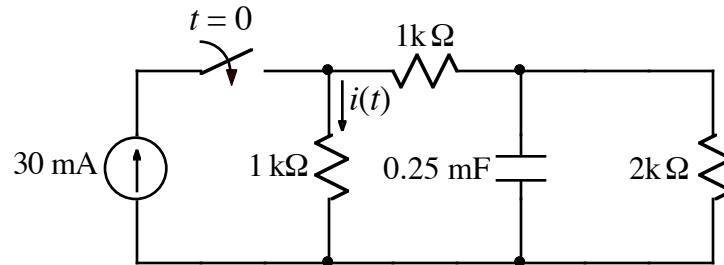


1.




After being open for a long time, the switch closes at $t = 0$.

Calculate the energy stored on the capacitor as $t \rightarrow \infty$.

2.


For the circuit in problem 1, write a numerical expression for $i(t)$ for $t > 0$.

3.

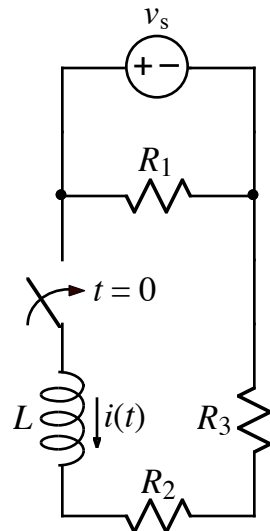


After being open for a long time, the switch closes at $t = 0$. Write an expression for $i_L(t > 0)$ in terms of no circuit quantities other than R_1 , R_2 , R_3 , v_s , and L .

4.

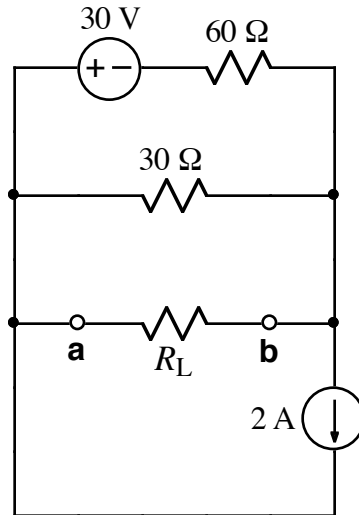

- a) Calculate the value of R_L that would absorb maximum power.
- b) Calculate that value of maximum power R_L could absorb.

5.

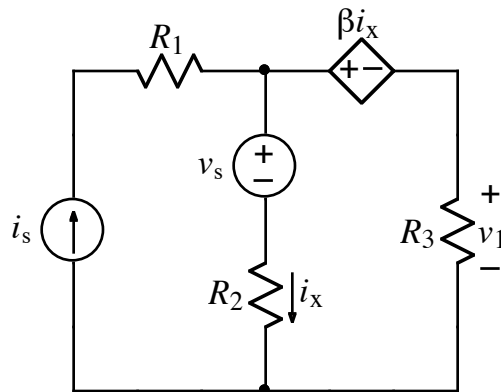

Using superposition, derive an expression for v_1 that contains no circuit quantities other than i_s , v_s , R_1 , R_2 , and β , where $\beta > 0$.