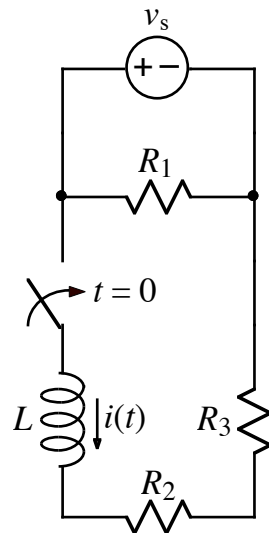



Ex:




After being open for a long time, the switch closes at $t = 0$. Write an expression for $i_L(t > 0)$ in terms of no circuit quantities other than R_1, R_2, R_3, v_s , and L .

sol'n: Since R_1 is directly across v_s , it is a 2nd circuit in parallel with the 1st circuit consisting of all components below it that is directly across v_s . Consequently, we can solve the circuits separately, as though each had its own v_s source. \therefore we ignore R_1 .

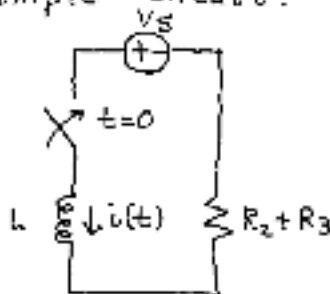We also combine R_2 and R_3 , yielding a simple circuit:




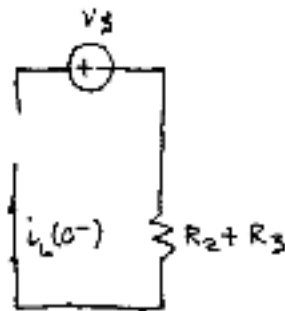$t=0^-$ model: $L = \text{wire}$, find $i_L(0^-)$




No current flows, owing to the open circuit.

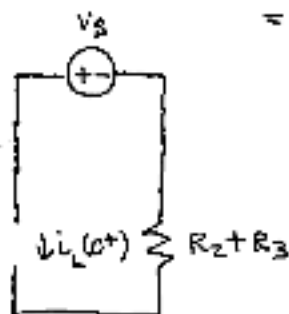$t=0^+$ model: $i_L(0^+) = i_L(0^-)$, $L = i$ source
 $= 0 \text{ A} = \text{open circuit}$




We have $i(0^+) = i_L(0^+) = i_L(0^-) = 0 \text{ A}$

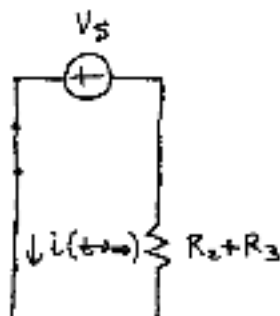$t \rightarrow \infty$ model: $L = \text{wire}$, find $i(t \rightarrow \infty)$



By Ohm's law, $i(t \rightarrow \infty) = \frac{V_S}{R_2 + R_3}$

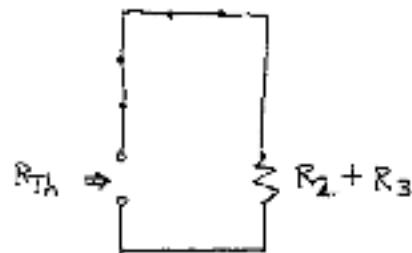$\tau = \frac{L}{R_{Th}}$: We find R_{Th} by turning off independent source V_S and looking into circuit from terminals where L is attached.



Clearly, $R_{Th} = R_2 + R_3$.

Now we use the general form of solution:

$$i(t) = i(t \rightarrow \infty) + [i(0^+) - i(t \rightarrow \infty)] e^{-t/\tau}, \quad t > 0$$

$$\text{or } i(t) = \frac{V_S}{R_2 + R_3} + \left[0 - \frac{V_S}{R_2 + R_3} \right] e^{-t/[L/(R_2 + R_3)]}, \quad t > 0$$

$$\text{or } i(t) = \frac{V_S}{R_2 + R_3} \left[1 - e^{-t(R_2 + R_3)/L} \right], \quad t > 0$$