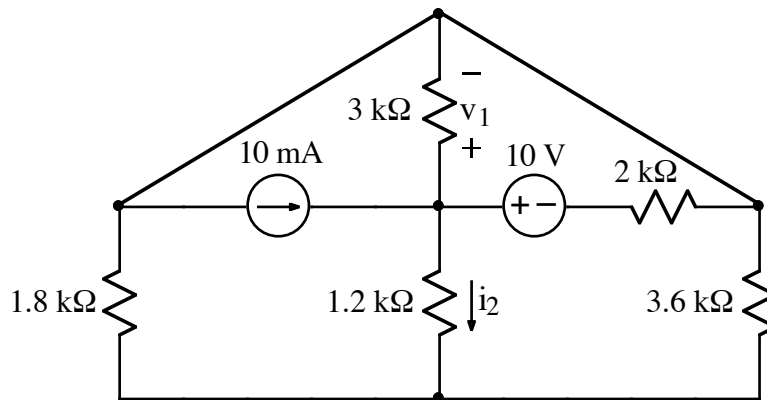


Ex:



- Use the node-voltage method to calculate v_1 and i_2 .
- Calculate the power in the $2\text{ k}\Omega$ resistor.

sol'n: Can put ref node where we like.
Putting ref at top is convenient for definition of v_1 . We note that all 3 nodes on top are the ref node.

$$v_1\text{-node eq'n: } \frac{v_1 - 0V}{3k\Omega} - 10mA + \frac{(v_1 - 10V) - 0V}{2k\Omega} + \frac{v_1 - v_2}{1.2k\Omega} = 0A$$

$$\text{or } v_1 \left(\frac{1}{3k\Omega} + \frac{1}{2k\Omega} + \frac{1}{1.2k\Omega} \right) + v_2 \left(\frac{-1}{1.2k\Omega} \right)$$

$$= 10mA + \frac{10V}{2k\Omega}$$

$$v_2\text{-node eq'n: } \frac{v_2 - 0V}{1.8k\Omega} + \frac{v_2 - v_1}{1.2k\Omega} + \frac{v_2 - 0V}{3.6k\Omega} = 0A$$

$$\text{or } v_1 \left(\frac{-1}{1.2k\Omega} \right) + v_2 \left(\frac{1}{1.8k\Omega} + \frac{1}{1.2k\Omega} + \frac{1}{3.6k\Omega} \right) = 0A$$

$$\text{consider } \frac{1}{3k\Omega} + \frac{1}{2k\Omega} + \frac{1}{1.2k\Omega} = \frac{1}{6k\Omega} (2+3+5) = \frac{10}{6k\Omega}$$

$$= \frac{5}{3k\Omega}$$

$$\text{and } \frac{1}{1.8k\Omega} + \frac{1}{1.2k\Omega} + \frac{1}{3.6k\Omega} = \frac{1}{7.2k\Omega} (4+6+2)$$

$$= \frac{12}{7.2k\Omega} = \frac{10}{6k\Omega} = \frac{5}{3k\Omega}$$

Our eqns become:

$$v_1 \left(\frac{5}{3k\Omega} \right) + v_2 \left(\frac{-1}{1.2k\Omega} \right) = 15mA$$

$$v_1 \left(\frac{-1}{1.2k\Omega} \right) + v_2 \left(\frac{5}{3k\Omega} \right) = 0mA$$

Mult both sides by $6k\Omega$:

$$v_1 (10) + v_2 (-5) = 90V$$

$$v_1 (-5) + v_2 (10) = 0V \quad \text{or } v_1 = 2v_2$$

$$2v_2 (10) + v_2 (-5) = 90V$$

$$15v_2 = 90V$$

$$v_2 = 6V \quad \text{and } v_1 = 12V$$

$$b) P_{2k\Omega} = (v_1 - 10V)^2 / 2k\Omega = 2mW$$