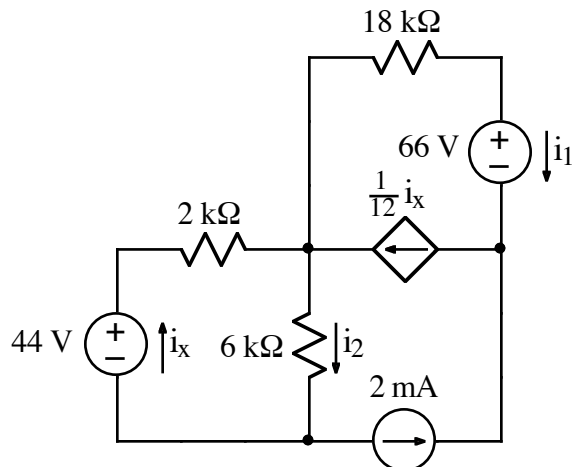


Ex:



- Use the mesh-current method to find  $i_1$  and  $i_2$ .
- Find the power dissipated by the dependent source.

sol'n: a)  $i_b = -2\text{mA}$  from  $2\text{mA}$  source on outside edge

$$i_x = i_c \quad (\text{dependent source})$$

Super mesh for  $i_a$  and  $i_b$  loops.

$i_a, i_b$  voltage loop for supermesh is not possible because of  $2\text{mA}$  source.

$\therefore$  we only have current eq'n for source between  $i_a$  and  $i_b$  loops:

$$\frac{1}{12} i_c = i_a - i_b = i_a + 2\text{mA}$$

V-loop for  $i_c$  gives

$$+44\text{V} - i_c 2\text{k}\Omega - i_c 6\text{k}\Omega + i_b 6\text{k}\Omega = 0\text{V}$$

---

$$\text{or } +i_c (2k\Omega + 6k\Omega) = +44V + (-2mA) 6k\Omega$$

$$\text{or } i_c = \frac{44V - 12V}{8k\Omega} = 4mA$$

$$\text{From earlier: } \frac{1}{12} i_c = i_a + 2mA$$

$$\text{or } i_a = \frac{i_c}{12} - 2mA = \frac{4mA}{12} - 2mA$$

$$i_a = -\frac{5}{3} mA$$

$$\text{Now we have } i_1 = i_a = -\frac{5}{3} mA$$

$$i_2 = i_c - i_b = 4mA - (-2mA) = 6mA$$

$$b) \quad p = i \cdot v = \frac{1}{12} i_c \cdot v_{\text{dep src}}$$

$$\text{From } i_a \text{ v-loop: } -i_a \cdot 18k\Omega - 66V - v_{\text{dep src}} = 0V$$

$$\text{or } v_{\text{dep src}} = -i_a \cdot 18k\Omega - 66V$$

$$= -\left(-\frac{5}{3}\right) \cdot 18k\Omega - 66V = -36V$$

$$p = \frac{1}{12} \cdot 4mA (-36V) = -12mW$$