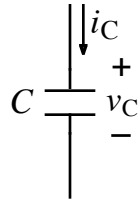
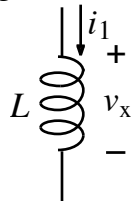


1. In (a)-(c), the voltage $v_C(t)$ across a $0.2 \mu\text{F}$ capacitor is listed. Find the current, $i_C(t)$, flowing in the capacitor in each case as a function of time:



- a) $v_C(t) = 3 \text{ V}$
- b) $v_C(t) = 1000t \text{ V/s}$
- c) $v_C(t) = 1 - e^{-t/4\text{ms}} \text{ V}$

2. In (a)-(c), the current $i_L(t)$ flowing into a 0.5 mH inductor is listed. Find the voltage, $v_L(t)$, across the inductor in each case as a function of time:



- a) $i_L(t) = 5 \text{ mA}$
- b) $i_L(t) = 5t \text{ mA/s}$
- c) $i_L(t) = 5 \sin(2\pi \cdot 100t) \text{ mA}$

3. The following equation describes the voltage, v_C , across a capacitor as a function of time. Find the time, t , at which v_C is equal to 2 V .

$$v_C(t) = 1 + 3(1 - e^{-t/8\text{ms}}) \text{ V}$$

4. The following equation describes the voltage, v_L , across an inductor as a function of time. Find an expression for the current, $i_L(t)$, through the inductor as a function of time. Assume that $i_L(t = 0) = 0 \text{ A}$.

$$v_L(t) = 2 + 6(1 - e^{-t/12.5\mu\text{s}}) \text{ kV}$$

5. Find the voltage, v_C , on the capacitor in the circuit below as a function of time if $v_C(t = 0) = 2.4 \text{ V}$.

