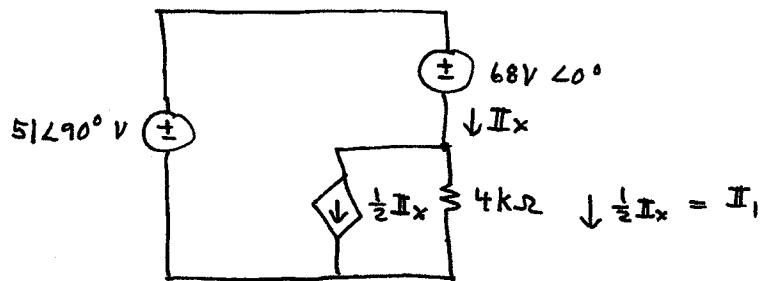


Sol'n: 3.a) The  $-j3k\Omega$  and  $j3k\Omega$  sum to zero and act like a wire. Thus, they do not affect  $\mathbb{I}_x$ . So we have:



Clearly,  $\frac{1}{2} \mathbb{I}_x$  flows thru the  $4k\Omega$  (for sum of currents at node above  $4k\Omega = 0$ ).

$$\text{But the current thru } 4k\Omega \text{ is } \frac{51 \angle 90^\circ V - 68 \angle 0^\circ V}{4k\Omega}$$

$$\text{or } \frac{1}{2} \mathbb{I}_x = \mathbb{I}_1 = \frac{17 \cdot 3 \angle 90^\circ - 17 \cdot 4 \angle 0^\circ V}{4k\Omega}$$

$$\mathbb{I}_1 = 17 \frac{j3 - 4}{4k\Omega} = \frac{17}{4} (-4 + j3) = \frac{17 \cdot 5}{4} \angle 143^\circ \text{ mA}$$

$$\boxed{\mathbb{I}_1 = -17 + j12.75 \text{ mA} = 21.25 \angle 143^\circ \text{ mA}}$$

b)

$$i_1(t) = 17 \cos(\pi t + 180^\circ) - 12.75 \sin(\pi t) \text{ mA}$$

$$" = 21.25 \cos(\pi t + 143^\circ) \text{ mA}$$