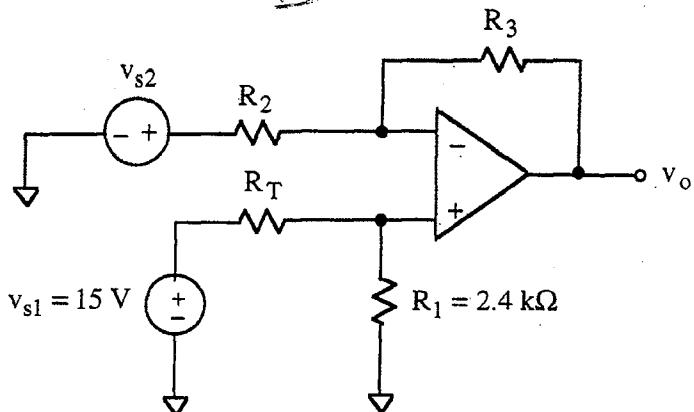


1. (70 points)

Rail voltage = ± 15 V

~~Design an electronic thermometer using the circuit diagram shown above. The voltage v_o is used to indicate temperature. Use a thermister with a resistance described by~~

~~$$R_T = R_0 e^{1120 \left(\frac{1}{T} - \frac{1}{300} \right)}$$~~

~~where $R_0 = 2490 \Omega$ and T is temperature in $^{\circ}\text{K}$.~~

Pts10. a. Calculate the numerical values of $R_T(273^{\circ}\text{K})$ and $R_T(373^{\circ}\text{K})$.25 b. Derive a symbolic expression for v_o . The expression must contain not more than the parameters v_{s1} , v_{s2} , R_T , R_1 , R_2 , and R_3 .

Hint: Use superposition.

25 c. Choose v_{s2} , R_2 , and R_3 that will produce the following:

~~$$\begin{aligned} v_o &= 0 \text{ V} && \text{when } T = 273^{\circ}\text{K} \\ v_o &= 10 \text{ V} && \text{when } T = 373^{\circ}\text{K} \end{aligned}$$~~

10 d. Using the component values you chose in (c), calculate v_o when $T = 323^{\circ}\text{K}$.

sol'n 1.a)

$$R_T(273^\circ\text{K}) = 2490 \times \frac{1}{273} - \frac{1}{300} = 3.6 \text{ k}\Omega$$

$$R_T(373^\circ\text{K}) = 2490 \times \frac{1}{373} - \frac{1}{300} = 1.2 \text{ k}\Omega$$

$R_T(273^\circ\text{K}) = 3.6 \text{ k}\Omega$

$R_T(373^\circ\text{K}) = 1.2 \text{ k}\Omega$

b) Superposition:

$$V_{S1} \text{ on}, V_{S2} \text{ off} \Rightarrow V_p = V_{S1} \cdot \frac{R_1}{R_1 + R_T}, \quad V_h = V_p$$

$$i_f (\text{thru } R_2) = \frac{0 - V_h}{R_2} = -V_{S1} \frac{R_1}{R_1 + R_T} \frac{1}{R_2}$$

$$i_f (\text{thru } R_3) = \frac{V_h - V_{O1}}{R_3} = -V_{S1} \frac{R_1}{R_1 + R_T} \frac{1}{R_3}$$

$$i_f (\text{thru } R_2) = i_f (\text{thru } R_3) \Rightarrow -\frac{V_h}{R_2} = \frac{V_h - V_{O1}}{R_3}$$

$$\text{or } V_{O1} = V_h \left(1 + \frac{R_3}{R_2}\right) = V_{S1} \frac{R_1}{R_1 + R_T} \left(1 + \frac{R_3}{R_2}\right)$$

$$V_{S1} \text{ off}, V_{S2} \text{ on} \Rightarrow V_p = 0V, \quad V_h = V_p$$

$$i_f (\text{thru } R_2) = \frac{V_{S2}}{R_2} \quad i_f (\text{thru } R_3) = -\frac{V_{O2}}{R_3}$$

$$i_f (\text{thru } R_2) = i_f (\text{thru } R_3) \Rightarrow V_{O2} = -V_{S2} \frac{R_3}{R_2}$$

$$V_o = V_{O1} + V_{O2}$$

$$V_o = V_{S1} \frac{R_1}{R_1 + R_T} \left(1 + \frac{R_3}{R_2}\right) - V_{S2} \frac{R_3}{R_2}$$

c) At 273°K , $V_{S1} \frac{R_1}{R_1 + R_T} = 15V \frac{2.4 \text{ k}\Omega}{2.4 \text{ k}\Omega + 3.6 \text{ k}\Omega} = 15V \cdot \frac{2}{5} = 6V = V_p$

At 373°K , $V_{S1} \frac{R_1}{R_1 + R_T} = 15V \frac{2.4 \text{ k}\Omega}{2.4 \text{ k}\Omega + 1.2 \text{ k}\Omega} = 15V \cdot \frac{2}{3} = 10V = V_p$

$$V_o = V_p \left(1 + \frac{R_3}{R_2}\right) - V_{S2} \frac{R_3}{R_2}$$

proportional
to V_p

The change in V_o vs change in V_p :

$$\Delta V_o = \Delta V_p \left(1 + \frac{R_3}{R_2}\right)$$

$$\Delta V_p = V_p(373^\circ\text{K}) - V_p(273^\circ\text{K}) = 10V - 6V = 4V$$

$$\Delta V_o = V_o(373^\circ\text{K}) - V_o(273^\circ\text{K}) = 10V - 0V = 10V$$

from prob
statement

Sol(n 1.c) cont.

$$AV_o = AV_p \left(1 + \frac{R_3}{R_2}\right) \quad \text{or} \quad 10V = 4V \left(1 + \frac{R_3}{R_2}\right)$$

$$\therefore 1 + \frac{R_3}{R_2} = 2.5 \quad \text{or} \quad \frac{R_3}{R_2} = 1.5$$

Let $R_3 = 15\text{ k}\Omega$, $R_2 = 10\text{ k}\Omega$.

$$V_o(273^\circ\text{K}) = 0V = V_p \left(1 + \frac{R_3}{R_2}\right) - V_{S2} \frac{R_3}{R_2} = 6V(2.5) - V_{S2}(1.5)$$

from prob statement

$$\text{or } V_{S2} = \frac{6(2.5)V}{1.5} \quad \text{or} \quad V_{S2} = 10V$$

d) $R_T(323^\circ\text{K}) = 2490 e^{1120 \left(\frac{1}{323} - \frac{1}{300}\right)} = 1.9\text{ k}\Omega$


$$V_p = 15V \cdot \frac{2.4\text{ k}\Omega}{2.4\text{ k}\Omega + 1.9\text{ k}\Omega} = 8.37V$$

$$V_o = V_p \left(1 + \frac{R_3}{R_2}\right) - V_{S2} \frac{R_3}{R_2} = 8.37(2.5) - 10(1.5) V$$

$$V_o(323^\circ\text{K}) = 5.9V$$

off by 18% from linear value
of 5V.

1. (75 points)

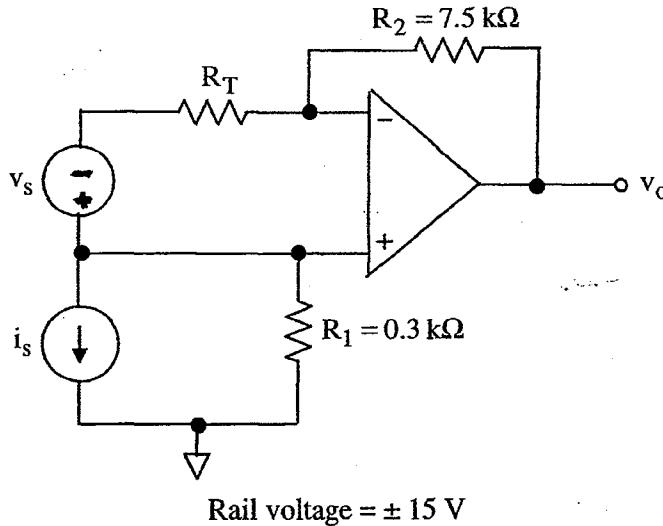

Design an electronic thermometer using the circuit diagram shown above. The voltage v_o is used to indicate temperature. Use a thermister with a resistance described by

$$R_T = R_0 e^{\beta \left(\frac{1}{T} - \frac{1}{300} \right)}$$

where $R_0 = 2.625$ kΩ, $\beta = 1200^\circ\text{K}$, and T is temperature in $^\circ\text{K}$.


Pts

- 30 a. Derive a symbolic expression for v_o . The expression must contain not more than the parameters i_s , V_s , R_1 , R_2 , and R_T . Hint: Use superposition.
- 10 b. Calculate the numerical values of R_T (273°K) and R_T (373°K).
- 15 c. Determine a value for v_s such that $v_o(T = 373^\circ\text{K}) - v_o(T = 273^\circ\text{K}) = 1\text{V}$
- 10 d. Using your answer to (c), determine a value of i_s such that
 $v_o(T = 273^\circ\text{K}) = 0\text{ V}$.
- 10 e. Using the component values you chose above, calculate v_o when $T = 323^\circ\text{K}$. Make a rough sketch of v_o vs. T on the basis of the values when $T = 273^\circ\text{K}$, 323°K , and 373°K . On the same axes, sketch the ideal linear response.

(4)

Sol'n: 1.a) Use superposition

Case I: v_s on, i_s off = open

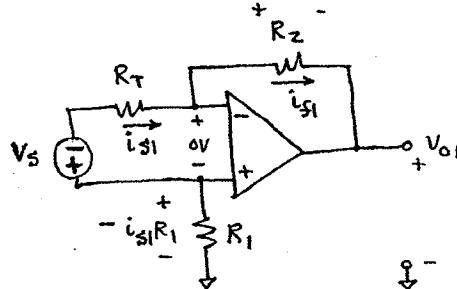

Negative feedback \Rightarrow OV across + and - terminals.

From v loop around v_s , R_T , and + - terminals,

$$\text{we have } i_{s1} = -\frac{v_s}{R_T}.$$

From v loop around R_1 , + - terminals, R_2 , and v_o ,


$$\text{we have } -i_{s1}R_1 + \text{OV} - i_{s1}R_2 - v_o = \text{OV}$$

Now use $i_{s1} = i_{f1}$ and solve for v_o :

$$-\frac{v_s}{R_T} R_1 + \text{OV} - \frac{v_s R_2}{R_T} - v_o = \text{OV}$$

$$v_o = v_s \frac{R_1 + R_2}{R_T}$$

Case II: i_s on, v_s off = wire

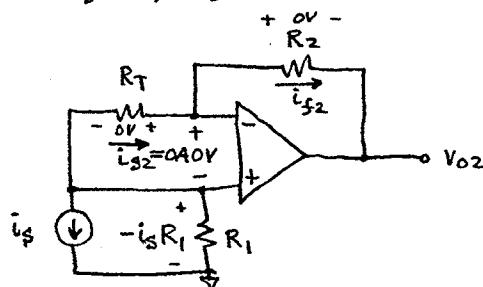

We OV across $R_T \Rightarrow i_s = 0$.

Since $i_{s2} = i_{f2} = 0A$, we have $v_{o2} = v_- = v_+$

$$v_+ = -i_s R_1 \Rightarrow v_{o2} = -i_s R_1$$

Sum

$$v_o = v_{o1} + v_{o2} = v_s \frac{R_1 + R_2}{R_T} - i_s R_1$$

sol'n: 1. b)

$$R_T(273\text{ K}) = 2.625 \text{ k}\Omega$$

$$1200\text{ K} \left(\frac{1}{273\text{ K}} - \frac{1}{300\text{ K}} \right)$$

$$R_T(273\text{ K}) \doteq 3.9 \text{ k}\Omega$$

$$R_T(373\text{ K}) = 2.625 \text{ k}\Omega$$

$$1200\text{ K} \left(\frac{1}{373\text{ K}} - \frac{1}{300\text{ K}} \right)$$

$$R_T(373\text{ K}) \doteq 1.2 \text{ k}\Omega$$

$$\begin{aligned}
 \text{c) } IV &= V_o(373\text{ K}) - V_o(273\text{ K}) = V_S \frac{(R_1 + R_2)}{R_T(373\text{ K})} - i_S R_1 \\
 &\quad - \left(V_S \frac{R_1 + R_2}{R_T(273\text{ K})} - i_S R_1 \right) \\
 &= V_S (R_1 + R_2) \left(\frac{1}{R_T(373\text{ K})} - \frac{1}{R_T(273\text{ K})} \right) \\
 &= V_S \underbrace{(0.3 \text{ k}\Omega + 7.5 \text{ k}\Omega)}_{7.8 \text{ k}\Omega} \left(\frac{1}{1.2 \text{ k}\Omega} - \frac{1}{3.9 \text{ k}\Omega} \right) \\
 V_S &= \frac{1.2 \text{ k}\Omega \parallel (-3.9 \text{ k}\Omega)}{7.8 \text{ k}\Omega} V = \frac{0.3 \text{ k}\Omega \cdot 4 \parallel -13}{0.3 \text{ k}\Omega \cdot 26} V = \frac{-4 \parallel 13}{(4-13) \cdot 26} V
 \end{aligned}$$


$$V_S = \frac{2}{9} V$$

$$\text{d) } OV = V_o(273\text{ K}) = V_S \frac{R_1 + R_2}{R_T(273\text{ K})} - i_S R_1 = \frac{2}{9} V \frac{7.8 \text{ k}\Omega}{3.9 \text{ k}\Omega} - i_S 0.3 \text{ k}\Omega$$


$$i_S 0.3 \text{ k}\Omega = \frac{4}{9} V \Rightarrow i_S = \frac{4}{9} \frac{1V}{0.3 \text{ k}\Omega} = \frac{4}{2.7} \text{ mA}$$

$$i_S \doteq 1.48 \text{ mA} \approx 1.5 \text{ mA}$$
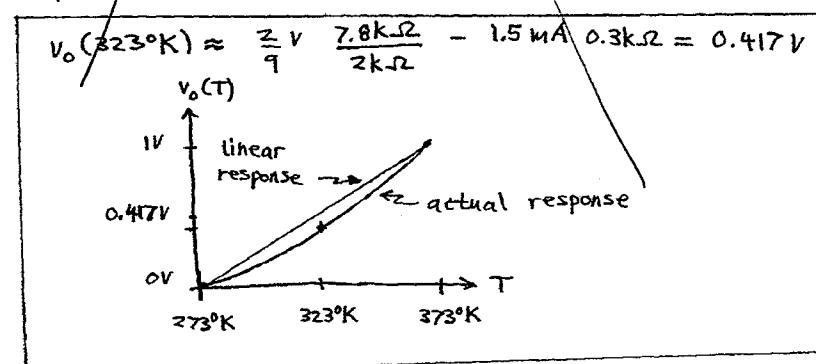
$$\text{e) } R_T(323\text{ K}) = 2.625 \text{ k}\Omega \text{ e } 1200\text{ K} \left(\frac{1}{323\text{ K}} - \frac{1}{300\text{ K}} \right) = 1.97 \text{ k}\Omega \approx 2 \text{ k}\Omega$$



sol(n: 1.a)

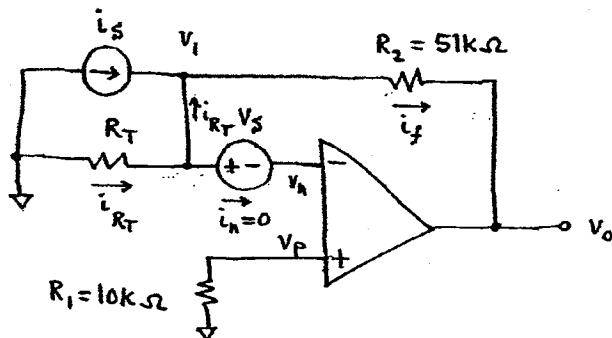

- Find v_p : $v_p = 0V$ since no current in R_1 , so no v-drop for R_1

$$v_h = v_p = 0V$$

- Find i_f on left side (total current into v_i node from i_s and R_T)

$$v_i = v_h + v_S = v_S, \text{ and no current flows thru } v_S \text{ since no current flows into op-amp.}$$

$$\therefore i_f \text{ on left side} = i_s + i_{R_T} = i_s + \frac{0 - v_i}{R_T} = i_s + \frac{-v_S}{R_T}$$

- Find i_f on right side

$$i_f \text{ on right side} = \frac{v_i - v_o}{R_2} = \frac{v_S - v_o}{R_2}$$

- Set i_f on left side = i_f on right side

$$i_s - \frac{v_S}{R_T} = \frac{v_S - v_o}{R_2} \quad \text{or} \quad v_o = v_S \left(1 + \frac{R_2}{R_T} \right) - i_s R_2$$

verify: Superposition $v_S = 0 \Rightarrow i_{R_T} = 0 \Rightarrow v_o = 0V - i_s R_2 \checkmark$

$$i_s = 0 \quad i_{R_T} = -\frac{v_S}{R_T} = i_f = \frac{v_S - v_o}{R_2}$$

Same as having $v_p = v_S \quad v_o = v_S \left(1 + \frac{R_2}{R_T} \right) \checkmark$


UNIVERSITY OF UTAH
ELECTRICAL AND COMPUTER ENGINEERING DEPARTMENT

ECE 1000

HOMEWORK #9

Spring 2005

1.

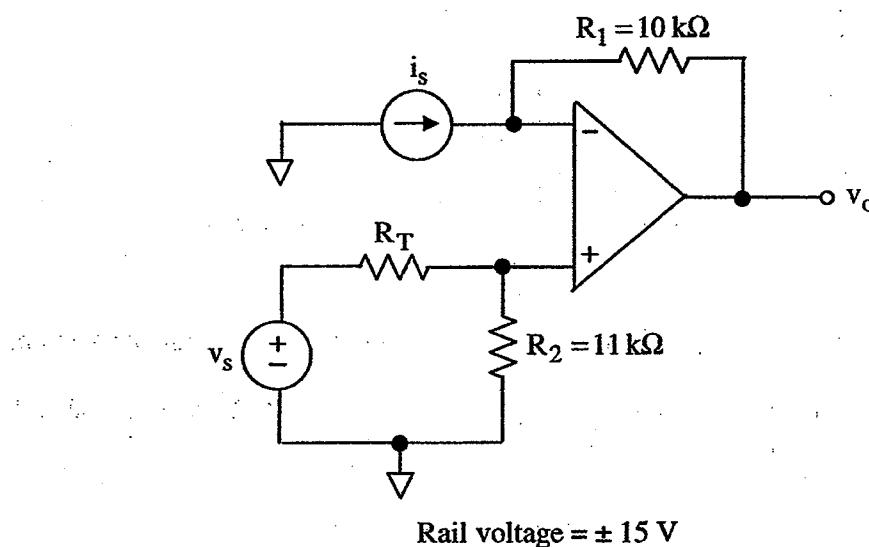


Design an electronic thermometer using the circuit diagram shown above. The voltage v_o is used to indicate temperature. Use a thermister with a resistance described by

$$R_T = R_0 e^{\left(\frac{1}{T} - \frac{1}{300}\right)}$$

where $R_0 = 12.25 \text{ k}\Omega$, $\beta = 170^\circ\text{K}$, and T is temperature in $^\circ\text{K}$. Derive a symbolic expression for v_o . The expression must contain not more than the parameters i_s , V_s , R_1 , R_2 , and R_T . Hint: Use superposition.

2. a. Calculate the numerical values of $R_T(273^\circ\text{K})$ and $R_T(373^\circ\text{K})$.
- b. Determine a value for v_s such that $v_o(T=373^\circ\text{K}) = v_o(T=273^\circ\text{K}) = 1\text{V}$
- c. Using your answer to (c), determine a value of i_s such that $v_o(T=273^\circ\text{K}) = 0\text{ V}$.
- d. Using the component values you chose above, calculate v_o when $T = 323^\circ\text{K}$. Make a rough sketch of v_o vs. T on the basis of the values when $T = 273^\circ\text{K}$, 323°K , and 373°K . On the same axes, sketch the ideal linear response.

sol'n: 1.

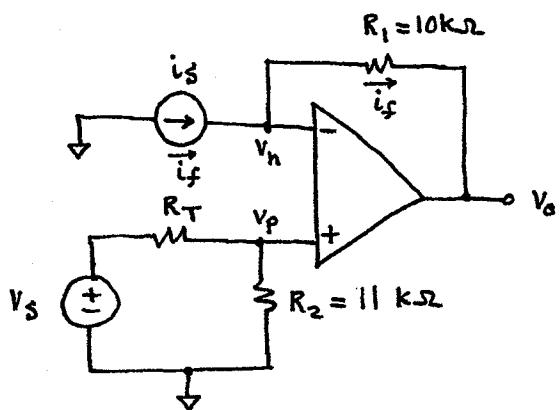Find V_p :

$$V_p = V_s \frac{R_2}{R_2 + R_T} \quad \text{V-divider}$$

$$V_h = V_p$$

Find i_f on left: $i_f = i_S$ Find i_f on right: $i_f = \frac{V_h - V_0}{R_1}$ Set i_f 's equal and use $V_h = V_p$

$$i_S = \frac{V_h - V_0}{R_1} \quad \text{or} \quad V_0 = V_h - i_S R_1$$

$$V_0 = V_s \frac{R_2}{R_2 + R_T} - i_S R_1$$

2.a) $R_T(273^\circ\text{K}) = 12.25 \text{ k}\Omega \cdot e^{170^\circ\text{K} \left(\frac{1}{273^\circ\text{K}} - \frac{1}{300^\circ\text{K}} \right)} = 13 \text{ k}\Omega$

$$R_T(373^\circ\text{K}) = 12.25 \text{ k}\Omega \cdot e^{170^\circ\text{K} \left(\frac{1}{373^\circ\text{K}} - \frac{1}{300^\circ\text{K}} \right)} = 11 \text{ k}\Omega$$

$$\boxed{R_T(273^\circ\text{K}) = 13 \text{ k}\Omega}$$

$$\boxed{R_T(373^\circ\text{K}) = 11 \text{ k}\Omega}$$


b) $\Delta V = V_0(373^\circ\text{K}) - V_0(273^\circ\text{K}) = V_s \frac{R_2}{R_2 + R_T(373^\circ\text{K})} - i_S R_1$

$$- \left(V_s \frac{R_2}{R_2 + R_T(273^\circ\text{K})} - i_S R_1 \right)$$

$$\Delta V = V_s \cdot 11 \text{ k}\Omega \cdot \left(\frac{1}{11 \text{ k}\Omega + 11 \text{ k}\Omega} - \frac{1}{11 \text{ k}\Omega + 13 \text{ k}\Omega} \right)$$

$$\boxed{V_s = \frac{\Delta V}{11 \text{ k}\Omega} \frac{22 \text{ k}\Omega \cdot 24 \text{ k}\Omega}{24 \text{ k}\Omega - 22 \text{ k}\Omega} = 24 \text{ V}}$$

1. (75 points)

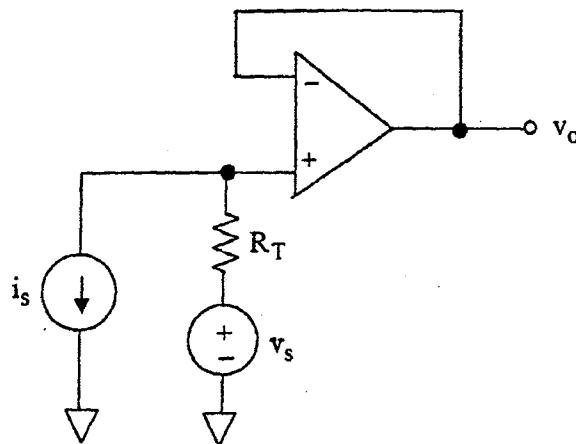

Rail voltage = ± 15 V


Design an electronic thermometer using the circuit diagram shown above. The voltage v_o is used to indicate temperature. Use a thermister with a resistance described by

$$R_T = R_0 e^{\beta \left(\frac{1}{T} - \frac{1}{300} \right)}$$

where $R_0 = 2.8 \text{ k}\Omega$, $\beta = 1300^\circ\text{K}$, and T is temperature in $^\circ\text{K}$.

- Pts 6
30 a. Derive a symbolic expression for v_o . The expression must contain not more than the parameters i_s , V_s , and R_T . Hint: Use superposition.
- 10 b. Calculate the numerical values of R_T (273°K) and R_T (373°K).
- 15 c. Determine a value for i_s such that $v_o(T = 373^\circ\text{K}) - v_o(T = 273^\circ\text{K}) = 1\text{V}$
- 10 d. Using your answer to (c), find the numerical value of V_s such that $v_o(T = 273^\circ\text{K}) = 0\text{ V}$.
- 10 e. Using the component values you chose above, calculate v_o when $T = 323^\circ\text{K}$. Make a rough sketch of v_o vs. T on the basis of the values when $T = 273^\circ\text{K}$, 323°K , and 373°K . On the same axes, sketch the ideal linear response.

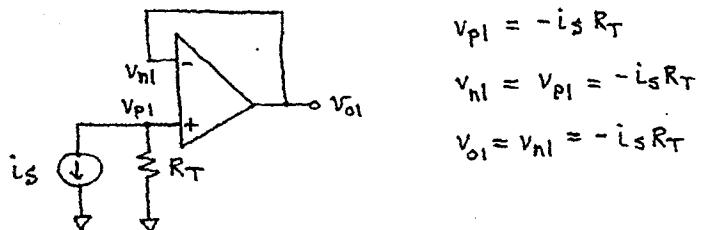sol'n: 1.a) Superposition case I: i_S on, v_S off = wire




$$v_{P1} = -i_S R_T$$

$$v_{N1} = v_{P1} = -i_S R_T$$

$$v_{O1} = v_{N1} = -i_S R_T$$

case II: i_S off = open, v_S on

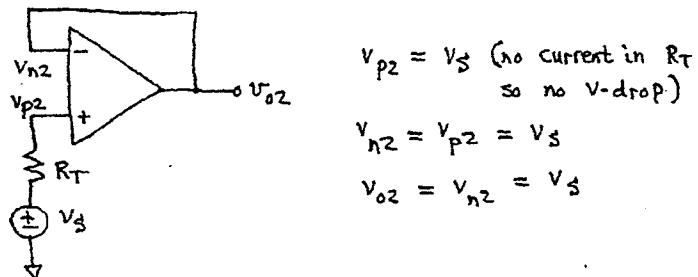

$$v_{P2} = v_S \text{ (no current in } R_T \text{ so no V-drop)}$$

$$v_{N2} = v_{P2} = v_S$$

$$v_{O2} = v_{N2} = v_S$$

$$v_o = v_{O1} + v_{O2}$$

$$v_o = -i_S R_T + v_S$$

b) $R_T(273^\circ\text{K}) = 2.8 \text{ k}\Omega$ $\frac{1}{R_T} = \frac{1}{273^\circ\text{K}} - \frac{1}{300^\circ\text{K}}$

$$R_T(273^\circ\text{K}) = 4.3 \text{ k}\Omega$$

$$R_T(373^\circ\text{K}) = 2.8 \text{ k}\Omega$$

$$R_T(373^\circ\text{K}) = 1.2 \text{ k}\Omega$$

c) Change in v_o : $\Delta v_o = -i_S \Delta R_T$ $\Delta \equiv \text{"change"}$
 (for $\Delta T = 100^\circ\text{K}$) $= 1V$ (desired). (v_S constant does not change with T)

$$\Delta R_T = 1.2 \text{ k}\Omega - 4.3 \text{ k}\Omega$$

$$\Delta R_T = -3.1 \text{ k}\Omega$$

$$\therefore i_S = \frac{-\Delta v_o}{\Delta R_T} = \frac{-1V}{-3.1 \text{ k}\Omega} = 0.323 \text{ mA}$$

$$i_S = 0.323 \text{ mA}$$

d) $v_o(273^\circ\text{K}) = 0V = -0.323 \text{ mA} \cdot 4.3 \text{ k}\Omega + v_S$
 $-i_S \cdot R_T$

$$\therefore v_S = 0.323 \text{ mA} \cdot 4.3 \text{ k}\Omega$$

$$v_S = 1.39 \text{ V or } 1.4 \text{ V}$$