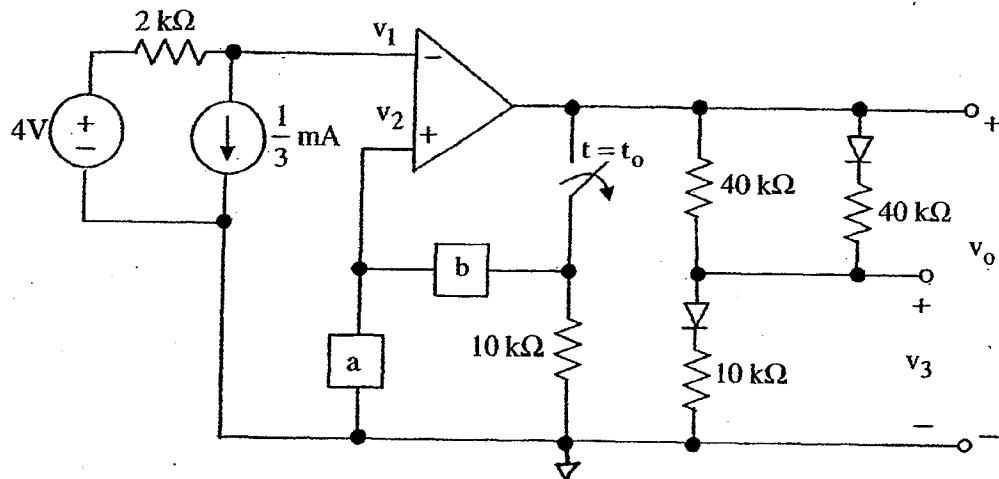
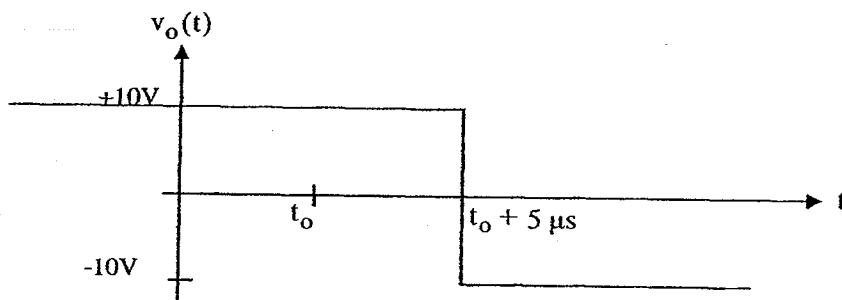


2.

Rail voltages = ± 10 VAfter being closed for a long time, the switch closes at $t = t_0$.

- Choose either an R or L to go in box a and either an R or L to go in box b to produce the $v_o(t)$ shown above. Specify which element goes in each box and its value.
- Sketch $v_1(t)$, showing numerical values appropriately.
- Sketch $v_2(t)$, showing numerical values appropriately.
- Sketch $v_3(t)$. Show numerical values for $t < t_0$, for $t_0 < t < t_0 + 5 \mu s$, and for $t_0 + 5 \mu s < t$. Use the ideal model of the diode: when forward biased, its resistance is zero; when reverse biased, its resistance is infinite.

Explain your work carefully.

HW #10 Cont.

ECE 1000


Su 05

Soln: 2.9) Consider possibilities.

$a=R$ and $b=R$ Doesn't work. v_2 would change at t_0 but never again. Delay of 5 μs not possible.

$a=L$ and $b=L$ Doesn't work. Before time t_0 , the L's look like wires and would short v_o to ref. But $v_o = \pm v_{rail} = \pm 10V$. Thus, we would have an invalid circuit.

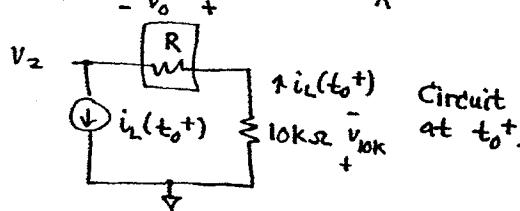$a=L$ and $b=R$ Before t_0 , the L looks like a wire, and $v_2 = 0V$. $i_L(t_0^-) = \frac{v_o}{R} = i_L(t_0^+)$.



At t_0^+ , the current in R will be $i_L(t_0^+) = i_L(t_0^-) = \frac{v_o}{R}$ or the same as at t_0^- . Thus, the v-drop for R at t_0^+ will be v_o . Current $i_L(t_0^+)$ flowing in the $10k\Omega$ will cause a voltage drop in series with the drop for R, resulting in a very negative voltage at v_2 . This would cause v_o to go low at $t = t_0^+$ rather than after a delay of 5 μs .
 \therefore This case doesn't work.

HW #10 Cont.

Su 05


ECE 1000

Sol'n: 2.a) cont.

$$a=R \text{ and } b=L$$

$$i_L(t_0^-) = \frac{v_0}{R} \text{ as in prev case.}$$
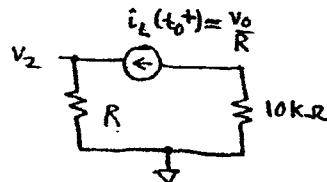
$$\text{At } t_0^+ \text{ with } i_L(t_0^+) = i_L(t_0^-) = \frac{v_0}{R} =$$



$$\text{we have } v_2(t_0^+) = \underbrace{\frac{v_0}{R}}_{i_L(t_0^+)} \cdot R = v_0.$$

So v_2 doesn't change immediately.
This will work!

For $t \rightarrow \infty$ we will have $v_2 = 0V$
since there is no power source.


Using the general formula for
 $v_2(t)$, we have:

$$v_2(t) = v_2(t \rightarrow \infty) + [v_2(t_0^+) - v_2(t \rightarrow \infty)] e^{-t/L_{TH}}$$

$\stackrel{0V}{\text{||}} \quad \stackrel{v_0}{\text{||}} \quad \stackrel{0V}{\text{||}}$

$$\text{where } R_{TH} = 10\text{k}\Omega + R$$

$$v_2(t) = v_0 e^{-t/L_{TH}}$$

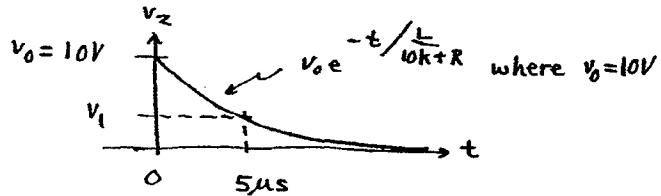

The output, v_0 , will drop at
 $t_0 + 5\mu\text{s}$ if $v_2(t_0 + 5\mu\text{s}) = v_1$.

[Assume $t_0 = 0$ for convenience.]


Now find v_1 .

HW #10 Cont.

ECE 1000

Su 05

sol'n: 2.a) cont.

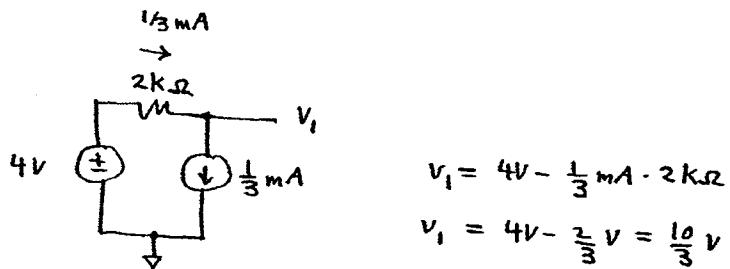

$$\therefore \text{we want } v_2(5\mu s) = v_1 = \frac{10}{3}V$$

$$\text{or } 10V e^{-\frac{5\mu s}{10k\Omega+R}} = \frac{10}{3}V$$

$$-\frac{5\mu s}{10k\Omega+R} = \ln \frac{1}{3} \doteq -1.1$$

$$\text{or } 5\mu s = 1.1 \frac{L}{10k\Omega+R}$$

If we use $R=12k\Omega$ we get a convenient value for L . Many solutions for R and L will work, however.


$$R=12k\Omega \text{ gives } L = 5\mu s \cdot \frac{10k\Omega + 12k\Omega}{1.1}$$

$$L = 5\mu s \cdot 20k\Omega = 100mH$$


$$R = 12k\Omega \quad L = 100mH$$

one solution
among many.

b)

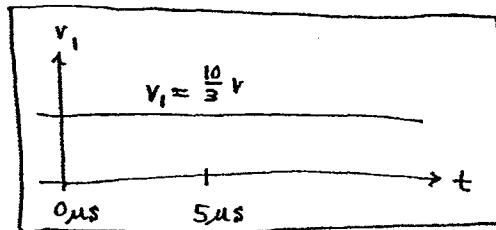

c)

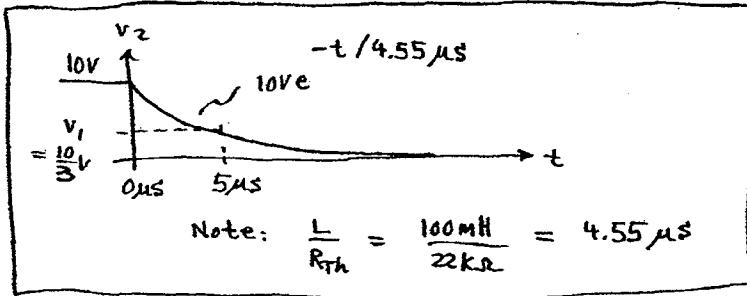


HW #10 Cont.


ECE 1000

Su 05

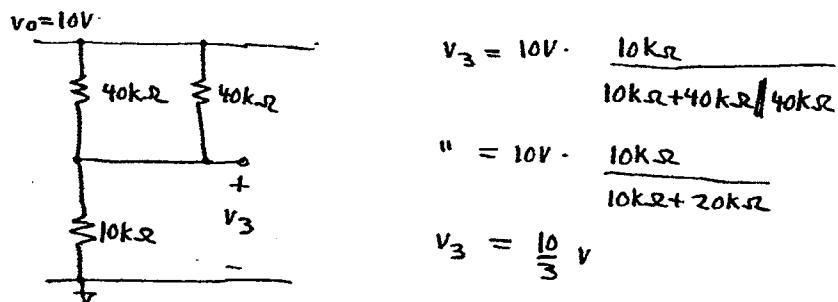Sol'n: 2.d) For $v_o = +10V$, both diodes are forward biased and look like wires.



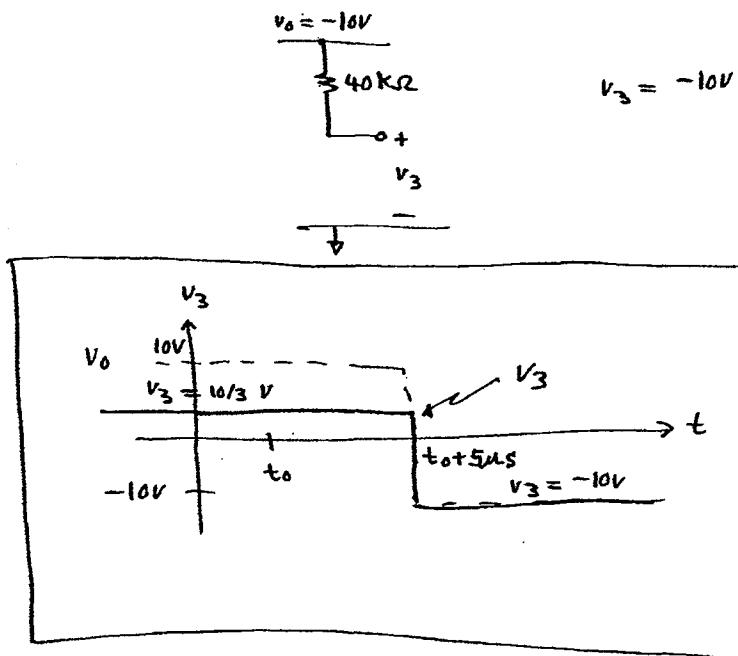For $v_o = -10V$, both diodes are reverse biased and look like open circuits.




UNIVERSITY OF UTAH
ELECTRICAL AND COMPUTER ENGINEERING DEPARTMENT

ECE 1000


HOMEWORK #10

Spring 2005

1.

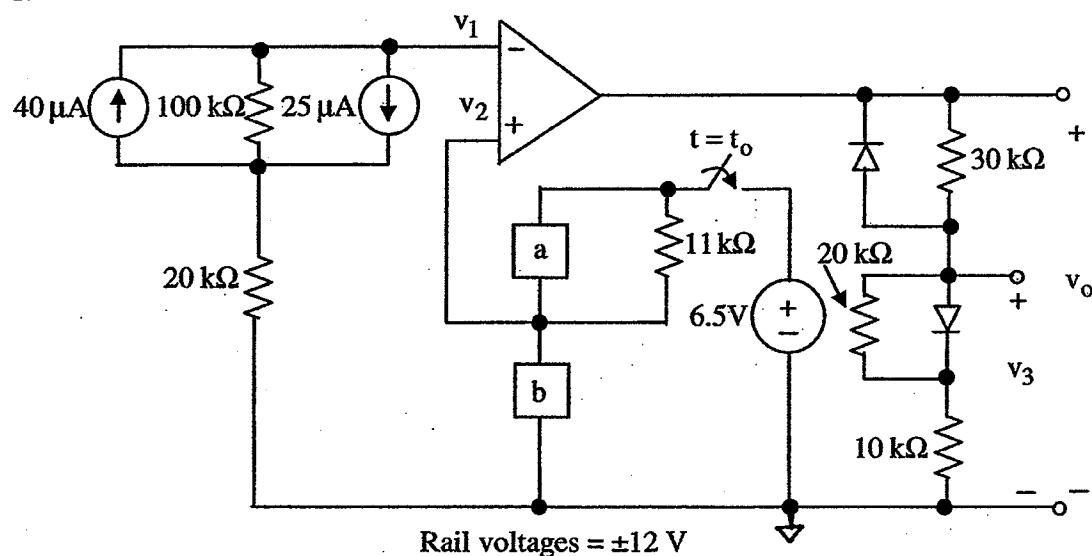

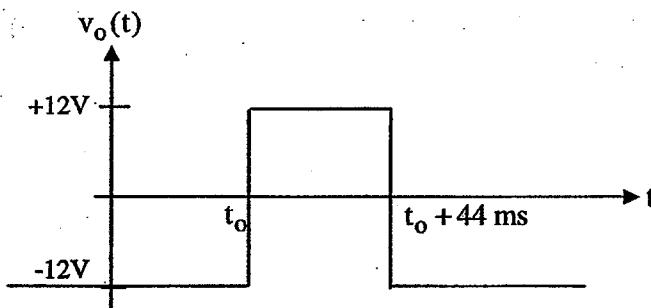After being open for a long time, the switch closes at $t = t_0$.



- a. Choose either an R or C to go in box a and either an R or C to go in box b to produce the $v_0(t)$ shown above. Specify which element goes in each box and its value. **Hint:** Use $v_2(t \rightarrow \infty) = 1V$
- b. Sketch $v_1(t)$, showing numerical values appropriately.
2. a. Sketch $v_2(t)$, showing numerical values appropriately.
- b. Sketch $v_3(t)$. Show numerical values for $t < t_0$, for $t_0 < t < t_0 + 44$ ms, and for $t_0 + 44$ ms $< t$. Use the ideal model of the diode: when forward biased, its resistance is zero; when reverse biased, its resistance is infinite.

Explain your work carefully.

sol'n: 1.a) Consider possibilities.

$a=R$ and $b=R$: v_2 would change at time $t=t_0$ but never change again. Thus, v_0 could not go high and then low again.

$a=C_1$ and $b=C_2$: Before $t=t_0$, there would be no path for C_2 in b to discharge. Thus, we would need to know $v_{C_2}(t=t_0^-)$. We would also have $v_{C_1}(t=t_0^-) = 0V$ since C_1 will discharge thru the R in parallel with it.

When the switch closes, we have an invalid circuit if $v_{C_2}(t_0^+) + v_{C_1}(t_0^+) \neq 6.5V$. This means we must have $v_{C_2}(t_0^+) = v_c(t_0^-) = 6.5V$ since $v_{C_1}(t_0^+) = v_c(t_0^-) = 0V$.

But if $v_{C_2}(t_0^+) = 6.5$, nothing changes when the switch closes. Thus, we could not get a waveform that goes high and then low again.

$a=R$ and $b=C$: As in the case of $a=C_1$ and $b=C_2$, we would have some value of $v_c(t_0^-) = v_c(t_0^+)$. Since $v_2 = v_c(t_0^+)$ at $t=t_0^+$, v_0 would not change at t_0 . Thus, this will not work.

$a=C$ and $b=R$: The C in a will discharge thru the R in parallel with it. $\therefore v_c(t_0^-) = 0V$. Also, no current flows in R for $t < t_0$ because there is no closed circuit path in which current could flow. Thus, $v_2(t_0^-) = i \cdot R = 0V$.

Sol'n: 1.a) cont.

At $t = t_0^+$, we have $v_2(t_0^+) = 6.5V - v_C(t_0^+)$

or $v_2(t_0^+) = 6.5V$ since $v_C(t_0^+) = v_C(t_0^-) = 0V$.

Thus, v_2 jumps from 0V to 6.5V at t_0 .

If $v_2(t_0^+) > v_1$, then v_o would go high,
(assuming $v_1 > 0V$ and $v_1 < 6.5V$).

After t_0 , C will charge and v_2 will start to drop. If v_2 eventually drops below v_1 , then v_o will go low again.

Thus, this will work.


Now find values of R and C:

v_1 : Since no current flows into the - input of the op amp, no current flows thru the $20k\Omega$ resistor (lower left).

Combining the parallel current sources, we have $40\mu A - 25\mu A = 15\mu A$. This current flows thru the $100k\Omega$ to produce voltage $15\mu A \cdot 100k\Omega = 1.5V$.

$$\therefore v_1 = 2.5V \text{ (constant)}$$

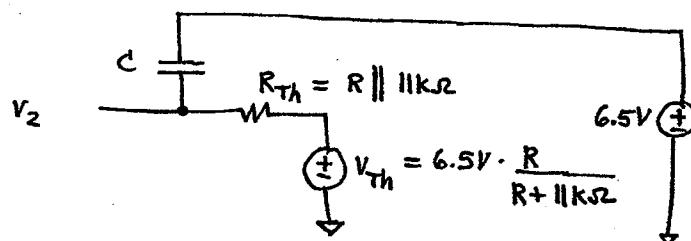v_2 : For $t > t_0$, we use a Thevenin equivalent circuit for the $6.5V$ source, the $11k\Omega$, and R in b.




Sol'n: 1.a) cont. We use the general RC sol'n for $v_2(t)$:

$$v_2(t) = v_2(t \rightarrow \infty) + [v_2(t_0^+) - v_2(t \rightarrow \infty)] e^{-t/R_{Th}C}$$

To find $v_2(t \rightarrow \infty)$, we observed that, when C is charged, no current flows in R_{Th} .

$$\text{Thus } v_2(t \rightarrow \infty) = V_{Th} = 6.5V \cdot \frac{R}{R+11k\Omega} < 6.5V.$$

From earlier, $v_2(t_0^+) = 6.5V$.

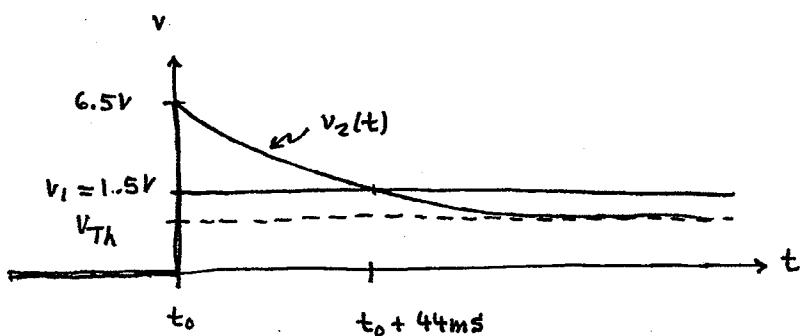

Any $V_{Th} < V_1$ will suffice. For convenience,

$$\text{let } V_{Th} = 1V = 6.5V \cdot \frac{R}{R+11k\Omega} \Rightarrow R = 2k\Omega$$

Assume $t_0 = 0$. For v_0 to switch at $t = 44ms$, we have $v_2(44ms) = V_1 = 1.5V$

$$\text{or } 1V + [6.5V - 1V] e^{-44ms/R_{Th}C} = 0.5V$$

$$\text{or } 5.5V e^{-44ms/R_{Th}C} = 0.5V \quad \text{where}$$

$$R_{Th} = R \parallel 11k\Omega = 2k \parallel 11k\Omega = \frac{22}{13} k\Omega.$$



Take \ln of both sides of exponential RC eqn:

$$-\frac{44ms}{\frac{22}{13} k\Omega \cdot C} = \ln \frac{0.5V}{5.5V} \doteq -2.39$$

$$C = \frac{2}{2.39} \frac{k\Omega}{13} \mu F = 10.9 \mu F$$

$$C = 11 \mu F$$

Sol'n: 1.b) $v_1(t) = 1.5V$ constant

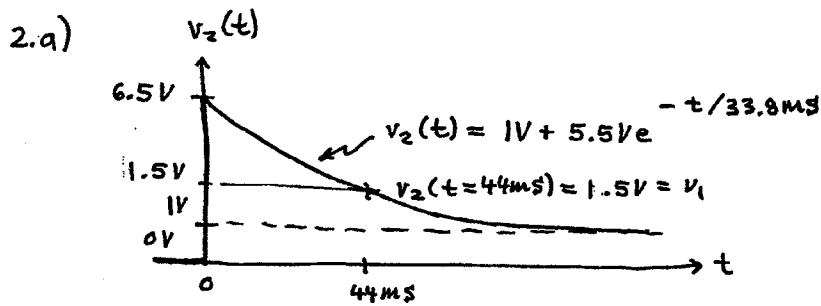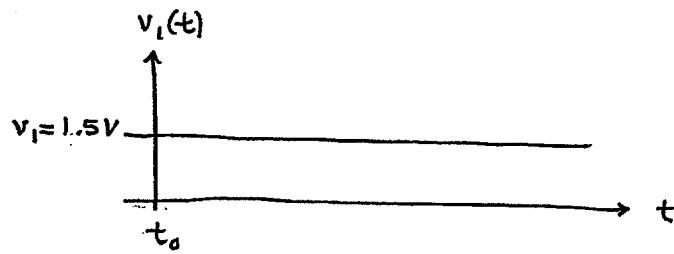


$$\text{Note: } R_{TH} C = \frac{22}{13} \text{ k}\Omega \cdot 20\mu\text{F} \doteq 33.8 \text{ ms}$$

Note: Assume $t_0 = 0$.

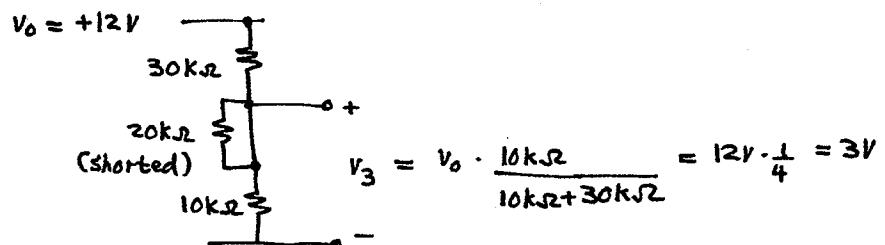
b) When $v_o = +12V$, top diode is reverse biased = open.

The bottom diode is forward biased = wire.




when $v_o = -12V$, top diode is forward biased = wire.


Thus, v_o is shorted to $-12V$.

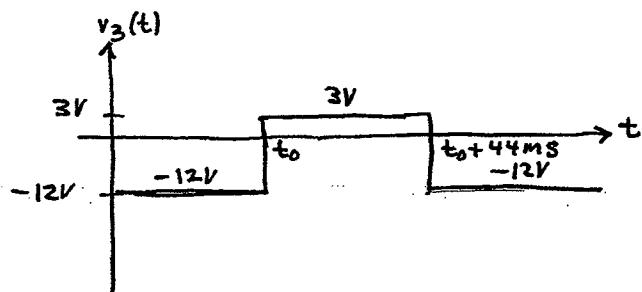

2. (65 points)

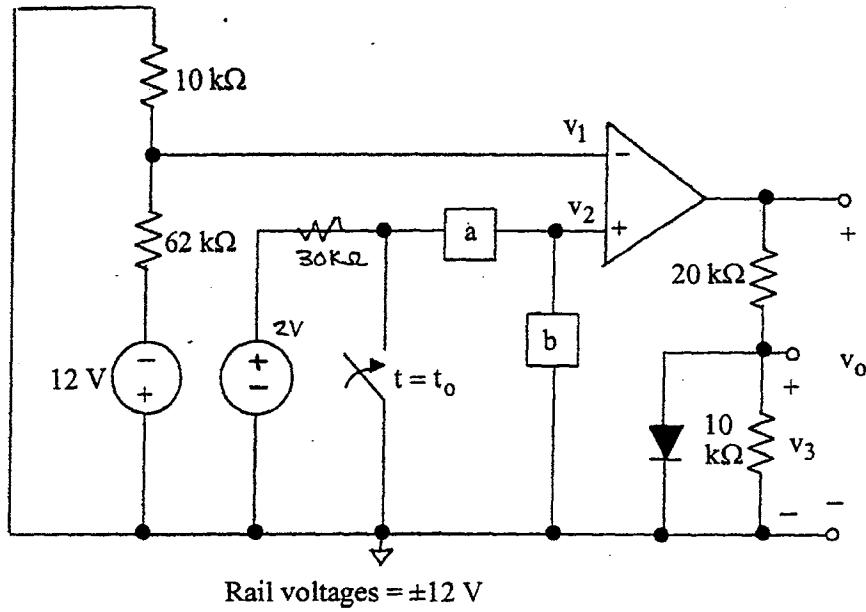

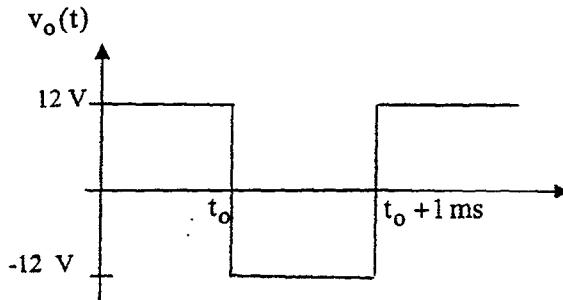After being open for a long time, the switch closes at $t = t_0$.



Pts

- 35 a. Choose either an R or C to go in box a and either an R or C to go in box b to produce the $v_0(t)$ shown above. Specify which element goes in each box and its value.
- 5 b. Sketch $v_1(t)$, showing numerical values appropriately.
- 15 c. Sketch $v_2(t)$, showing numerical values appropriately.
- 10 d. Sketch $v_3(t)$. Show numerical values for $t < t_0$, for $t_0 < t < t_0 + 1$ ms, and for $t > t_0 + 1$ ms. Use the ideal model of the diode: when forward biased, its resistance is zero; when reverse biased, its resistance is infinite.

sol'n: 2. a) At $t = t_0^-$: $v_1 = -12V \frac{10k\Omega}{10k\Omega + 6k\Omega} V\text{-divider}$

$$v_1 = -\frac{5}{3}V \quad \text{Actually, } v_1 = -\frac{5}{3}V \text{ for all } t$$

$$v_o = +12V \Rightarrow v_2 > v_1 = -\frac{5}{3}V$$

Consider $a=R, b=R$: v_o would never switch because v_2 would be $0V$ after switch closed, and $v_2 > v_1$ for all time. Will not work.

Consider $a=C, b=C$: C 's will charge to $v_{tot} = 2V$.

Part of $2V$ across a , part across b .

When switch closes, the C 's instantly charge to $v_{tot} = 2V$.

Then their voltages remain fixed.

$\therefore v_o$ would not switch after 1ms. Will not work.

Consider $a=R, b=C$: C will charge to $2V$. $v_2 = 2V$

When switch closes, v_2 will start at $0V$ and charge toward $2V$.


$v_2 > v_1$ for all time.

v_o never switches.

Will not work.


Consider $a=C, b=R$: C will charge to $2V$ at t_0^-
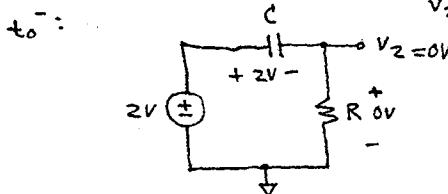
$$v_2 > v_1 \text{ so } v_o = +12V \text{ at } t_0^- \checkmark$$



When switch closes, v_C will stay at $2V$ for $t=t_0^+$:

t_0^+ :

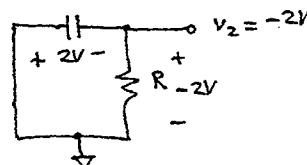

Thus, v_2 drops to $-2V$.


Then $v_2 < v_1$ and v_o drops to $-12V$. \checkmark

$t > t_0$: C charges to $0V$ and v_2 climbs toward $0V$.

We want $v_2 = v_1 = -\frac{5}{3}V$ at $t_0 + 1ms$. \checkmark

works

sol'n: 2.a) (cont.)

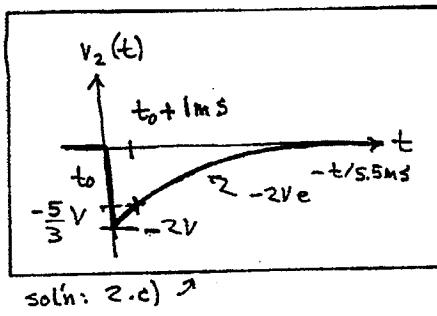

$$\text{Let } t_0 = 0 \quad -t/RC$$

$$v_2(t) = -2V e^{-t/RC}$$

$$v_2(1ms) = -2V e^{-1ms/RC} = -\frac{5}{3}V$$

$$e^{-1ms/RC} = \frac{5}{6}$$

$$-1ms/RC = \ln \frac{5}{6}$$

$$RC = -\frac{1ms}{\ln \frac{5}{6}} = 5.48ms$$

$$RC \approx 5.5 ms$$

Let $C = 1\mu F$, $R = 5.5k\Omega$ or $5.6k\Omega$ (standard value)


Any $RC = 5.5 ms$ acceptable if $1\mu F < C < 1F$
and $1\Omega < R < 1G\Omega$.

Note: If R is $\frac{1}{8}W$ then we would really want $\max i_R^2 R < \frac{1}{8}W$.

$$\max i_R^2 = \left(\frac{2V}{R}\right)^2 \Rightarrow \max i_R^2 R = \frac{4V^2}{R} < \frac{1}{8}W$$

$$\therefore R > \frac{4V^2}{1/8W} = 32\Omega \text{ required.}$$


2.b) $v_1 = -\frac{5}{3}V$ for all t

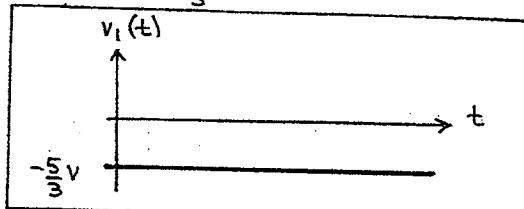

2.c) See plot of $v_2(t)$ in sol'n to 2.a), above.

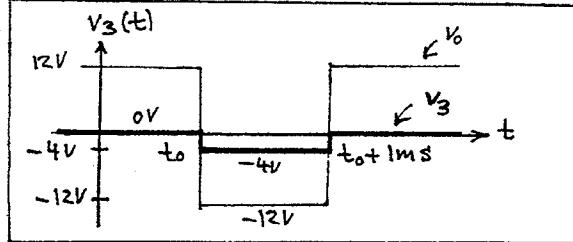
2.d) When $v_o > 0V$, diode forward biased = wire. $\therefore v_3 = 0V$

when $v_o < 0V$, diode reverse biased = open. $\therefore v_3 = v_o \frac{10k\Omega}{10k\Omega + 20k\Omega}$




$$v_3 = -12V \cdot \frac{1}{3} = -4V$$

2. (70 points)

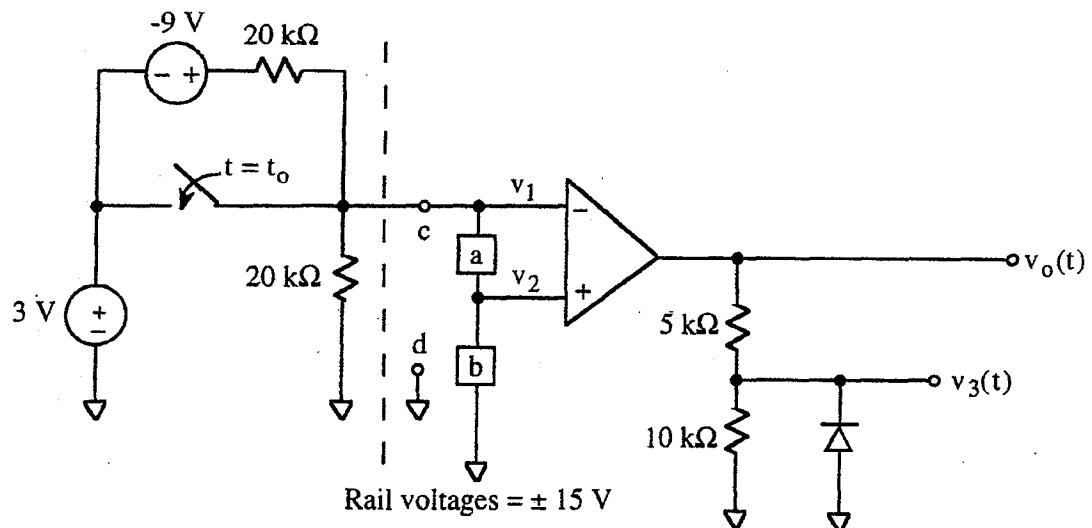

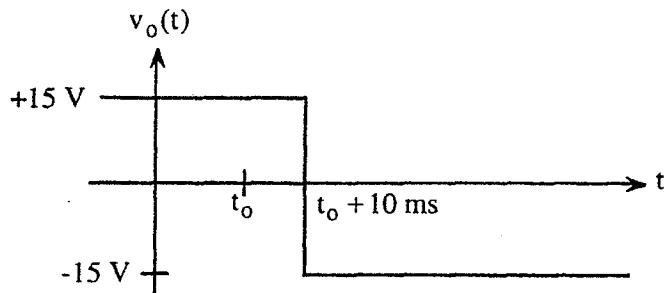After being open for a very long time, the switch closes at $t = t_0$.




Pts

- 10 a. Find the Thevenin equivalent of the circuit left of the dashed line with respect to terminals c, d for $t < t_0$.
- 10 b. Find the Thevenin equivalent of the circuit left of the dashed line with respect to terminals c, d for $t > t_0$.
- 20 c. Choose either an R or C to go in box a and either an R or C to go in box b to produce the $v_o(t)$ shown above. Specify which element goes in each box and its value.
- 20 d. Using the elements found in (b), sketch $v_2(t)$. Show numerical values appropriately.
- 10 e. Sketch $v_3(t)$. Show numerical values for $t < t_0$, $t_0 < t < t_0 + 10\text{ ms}$, and $t > t_0 + 10\text{ ms}$. Use the ideal model of the diode: when forward biased, its resistance is zero; when reverse biased, its resistance is infinite.

Explain your work carefully.

sol'n 2.4) $t < t_0$ switch is open

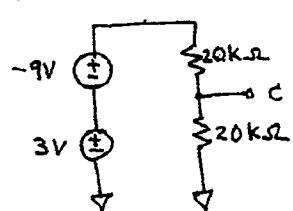


$$V_{Th} = (3V - 9V) \frac{20k\Omega}{20k\Omega + 20k\Omega} = -6V \cdot \frac{1}{2} = -3V$$


C use V-divider

$$R_{Th} = R \text{ looking into } C \text{ with } V \text{ sources shorted}$$
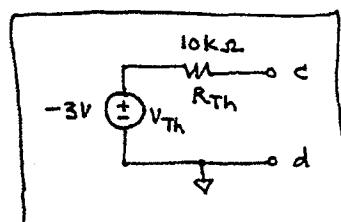
$$= 20k\Omega \parallel 20k\Omega = 10k\Omega$$



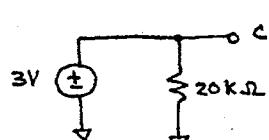
b) $t > t_0$ switch is closed ($-9V$ source and $20k\Omega$ bypassed)



$$V_{Th} = 3V \text{ since } C \text{ connected to } 3V \text{ source}$$

$$R_{Th} = R \text{ looking into } C \text{ with } 3V \text{ source shorted}$$
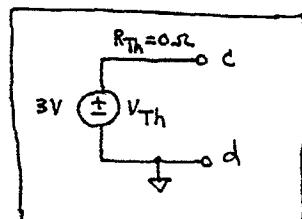
$$= 0\Omega \text{ (20k}\Omega \text{ bypassed by short)}$$




c) R in a and C in b would immediate switching: wrong

\therefore C in a and R in b must be correct.

$t < t_0$ circuit:

$(t = t_0^-)$

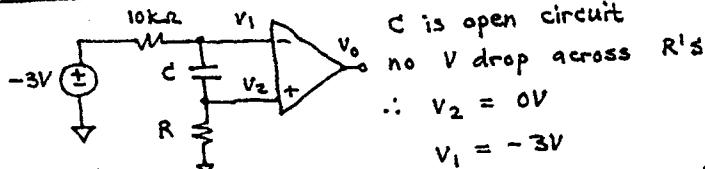


C is open circuit
no V drop across R's
 $\therefore V_2 = 0V$

$$V_1 = -3V$$

$$V_1 < V_2 \Rightarrow V_o = +15V \text{ (rail)}$$

$t = t_0^+$ circuit:

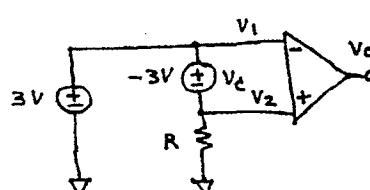


C acts like $-3V$ source

$$\therefore V_1 = 3V$$

$$V_2 = 3V - -3V = 6V$$

$$V_1 < V_2 \Rightarrow V_o = +15V \text{ (rail)}$$

$t \rightarrow \infty$ circuit:

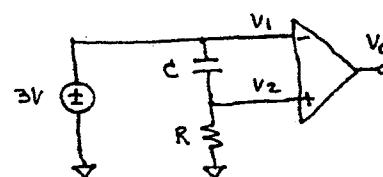

C acts like open circuit
no V drop across R

$$\therefore V_1 = 3V$$

$$V_2 = 0V$$

$$V_1 > V_2 \Rightarrow V_o = -15V \text{ (rail)}$$

sol'n 2.c) cont. Let $t_0 = 0$. Want $v_1 = v_2$ at $\Delta t \approx 10ms$ for v_o transition.

$$v_1 = 3V \text{ for } t > t_0 = 0$$

$$v_2 = 3V - v_c \text{ for } t > t_0.$$

$$v_2(t > 0) = v_2(t \rightarrow \infty) + [v_2(0^+) - v_2(t \rightarrow \infty)] e^{-t/RC}$$

$$" = 0V + [6V - 0V] e^{-t/RC} = 6V e^{-t/RC}$$


$$\text{We want } v_2(\Delta t) = 3V. \therefore 6V e^{-4t/RC} = 3V$$

$$e^{-4t/RC} = \frac{3V}{6V} = \frac{1}{2} \text{ or } -\frac{4t}{RC} = \ln \frac{1}{2}$$


$$RC = \frac{-\Delta t}{\ln \frac{1}{2}} = \frac{\Delta t}{\ln 2} = \frac{10ms}{\ln 2} = 14.4 \text{ ms}$$

Use C = 1 \mu F, R = 14.4 k\Omega (15k\Omega is closest standard value)


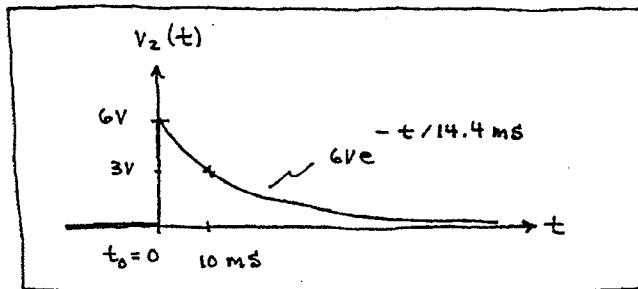
d) $v_2(t < 0) = 0V \quad v_2(t > 0) = 6V e^{-t/14.4 \text{ ms}} \quad v_2(10ms) = 3V$



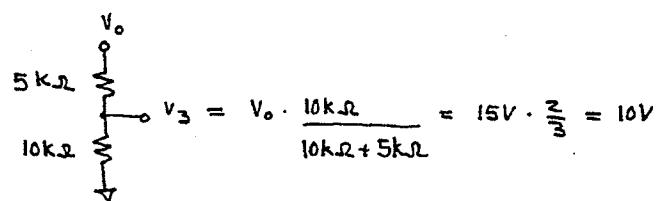
e) When $v_o = +15V$, the diode is reverse biased \Rightarrow open circuit (i.e. disappears)



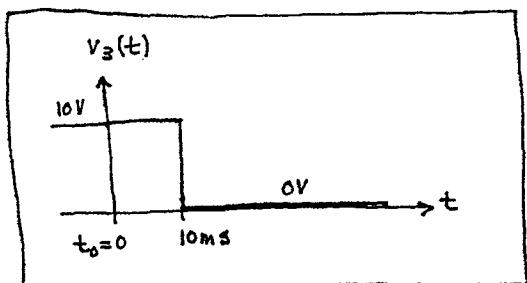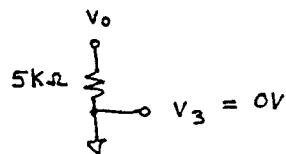When $v_o = -15V$, the diode is forward biased \Rightarrow short




2. (65 points)

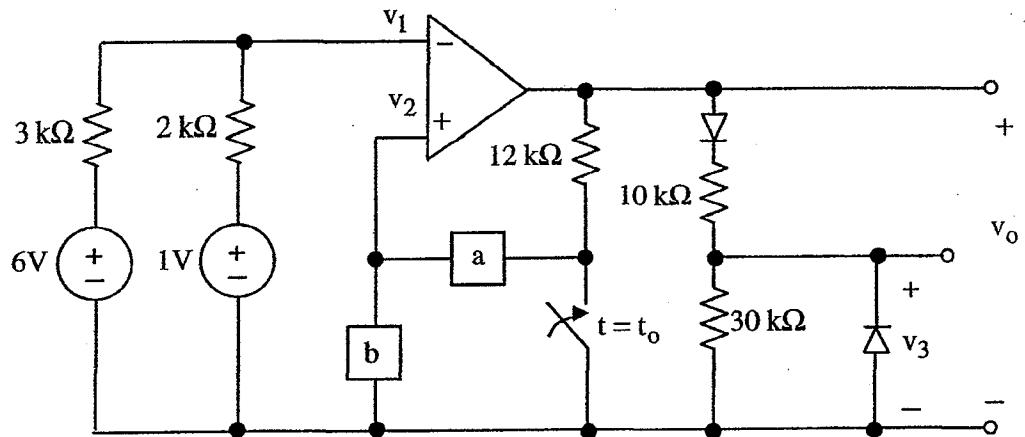

Rail voltages = ± 12 V

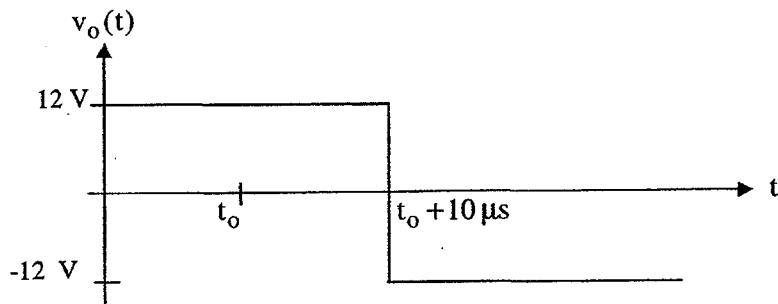After being open for a long time, the switch closes at $t = t_0$.



Pts

- 35 a. Choose either an R or L to go in box a and either an R or L to go in box b to produce the $v_o(t)$ shown above. Specify which element goes in each box and its value.
- 5 b. Sketch $v_1(t)$, showing numerical values appropriately.
- 15 c. Sketch $v_2(t)$, showing numerical values appropriately.
- 10 d. Sketch $v_3(t)$. Show numerical values for $t < t_0$, for $t_0 < t < t_0 + 10 \mu s$, and for $t_0 + 10 \mu s < t$. Use the ideal model of the diode: when forward biased, its resistance is zero; when reverse biased, its resistance is infinite.

Explain your work carefully.

sol'n: 2.a) Ignore diode and resistor network on output (since it doesn't affect v_o).

For $t < t_0$, $v_o = +12V \Rightarrow v_2 > v_1$.

Calculate v_1 using node-v method: $\frac{v_1 - 6V}{3k\Omega} + \frac{v_1 - 1V}{2k\Omega} = 0A$


$$v_1 \left(\frac{1}{3k\Omega} + \frac{1}{2k\Omega} \right) = \frac{6V}{3k\Omega} + \frac{1V}{2k\Omega}$$

mult both sides by $6k\Omega$

$$v_1 (2+3) = 6V \cdot 2 + 1V \cdot 3 = 15V, \quad v_1 = \frac{15V}{5} = 3V$$

So we need $v_2 > 3V$.

Circuit model: $v_o = 12V$, switch open

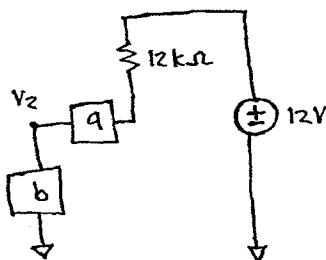

If we have an L, it will be equivalent to a wire.

Consider possibilities:

case I: $a = L$ and $b = L$ $L = \text{wire}$

$v_2 = 0V$ from v divider

Doesn't work.

case II: $a = R$ and $b = L = \text{wire}$

$v_2 = 0V$ from v divider

Doesn't work.

case III: $a = R_1$ and $b = R_2$

We can choose R_1 and R_2 to achieve $v_2 > 3V$, but we cannot get a delay in v_o dropping from $+12V$ to $-12V$.

case IV: $a = L$ and $b = R$

Since $L = \text{wire}$ and we can pick R , we can achieve $v_2 > 3V$. When switch moves, the L continues to carry same current initially. Thus, $v_2 > v_1$ is sustained for delay. Should work.


sol'n: 2.a) cont. When switch closes, we have RL circuit that determines v_2 . Time constant $\tau = L/R$. Output v_0 drops when v_2 drops below 3V.

As $t \rightarrow \infty$, the L in 'a' acts like a wire and the switch is closed $\Rightarrow v_2(t \rightarrow \infty) = 0V$

Without additional constraints, we may choose any v_2 between 3V and 12V. One choice is

$$v_2(0^-) = 6V. \text{ Using } v\text{-divider of } 12k\Omega \text{ and 'b', } b = 12k\Omega.$$

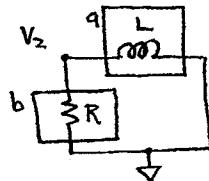We want $v_2(t = 10\mu s) = 3V$ so v_0 drops at time $t_0 + 10\mu s$. (Assume $t_0 = 0s$)




$$\begin{aligned} v_2(t > 0) &= v_2(t \rightarrow \infty) + [v_2(0^+) - v_2(t \rightarrow \infty)] e^{-t/\tau} \\ &= 0V + [v_2(0^+) - 0V] e^{-t/\tau} \\ &= v_2(0^+) e^{-t/\tau}, \text{ Now find } v_2(0^+). \end{aligned}$$

Consider $t = 0^-$: $L = \text{wire}$ $R = 12k\Omega$

$$i_L(0^-) = \frac{12V}{12k\Omega + 12k\Omega} = \frac{1}{2} mA$$

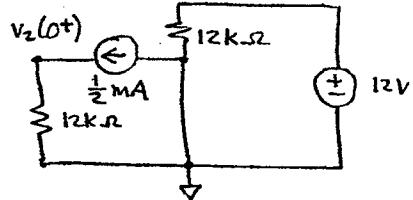$t = 0^+$: $L = i$ src where $i_L(0^+) = i_L(0^-) = \frac{1}{2} mA$



$$\begin{aligned} v_2(0^+) &= \frac{1}{2} mA \cdot 12k\Omega \\ v_2(0^+) &= 6V \end{aligned}$$

$$v_2(t > 0) = 6Ve^{-t/\tau}$$

We want $v_2(10\mu s) = 3V = 6Ve^{-10\mu s/\tau}$


$$\frac{3V}{6V} = \frac{1}{2} = e^{-10\mu s/\tau}, \quad \ln \frac{1}{2} = -10\mu s / \tau$$

$$\tau = \frac{-10\mu s}{\ln \frac{1}{2}} = \frac{10\mu s}{\ln 2} = 14.4\mu s = \frac{L}{R} = \frac{L}{12k\Omega}$$

$$L = 14.4\mu s \cdot 12k\Omega = 173 mH$$


Summary:	$a = L = 173 mH$
	$b = R = 12k\Omega$

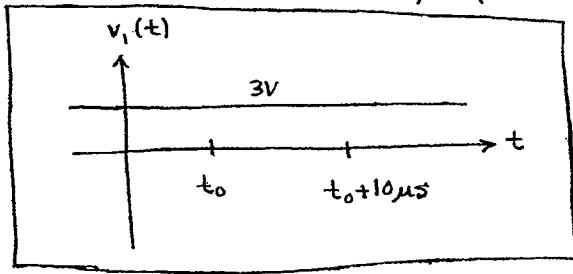Sol'n: 2.b) As shown in sol'n for (a), $v_1(t) = 3V$. It never changes.




c) From sol'n to (a), we have $v_2(t>0) = 6Ve^{-t/14.4\mu s}$

For $v_2(t<0)$, we have $v_2(t<0) = 6V$.

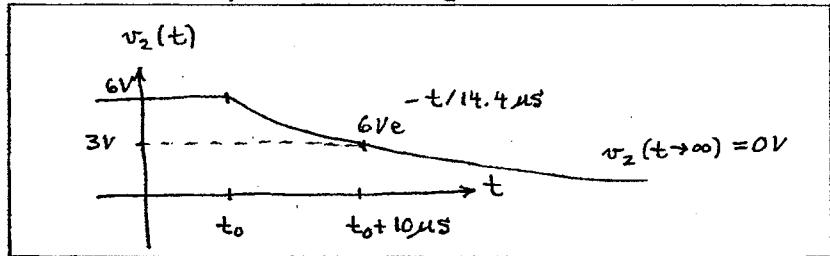

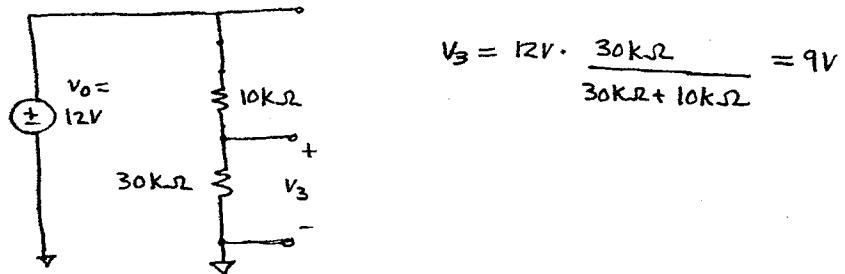d) When $v_o > 0V$, top diode = wire, bottom diode = open.



When $v_o < 0V$, top diode = open, bottom diode doesn't matter since no current

