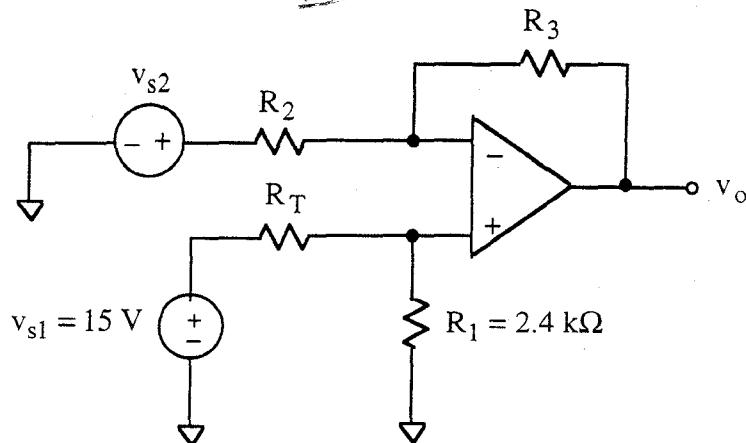


1. (70 points)

Rail voltage = ± 15 V

Design an electronic thermometer using the circuit diagram shown above. The voltage v_o is used to indicate temperature. Use a thermister with a resistance described by

$$R_T = R_0 e^{1120 \left(\frac{1}{T} - \frac{1}{300} \right)}$$

where $R_0 = 2490 \Omega$ and T is temperature in $^{\circ}\text{K}$.

Pts

- 10 a. Calculate the numerical values of R_T (273°K) and R_T (373°K).
- 25 b. Derive a symbolic expression for v_o . The expression must contain not more than the parameters v_{s1} , v_{s2} , R_T , R_1 , R_2 , and R_3 .
Hint: Use superposition.
- 25 c. Choose v_{s2} , R_2 , and R_3 that will produce the following:

$$\begin{aligned} v_o &= 0 \text{ V} & \text{when } T &= 273^{\circ}\text{K} \\ v_o &= 10 \text{ V} & \text{when } T &= 373^{\circ}\text{K} \end{aligned}$$

- 10 d. Using the component values you chose in (c), calculate v_o when $T = 323^{\circ}\text{K}$.

$$\text{sol'n 1.a)} \quad R_T(273^\circ\text{K}) = 2490 e^{1120 \left(\frac{1}{273} - \frac{1}{300}\right)} = 3.6 \text{ k}\Omega \quad \boxed{R_T(273^\circ\text{K}) = 3.6 \text{ k}\Omega}$$

$$R_T(373^\circ\text{K}) = 2490 e^{1120 \left(\frac{1}{373} - \frac{1}{300}\right)} = 1.2 \text{ k}\Omega \quad \boxed{R_T(373^\circ\text{K}) = 1.2 \text{ k}\Omega}$$

b) Superposition:

$$v_{S1} \text{ on}, v_{S2} \text{ off} \Rightarrow v_p = v_{S1} \cdot \frac{R_1}{R_1 + R_T}, \quad v_h = v_p$$

$$i_f \text{ (thru } R_2) = \frac{0 - v_h}{R_2} = -v_{S1} \frac{R_1}{R_1 + R_T} \frac{1}{R_2}$$

$$i_f \text{ (thru } R_3) = \frac{v_h - v_{O1}}{R_3} = -v_{S1} \frac{R_1}{R_1 + R_T} \frac{1}{R_3}$$

$$i_f \text{ (thru } R_2) = i_f \text{ (thru } R_3) \Rightarrow -\frac{v_h}{R_2} = \frac{v_h - v_{O1}}{R_3}$$

$$\text{or } v_{O1} = v_h \left(1 + \frac{R_3}{R_2}\right) = v_{S1} \frac{R_1}{R_1 + R_T} \left(1 + \frac{R_3}{R_2}\right)$$

$$v_{S1} \text{ off}, v_{S2} \text{ on} \Rightarrow v_p = 0V, \quad v_h = v_p$$

$$i_f \text{ (thru } R_2) = \frac{v_{S2}}{R_2} \quad i_f \text{ (thru } R_3) = -\frac{v_{O2}}{R_3}$$

$$i_f \text{ (thru } R_2) = i_f \text{ (thru } R_3) \Rightarrow v_{O2} = -v_{S2} \frac{R_3}{R_2}$$

$$v_o = v_{O1} + v_{O2}$$

$$\boxed{v_o = v_{S1} \frac{R_1}{R_1 + R_T} \left(1 + \frac{R_3}{R_2}\right) - v_{S2} \frac{R_3}{R_2}}$$

c) At 273°K , $v_{S1} \frac{R_1}{R_1 + R_T} = 15V \frac{2.4 \text{ k}\Omega}{2.4 \text{ k}\Omega + 3.6 \text{ k}\Omega} = 15V \cdot \frac{2}{5} = 6V = v_p$

At 373°K , $v_{S1} \frac{R_1}{R_1 + R_T} = 15V \frac{2.4 \text{ k}\Omega}{2.4 \text{ k}\Omega + 1.2 \text{ k}\Omega} = 15V \cdot \frac{2}{3} = 10V = v_p$

$$v_o = \underbrace{v_p \left(1 + \frac{R_3}{R_2}\right)}_{\substack{\text{proportional} \\ \text{to } v_p}} - \underbrace{v_{S2} \frac{R_3}{R_2}}_{\text{constant}} \quad \begin{aligned} &\text{The change in } v_o \text{ vs change in } v_p: \\ &\Delta v_o = \Delta v_p \left(1 + \frac{R_3}{R_2}\right) \end{aligned}$$

$$\Delta v_p = v_p(373^\circ\text{K}) - v_p(273^\circ\text{K}) = 10V - 6V = 4V$$

$$\Delta v_o = v_o(373^\circ\text{K}) - v_o(273^\circ\text{K}) = 10V - 0V = 10V$$

from prob
statement

sol'n 1.c) cont. $\Delta V_o = \Delta V_p \left(1 + \frac{R_3}{R_2}\right)$ or $10V = 4V \left(1 + \frac{R_3}{R_2}\right)$

$$\therefore 1 + \frac{R_3}{R_2} = 2.5 \quad \text{or} \quad \frac{R_3}{R_2} = 1.5$$

Let $R_3 = 15\text{ k}\Omega$, $R_2 = 10\text{ k}\Omega$.

$$V_o(273^\circ\text{K}) = 0V = \underset{\substack{\text{from} \\ \text{prob} \\ \text{statement}}}{V_p \left(1 + \frac{R_3}{R_2}\right)} - V_{S2} \frac{R_3}{R_2} = 6V(2.5) - V_{S2}(1.5)$$

or $V_{S2} = \frac{6(2.5)V}{1.5}$ or $V_{S2} = 10V$


d) $R_T(323^\circ\text{K}) = 2490 e^{1120 \left(\frac{1}{323} - \frac{1}{300}\right)} = 1.9\text{ k}\Omega$

$$V_p = 15V \cdot \frac{2.4\text{ k}\Omega}{2.4\text{ k}\Omega + 1.9\text{ k}\Omega} = 8.37V$$


$$V_o = V_p \left(1 + \frac{R_3}{R_2}\right) - V_{S2} \frac{R_3}{R_2} = 8.37(2.5) - 10(1.5) V$$

$V_o(323^\circ\text{K}) = 5.9V$ off by 18% from linear value of 5V.

2. (70 points)

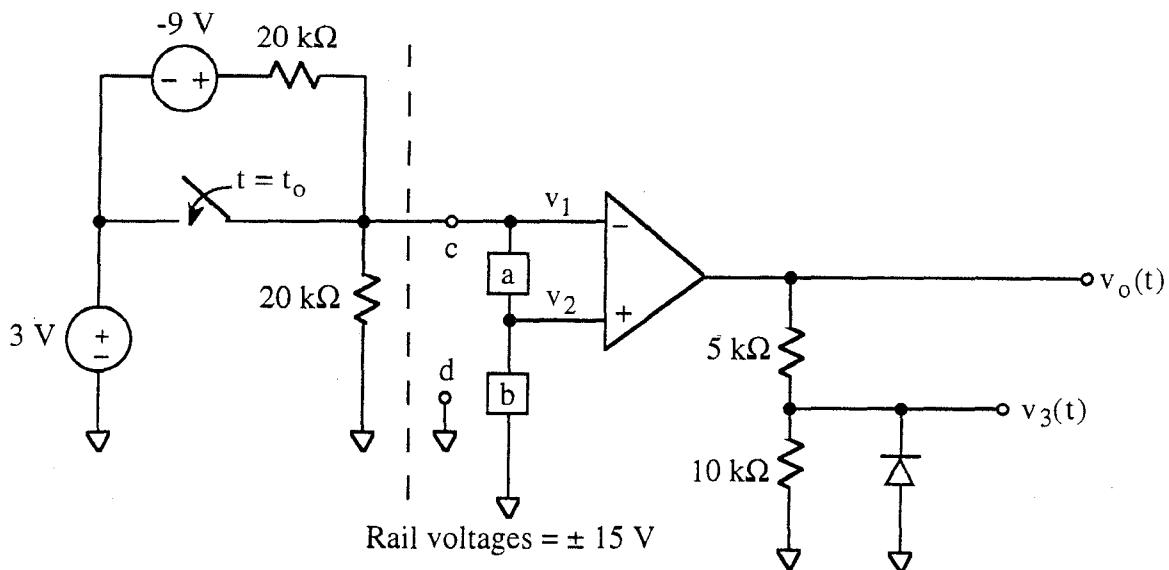

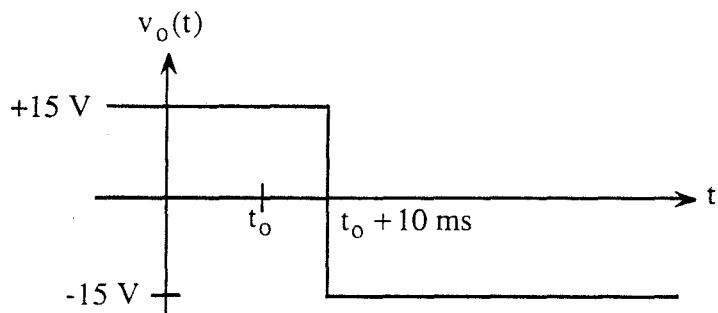
After being open for a very long time, the switch closes at $t = t_0$.



- Pts
- 10 a. Find the Thevenin equivalent of the circuit left of the dashed line with respect to terminals c, d for $t < t_0$.
- 10 b. Find the Thevenin equivalent of the circuit left of the dashed line with respect to terminals c, d for $t > t_0$.
- 20 c. Choose either an R or C to go in box a and either an R or C to go in box b to produce the $v_0(t)$ shown above. Specify which element goes in each box and its value.
- 20 d. Using the elements found in (b), sketch $v_2(t)$. Show numerical values appropriately.
- 10 e. Sketch $v_3(t)$. Show numerical values for $t < t_0$, $t_0 < t < t_0 + 10 \text{ ms}$, and $t > t_0 + 10 \text{ ms}$. Use the ideal model of the diode: when forward biased, its resistance is zero; when reverse biased, its resistance is infinite.

Explain your work carefully.

Sol'n 2.9) $t < t_0$ switch is open

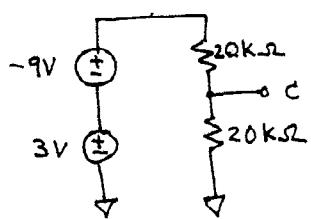


$$V_{Th} = (3V - 9V) \frac{20k\Omega}{20k\Omega + 20k\Omega} = -6V \cdot \frac{1}{2} = -3V$$


use V-divider

$$R_{Th} = R \text{ looking into } C \text{ with } V \text{ sources shorted}$$

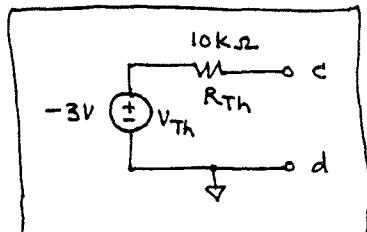
$$= 20k\Omega \parallel 20k\Omega = 10k\Omega$$



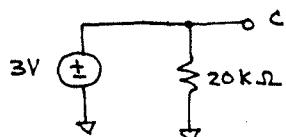b) $t > t_0$ switch is closed ($-9V$ source and $20k\Omega$ bypassed)


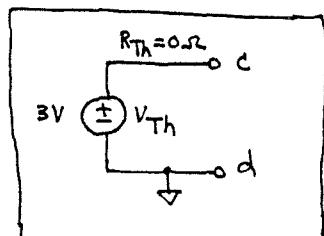
$$V_{Th} = 3V \text{ since } C \text{ connected to } 3V \text{ source}$$




$$R_{Th} = R \text{ looking into } C \text{ with } 3V \text{ source shorted}$$

$$= 0\Omega \text{ (20kΩ bypassed by short)}$$

c) R in a and C in b would immediate switching: wrong

$\therefore C$ in a and R in b must be correct.

$t < t_0$ circuit:
($t = t_0^-$)

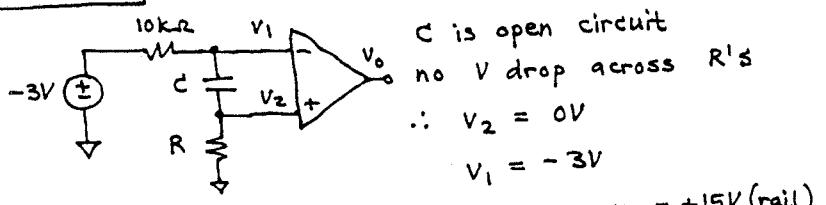

C is open circuit


no V drop across R's

$$\therefore V_2 = 0V$$

$$V_1 = -3V$$

$$V_1 < V_2 \Rightarrow V_0 = +15V \text{ (rail)}$$

$t = t_0^+$ circuit:

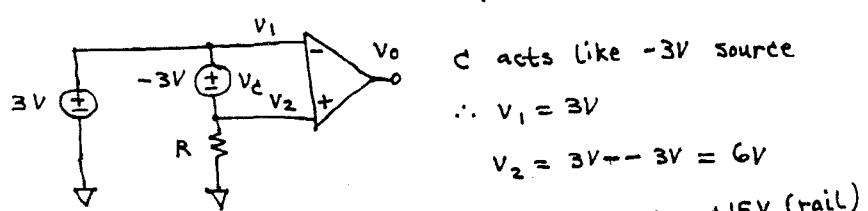


C acts like -3V source

$$\therefore V_1 = 3V$$

$$V_2 = 3V - -3V = 6V$$

$$V_1 < V_2 \Rightarrow V_0 = +15V \text{ (rail)}$$

$t \rightarrow \infty$ circuit:

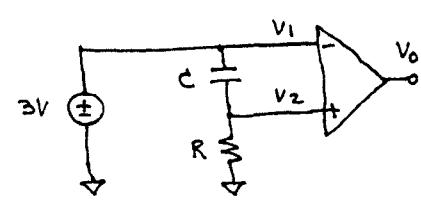

C acts like open circuit

no V drop across R

$$\therefore V_1 = 3V$$

$$V_2 = 0V$$

$$V_1 > V_2 \Rightarrow V_0 = -15V \text{ (rail)}$$

sol'n z.c) cont. Let $t_0 = 0$. Want $v_1 = v_2$ at $\Delta t \equiv 10\text{ms}$ for v_o transition.

$$v_1 = 3V \text{ for } t > t_0 = 0$$

$$v_2 = 3V - v_c \text{ for } t > t_0.$$

$$v_2(t > 0) = v_2(t \rightarrow \infty) + [v_2(0^+) - v_2(t \rightarrow \infty)] e^{-t/RC}$$

$$" = 0V + [6V - 0V] e^{-t/RC} = 6V e^{-t/RC}$$


$$\text{We want } v_2(\Delta t) = 3V. \therefore 6V e^{-4t/RC} = 3V$$

$$e^{-4t/RC} = \frac{3V}{6V} = \frac{1}{2} \text{ or } -\frac{\Delta t}{RC} = \ln \frac{1}{2}$$


$$RC = \frac{-\Delta t}{\ln \frac{1}{2}} = \frac{\Delta t}{\ln 2} = \frac{10\text{ms}}{\ln 2} = 14.4\text{ ms}$$

Use $C = 1\mu\text{F}, R = 14.4\text{ k}\Omega$ (15k Ω is closest standard value)

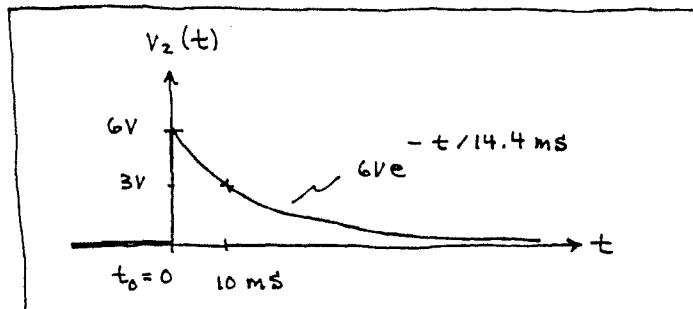
d) $v_2(t < 0) = 0V \quad v_2(t > 0) = 6V e^{-t/14.4\text{ ms}} \quad v_2(10\text{ms}) = 3V$



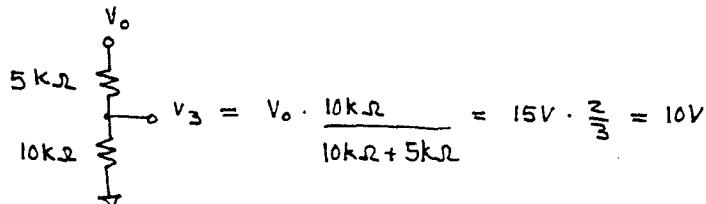
e) When $v_o = +15V$, the diode is reverse biased \Rightarrow open circuit (i.e. disappears)



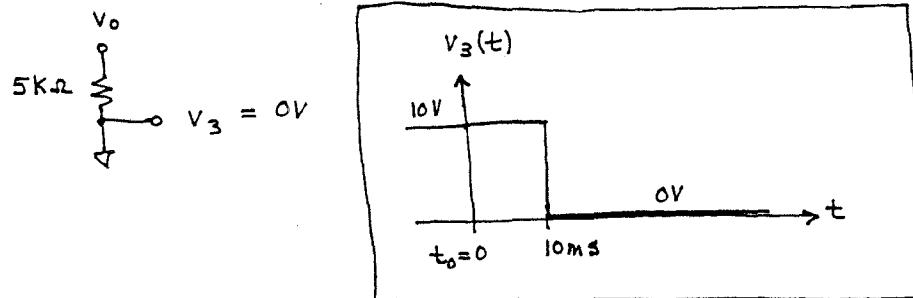When $v_o = -15V$, the diode is forward biased \Rightarrow short




3. (30 points)

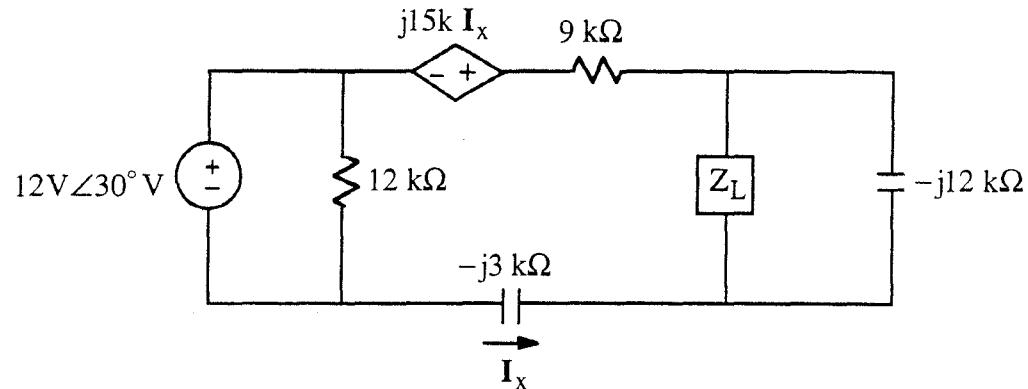


Pts

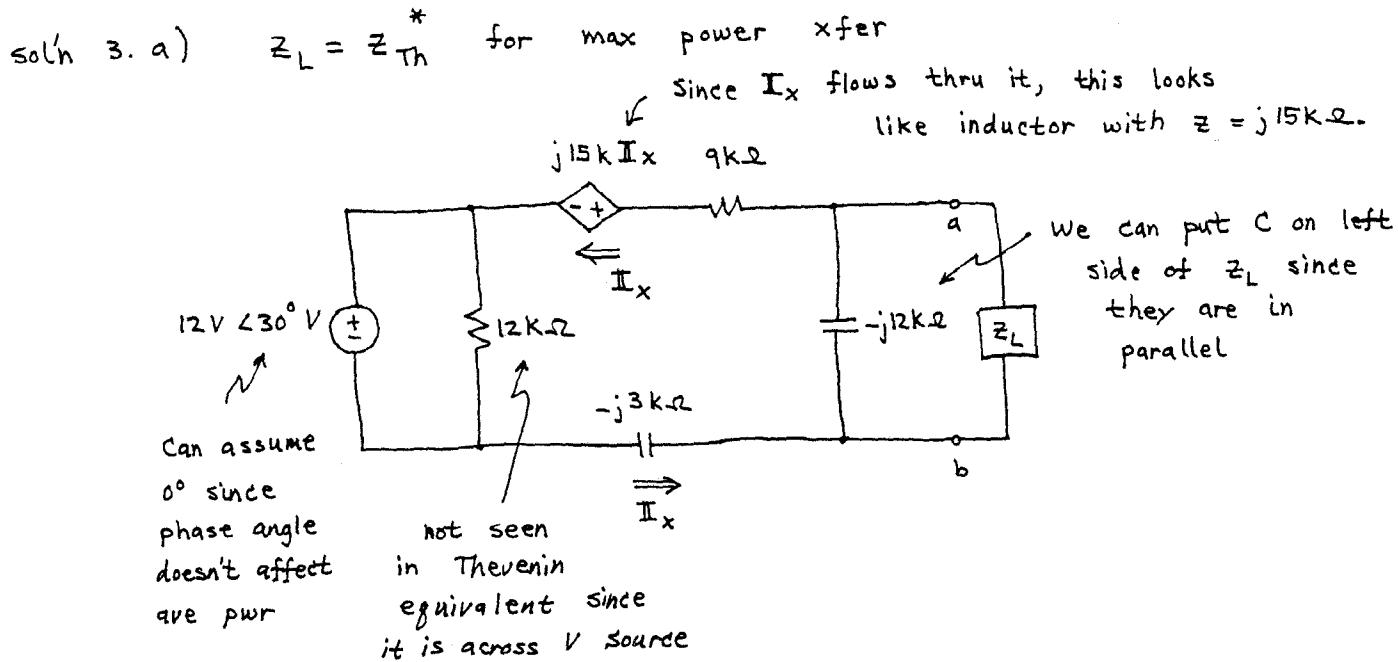- 15 a. Choose the value of Z_L that will absorb maximum average power.
15 b. Calculate the value of that maximum average power absorbed by Z_L .



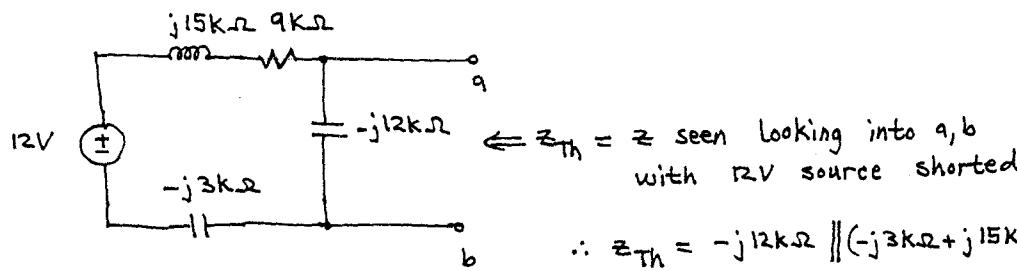Circuit for determining Thevenin equivalent:



$$Z_L = Z_{Th}^* = 16k\Omega + j12k\Omega$$


$$\therefore Z_{Th} = -j12k\Omega \parallel (-j3k\Omega + j15k\Omega + 9k\Omega)$$

$$" = -j12k\Omega \parallel (9k\Omega + j12k\Omega)$$

$$" = \frac{-j12k\Omega (9k\Omega + j12k\Omega)}{-j12k\Omega + 9k\Omega + j12k\Omega}$$

$$" = -j \frac{12k\Omega (9k\Omega + j12k\Omega)}{9k\Omega}$$

$$" = -j12k\Omega + 16k\Omega$$

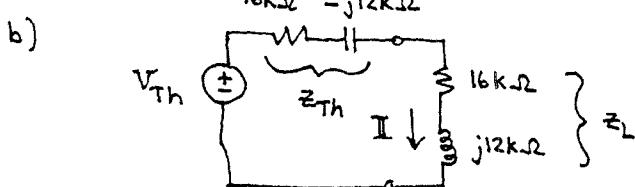


$$P = (\text{ave pwr in } Z_L) = \frac{|I|^2}{2} R \text{ where } R = 16k\Omega \text{ in } Z_L$$

$$I = \frac{V_{Th}}{16k\Omega - j12k\Omega + 16k\Omega + j12k\Omega} = \frac{V_{Th}}{32k\Omega}$$

$$V_{Th} = 12V \cdot \frac{-j12k\Omega}{-j12k\Omega + -j3k\Omega + j15k\Omega + 9k\Omega} = 12V \left(\frac{-j12k\Omega}{9k\Omega} \right) = -j16V$$

$$\therefore P = \left| \frac{-j16V}{32k\Omega} \right|^2 \cdot 16k\Omega = \frac{|-j|^2 V^2}{|12k\Omega|^2} \cdot \frac{16k\Omega}{2} = \frac{1V^2 \cdot 8}{4k\Omega} \text{ or } P = 2 \text{ mW}$$

4. (30 points)

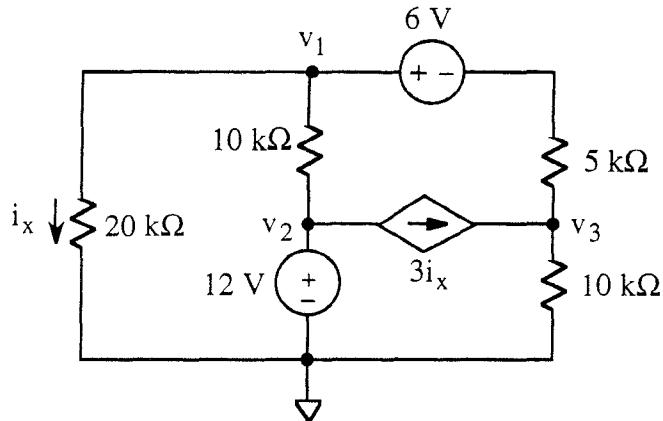

Pts

- 15 a. Write equations for node voltages v_1 , v_2 , and v_3 in the form:

$$g_{11}v_1 + g_{12}v_2 + g_{13}v_3 = i_1$$

$$g_{21}v_1 + g_{22}v_2 + g_{23}v_3 = i_2$$

$$g_{31}v_1 + g_{32}v_2 + g_{33}v_3 = i_3$$

List the numerical values of g_{ij} 's and i 's.

- 15 b. Show exactly what you would type into MATLAB™ to:

- i. Create a vertical array (called "ivec") containing your values for i_1 , i_2 , and i_3 ,
- ii. Using ivec, create an array (called "ivec2") containing values for i_1^2 , i_2^2 , and i_3^2 ,
- iii. Using ivec2, create a variable (called "sum_sq_i") equal to $i_1^2 + i_2^2 + i_3^2$.

$$\text{sol'n 4a)} \quad i_x = \frac{v_1}{20\text{k}\Omega} + \frac{v_1 - v_2}{10\text{k}\Omega} + \frac{(v_1 - 6V) - v_3}{5\text{k}\Omega} = 0A$$

$v_2 = 12V$ (connected to ref by V source)

$$\frac{v_3}{10\text{k}\Omega} - 3 \frac{v_1}{20\text{k}\Omega} + \frac{v_3 - (v_1 - 6V)}{5\text{k}\Omega} = 0A$$

$$g_{11} = \frac{1}{20\text{k}\Omega} + \frac{1}{10\text{k}\Omega} + \frac{1}{5\text{k}\Omega} = \frac{7}{20\text{k}\Omega} \quad g_{12} = -\frac{1}{10\text{k}\Omega} \quad g_{13} = -\frac{1}{5\text{k}\Omega} \quad i_1 = \frac{6V}{5\text{k}\Omega}$$

$$g_{21} = 0 \quad g_{22} = \frac{1}{\Omega} \quad g_{23} = 0 \quad i_2 = 12A$$

$$g_{31} = -\frac{1}{20\text{k}\Omega} - \frac{1}{5\text{k}\Omega} = -\frac{5}{20\text{k}\Omega} \quad g_{32} = 0 \quad g_{33} = \frac{1}{10\text{k}\Omega} + \frac{1}{5\text{k}\Omega} = \frac{3}{10\text{k}\Omega} \quad i_3 = -\frac{6V}{5\text{k}\Omega}$$

b) i. $\text{ivec} = [6/5000; 12; -6/5000]$

ii. $\text{ivec2} = \text{ivec} .* \text{ivec}$

iii. $\text{sum_sg-i} = \text{sum}(\text{ivec2})$

wj
EL EN 1000
Final Exam
May 2, 2001

Name _____

SCORE:

Problem 1 _____ of a possible 70 points

Problem 2 _____ of a possible 70 points

Problem 3 _____ of a possible 30 points

Problem 4 _____ of a possible 30 points

Total _____ of a possible 200 points