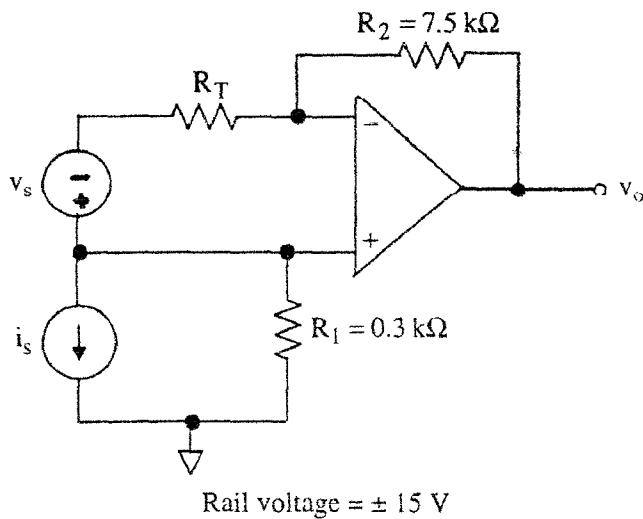


Homework #9 Solution

1. (75 points)



Design an electronic thermometer using the circuit diagram shown above. The voltage v_o is used to indicate temperature. Use a thermister with a resistance described by

$$R_T = R_0 e^{\beta \left(\frac{1}{T} - \frac{1}{300} \right)}$$


where $R_0 = 2.625 \text{ k}\Omega$, $\beta = 1200^\circ\text{K}$, and T is temperature in $^\circ\text{K}$.

Pts

- 30 a. Derive a symbolic expression for v_o . The expression must contain not more than the parameters i_s , V_s , R_1 , R_2 , and R_T . **Hint: Use superposition.**
- 10 b. Calculate the numerical values of R_T (273°K) and R_T (373°K).
- 15 c. Determine a value for v_s such that $v_o(T = 373^\circ\text{K}) - v_o(T = 273^\circ\text{K}) = 1\text{V}$
- 10 d. Using your answer to (c), determine a value of i_s such that
 $v_o(T = 273^\circ\text{K}) = 0\text{ V}$.
- 10 e. Using the component values you chose above, calculate v_o when $T = 323^\circ\text{K}$. Make a rough sketch of v_o vs. T on the basis of the values when $T = 273^\circ\text{K}$, 323°K , and 373°K . On the same axes, sketch the ideal linear response.

Sol'n: 1.a) Use superposition

Case I: v_s on, i_s off = open

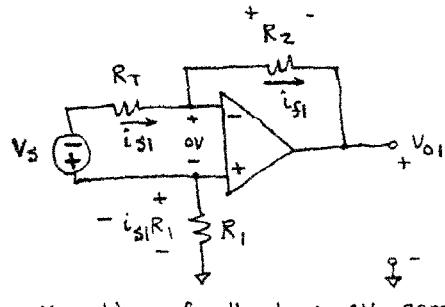

Negative feedback \Rightarrow 0V across + and - terminals.

From v loop around v_s , R_T , and +- terminals,

$$\text{we have } i_{S1} = -\frac{v_s}{R_T}.$$

From v loop around R_1 , +- terminals, R_2 , and v_o ,


$$\text{we have } -i_{S1}R_1 + 0V - i_{f1}R_2 - v_o = 0V$$

Now use $i_{S1} = i_{f1}$ and solve for v_o :

$$-\frac{v_s}{R_T} R_1 + 0V - \frac{v_s R_2}{R_T} - v_o = 0V$$

$$v_o = v_s \frac{R_1 + R_2}{R_T}$$

Case II: i_s on, v_s off = wire

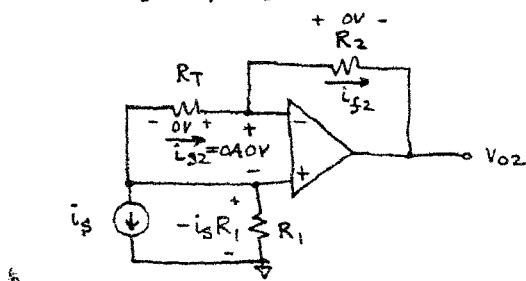

We 0V across $R_T \Rightarrow i_s = 0$.

Since $i_{S2} = i_{f2} = 0A$, we have $v_{o2} = v_- = v_+$

$$v_+ = -i_{S1}R_1 \Rightarrow v_{o2} = -i_{S1}R_1$$

sum

$$v_o = v_{o1} + v_{o2} = v_s \frac{R_1 + R_2}{R_T} - i_{S1}R_1$$

$$\text{sol'n: 1.b)} \quad R_T(273^\circ\text{K}) = 2.625 \text{ k}\Omega \text{ e}^{1200^\circ\text{K} \left(\frac{1}{273^\circ\text{K}} - \frac{1}{300^\circ\text{K}} \right)}$$

$$R_T(273^\circ\text{K}) \doteq 3.9 \text{ k}\Omega$$

$$R_T(373^\circ\text{K}) = 2.625 \text{ k}\Omega \text{ e}^{1200^\circ\text{K} \left(\frac{1}{373^\circ\text{K}} - \frac{1}{300^\circ\text{K}} \right)}$$

$$R_T(373^\circ\text{K}) \doteq 1.2 \text{ k}\Omega$$

$$\begin{aligned} c) \quad IV = V_o(373^\circ\text{K}) - V_o(273^\circ\text{K}) &= V_S \left(\frac{R_1 + R_2}{R_T(373^\circ\text{K})} - i_S R_1 \right. \\ &\quad \left. - \left(V_S \frac{R_1 + R_2}{R_T(273^\circ\text{K})} - i_S R_1 \right) \right) \\ &= V_S (R_1 + R_2) \left(\frac{1}{R_T(373^\circ\text{K})} - \frac{1}{R_T(273^\circ\text{K})} \right) \\ &= V_S \underbrace{(0.3 \text{ k}\Omega + 7.5 \text{ k}\Omega)}_{7.8 \text{ k}\Omega} \left(\frac{1}{1.2 \text{ k}\Omega} - \frac{1}{3.9 \text{ k}\Omega} \right) \\ V_S &= \frac{1.2 \text{ k}\Omega (3.9 \text{ k}\Omega)}{7.8 \text{ k}\Omega} V = \frac{0.3 \text{ k}\Omega}{0.3 \text{ k}\Omega} \cdot \frac{4 \parallel -13}{26} V = \frac{-4+13}{(4-13) 26} V \end{aligned}$$


$$V_S = \frac{2}{9} V$$

$$d) \quad OV = V_o(273^\circ\text{K}) = V_S \frac{R_1 + R_2 - i_S R_1}{R_T(273^\circ\text{K})} = \frac{2}{9} V \frac{7.8 \text{ k}\Omega}{3.9 \text{ k}\Omega} - i_S 0.3 \text{ k}\Omega$$


$$i_S 0.3 \text{ k}\Omega = \frac{4}{9} V \Rightarrow i_S = \frac{4}{9} \frac{1}{0.3 \text{ k}\Omega} V = \frac{4}{2.7} \text{ mA}$$

$$i_S \doteq 1.48 \text{ mA} \approx 1.5 \text{ mA}$$
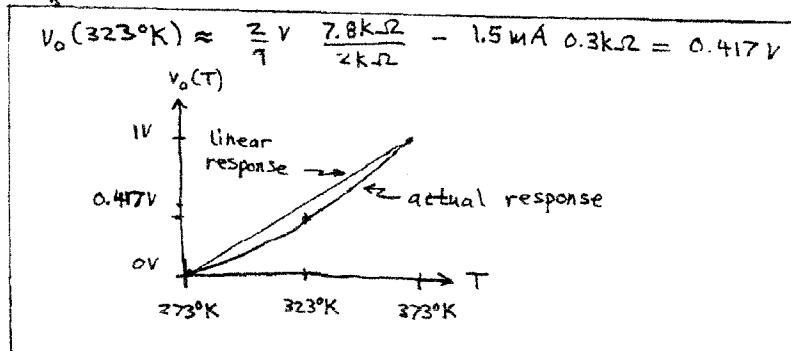
$$e) \quad R_T(323^\circ\text{K}) = 2.625 \text{ k}\Omega \text{ e}^{1200^\circ\text{K} \left(\frac{1}{323^\circ\text{K}} - \frac{1}{300^\circ\text{K}} \right)} = 1.97 \text{ k}\Omega \approx 2 \text{ k}\Omega$$




2. (65 points)

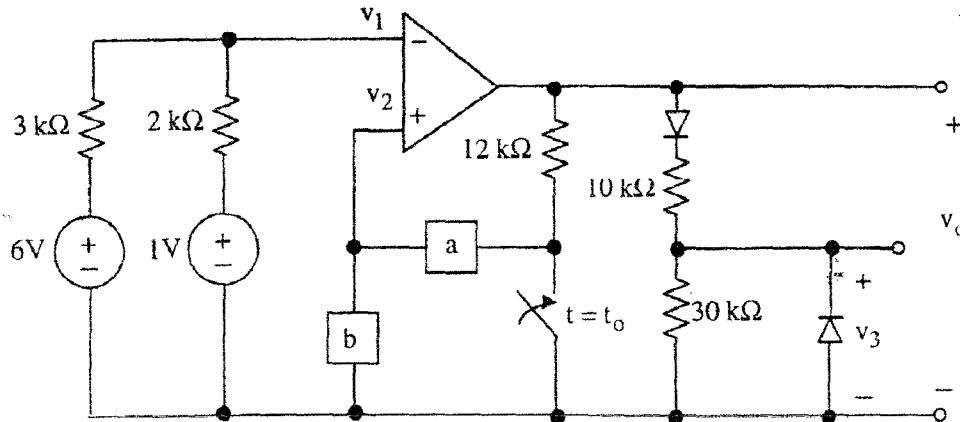

$$\text{Rail voltages} = \pm 12 \text{ V}$$

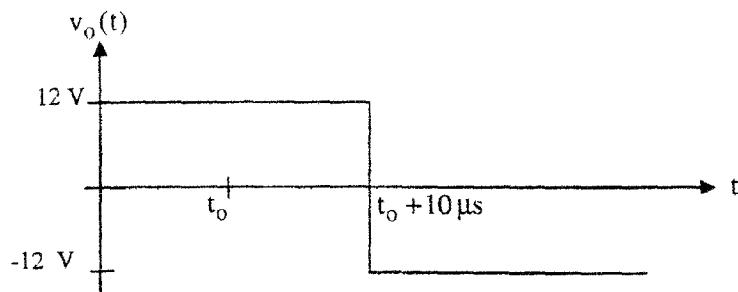After being open for a long time, the switch closes at $t = t_0$.



Pts

- 35 a. Choose either an R or L to go in box a and either an R or L to go in box b to produce the $v_o(t)$ shown above. Specify which element goes in each box and its value.
- 5 b. Sketch $v_1(t)$, showing numerical values appropriately.
- 15 c. Sketch $v_2(t)$, showing numerical values appropriately.
- 10 d. Sketch $v_3(t)$. Show numerical values for $t < t_0$, for $t_0 < t < t_0 + 10 \mu s$, and for $t_0 + 10 \mu s < t$. Use the ideal model of the diode: when forward biased, its resistance is zero; when reverse biased, its resistance is infinite.

Explain your work carefully.

sol(n: 2.a) Ignore diode and resistor network on output (since it doesn't affect v_o).

For $t < t_0$, $v_o = +12V \Rightarrow v_2 > v_1$.

Calculate v_1 using node-v method: $\frac{v_1 - 6V}{3k\Omega} + \frac{v_1 - 1V}{2k\Omega} = 0A$


$$v_1 \left(\frac{1}{3k\Omega} + \frac{1}{2k\Omega} \right) = \frac{6V}{3k\Omega} + \frac{1V}{2k\Omega}$$

mult both sides by $6k\Omega$

$$v_1 (2+3) = 6V \cdot 2 + 1V \cdot 3 = 15V, \quad v_1 = \frac{15V}{5} = 3V$$

So we need $v_2 > 3V$.

Circuit model: $v_o = 12V$, switch open

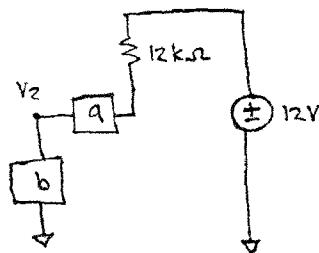

If we have an L, it will be equivalent to a wire.

Consider possibilities:

case I: $a = L$ and $b = l$ L=wire

$$v_2 = 0V \text{ from } v \text{ divider}$$

Doesn't work.

case II: $a = R$ and $b = L = \text{wire}$

$$v_2 = 0V \text{ from } v \text{ divider}$$

Doesn't work.

case III: $a = R_1$ and $b = R_2$

We can choose R_1 and R_2 to achieve

$v_2 > 3V$, but we cannot get a delay in v_o dropping from $+12V$ to $-12V$.

case IV: $a = L$ and $b = R$

Since $L = \text{wire}$ and we can pick R , we can achieve $v_2 > 3V$. When switch moves, the L continues to carry same current initially. Thus, $v_2 > v_1$ is sustained for delay. Should work.

sol'n: 2.a) cont.


When switch closes, we have RL circuit that determines v_2 . Time constant $\tau = L/R$. Output v_0 drops when v_2 drops below 3V.

As $t \rightarrow \infty$, the L in 'a' acts like a wire and the switch is closed $\Rightarrow v_2(t \rightarrow \infty) = 0V$

Without additional constraints, we may choose any v_2 between 3V and 12V. One choice is

$$v_2(0^-) = 6V. \text{ Using } v\text{-divider of } 12k\Omega \text{ and 'b', } b = 12k\Omega.$$

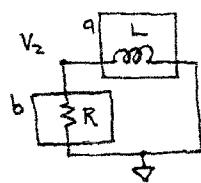We want $v_2(t = 10\mu s) = 3V$ so it drops at time $t_0 + 10\mu s$. (Assume $t_0 = 0s$)




$$\begin{aligned} v_2(t > 0) &= v_2(t \rightarrow \infty) + [v_2(0^+) - v_2(t \rightarrow \infty)] e^{-t/\tau} \\ &= 0V + [v_2(0^+) - 0V] e^{-t/\tau} \\ &= v_2(0^+) e^{-t/\tau}; \text{ Now find } v_2(0^+). \end{aligned}$$

Consider $t = 0^-$: $L = \text{wire}$ $R = 12k\Omega$

$$i_L(0^-) = \frac{12V}{12k\Omega + 12k\Omega} = \frac{1}{2} mA$$

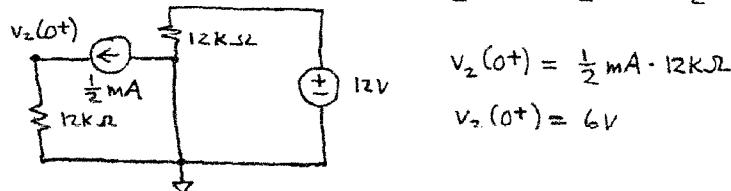$t = 0^+$: $L = i_{\text{src}}$ where $i_L(0^+) = i_L(0^-) = \frac{1}{2} mA$



$$v_2(t > 0) = 6V e^{-t/\tau}$$

We want $v_2(10\mu s) = 3V = 6V e^{-10\mu s/\tau}$


$$\frac{3V}{6V} = \frac{1}{2} = e^{-10\mu s/\tau}, \quad \ln \frac{1}{2} = -10\mu s / \tau$$

$$\tau = \frac{-10\mu s}{\ln \frac{1}{2}} = \frac{10\mu s}{\ln 2} = 14.4\mu s = \frac{L}{R} = \frac{L}{12k\Omega}$$

$$L = 14.4\mu s \cdot 12k\Omega = 173 mH$$


Summary: $a = L = 173 mH$
 $b = R = 12k\Omega$

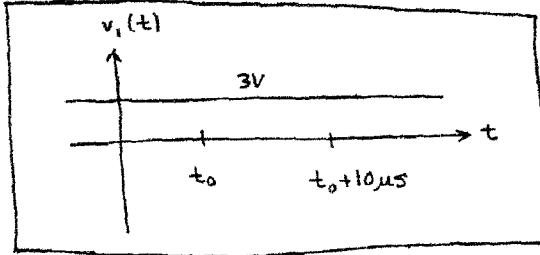sol'n: 2.b) As shown in sol'n for (a), $v_1(t) = 3V$. It never changes.




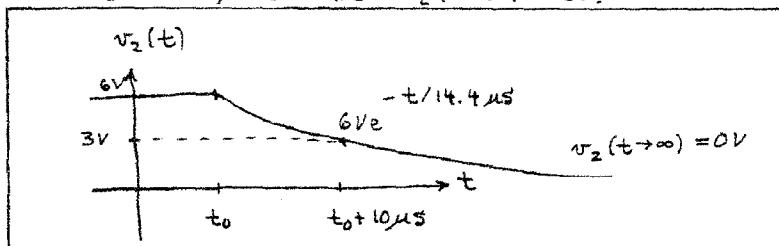c) From sol'n to (a), we have $v_2(t > 0) = 6V e^{-t/14.4\mu s}$



For $v_2(t < 0)$, we have $v_2(t < 0) = 6V$.



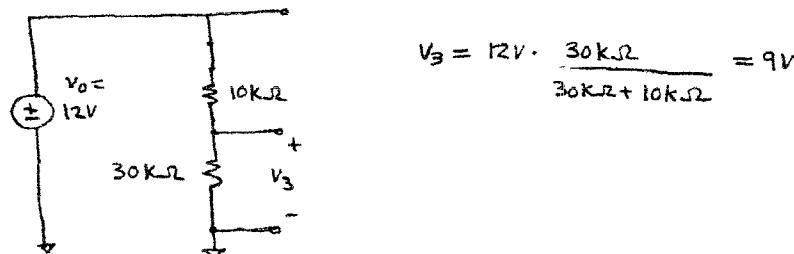
d) When $v_o > 0V$, top diode = wire, bottom diode = open.



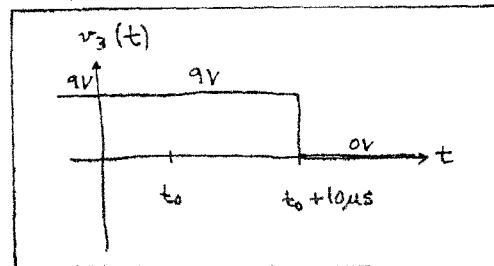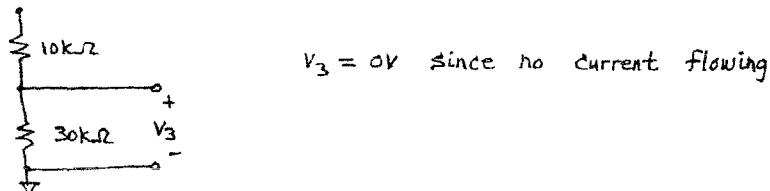When $v_o < 0V$, top diode = open, bottom diode doesn't matter since no current



3. (35 points)

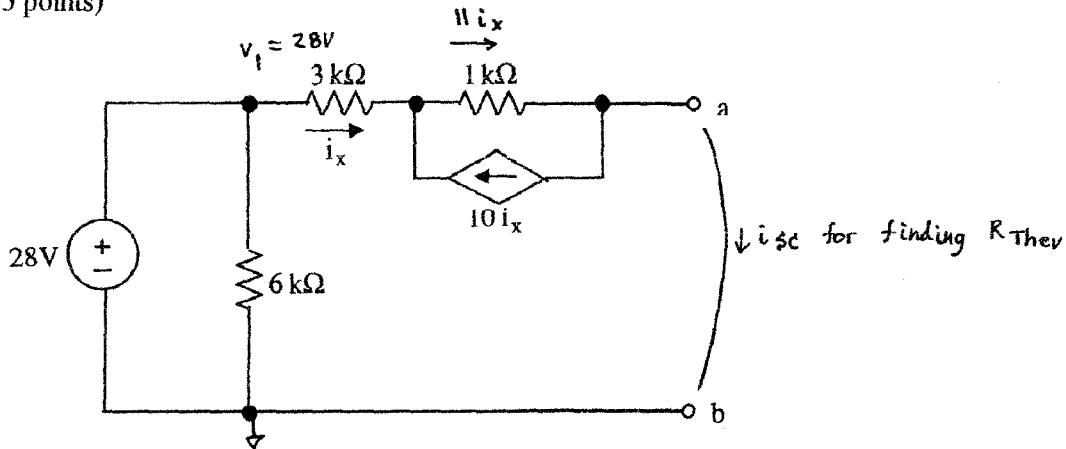

Pts

25 a. Find the Thevenin equivalent of the above circuit relative to terminals a and b.

5 b. If we attach R_L to terminals a and b, find the value of R_L that will absorb maximum power.

5 c. Calculate the value of that maximum power absorbed by R_L .

Sol'n: a) The $6\text{k}\Omega$ resistor is across the 28V source, so it may be ignored.

For V_{Thev} we use $V_{a,b}$ with no load. Since no current flows out of the 'a' terminal, $i_x = 0$.
 $\therefore 10i_x = 0\text{A}$ and v drop across $3\text{k}\Omega$ and $1\text{k}\Omega$ is zero.
 $\therefore V_{a,b} = 28\text{V}$ from v src $\therefore V_{\text{Thev}} = 28\text{V}$


Now find i_{sc} flowing in wire connected from a to b.

From current sum at node on left end of $1\text{k}\Omega$, we have current $11i_x$ flowing in $1\text{k}\Omega$ resistor.

Using v drops for $3\text{k}\Omega$ and $1\text{k}\Omega$, we must have
 $i_x \cdot 3\text{k}\Omega + 11i_x \cdot 1\text{k}\Omega = 28\text{V}$ or $14\text{k}\Omega \cdot i_x = 28\text{V}$

or $i_x = 2\text{mA}$. Since $i_{sc} = i_x$ and $R_{\text{Th}} = \frac{V_{\text{Th}}}{i_{sc}}$,
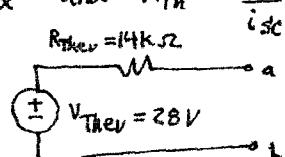
$$R_{\text{Th}} = \frac{28\text{V}}{2\text{mA}} = 14\text{k}\Omega$$




Sol'n: 3.b) Max pwr when $R_L = R_{Th\text{ev}} = 14\text{k}\Omega$

$$3.c) \quad \text{Max pwr} = \frac{V_{Th\text{ev}}^2}{4R_{Th\text{ev}}} = \frac{(20V)^2}{4 \cdot 14\text{k}\Omega} = 7(2)\text{W}$$

$$\boxed{\text{Max pwr} = 14\text{W}}$$

4. (25 points)

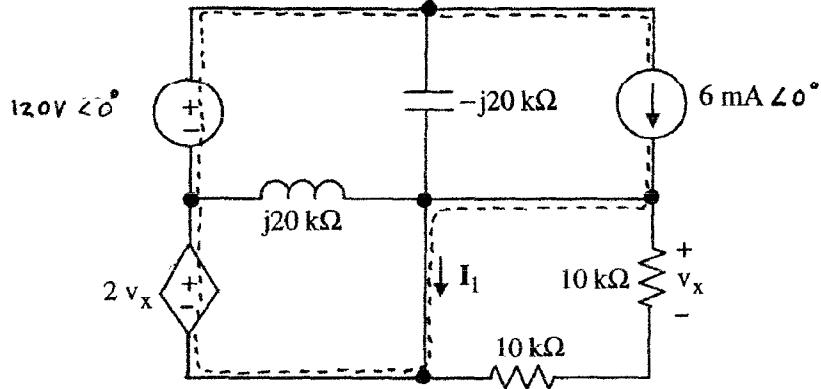

Pts

- 20 a. A frequency-domain circuit is shown above. Write the value of phasor I_1 in polar form.

- 5 b. Given $\omega = \pi$ rad/s, write a numerical time-domain expression for $i_1(t)$, the inverse phasor of I_1 .

Sol'n: a) Since the two $10\text{k}\Omega$ resistors are shorted by wires.
 \therefore There is no v drop across the $10\text{k}\Omega$ resistors,
and $v_x = 0\text{V}$.

Thus, the $2v_x$ dependent source $= 0\text{V} = \text{wire}$
Superposition Case I: 6mA on, 120V off = wire.
It follows that all of the 6mA from the
independent current source flows in the wires
(shown as dashed lines above).

$$\therefore I_{11} = 6\text{mA} < 0^\circ$$

Case II: 120V on, 6mA off = open circuit
we observe that the $-j20\text{k}\Omega$ is directly across
the 120V source, given the wires shown as
dashed lines.


$$\therefore I_{12} = \frac{120\text{V} < 0^\circ}{-j20\text{k}\Omega} = j6\text{mA} = 6\text{mA} < 90^\circ$$

$$\text{Thus, } I_1 = I_{11} + I_{12} = 6\text{mA} \cdot (1+j)$$

or $I_1 = \sqrt{2} \cdot 6\text{mA} < 45^\circ$

b) $i_1(t) = \sqrt{2} \cdot 6\text{mA} \cos(\pi t + 45^\circ)$

1. (75 points)

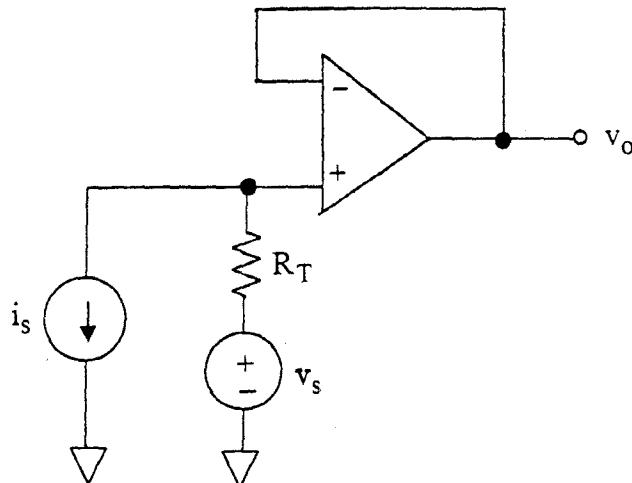Rail voltage = ± 15 V

Design an electronic thermometer using the circuit diagram shown above. The voltage v_o is used to indicate temperature. Use a thermister with a resistance described by


$$R_T = R_0 e^{\beta \left(\frac{1}{T} - \frac{1}{300} \right)}$$

where $R_0 = 2.8 \text{ k}\Omega$, $\beta = 1300^\circ\text{K}$, and T is temperature in $^\circ\text{K}$.

Pts

- 30 a. Derive a symbolic expression for v_o . The expression must contain not more than the parameters i_s , V_s , and R_T . **Hint: Use superposition.**
- 10 b. Calculate the numerical values of R_T (273°K) and R_T (373°K).
- 15 c. Determine a value for i_s such that $v_o(T = 373^\circ\text{K}) - v_o(T = 273^\circ\text{K}) = 1\text{V}$
- 10 d. Using your answer to (c), find the numerical value of v_s such that
 $v_o(T = 273^\circ\text{K}) = 0 \text{ V}$.
- 10 e. Using the component values you chose above, calculate v_o when $T = 323^\circ\text{K}$. Make a rough sketch of v_o vs. T on the basis of the values when $T = 273^\circ\text{K}$, 323°K , and 373°K . On the same axes, sketch the ideal linear response.

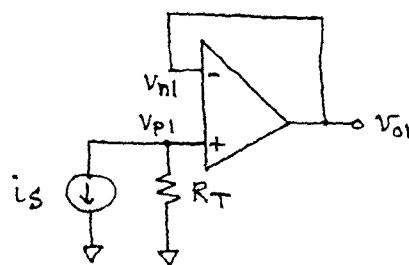sol'n: 1.a) Superposition case I: i_s on, v_s off = wire




$$v_{p1} = -i_s R_T$$

$$v_{n1} = v_{p1} = -i_s R_T$$

$$v_{o1} = v_{n1} = -i_s R_T$$

case II: i_s off = open, v_s on

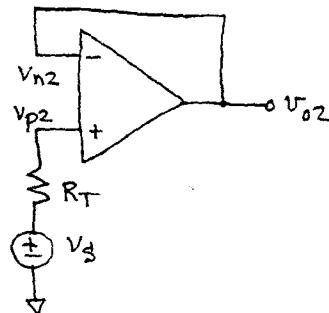

$$v_{p2} = v_s \text{ (no current in } R_T \text{ so no V-drop)}$$

$$v_{n2} = v_{p2} = v_s$$

$$v_{o2} = v_{n2} = v_s$$

$$v_o = v_{o1} + v_{o2}$$

$$v_o = -i_s R_T + v_s$$

b) $R_T(273^\circ K) = 2.8 k\Omega e^{1300^\circ K \left(\frac{1}{273^\circ K} - \frac{1}{300^\circ K} \right)}$

$$R_T(273^\circ K) = 4.3 k\Omega$$

$$R_T(373^\circ K) = 2.8 k\Omega e^{1300^\circ K \left(\frac{1}{373^\circ K} - \frac{1}{300^\circ K} \right)}$$

$$R_T(373^\circ K) = 1.2 k\Omega$$

c) Change in v_o : $\Delta v_o = -i_s \Delta R_T$ $\Delta \equiv \text{"change"}$
 (for $\Delta T = 100^\circ K$) $= 1V$ (desired) (v_s constant does not change with T)

$$\Delta R_T = 1.2 k\Omega - 4.3 k\Omega$$

$$\Delta R_T = -3.1 k\Omega$$

$$\therefore i_s = \frac{-\Delta v_o}{\Delta R_T} = \frac{-1V}{-3.1 k\Omega} = 0.323 mA$$

$$i_s = 0.323 mA$$

d) $v_o(273^\circ K) = 0V = -0.323 mA \cdot 4.3 k\Omega + v_s$
 $- i_s \cdot \frac{v_s}{R_T}$

$$\therefore v_s = 0.323 mA \cdot 4.3 k\Omega$$

$$v_s = 1.39 V \text{ or } 1.4 V$$

sol'n: 1. e)


$$v_o(323^\circ K) = -i_s R_T(323^\circ K) + v_s$$

$$R_T(323^\circ K) = 2.8 k\Omega \text{ e}^{1300^\circ K \left(\frac{1}{323^\circ K} - \frac{1}{300^\circ K}\right)}$$


$$= 2.06 k\Omega$$

$$v_o(323^\circ K) = -0.323 \text{ mA } 2.06 \text{ k}\Omega + 1.39 V$$


$v_o(323^\circ K) = 0.725 V$

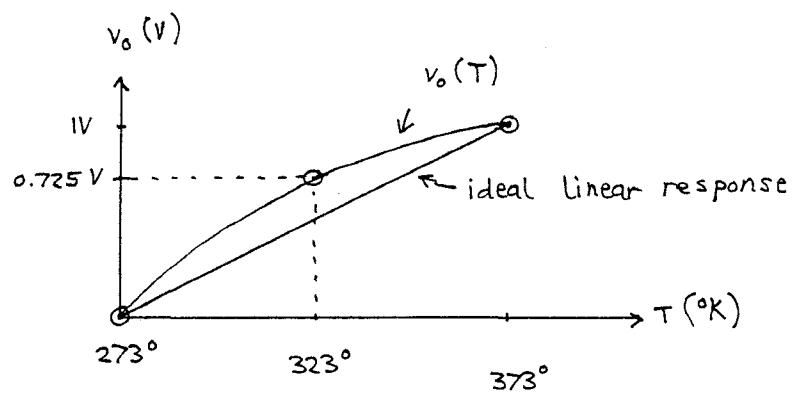

2. (65 points)

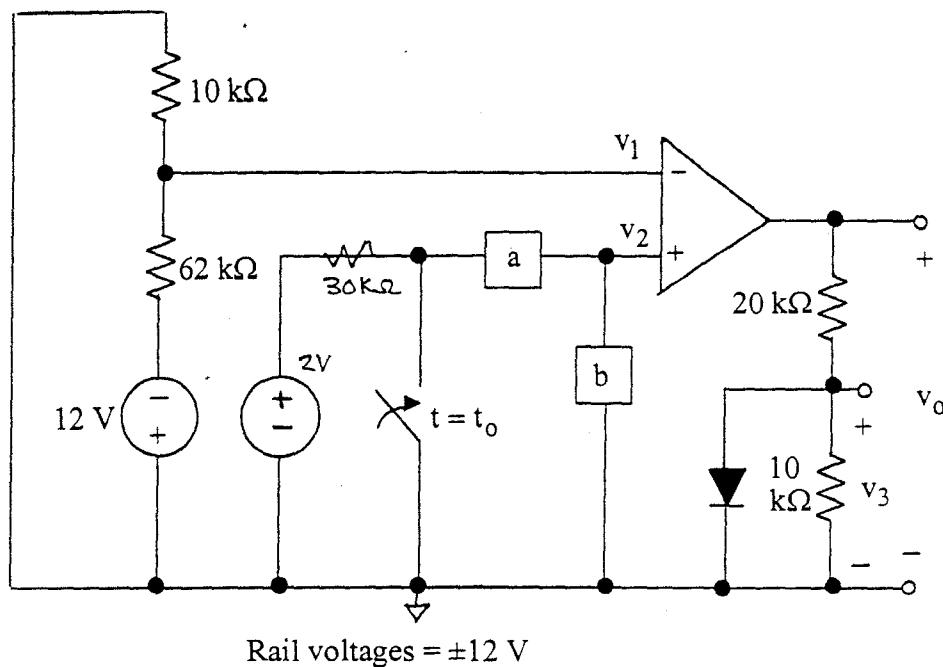

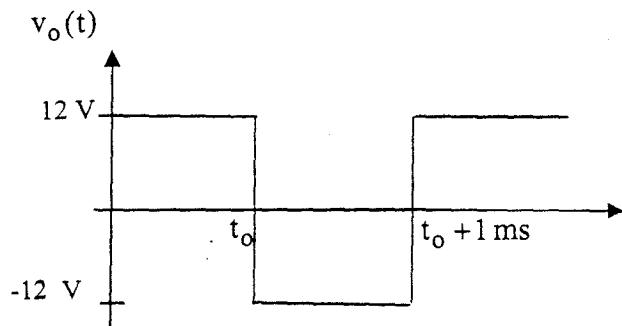After being open for a long time, the switch closes at $t = t_0$.



Pts

- 35 a. Choose either an R or C to go in box a and either an R or C to go in box b to produce the $v_o(t)$ shown above. Specify which element goes in each box and its value.
- 5 b. Sketch $v_1(t)$, showing numerical values appropriately.
- 15 c. Sketch $v_2(t)$, showing numerical values appropriately.
- 10 d. Sketch $v_3(t)$. Show numerical values for $t < t_0$, for $t_0 < t < t_0 + 1$ ms, and for $t > t_0 + 1$ ms. Use the ideal model of the diode: when forward biased, its resistance is zero; when reverse biased, its resistance is infinite.

sol'n: 2. a) At $t = t_0^-$: $v_1 = -12V \frac{10k\Omega}{10k\Omega + 62k\Omega}$ V-divider

$$v_1 = -\frac{5}{3}V \quad \text{Actually, } v_1 = -\frac{5}{3}V \text{ for all } t$$

$$v_o = +12V \Rightarrow v_2 > v_1 = -\frac{5}{3}V$$

Consider $a = R, b = R$: v_o would never switch because v_2 would be $0V$ after switch closed, and $v_2 > v_1$ for all time. Will not work.

Consider $a = C, b = C$: C 's will charge to $v_{tot} = 2V$.

Part of $2V$ across a , part across b .

When switch closes, the C 's instantly charge to $v_{tot} = 2V$.

Then their voltages remain fixed.
 $\therefore v_o$ would not switch after 1ms.
 Will not work.


Consider $a = R, b = C$: C will charge to $2V$. $v_2 = 2V$

When switch closes, v_2 will start at v_2 and charge toward $0V$. $v_2 > v_1$ for all time.

v_o never switches.
 Will not work.


Consider $a = C, b = R$: C will charge to $2V$ at t_0^-

$v_2 > v_1$ so $v_o = +12V$ at t_0^- ✓

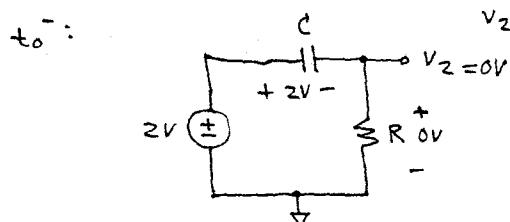

When switch closes, v_C will stay at $2V$ for $t = t_0^+$:

t_0^+ :

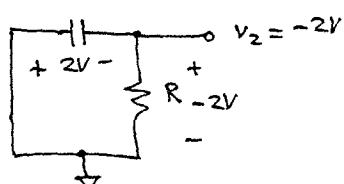


Thus, v_2 drops to $-2V$.

Then $v_2 < v_1$ and v_o drops to $-12V$. ✓

$t > t_0$: C charges to $0V$ and v_2 climbs toward $0V$.

We want $v_2 = v_1 = -\frac{5}{3}V$ at $t_0 + 1ms$. ✓
works

sol'n: 2.a) (cont.)

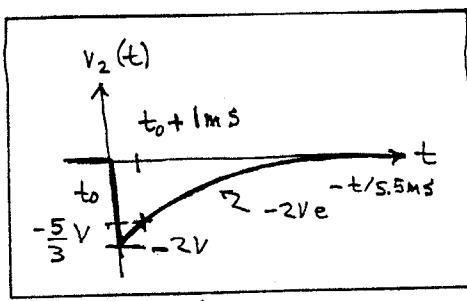

$$\begin{aligned} \text{Let } t_0 &= 0 & -t/RC \\ v_2(t) &= -2V e^{-t/RC} \\ v_2(1\text{ms}) &= -2V e^{-1\text{ms}/RC} = -\frac{5}{3}V \\ e^{-1\text{ms}/RC} &= \frac{5}{6} \end{aligned}$$

$$-1\text{ms}/RC = \ln \frac{5}{6}$$

$$RC = \frac{-1\text{ms}}{\ln \frac{5}{6}} = 5.48\text{ms}$$

$$RC \approx 5.5\text{ ms}$$

Let $C = 1\mu\text{F}$, $R = 5.5\text{k}\Omega$ or $5.6\text{k}\Omega$ (standard value)


Any $RC = 5.5\text{ ms}$ acceptable if $1\text{pF} < C < 1\text{F}$
and $1\text{ }\Omega < R < 1\text{G}\Omega$.

Note: If R is $\frac{1}{8}\text{W}$ then we would really want $\max i_R^2 R < \frac{1}{8}\text{W}$.

$$\max i_R^2 = \left(\frac{2V}{R}\right)^2 \Rightarrow \max i_R^2 R = \frac{4V^2}{R} < \frac{1}{8}\text{W}$$

$$\therefore R > \frac{4V^2}{1/8\text{W}} = 32\text{ }\Omega \text{ required.}$$


2.b) $v_1 = -\frac{5}{3}V$ for all t

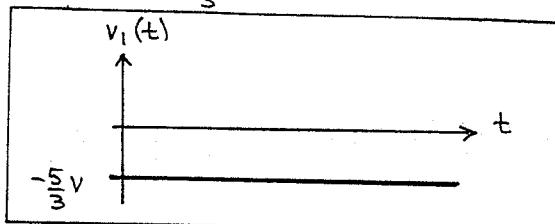

2.c) See plot of $v_2(t)$ in sol'n to 2.a), above.

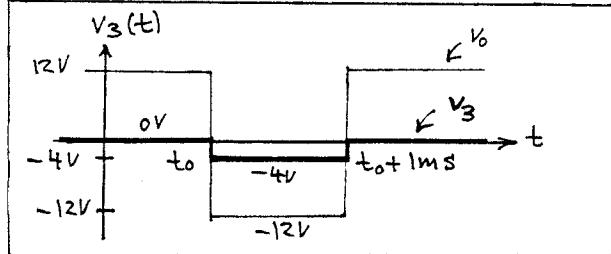
2.d) When $v_o > 0\text{V}$, diode forward biased = wire. $\therefore v_3 = 0\text{V}$

when $v_o < 0\text{V}$, diode reverse biased = open. $\therefore v_3 = v_o \frac{10\text{k}\Omega}{10\text{k}\Omega + 20\text{k}\Omega}$



$$v_3 = -12V \cdot \frac{1}{3} = -4V$$

3. (30 points)

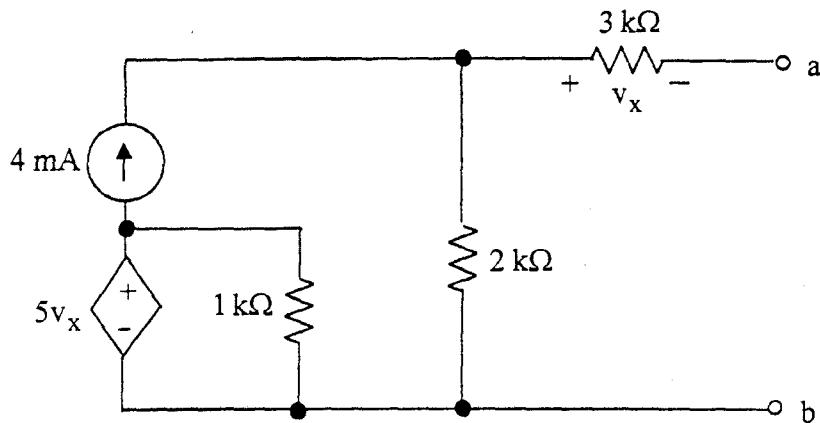

Pts

- 20 a. Find the Thevenin equivalent of the above circuit relative to terminals a and b.
- 5 b. If we attach R_L to terminals a and b, find the value of R_L that will absorb maximum power.
- 5 c. Calculate the value of that maximum power absorbed by R_L .


$$\text{sol'n: a) } V_{Th} = V_{a,b} \text{ open circuit}$$

open circuit $\Rightarrow v_x = 0$ since no current in $3\text{k}\Omega$.

$\therefore 5v_x \text{ src} = 0V = \text{wire}$

$1\text{k}\Omega$ across v_x shorted so can be ignored.

So we have:

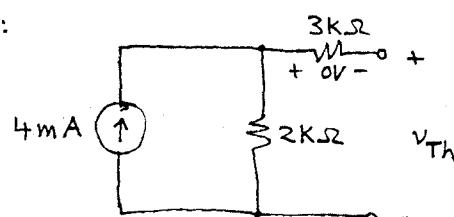

$$V_{Th} = 4\text{mA} \cdot 2\text{k}\Omega = 8\text{V}$$

$$\boxed{V_{Th} = 8\text{V}}$$

$$R_{Th} = \frac{V_{Th}}{i_{sc}} \quad \text{If we short a,b we have current divider. } i_{sc} = 4\text{mA} \cdot \frac{2\text{k}\Omega}{2\text{k}\Omega + 3\text{k}\Omega} = \frac{8}{5} \text{mA}$$

$$R_{Th} = \frac{8\text{V}}{8/5 \text{mA}} = 5\text{k}\Omega \quad \boxed{R_{Th} = 5\text{k}\Omega}$$


Note: Easier sol'n is to say $5v_x$ and $1\text{k}\Omega$ don't matter because they are in series with current source. Then $R_{Th} = 2\text{k}\Omega + 3\text{k}\Omega$ seen from a,b with 4mA off.

sol'n: 3.b) max pwr when $R_L = R_{Th} = 5\text{ k}\Omega$

$$3.c) \text{max pwr} = \frac{V_{Th}^2}{4R_{Th}} = \frac{(8V)^2}{4 \cdot 5\text{k}\Omega} = \frac{64}{20} \text{ mW} = 3.2 \text{ mW}$$

$$\boxed{\text{max pwr} = 3.2 \text{ mW}}$$

4. (25 points)

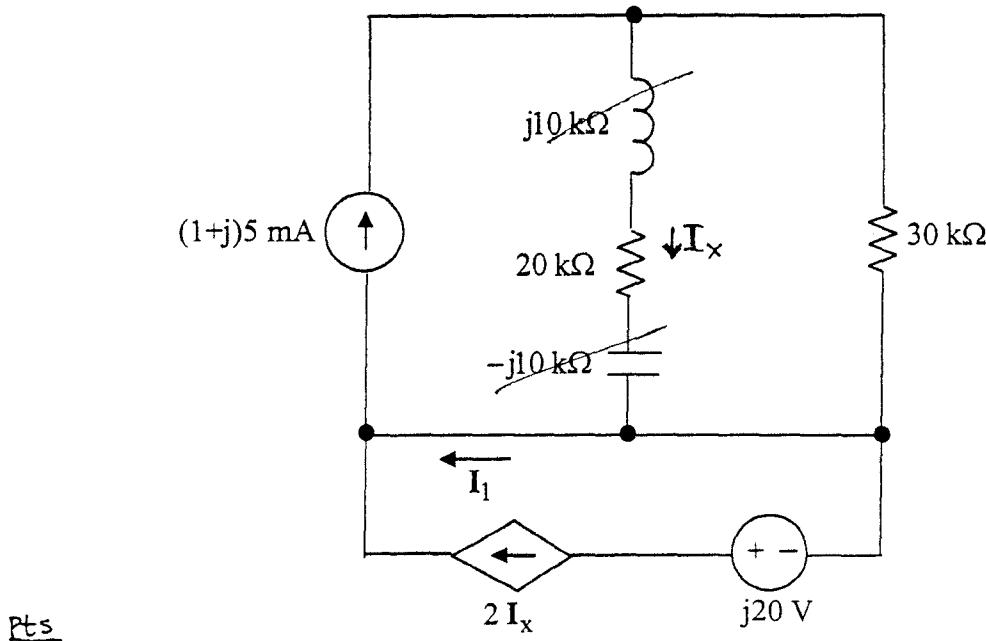

pts

20 pts a. A frequency-domain circuit is shown above. Write the value of I_1 in polar form.

5 pts b. Given $\omega = 100 \text{ k rad/s}$, write a numerical time-domain expression for $i_1(t)$, the inverse phasor of I_1 .

sol'n: 4. a) $j10\text{k}\Omega - j10\text{k}\Omega = 0\Omega$ so L and C cancel.

Current divider for $20\text{k}\Omega$ and $30\text{k}\Omega$.

$$\therefore I_x = (1+j)5\text{mA} \cdot \frac{30\text{k}\Omega}{20\text{k}\Omega + 30\text{k}\Omega} = (1+j)3\text{mA}$$

Find I_1 from sum of currents at node
on left side:

$$(1+j)5\text{mA} - 2 \underbrace{(1+j)3\text{mA}}_{I_x} - I_1 = 0$$

$$I_1 = (1+j)5\text{mA} - 2(1+j)3\text{mA} = (1+j)(5-6)\text{mA}$$

$$I_1 = (1+j)(-1)\text{mA} = -(1+j)\text{mA}$$

$I_1 = -\sqrt{2} \angle 45^\circ \text{mA}$	$= \sqrt{2} \angle -135^\circ \text{mA}$
	or 225°

b) $i_1(t) = \sqrt{2} \cos(100kt - 135^\circ) \text{mA}$