

UNIVERSITY OF UTAH
ELECTRICAL AND COMPUTER ENGINEERING DEPARTMENT

ECE 1000


HOMEWORK #8

Spring 2005

1. Give numerical answers to each of the following questions:

- Rationalize $\frac{23+j7}{15-j8}$. Express your answer in rectangular form.
- Find the polar form of $(2+j3)(3+j2)+[3+j16]^*$. Note the asterisk that means "conjugate".
- Find the following phasor: $P[-5\sin(100t-30^\circ)]$.
- Find the magnitude of $\frac{100(3+j4)(4+j3)}{(7+j)(7-j)}$.
- Find the imaginary part of $(1+j)e^{-j45^\circ}(j2)$.

2.

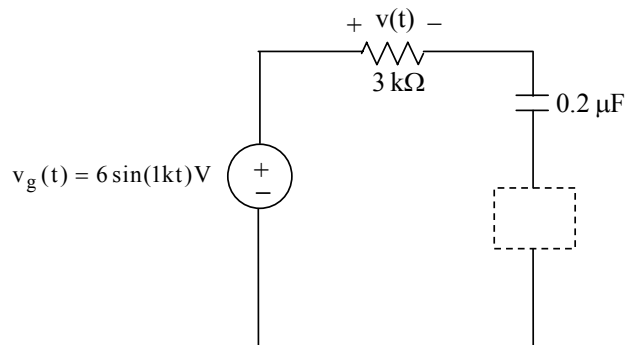


Choose an R, an L, or a C to be placed in the dashed-line box to make

$$v(t) = V_0 \cos(1kt - 45^\circ)V$$

where V_0 is a real constant. State the value of the component you choose.

3. With your component from problem 2 in the circuit, calculate the resulting value of V_0 .

4.

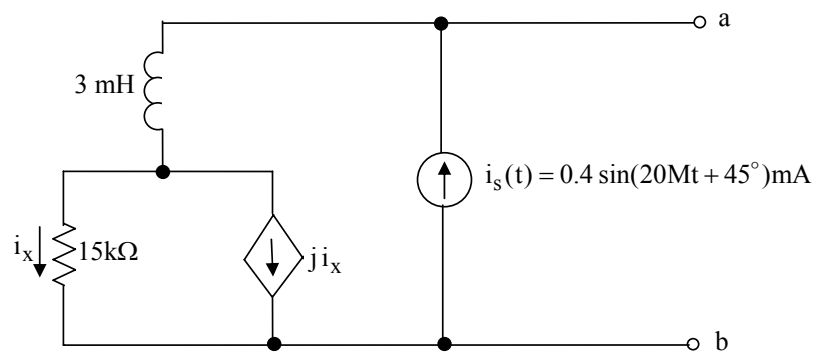

Find the Thevenin equivalent (in the frequency domain) for the above circuit. Give the numerical phasor value for V_{Th} and the numerical impedance value of z_{Th} .

1. (25 points)

Give numerical answers to each of the following questions:

pts

- (5) a. Rationalize $\frac{23+j7}{15-j8}$. Express your answer in rectangular form.
- (5) b. Find the polar form of $(2+j3)(3+j2)+[+j16]^*$. Note the asterisk that means "conjugate".
- (5) c. Find the following phasor: $P[-5\sin(100t-30^\circ)]$.
- (5) d. Find the magnitude of $\frac{100(3+j4)(4+j3)}{(7+j)(7-j)}$.
- (5) e. Find the imaginary part of $(1+j)e^{-j45^\circ}(j2)$.

$$a+jb = \sqrt{a^2+b^2} e^{j \tan^{-1}(b/a)}$$

$$re^{j\phi} = r \cos\phi + j r \sin\phi$$

$$\sin(x) = \cos(x - 90^\circ)$$

sol'n: 1. a) $\frac{23+j7}{15-j8} \cdot \frac{15+j8}{15+j8} = \frac{-7(8) + (23)15 + j[23(8) + 7(15)]}{15^2 + 8^2} = \frac{289 + j289}{289} = \boxed{1+j}$

b) $(2+j3)(3+j2) + [j16]^* = (2+j3)(3+j2) - j16 = 6-6 + j(9+4) - j16 = j3 = 3 \angle -90^\circ$ or $3e^{-j90^\circ}$

$\cos(100t-30-90^\circ) = -j3$

c) $P[-5\sin(100t-30^\circ)] = 5 \angle 180^\circ \cdot 1 \angle (-30^\circ - 90^\circ) = 5 \angle 60^\circ$


$\frac{1}{e^{j30^\circ}} = e^{-j30^\circ}$

d) $\left| \frac{100(3+j4)(4+j3)}{(7+j)(7-j)} \right| = 100 \frac{|3+j4||4+j3|}{|7+j||7-j|} = \frac{100 \cdot \sqrt{3^2+4^2} \sqrt{4^2+3^2}}{\sqrt{7^2+1^2} \sqrt{7^2+1^2}} = \frac{100 \cdot 5^2}{50} = \boxed{50}$

e) $\text{Im}[(1+j)e^{-j45^\circ}(j2)] = \text{Im}[\sqrt{2} \angle 45^\circ \cdot 1 \angle -45^\circ \cdot 2 \angle 90^\circ] = \text{Im}[2\sqrt{2} \angle 90^\circ] = \text{Im}[j2\sqrt{2}] = \boxed{2\sqrt{2}}$

$$\text{Im}[2\sqrt{2} \angle 66^\circ] = \text{Im}[2\sqrt{2} \cos(66^\circ) + 2\sqrt{2} \sin(66^\circ)j]$$

3. (35 points)

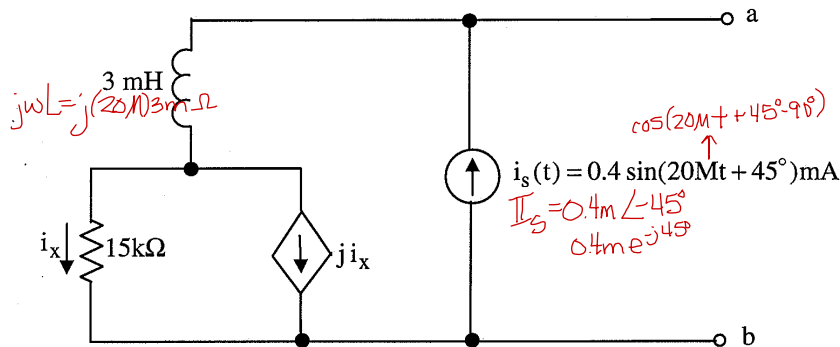

pts

- (15) a. Draw a frequency-domain equivalent of the above circuit. Show a numerical phasor value for $i_s(t)$, and show numerical impedance values for R, and L. Label the dependent source appropriately.
- (25) b. Find the Thevenin equivalent (in the frequency domain) for the above circuit. Give the numerical phasor value for V_{Th} and the numerical impedance value of Z_{Th} .

sol'n: 3.a) $\omega = 20M$ from $i_s(t)$ $j\omega L = j 20M 3m = j 60k\Omega$

$$+I_x(15k) + 60k j (.4me^{j45^\circ}) = V_{th}$$

$$I_x + jI_x = .4me^{j45^\circ}$$

$$I_x = \frac{.4me^{j45^\circ}}{(1+j)}$$

$$I_x = \frac{.4m}{\sqrt{2}} e^{j(45^\circ - 45^\circ)}$$

$$I_x = \frac{.4m}{\sqrt{2}} e^{j0^\circ}$$

$$I_x = \frac{.4m}{\sqrt{2}}$$

$$I_x = \frac{.4m}{\sqrt{2}}$$

$$I_x = \frac{.4m}{\sqrt{2}}$$

$$I_x = \frac{.4m}{\sqrt{2}}$$

$$I_x = \frac{.4m}{\sqrt{2}}$$

$$I_x = \frac{.4m}{\sqrt{2}}$$

$$I_x = \frac{.4m}{\sqrt{2}}$$

$$I_x = \frac{.4m}{\sqrt{2}}$$

$$I_x = \frac{.4m}{\sqrt{2}}$$

$$I_x = \frac{.4m}{\sqrt{2}}$$

$$I_x = \frac{.4m}{\sqrt{2}}$$

$$I_x = \frac{.4m}{\sqrt{2}}$$

$$I_x = \frac{.4m}{\sqrt{2}}$$

$$I_x = \frac{.4m}{\sqrt{2}}$$

$$I_x = \frac{.4m}{\sqrt{2}}$$


$$I_x = \frac{.4m}{\sqrt{2}}$$

$$I_x = \frac{.4m}{\sqrt{2}}$$

$$I_x = \frac{.4m}{\sqrt{2}}$$

$$I_x = \frac{.4m}{\sqrt{2}}$$

$$I_x = \frac{.4m}{\sqrt{2}}$$

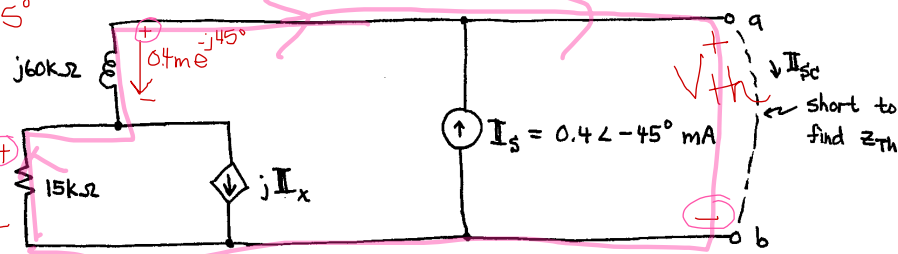

b) Use $z_{eq} = \frac{I_x 15k\Omega}{I} = -j15k\Omega$, (from $\frac{V}{I} = z$), for dependent src.

$$V_{th} = \frac{.4m}{\sqrt{2}} \cdot 15k(-j) + 60k e^{j0^\circ} (.4me^{j45^\circ}) j I_x$$


$$V_{Th} = V_{ab} \text{ no load} = I_s \cdot (j60k + 15k \parallel -j15k) \Omega \quad 15k\Omega \cdot \frac{1 \parallel -j}{1-j} = 15k\Omega \frac{-j}{1-j}$$

$$= \frac{3}{5} \angle -45^\circ \text{ mA} \cdot \left(\frac{15}{2} k + j \frac{15}{2} k \cdot 7 \right) \Omega = \frac{3}{5} \frac{(1-j)}{\sqrt{2}} \frac{15}{2} (1+j7) \text{ V}$$

$$= \frac{3}{\sqrt{2}} [1+7 + j(7-1)] \text{ V} = \frac{3(8+j6)}{\sqrt{2}} = \frac{24}{\sqrt{2}} + j \frac{18}{\sqrt{2}} \text{ V} \text{ or } \frac{30}{\sqrt{2}} \angle 37^\circ \text{ V} = V_{Th}$$

$$Z_{Th} = \frac{V_{Th}}{I_{sc}}, \quad I_{sc} = I_s \text{ since } 0V \text{ across } z's \text{ on left, } I_x = 0 \text{ is sol'n.}$$
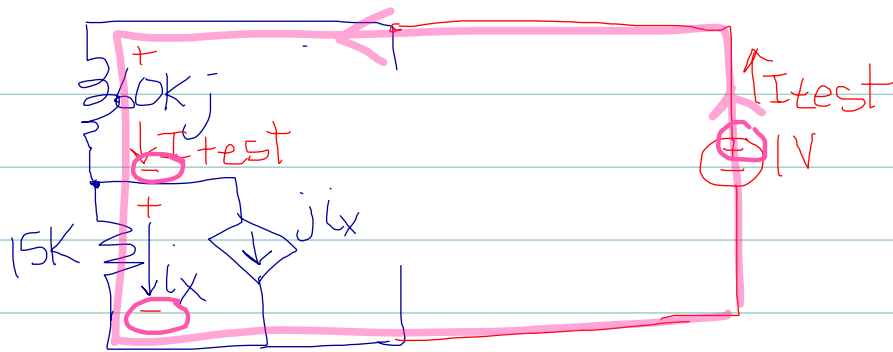
$$Z_{Th} = j60k + 15k \parallel -j15k \Omega = \frac{15}{2} k + j \frac{105}{2} k \Omega \text{ or } 15k \sqrt{50} \angle 81^\circ \Omega$$



$$I_{test} = i_x + j i_x$$

$$-I_{test}(60k) + 1 - 15k i_x = 0$$

$$i_x = \frac{-60k j I_{test} + 1}{15k}$$

$$I_{test} = \left[\frac{-60k j I_{test} + 1}{15k} \right] (1 + j)$$

$$15k I_{test} = -60k j I_{test} - 60k j^2 I_{test} + 1 + j$$

$$I_{test} (15k + 60k j - 60k) = \frac{1 + j}{(-45k + 60k j)}$$

$$Z_{th} = \frac{1}{I_{test}} = \frac{(-45k + 60k j)}{(1 + j)}$$


2. (40 points)

$$I = \frac{-6j}{3k - 5kj + z}$$

$$V = I \cdot 3k$$

$$V = \frac{-6j \cdot 3k}{3k - 5kj + z} \quad v_g(t) = 6 \sin(1kt) \text{ V} = 6 \angle -90^\circ = 6(-j)$$
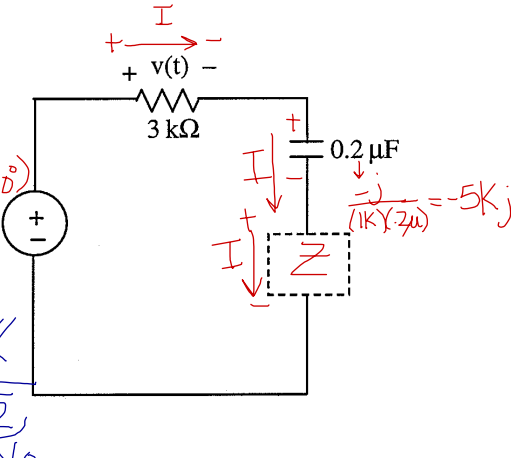
$$R = 2k \quad V = \frac{+8k e^{-j90}}{\frac{5k - 5kj}{\sqrt{5k^2 + 5k^2}} e^{-j45}} = \frac{18k}{5\sqrt{2}}$$



(25) a. Choose an R, an L, or a C to be placed in the dashed-line box to make

$$v(t) = V_0 \cos(1kt - 45^\circ) \text{ V}$$

where V_0 is a real constant. State the value of the component you choose.

(10) b. With your component from (a) in the circuit, calculate the resulting value of


V_0 .

sol'n: 2. a) $V = V_0 \angle -45^\circ \text{ V}$, $V_g = 6 \angle -90^\circ \text{ V}$, $V = V_g \frac{R}{R + j\omega L + z_{box}}$ v-divider

$$\angle V = \angle V_g + \angle R - \angle (R + j\omega L + z_{box})$$

$$-45^\circ = -90^\circ + 0^\circ - \angle (R + j\omega L + z_{box}) \Rightarrow \angle (R + j\omega L + z_{box}) = -45^\circ$$
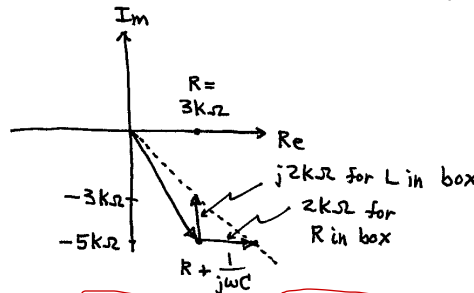
$$R = 3k\Omega, \quad j\omega L = \frac{1}{j\omega C} = \frac{1}{j \cdot 1k \cdot 0.2\mu} = -j5k\Omega, \quad \omega = 1k \text{ r/s}$$



if L in box, $j\omega L = j2k\Omega$
 $L = 2 \text{ H}$

if R in box, $R = 2k\Omega$


$$b) \quad V_0 = |V| = \frac{|V_g| \cdot |R|}{|R + j\omega L + z_{box}|} = 6 \frac{3k\Omega}{\sqrt{2} \cdot 3k\Omega \text{ for L} / \sqrt{2} \cdot 3k\Omega \text{ for R}} = \frac{6}{\sqrt{2}} \text{ for L} = \frac{18}{5\sqrt{2}} \text{ for R}$$

$$V_0 e^{-j45^\circ} = \frac{-18Kj}{3K - 5Kj + Z}$$

$$\angle -45^\circ = \angle -90^\circ$$

need $\angle -45^\circ$
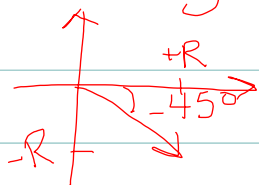
$$\angle(3K - 5Kj + Z) = \angle -45^\circ$$



Need Real = -Im. for -45°

so $R = 2K \rightarrow$ Real = $5K$, Im = $-5K$

$$L \rightarrow 3K - 5Kj + j(1K)L$$

$$= 3K?$$

Yes if $L = 2H$

Cap $\rightarrow 3K - 5Kj - \frac{1}{jK} \text{ NOT possible}$