


UNIVERSITY OF UTAH
ELECTRICAL & COMPUTER ENGINEERING DEPARTMENT

ECE 1270


HOMEWORK #6 Solution

Summer 2009

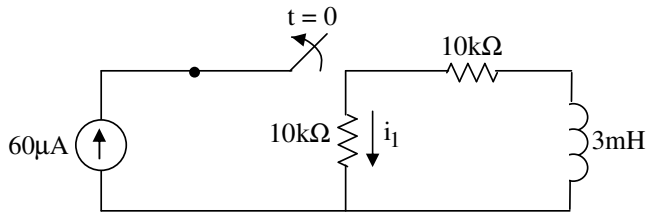1. After being closed a long time, the switch opens at $t = 0$. Find $i_1(t)$ for $t > 0$.



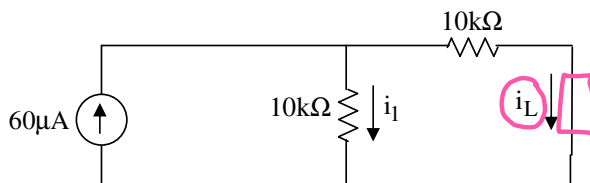
Step 1: (Redraw circuit at $t=0^-$ and solve for i_L . Inductor acts as a wire since it has sat for a long time)



This circuit is a current divider:

$$i_L = \frac{60\mu \cdot 10k}{10k + 10k} = 30\mu A$$

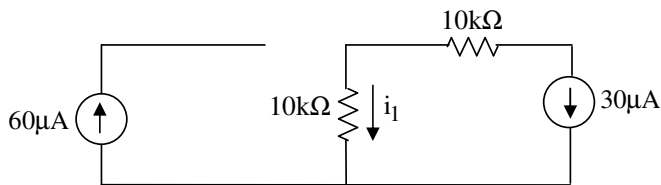
Step 2: **Initial Value** (Redraw circuit at $t=0^+$ and solve for unknown variable. Inductor acts as a **current source** since the current in the inductor has to remain the same.)



Only one current in the branch:


$$i_1 = -30\mu$$

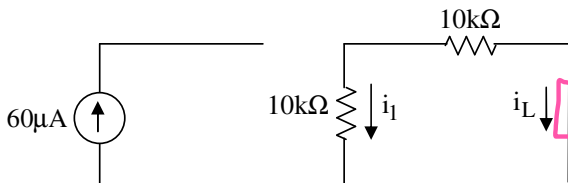Step 3: **Final Value** (Redraw circuit at $t=\infty$ and solve for unknown variable. Inductor acts as a wire since it has sat for a long time in this position.)



There are no sources connected to the final circuit:

$$i_1 = 0A$$

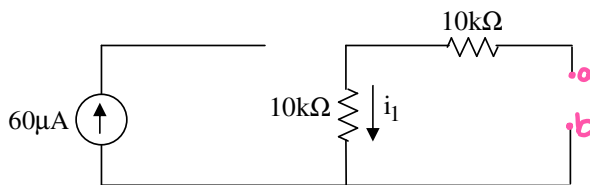


To find R_{eq} the inductor is removed from the final circuit to find path from top of inductor to bottom of inductor:

$$\tau = \frac{L}{R_{eq}} = \frac{3m}{10k + 10k} = 150nsec$$


Step 4: Plug values into general equation:

$$i_1(t) = 0 + [-30\mu - 0]e^{-t/150nsec} A = -30\mu e^{-t/150nsec} A$$

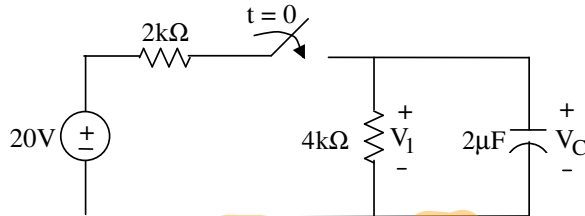2. After being open for a long time, the switch closes at $t = 0$. Find $V_1(t)$ for $t > 0$.




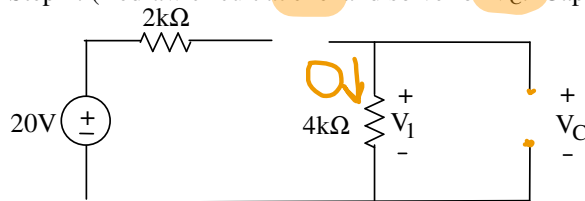Step 1: (Redraw circuit at $t=0^-$ and solve for V_C . Capacitor acts as an open since it has been a long time)




There is no source connected between V_C so $V_1 = V_C = 0$

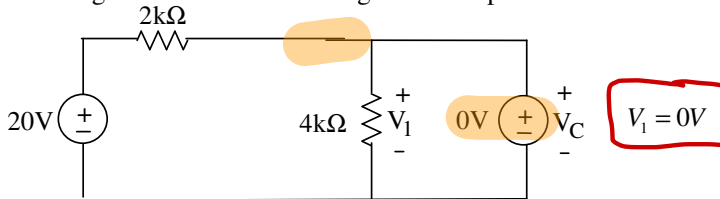Step 2: **Initial Value** (Redraw circuit at $t=0^+$ and solve for unknown variable. Capacitor acts as a voltage source since the voltage across capacitor has to remain the same.)



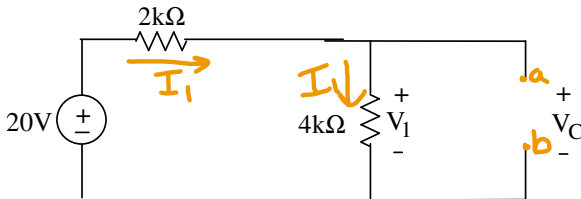Step 3: **Final Value** (Redraw circuit at $t=\infty$ and solve for unknown variable. Capacitor acts as an open since it has sat for a long time in this position.)



V_1 is found by a voltage divider:


$$V_1 = \frac{20 \cdot 4k}{2k + 4k} = \frac{80k}{6k} = \frac{40}{3} V$$

To find R_{eq} the capacitor is removed from the final circuit (same circuit) to find path from top to bottom of capacitor. Independent sources are removed and the equivalent resistance is found:


$$\tau = R_{eq} \cdot C = (4k \parallel 2k) \cdot 2\mu = \left(\frac{1}{\frac{1}{4k} + \frac{1}{2k}} \right) \cdot 2\mu = \frac{16m}{6} \text{ sec}$$

Step 4: Plug values into general equation:

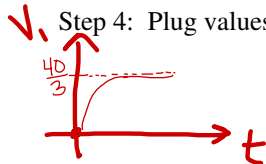
$$V_1(t) = \frac{40}{3} + \left[0 - \frac{40}{3} \right] e^{-6t/16msec} V = \frac{40}{3} (1 - e^{-6t/16msec}) V$$



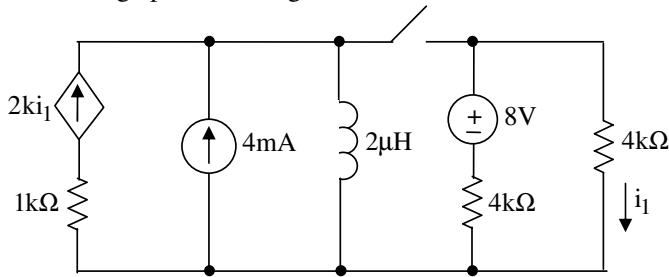3. After being open for a long time, the switch closes at $t = 0$. Find $i_1(t)$ for $t > 0$.



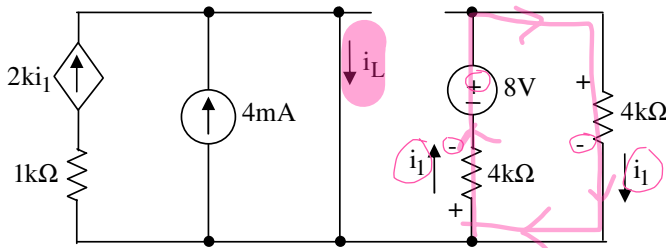Step 1: (Redraw circuit at $t=0^-$ and solve for i_L . Inductor acts as a wire since it has sat for a long time)




When the circuit contains a dependent source, an extra step is needed to determine the value of the dependent variable:

$$\text{Note: } -i_1 \cdot 4k + 8 - i_1 \cdot 4k = 0 \Rightarrow i_1 = \frac{8}{8k} = 1mA$$

Taking a current summation at the top node can be used to find i_L gives:

$$i_L = 2k \cdot i_1 + 4m \Rightarrow i_L = 2k \cdot 1m + 4m = 2.004A$$

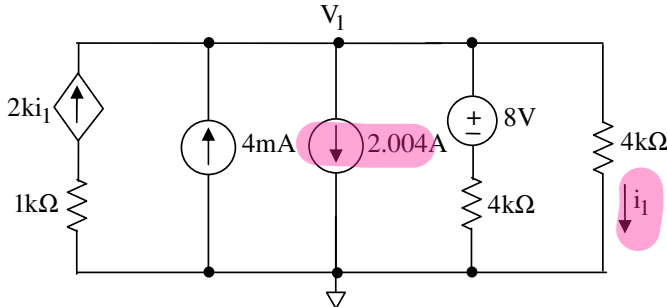Step 2: **Initial Value** (Redraw circuit at $t=0^+$ and solve for unknown variable. Inductor acts as a current source since the current in the inductor has to remain the same.)



Solve the circuit for i_1 . Mesh currents or node-voltage can be used. Node-voltage method:

- With dependent sources: solve for dependent variable in terms of either the mesh current or the node-voltage.

$$i_1 = \left(\frac{V_1}{4k} \right)$$


$$-2k \cdot i_1 - 4m + 2.004 + \left(\frac{V_1 - 8}{4k} \right) + i_1 = 0$$

$$-2k \cdot \left(\frac{V_1}{4k} \right) - 4m + 2.004 + \left(\frac{V_1 - 8}{4k} \right) + \left(\frac{V_1}{4k} \right) = 0$$

$$V_1 \left(\frac{-2k}{4k} + \frac{1}{4k} + \frac{1}{4k} \right) = +4m - 2.004 + \frac{8}{4k} \Rightarrow V_1 = -1.998 \cdot \left(\frac{4k}{-2.002k} \right) \approx 4V$$


The desired variable is i_1 :
$$i_1 = \left(\frac{V_1}{4k} \right) = \frac{4}{4k} = 1mA$$

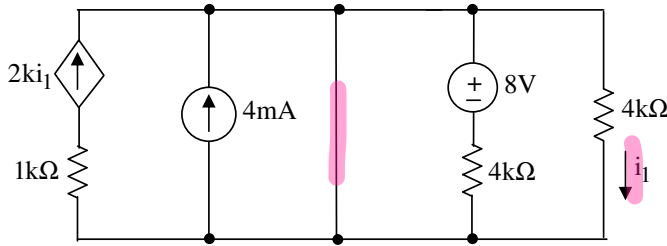Step 3: **Final Value** (Redraw circuit at $t = \infty$ and solve for unknown variable. Inductor acts as a wire since it has sat for a long time in this position.)



This wire puts 0V across 4k ohm resistor so:

$$i_1 = 0$$

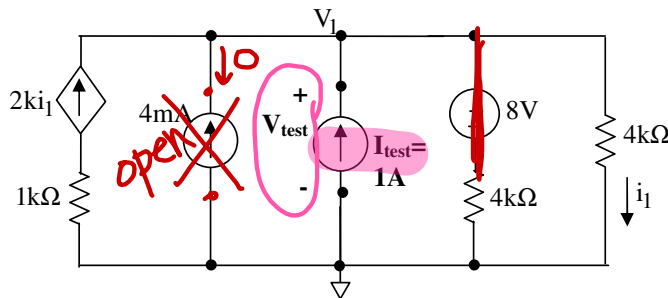

To find R_{eq} the inductor is removed from the final circuit to find path from top of inductor to bottom of inductor (Thevenin Resistance):

$$\text{Using a test source: } R_{th} = \frac{V_{test}}{I_{test}}$$

Setting $I_{test} = 1A$ means that only V_{test} needs to be found.

$$V_{test} = V_1$$

~~$$i_1 = \left(\frac{V_1}{4k}\right)$$~~

~~$$-2k \cdot i_1 - 4m - 1 + \left(\frac{V_1 - 8}{4k}\right) + i_1 = 0$$~~

~~$$-2k \cdot \left(\frac{V_1}{4k}\right) - 4m - 1 + \left(\frac{V_1 - 8}{4k}\right) + \left(\frac{V_1}{4k}\right) = 0$$~~

~~$$V_1 \left(\frac{-2k}{4k} + \frac{1}{4k} + \frac{1}{4k}\right) = +4m + 1 + \frac{8}{4k} \Rightarrow V_1 = 1.006 \cdot \left(\frac{4k}{-2.002k}\right) \approx -2V$$~~

~~$$V_{test} = -2V$$~~


~~$$R_{th} = \frac{V_{test}}{I_{test}} = \frac{-2V}{1A} = 2\Omega$$~~

~~$$\tau = \frac{L}{R_{eq}} = \frac{2\mu}{2} = 1\mu\text{sec}$$~~

$$-2k \left[\frac{V_1}{4k} \right] - 1 + \frac{V_1}{4k} + \frac{V_1}{4k} = 0$$

$$V_1 \left[\frac{-2k + 2}{4k} \right] = 1 \rightarrow V_1 \approx 1 \left(\frac{4k}{2.002} \right)$$


$$V_1 \approx -2V$$

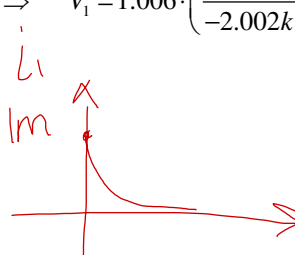


Step 4: Plug values into general equation:

$$i_1(t) = 0 + [1m - 0] e^{-t/1\mu\text{sec}} A = 1m e^{-t/1\mu\text{sec}} A$$

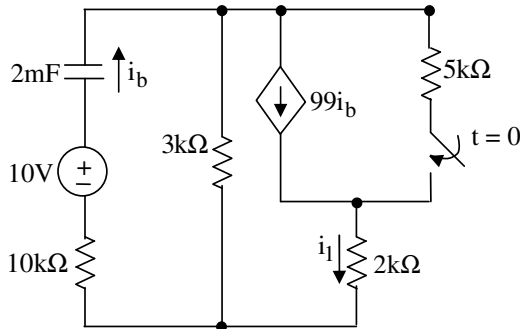4. After being open for a long time, the switch closes at $t = 0$. Find $i_1(t)$ for $t > 0$.




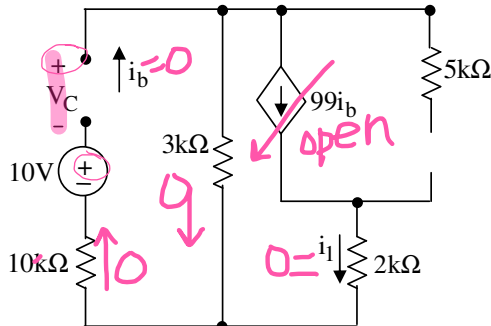Step 1: (Redraw circuit at $t=0^-$ and solve for V_c . Capacitor acts as an open since it has been a long time)



Solving for the dependent variable:
 $i_b = 0$ which opens the dependent source $\Rightarrow 99i_b = 0$
 Taking a V-loop to get V_c value (Be Careful- It is **not** 0 when there is a path with a V src.)
 $+0 + 10 + V_c - 0 = 0 \Rightarrow V_c = -10V$

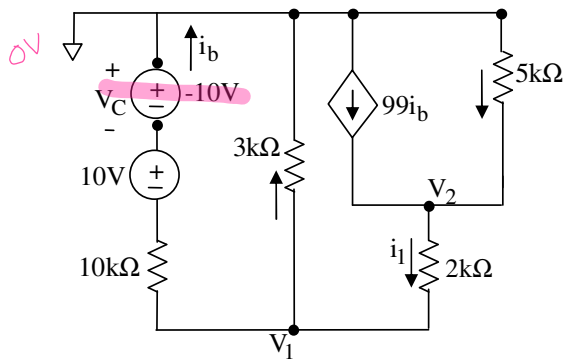Step 2: **Initial Value** (Redraw circuit at $t=0^+$ and solve for unknown variable. Capacitor acts as a voltage source since the voltage across capacitor has to remain the same.)



Using node-voltage to solve this circuit to find i_1 :
 First find dependent variable in terms of node-voltage variable, V_1 .

$$i_b = \frac{V_1 - (-10) - (-(-10))}{10k} = \frac{V_1}{10k}$$

Next, take current summation equation at V_1 node:

$$\frac{V_1}{10k} + \frac{V_1}{3k} - \frac{(V_1 - V_2)}{2k} = 0$$

Current summation equation at V_2 node:

$$\frac{(V_2 - V_1)}{2k} - 99 \cdot \frac{V_1}{10k} - \frac{(0 - V_2)}{5k} = 0$$


Using the first equation and solving for V_1 :

$$\begin{aligned} \frac{V_1}{10k} + \frac{V_1}{3k} - \frac{V_1}{2k} &= \frac{V_2}{2k} \\ V_1 \left(\frac{6}{60k} + \frac{20}{60k} - \frac{30}{60k} \right) &= \frac{V_2}{2k} \\ V_1 &= \frac{V_2}{2k} \left(\frac{60k}{-4} \right) = \frac{-15V_2}{2} \end{aligned}$$

Plugging into the second equation:

$$\begin{aligned} \frac{V_2}{2k} - \left(\frac{-15V_2}{4} \right) \left(\frac{1}{2k} \right) - 99 \cdot \frac{1}{10k} \left(\frac{-15V_2}{4} \right) + \frac{V_2}{5k} &= 0 \\ V_2 \left(\frac{1}{2k} + \frac{15}{8k} + \frac{99(15)}{40k} + \frac{1}{5k} \right) &= 0 \Rightarrow V_2 = 0 \\ V_1 &= 0 \\ i_1 &= 0 \end{aligned}$$

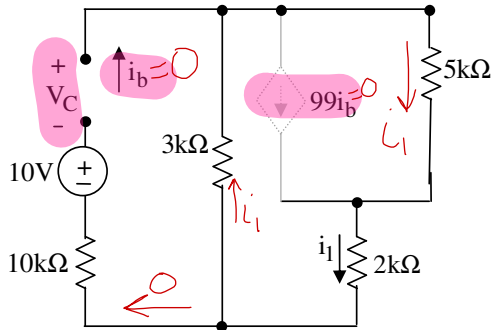Step 3: **Final Value** (Redraw circuit at $t=\infty$ and solve for unknown variable. Capacitor acts as an open since it has sat for a long time in this position.)




$i_b=0$ this means that $99i_b$ source becomes open.

$$i_1=0$$


Since i_1 is always the same $\Rightarrow i_1(t)=0$.

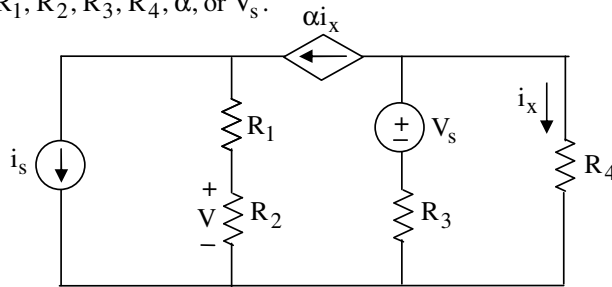5. Using superposition, derive an expression for V that contains no circuit quantities other than $i_s, R_1, R_2, R_3, R_4, \alpha,$ or V_s .



Step 1: $i_s=0$ (off), $V_s=on$

Using mesh currents:

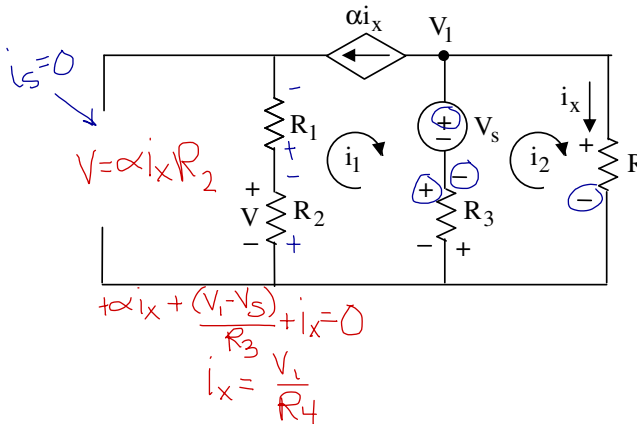

$$i_1 = -\alpha i_x$$

$$i_2 = i_x$$

Using a voltage loop and then substituting above eq:

$$(+i_1 - i_2)R_3 + V_s - i_2R_4 = 0$$

$$(-\alpha i_x - i_x)R_3 + V_s - i_xR_4 = 0$$


$$i_x(+\alpha R_3 + R_3 + R_4) = V_s$$

$$i_x = \frac{V_s}{(+\alpha R_3 + R_3 + R_4)}$$

$$V = \alpha i_x R_2 = \frac{\alpha V_s R_2}{(+\alpha R_3 + R_3 + R_4)}$$

Step 1: $i_s=on$, $V_s=0$ (off)

Using mesh currents:

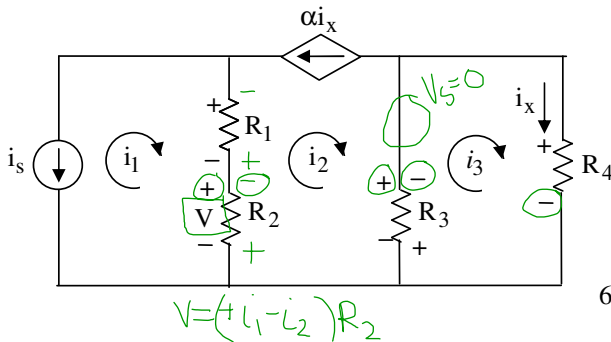

$$i_1 = i_s \quad i_3 = -i_s$$

$$i_2 = -\alpha i_x$$


$$i_3 = i_x$$

Using a voltage loop and then substituting above eq:

$$\begin{aligned} (+i_2 - i_3)R_3 - i_3R_4 &= 0 \\ (-\alpha i_x - i_x)R_3 - i_xR_4 &= 0 \\ i_x(+\alpha R_3 + R_3 + R_4) &= 0 \\ \frac{i_x}{i_2} &= 0 \\ \frac{i_2}{V} &= \frac{-i_s R_2}{i_s R_2} \end{aligned}$$

The total V is the sum of both solutions:
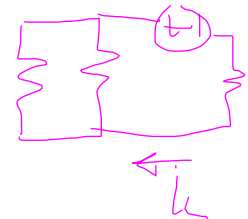
$$V = i_s R_2 + \frac{\alpha V_s R_2}{(+\alpha R_3 + R_3 + R_4)}$$



6. After being closed for a long time, the switch opens at $t=0$.
- Calculate the energy stored on the inductor as $t \rightarrow \infty$.
 - Write a numerical expression for $v(t)$ for $t > 0$.

Sol'n: a) As $t \rightarrow \infty$, the switch is open and the L acts like a wire. The $20\text{ k}\Omega$ and the $30\text{ k}\Omega$ are in parallel, (which is $12\text{ k}\Omega$), and we use Ohm's law to find $i_L(t \rightarrow \infty)$:

$$i_L(t \rightarrow \infty) = \frac{300\text{ mV}}{12\text{ k}\Omega + 3\text{ k}\Omega} = \frac{300\text{ mV}}{15\text{ k}\Omega} = 20\text{ }\mu\text{A}$$

The stored energy is a function of the square of the current in the inductor:

$$w_L(t \rightarrow \infty) = \frac{1}{2} L i_L^2(t \rightarrow \infty) = \frac{1}{2} 150\text{ m} \cdot (20\text{ }\mu)^2 = 30\text{ }\mu\text{J}$$

- b) We first find the current in the inductor for $t = 0^-$. The switch is closed, shorting out both the $20\text{ k}\Omega$ and $30\text{ k}\Omega$ resistors. The inductor looks like a wire. This leaves only the 300 mV source and $3\text{ k}\Omega$ resistor:

$$i_L(0^-) = \frac{300\text{ mV}}{3\text{ k}\Omega} = 100\text{ }\mu\text{A}$$

At $t = 0^+$, the switch is open, the $20\text{ k}\Omega$ and the $30\text{ k}\Omega$ are in parallel, (which is $12\text{ k}\Omega$), and the inductor acts like a current source with the same current as the inductor had at $t = 0^-$. The voltage, $v(t = 0^+)$, is given by the inductor current times the parallel resistance of $12\text{ k}\Omega$.

$$v(t = 0^+) = 100\text{ }\mu\text{A} \cdot 12\text{ k}\Omega = 1.2\text{ V}$$

From earlier, we have that the inductor current as t approaches infinity is $20\text{ }\mu\text{A}$. The voltage, $v(t \rightarrow \infty)$, is given by this inductor current times the parallel resistance of $12\text{ k}\Omega$.


$$v(t \rightarrow \infty) = 20\text{ }\mu\text{A} \cdot 12\text{ k}\Omega = 0.24\text{ V}$$

Now we use the general form of solution for RL problems:

$$v(t > 0) = v(t \rightarrow \infty) + [v(0^+) - v(t \rightarrow \infty)]e^{-t/(L/R_{Th})}$$

or, with $L/R_{Th} = 150\text{ mH}/(12\text{ k}\Omega + 3\text{ k}\Omega) = 10\text{ }\mu\text{s}$:

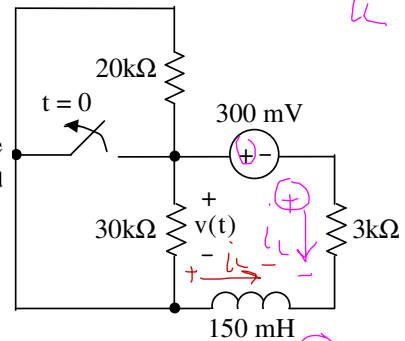
$$v(t > 0) = 0.24 + [1.2 - 0.24]e^{-t/10\text{ }\mu\text{s}} = 0.24 + 0.96e^{-t/10\text{ }\mu\text{s}}\text{ V}$$




Handwritten notes for the circuit diagram:

$$+i_L(3\text{K}) + 300\text{mV} = 0$$

$$i_L = -100\text{ }\mu\text{A}$$

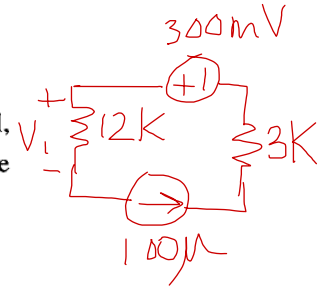

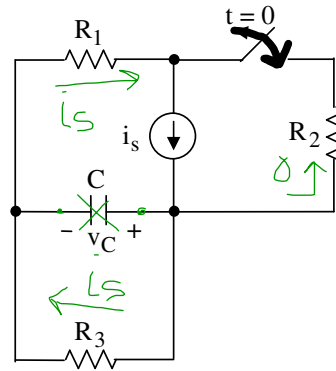7. After being open for a long time, the switch closes at $t=0$.
- Write an expression for $v_C(t=0^+)$.
 - Write an expression for $v_C(t>0)$ in terms of $i_s, R_1, R_2, R_3,$ and C .



SOL'N: a) We first find the voltage across the capacitor for $t = 0^-$. The switch is open, eliminating R_2 from consideration. The capacitor looks like an open. This leaves only the i_s source driving R_1 and R_3 in series. The capacitor is directly across R_3 and so has the same voltage as R_3 :

$$v_C(0^-) = i_s R_3$$

At $t = 0^+$, the capacitor has the same voltage as at $t = 0^-$.

$$v_C(0^+) = i_s R_3$$

- b) As $t \rightarrow \infty$, the switch is closed, the C acts like an open, and we have a current divider with R_2 on one side and $R_1 + R_3$ on the other. The current through R_3 is

$$I_3 = i_s \frac{R_2}{R_1 + R_2 + R_3}$$

The voltage, v_C , as $t \rightarrow \infty$ is the same as the voltage across R_3 , and is given by i times R_3 :

$$v_C(t \rightarrow \infty) = i_s \frac{R_2 R_3}{R_1 + R_2 + R_3}$$


For the time constant of the circuit, we take the Thevenin resistance from the terminals where the C is attached with the switch closed for $t > 0$. Since we have only an independent source, we turn off the source, i_s , and look into the circuit from the terminals where C is attached (but without the C). We see R_3 in parallel with $R_1 + R_2$.

$$R_{Th} = R_3 \parallel (R_1 + R_2)$$

Now we use the general formula for RC circuit solutions:


$$v(t > 0) = v(t \rightarrow \infty) + [v(0^+) - v(t \rightarrow \infty)] e^{-t/R_{Th}C}$$
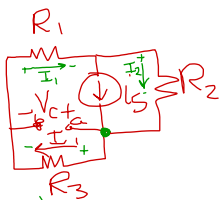
$$v(t > 0) = i_s \frac{R_2 R_3}{R_1 + R_2 + R_3} + [i_s R_3 - i_s \frac{R_2 R_3}{R_1 + R_2 + R_3}] e^{-t/R_3 \parallel (R_1 + R_2) C}$$



$$\begin{aligned} -i_s + I_1 - I_2 &= 0 \\ -I_1(R_3 + R_1) - I_2 R_2 &= 0 \\ I_2 &= I_1 - i_s \\ -I_1(R_1 + R_3) - R_2(I_1 - i_s) &= 0 \end{aligned}$$
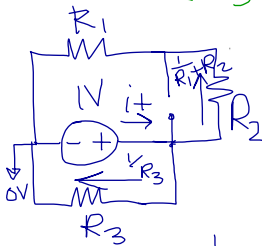
$$I_1 = \frac{i_s R_2}{R_1 + R_2 + R_3}$$



$$-i_t + \frac{1}{R_3} + \frac{1}{R_1 + R_2} = 0$$

or

Use the circuit below for both problem 8 and 9.

8. Calculate the value of R_L that would absorb maximum power.

Use $R_L = R_{Th}$ for maximum power transfer. To find R_{Th} , we turn off the independent sources and look in from the terminals where R_L is attached (with R_L removed). The voltage source becomes a wire, and the current source becomes an open circuit.

$$R_{Th} = (2 \text{ k}\Omega + 22 \text{ k}\Omega) \parallel 24 \text{ k}\Omega + 3 \text{ k}\Omega = 12 \text{ k}\Omega + 3 \text{ k}\Omega = 15 \text{ k}\Omega$$

We use this Thevenin resistance value for R_L :

$$R_L = 15 \text{ k}\Omega$$

9. Calculate that value of maximum power R_L could absorb.

The maximum power transferred is


$$p_{\max} = \frac{v_{Th}^2}{4R_{Th}}$$

The Thevenin equivalent voltage is the voltage across R_L without R_L . Since there is no R_L , the 3 mA current must all flow through the 3 k Ω resistance and then divide as it flows through the other resistors. It turns out that the 3 mA flows through R_{Th} , and the voltage arising from the 3 mA is found using Ohm's law. To this voltage, we add the 15 V from the voltage source to get v_{Th} .


$$v_{Th} = 3 \text{ mA} \cdot 15 \text{ k}\Omega + 15 \text{ V} = 45 + 15 \text{ V} = 60 \text{ V}$$

Now we use the formula for maximum power transferred:
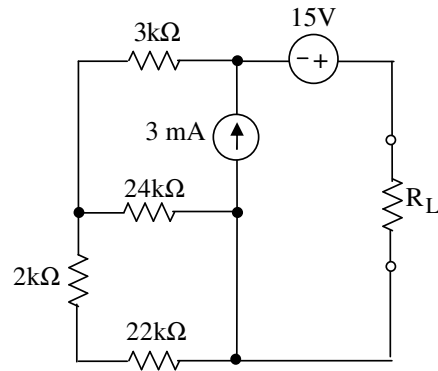
$$p_{\max} = \frac{v_{Th}^2}{4R_{Th}} = \frac{60^2}{4 \cdot 15 \text{ k}} \text{ W} = 60 \text{ mW}$$



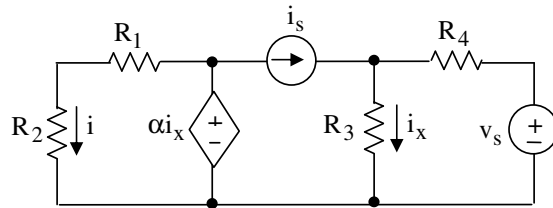10. Using superposition, derive an expression for i that contains no circuit quantities other than i_s , R_1 , R_2 , R_3 , R_4 , α , or V_s .



SOL'N: First, we turn off the independent source, i_s . This means the current source turns into an open circuit, separating the circuit into two pieces. On the right, we have v_s in series with R_3 and R_4 .

$$i_{x1} = \frac{v_s}{R_3 + R_4}$$

On the left side, we have the dependent voltage source (whose voltage is now known) and R_1 in series with R_2 .

$$i_1 = \frac{\alpha i_{x1}}{R_1 + R_2} = \frac{\alpha v_s}{(R_1 + R_2)(R_3 + R_4)}$$

Second, we turn off the independent source, v_s . This turns the voltage source into a wire, and we have a current divider for i_s flowing through R_3 parallel R_4 .

$$i_{x2} = \frac{i_s R_4}{R_3 + R_4}$$

On the left side, the dependent source fixes the voltage across R_1 and R_2 . Thus, we have the dependent voltage source (whose voltage is now known) and R_1 in series with R_2 , just as we did before.

$$i_2 = \frac{\alpha i_{x2}}{R_1 + R_2} = \frac{\alpha i_s R_4}{(R_1 + R_2)(R_3 + R_4)}$$

We sum the two currents to find the total value of i :

$$i = i_1 + i_2 = \frac{\alpha(v_s + i_s R_4)}{(R_1 + R_2)(R_3 + R_4)}$$