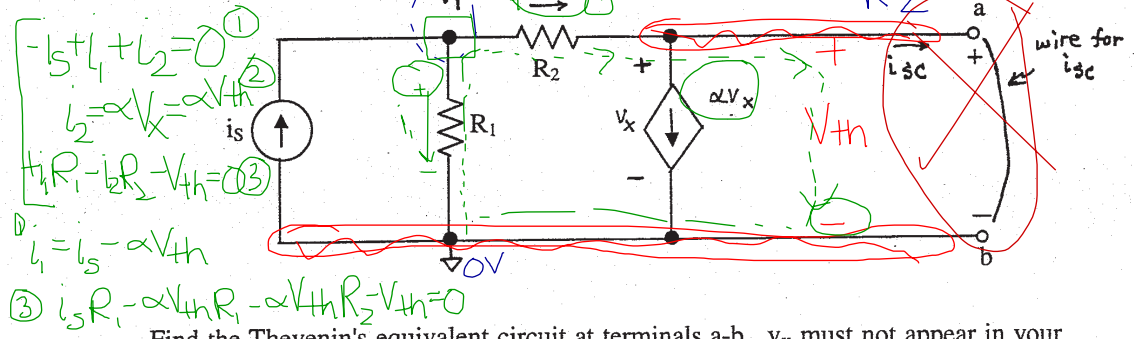


2. (25 points)

$$-i_s + \frac{V_1}{R_1} + \frac{(V_1 - V_{th})}{R_2} = 0, \quad \frac{V_{th} - V_1}{R_2} + \alpha V_{th} = 0$$



$$-i_s + i_1 + i_2 = 0$$

$$i_2 = \alpha V_x = \alpha V_{th}$$

$$i_1 R_1 - i_2 R_2 - V_{th} = 0$$

$$i_1 = i_s - \alpha V_{th}$$

$$i_s R_1 - \alpha V_{th} R_1 - \alpha V_{th} R_2 - V_{th} = 0$$

Find the Thevenin's equivalent circuit at terminals a-b.  $v_x$  must not appear in your solution. **Hint:** Use node voltage method to find  $v$  above  $R_1$ . **Note:**  $\alpha > 0$ .

$$V_{th}(\alpha R_1 + \alpha R_2 + 1) = i_s R_1$$
 sol'n:  $V_{Th} = V_{ab}$  with no load connected to a, b.

$$R_{Th} = \frac{V_{Th}}{i_{sc}}$$
 where  $i_{sc} = i$  out of 'a' terminal with wire from a to b

Find  $v_1$ : Use Node V method

write  $v_x$  in terms of  $v_1$ :  $V_x = v_1 - \alpha V_x R_2$   
 $V_x = v_1 / (1 + \alpha R_2)$

Node  $v_1$  eqn:  $-i_s + \frac{v_1}{R_1} + \frac{v_1 - V_x}{R_2} = 0$

$$v_1 \left( \frac{1}{R_1} + \frac{\alpha}{1 + \alpha R_2} \right) = i_s$$

$$v_1 = i_s \frac{1}{\frac{1}{R_1} + \frac{\alpha}{1 + \alpha R_2}}$$

$$= v_1 \left( 1 - \frac{1}{1 + \alpha R_2} \right) = \frac{1 + \alpha R_2}{1 + \alpha R_2} \cdot \frac{1}{R_2} = \frac{1}{R_2}$$

$$= v_1 \frac{\alpha}{1 + \alpha R_2}$$

$$= v_1 \left( 1 - \frac{\alpha R_2}{R_1} \right)$$


$$V_{Th} = v_x = \frac{v_1}{1 + \alpha R_2} = i_s \frac{1}{\frac{1 + \alpha R_2}{R_1} + \alpha}$$

$$V_{Th} = \frac{i_s}{\frac{1 + \alpha R_2}{R_1} + \alpha} = i_s \left[ R_1 \parallel (R_2 + 1/\alpha) \right] \cdot \frac{1/\alpha}{R_2 + 1/\alpha}$$
 Latter formula from using  $1/\alpha$  for Reg of dep. s.

$$R_{Th} = \frac{V_{Th}}{i_{sc}}$$
 For  $i_{sc}$  we have  $V_x = 0V$ .  
 Then  $v_1 = i_s \cdot R_1 \parallel R_2$  (no dep src)

$$R_{Th} = \frac{i_s}{\frac{1 + \alpha R_2}{R_1} + \alpha} \cdot \frac{R_1 + R_2}{i_s R_1}$$
 and  $i_{sc} = \frac{i_s R_1}{R_1 + R_2}$
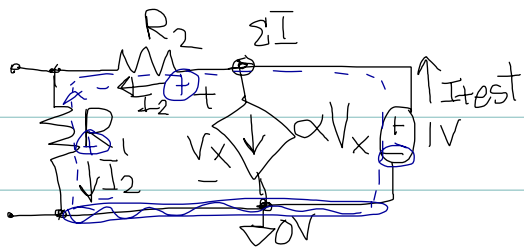
$$R_{Th} = \frac{R_1 + R_2}{1 + \alpha(R_1 + R_2)} = R_1 \parallel (R_2 + \frac{1}{\alpha})$$
 Latter formula from using  $1/\alpha$  for dep src and looking in from a, b with  $i_s$  src off.




$$+I_2 + \alpha V_x - I_{test} = 0$$

$$+I_2(R_1) + I_2 R_2 - I = 0$$

$$I_2 = \frac{I}{R_1 + R_2}$$

$$I_{test} = \alpha(I) + \frac{I}{R_1 + R_2} = \frac{\alpha(R_1 + R_2) + 1}{(R_1 + R_2)} I$$
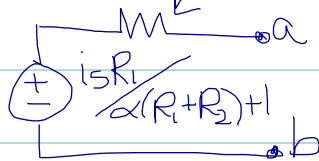
$$R_{th} = \frac{I}{I_{test}} = \frac{R_1 + R_2}{\alpha(R_1 + R_2) + 1}$$



Homework #4 Examples

Sp 05


Dr. Neil Cotter

89

5.

$$-1(5) - v - 10 = 0$$

$$v = -15$$

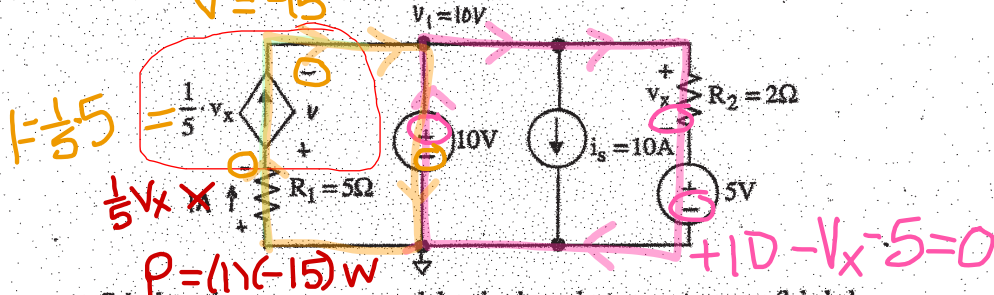

Calculate the power consumed by the dependent current source, (labeled  $\frac{1}{5}v_x$ ). Note: If a source supplies power, the power it consumes is negative.

sol'n:  $v$  on top rail = 10V from 10V src (if ref on bottom).

Then  $v_x = 5V = 10V - 5V$

$\therefore \frac{1}{5}v_x = \frac{1}{5}5V = 1A$  for dependent src

Using  $v$ -loop on left,  $-1A \cdot R_1 - v - 10V = 0V$

or  $v = -10V - 1A \cdot R_1 = -15V$

power  $\equiv P = \frac{1}{5}v_x \cdot v = 1A(-15V) = -15W$


$P = -15W$

90

$$P = \frac{1}{3} \cdot (18)(-24) =$$

$$V = -24$$

3. (25 points)

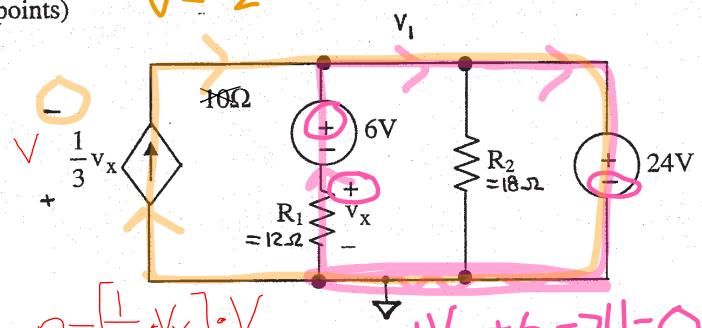

$$P = \left[ \frac{1}{3} \cdot v_x \right] \cdot V$$

$$+v_x + 6 - 24 = 0 \rightarrow v_x = 18$$

Calculate the power consumed by the dependent current source, (labeled  $\frac{1}{3}v_x$ ). **Note:** If a source supplies power, the power it consumes is negative.

sol'n: Find  $v_1$ . Then  $v$  across dep src is  $-v_1$ .  
 Write  $v_x$  in terms of  $v_1$ :  $v_x = v_1 - 6V$

Node V for  $v_1$  node:  $-\frac{1}{3}(v_1 - 6V) + \frac{v_1 - 6V}{R_1} + \frac{v_1}{R_2} + ?!$

We don't need eq'n!  $v_1 = 24V$  from src on right.


$$\therefore P = \frac{1}{3} v_x \cdot (-v_1) = \frac{1}{3} (v_1 - 6V) (-v_1)$$

$$= \frac{1}{3} (24V - 6V)(-24V)$$

$$= \frac{1}{3} (18V)(-24V)$$

$$P = -144 W$$


EX:

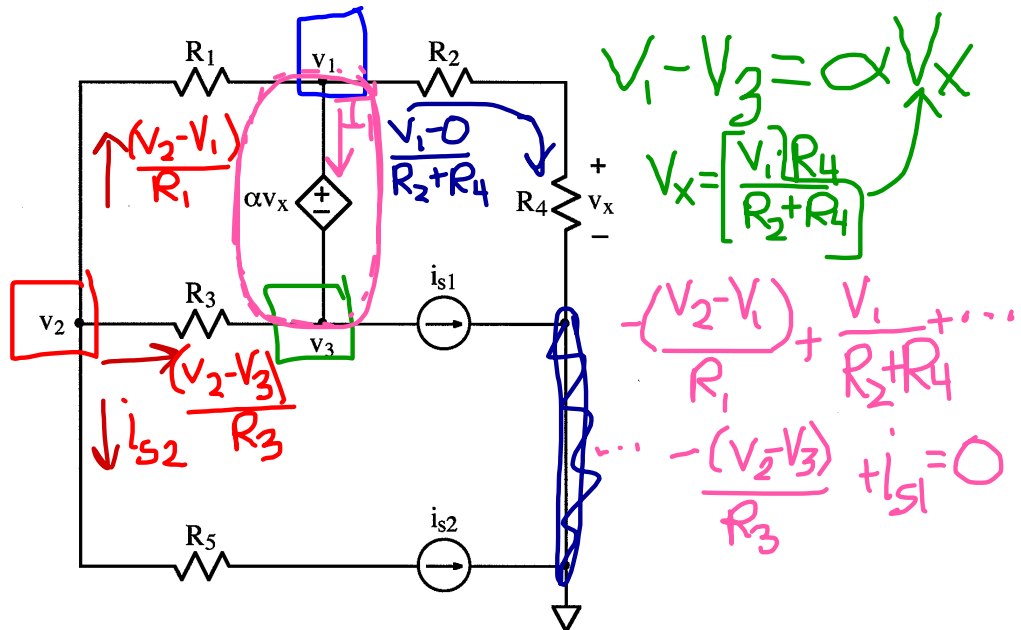

For the circuit shown, write three independent equations for the node-voltages,  $v_1, v_2$ , and  $v_3$ . The quantity  $v_x$  must not appear in the equations.

sol'n: We first write  $v_x$  in terms of node-v's.

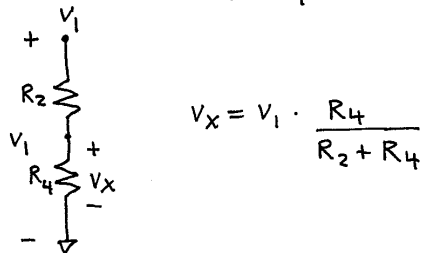We use a v-divider since we have  $v_1$  across  $R_2$  in series with  $R_4$ :



We have a v-src connecting  $v_1$  to  $v_3$ . So  $v_1, v_3$  form a supernode.

We write a current summation eq'n for  $v_1, v_3$ . We find sum of i's flowing out of bubble containing  $v_1, v_3$ , and the dependent  $v$ -src.

$$(1) \quad v_1, v_3 \text{ node: } \frac{v_1 - v_2}{R_1} + \frac{v_1 - 0V}{R_2 + R_4} + \frac{v_3 - v_2}{R_3} + i_{s1} = 0A$$

We also write a voltage eq'n for  $v_1$  and  $v_3$ . Note that we substitute for  $v_x$  to obtain an eq'n containing only node voltages.


$$(2) \quad v_1 = v_3 + \underbrace{\alpha \left( \frac{v_1 R_4}{R_2 + R_4} \right)}_{v_x}$$

For  $v_2$ , we just sum currents out of node.

$$(3) \quad v_2 \text{ node: } \frac{v_2 - v_1}{R_1} + \frac{v_2 - v_3}{R_3} + i_{s2} = 0A$$

We now have our 3 eq'ns for  $v_1, v_2$ , and  $v_3$ .

Ex:

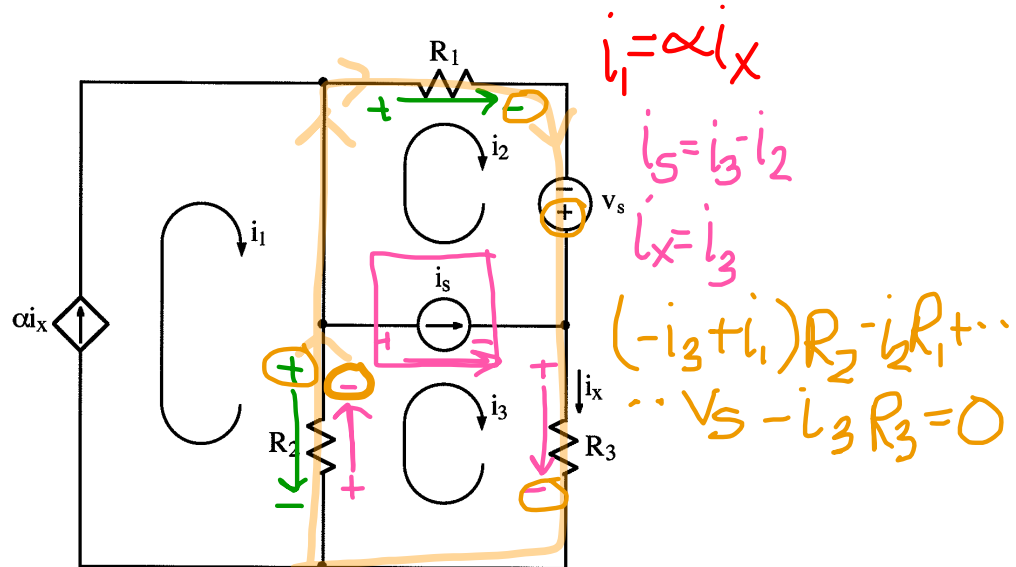

For the circuit shown, write three independent equations for the three mesh currents,  $i_1$ ,  $i_2$ , and  $i_3$ . The quantity  $i_x$  must not appear in the equations.


sol'n: We first write  $i_x$  in terms of mesh currents.

Since  $i_x$  is a current on the outside edge of the circuit, (flowing thru  $R_3$ ), it is equal to the mesh (also called "loop") current.

$$i_x = i_3$$

Next we look for super meshes where a current src is between two loops. We have a supermesh for  $i_2$ ,  $i_3$  with  $i_s$  in between.

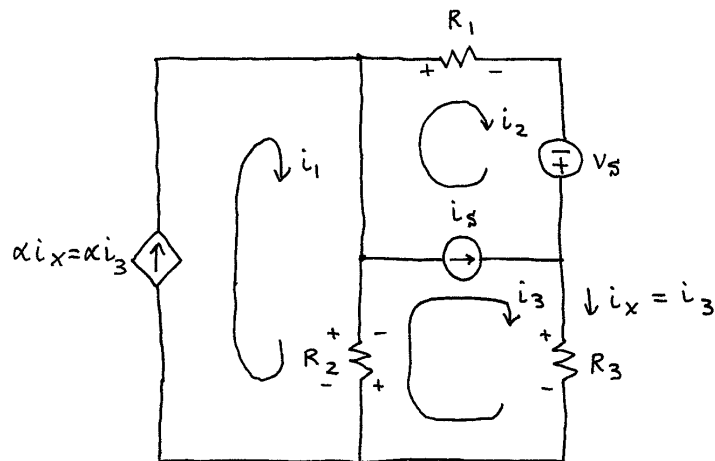We draw the circuit model before writing our eq'n's.



$i_2, i_3$  loop:  $-i_3 R_2 + i_1 R_2 - i_2 R_1 - i_3 R_3 = 0V$   
 (supermesh uses loop around right half of circuit)

We add a current eq'n for  $i_s$  src between loops.

$i_s = i_3 - i_2$  ( $i_2$  has - sign because it is measured in direction opposite to direction of  $i_s$ )

$i_2 = i_3 - i_s$


Finally, for the  $i_1$  loop we encounter a curious situation. Since we have a current source on the outside edge of the circuit, we must have that  $i_1 =$  current for src.

Thus,  $i_1 = \alpha i_3$ . This is the eq'n for  $i_1$ .

We now have 3 eq'ns in  $i_1, i_2, i_3$  which we could solve to find  $i_1, i_2,$  and  $i_3$ .




EX:

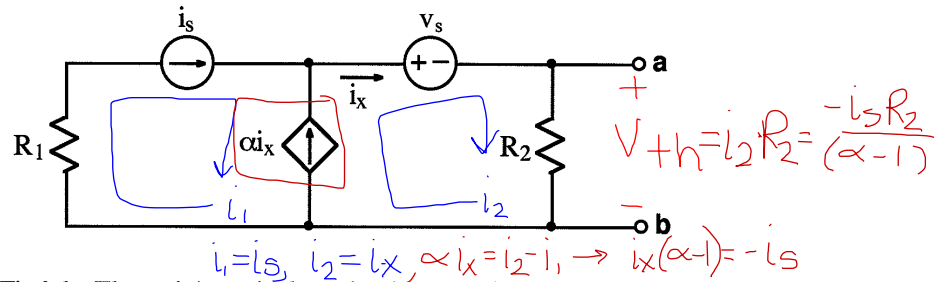


Find the Thevenin's equivalent circuit at terminals a-b.  $i_x$  must not appear in your solution. Note:  $\alpha \neq 1$ .

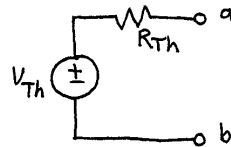sol'n: We must find  $V_{Th}$  and  $R_{Th}$  for the Thevenin equivalent circuit that has the same behavior as the above circuit when viewed from a,b terminals.




$V_{Th} = V_{a,b}$  for circuit with nothing connected across a,b.

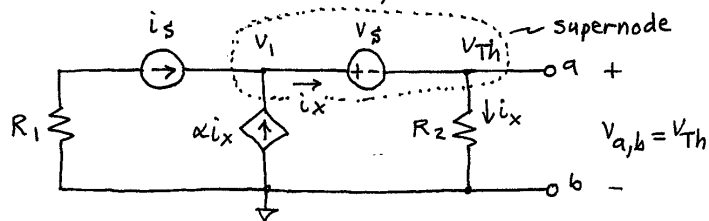We can use node-v method or another method of our choice to find  $V_{a,b}$



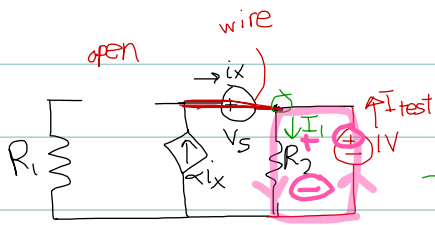We first define  $i_x$  in terms of node voltages. Here,  $i_x$  flows thru  $R_2$ . Thus  $i_x = \frac{V_{Th}}{R_2}$ .



$$-i_x + I_1 - I_{test} = 0$$

$$I_1 = I_{test}$$

$$i_x = \alpha i_x$$

$$i_x - \alpha i_x = 0$$


$$i_x(1 - \alpha) = 0$$

$$i_x = 0$$

$$+1 - I_{test} \cdot R_2 = 0$$

$$I_{test} = \frac{1}{R_2}$$

$$R_{th} = \frac{1}{I_{test}} = R_2$$

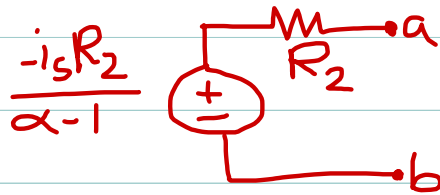

We have a supernode for  $v_i$  and  $v_{Th}$ .

So we sum currents out of a bubble around  $v_i$ ,  $v_{Th}$ , and  $v_s$ .

$$v_i, v_{Th} \text{ node: } -i_s - \alpha \frac{v_{Th}}{R_2} + \frac{v_{Th}}{R_2} = 0A$$

We could continue on to write a voltage eq'n for  $v_i$  and  $v_{Th}$ :  $v_i = v_{Th} + v_s$

But our first eq'n has only  $v_{Th}$  in it; we can solve the first eq'n for  $v_{Th}$  and stop there.


$$\text{Rearranging gives } v_{Th} \left( \frac{1}{R_2} - \frac{\alpha}{R_2} \right) = i_s$$
$$\text{or } v_{Th} = \frac{i_s R_2}{1-\alpha}$$

To find  $R_{Th}$ , we can use the method of shorting out a and b and measuring the current in the wire. This is  $i_{sc}$  for short circuit. If we look at a Thevenin

equivalent circuit with a wire from a to b, we have current  $i_{sc} = \frac{v_{Th}}{R_{Th}}$ .

$$\text{Thus, } R_{Th} = \frac{v_{Th}}{i_{sc}}$$

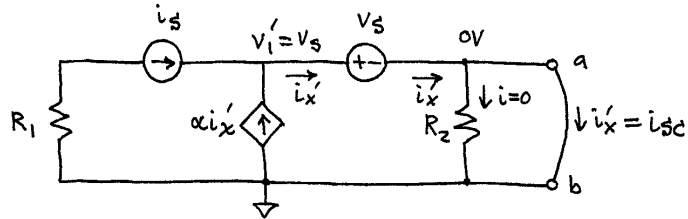We redraw our circuit with a wire from a to b.



This is a different circuit than before.  
We have 0V at **a**, (instead of  $v_{Th}$ ), and  
no current flows in  $R_2$  since it is  
bypassed by a wire. Also,  $i_{sc} = i_x'$ .

We also have  $v_1 = 0V + v_s = v_s$ . Circuit is solved.  
or is it? We still need to find  $i_{sc} = i_x'$

Using a current summation at  $v_1$ , we have

$$-i_s - \alpha i_x' + i_x' = 0A$$

$$\text{or } i_x' (1 - \alpha) = i_s$$

$$\text{or } i_x' = \frac{i_s}{1 - \alpha} = i_{sc}$$

$$\text{Using } R_{Th} = \frac{v_{Th}}{i_{sc}} \text{ gives } R_{Th} = \frac{i_s R_2}{\frac{i_s}{1 - \alpha}}$$

$$\text{or } R_{Th} = R_2 \text{ (Nothing else plays a role in } R_{Th}\text{)}$$


Consistency check: Set  $\alpha = 0 \Rightarrow$  dependent src = open.

Then  $R_1, v_s$  in series with current src  $i_s$  irrelevant.

We have Norton equiv,  $i_s$  and  $R_2$ :  $v_{Th} = i_s R_2$ ,  $R_{Th} = R_2$  ✓

$$+V_1 - I_2 \left(\frac{1}{3}\right) = 0 \rightarrow V_1 = 1$$

Ex:

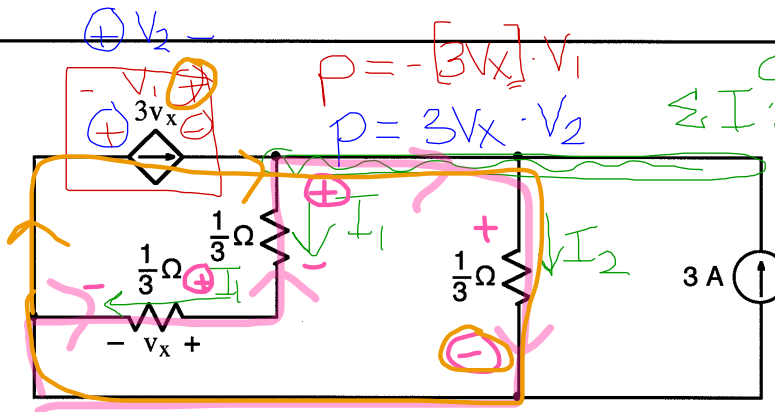

$$P = -[3v_x] \cdot V_1$$

$$P = 3v_x \cdot V_2$$

$$\sum I = -3v_x + I_1 + I_2 - 3$$

$$v_x = I_1 \left(\frac{1}{3}\right)$$

$$-3\left(\frac{1}{3}\right)I_1 + I_1$$

$$I_2 = 3$$


Calculate the power dissipated in the dependent current source, (labeled  $3v_x$ ).

$$+ \frac{2}{3}I_1 = \frac{1}{3}(3) \rightarrow I_1 = \frac{3}{2} \rightarrow v_x = \frac{1}{2}$$

sol'n: Any method of solution is allowed, (provided it is a valid approach)

$$P = -3 \cdot \frac{1}{2}(1) = -\frac{3}{2} \text{ W}$$

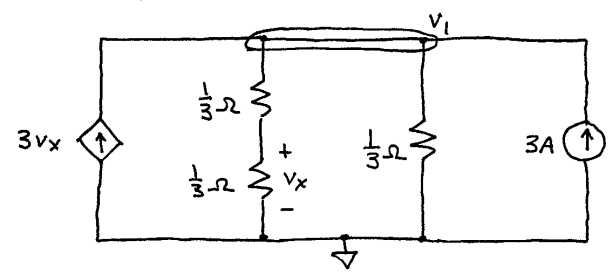We'll use node-voltage method with reference on bottom and  $v_1$  on top. It also helps to redraw circuit.



We write  $v_x$  in terms of  $v_1$  by using a voltage divider:


$$v_x = v_1 \cdot \frac{\frac{1}{3} \Omega}{\frac{1}{3} \Omega + \frac{1}{3} \Omega} = \frac{v_1}{2}$$

Now we write the current summation eq'n for node  $v_1$ .

$$-3 \left( \frac{v_1}{2} \right) + \frac{v_1}{\frac{1}{3}\Omega + \frac{1}{3}\Omega} + \frac{v_1}{\frac{1}{3}\Omega} - 3A = 0A$$

$$\text{or } v_1 \left( -\frac{3}{2\Omega} + \frac{3}{2\Omega} + \frac{3}{\Omega} \right) = 3A$$
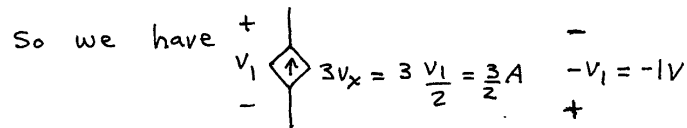
$$\text{or } v_1 = 1A \cdot \Omega = 1V$$




Power is  $p = iv$  where  $i, v$  follow passive sign convention.

$$p = \frac{3}{2}A \cdot (-1V) = -\frac{3}{2}W$$


Note: In this problem we can replace the dependent src with a resistor, (even before we know the value of  $v_1$ ).

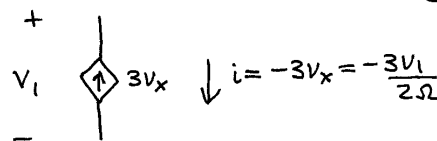We have voltage  $v_1$  across dependent src and current  $-3v_x = -\frac{3v_1}{2}$




Then  $R_{eq} = \frac{v_1}{-\frac{3v_1}{2\Omega}} = -\frac{2}{3}\Omega$

Use this instead of dependent src:

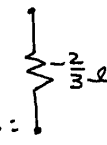


EX:

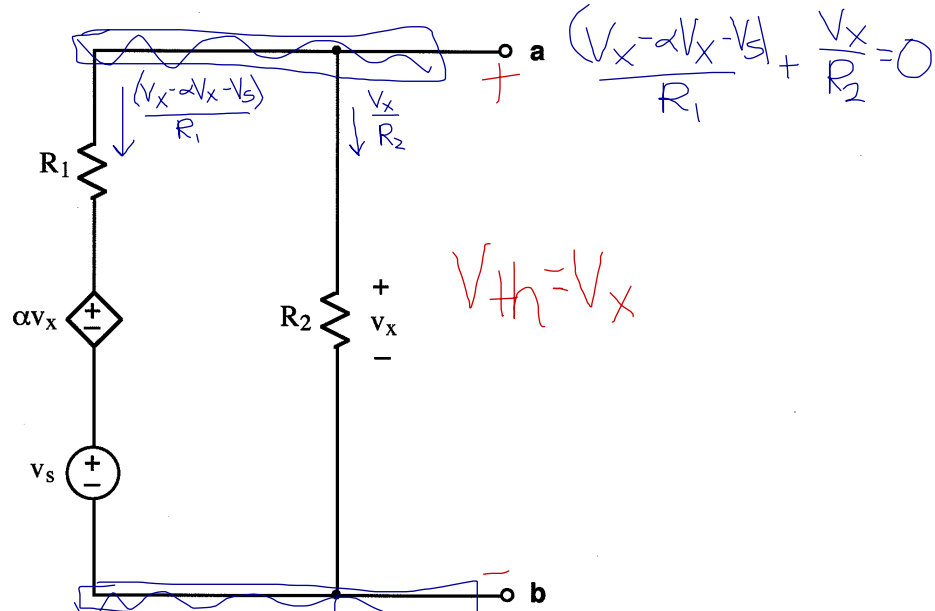

Find the Thevenin equivalent circuit at terminals a-b.  $v_x$  must not appear in your solution. **Hint:** Use the node-voltage method. **Note:**  $0 < \alpha < 1$ .

sol'n:  $V_{Th} = v_{a,b}$  with nothing connected across a, b

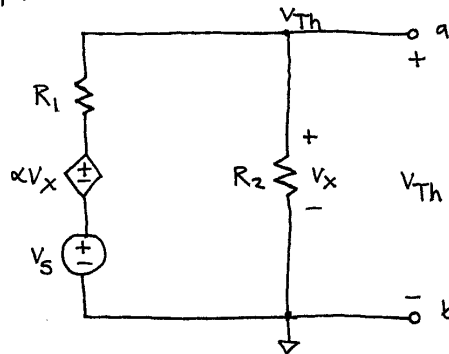Using the node-voltage method, with the reference at the bottom and  $v_{Th}$  at the top, our circuit is as follows:



We write  $v_x$  in terms of  $v_{Th}$ :

$$v_x = v_{Th}$$

The current summation for the  $v_1$  node has only two terms:

$$\frac{v_{Th} - (v_s + \alpha v_{Th})}{R_1} + \frac{v_{Th}}{R_2} = 0 \text{ mA}$$

or

$$v_{Th} \left( \frac{1}{R_1} - \frac{\alpha}{R_1} + \frac{1}{R_2} \right) = \frac{v_s}{R_1}$$

Multiplying both sides by  $R_1$  yields

$$v_{Th} \left( 1 - \alpha + \frac{R_1}{R_2} \right) = v_s$$

or

$$v_{Th} = \frac{v_s}{1 - \alpha + \frac{R_1}{R_2}} = v_s \frac{R_2}{R_2(1 - \alpha) + R_1}$$


To find  $R_{Th}$ , we use  $R_{Th} = \frac{v_{Th}}{i_{sc}}$

where  $i_{sc} \equiv$  short circuit current flowing in a wire from a to b.

With a wire connecting a and b,  $v_x = 0V$  and the dependent source becomes a wire.

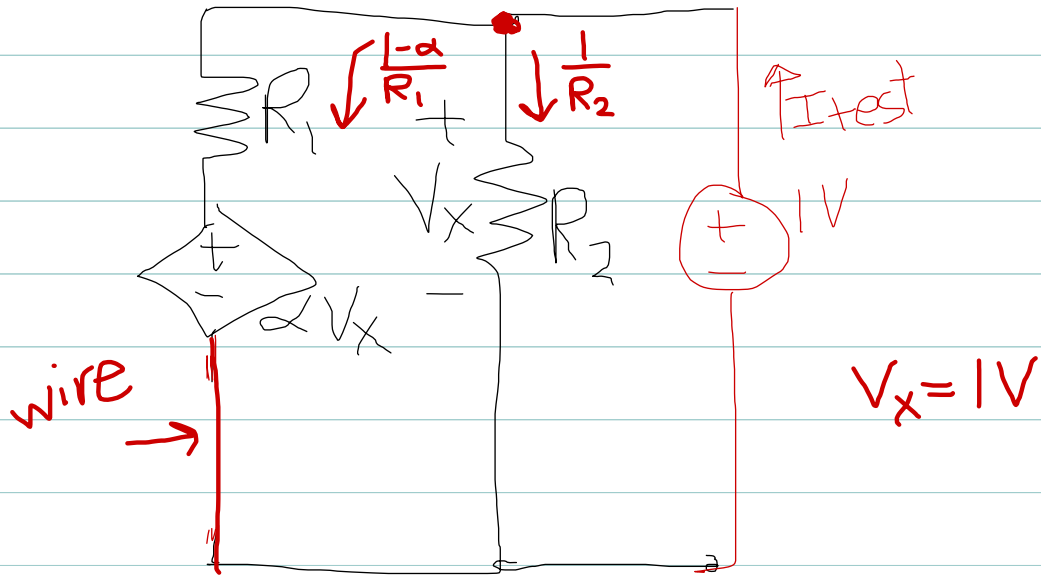Also, no current will flow thru  $R_2$ , and we may ignore  $R_2$ .







$$\sum I: -I_{\text{test}} + \frac{1}{R_2} + \frac{1-\alpha}{R_1} = 0$$

$$I_{\text{test}} = \frac{R_1 + R_2(1-\alpha)}{R_1 R_2}$$
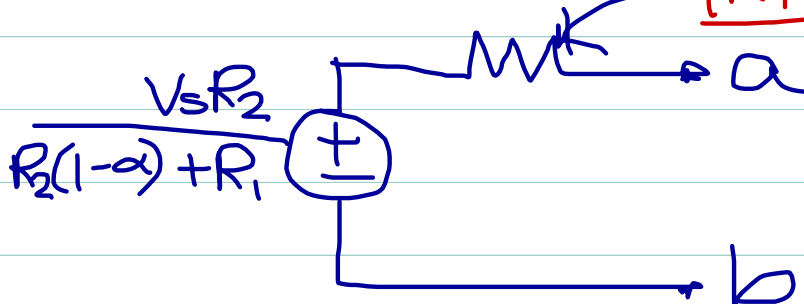
$$R_{\text{th}} = \frac{1}{I_{\text{test}}} = \frac{R_1 R_2}{R_1 + R_2(1-\alpha)}$$



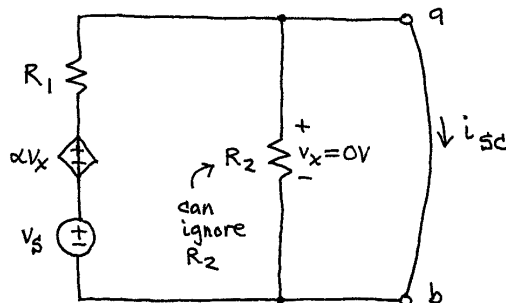

If we ignore  $R_2$ , we calculate  $i_{sc}$  from the outer loop:

$$i_{sc} = \frac{V_s}{R_1}$$

Thus, we have


$$R_{Th} = \frac{V_{Th}}{i_{sc}} = \frac{V_s}{1 - \alpha + \frac{R_1}{R_2}} = \frac{R_1}{1 - \alpha + \frac{R_1}{R_2}}$$

Other equivalent forms for  $R_{Th}$ :

$$R_{Th} = \frac{R_1 R_2}{R_2(1 - \alpha) + R_1}$$

$$R_{Th} = \frac{1}{\frac{1 - \alpha}{R_1} + \frac{1}{R_2}} = \frac{R_1}{1 - \alpha} \parallel R_2$$

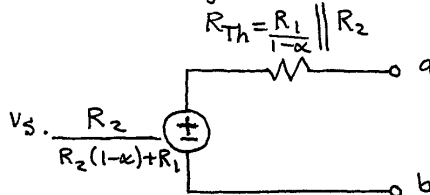The circuit diagram for the Thevenin equivalent:



Note: For the first part of this problem, when we calculate  $V_{Th}$ , we may use an equivalent resistance in place of the dependent source.

With  $a, b$  open circuit, the same current,  $i$ , flows in  $R_2$  and the dependent source.

$$\therefore V_x = i R_2 \quad \text{or} \quad i = \frac{V_x}{R_2}$$

The equivalent  $R$  for the dependent source is

$$R_{eq} = \frac{\alpha V_x}{-i} = \frac{\alpha V_x}{-\frac{V_x}{R_2}} = -\alpha R_2$$

Using  $R_{eq}$  in place of  $\alpha V_x$  allows us to obtain  $V_{Th}$  from a  $v$ -divider formula:

$$V_{Th} = V_s \frac{R_2}{R_2 - \alpha R_2 + R_1} = V_s \frac{R_2}{R_2(1 - \alpha) + R_1}$$

This agrees with our node-voltage result.