

**Class Load**

Syllabus & tentative schedule outline the workload for this semester. This is a very busy class. Every week will require **AT LEAST 10 HOURS** of outside studying to pass class.


ECE3700 + ECE2280 = Very busy semester – **Organize your time!**

**How can you survive??**

- Easiest way to get through school is to actually learn and try to retain what you are asked to learn.
  - Even if you're too busy, don't lose your good study practices. What you "just get by" on today will cost you later.
  - Don't fall for the "I'll never need to know this" trap. Sure, much of what you learn you may not use, but some you will need, either in the current class, or future classes, or maybe sometime in your career. Don't waste time second-guessing the curriculum, It'll still be easier to just do your best to learn and retain.
- Don't fall for the "traps".
  - Homework answers, Extra problem solutions, Posted solutions, Lecture notes.
- KEEP UP! Use calendar.
- Make "PERMANENT NOTES" after you've finished a subject and feel that you know it.

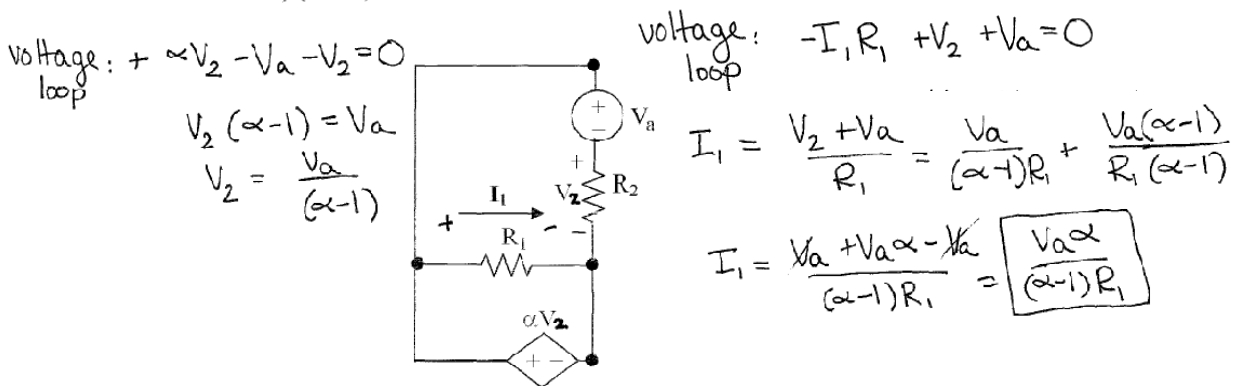**REVIEW:**


- KVL, KCL, OHM'S LAW, THEVENIN EQUIVALENCE, OPAMPS
  - Derive an expression for  $I_1$ . The expression must not contain more than the circuit parameters  $\alpha$ ,  $V_a$ ,  $R_1$ , and  $R_2$ . (**Make sure to eliminate  $V_2$  from the answer**) ( $\alpha \neq 1$ )



Dr. Rasmussen

Spring 2011

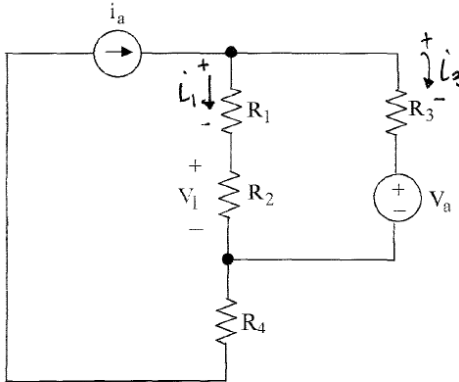Derive an expression for  $v_1$ . The expression must not contain more than the circuit parameters  $V_a$ ,  $i_a$ ,  $R_1$ ,  $R_2$ ,  $R_3$ , and  $R_4$ . (Hint: It is not just a simple voltage divider)



Ohm's Law:  $V = I \cdot R$

$$V_1 = i_1 R_1$$

KCL: Summation of currents:  $i_a - i_1 - i_3 = 0$  ①

KVL: voltage loop:  $+i_1(R_2) + i_1(R_1) - i_3(R_3) - V_a = 0$  ②

From ①  $\Rightarrow i_3 = i_a - i_1$  (plugging this into ②)

$$i_1(R_1 + R_2) - (i_a - i_1)R_3 - V_a = 0$$

$$i_1(R_1 + R_2 + R_3) = i_a R_3 + V_a$$

$$\therefore i_1 = \frac{i_a R_3 + V_a}{R_1 + R_2 + R_3}$$

$$V_1 = i_1 R_1 = \frac{i_a R_3 R_1 + V_a R_1}{R_1 + R_2 + R_3}$$




### Thevenin Equivalence:

**CASE 1:** Thevenin Equivalent (circuit with only independent sources)

Step 1. Turn off all independent sources. (This means  $V=0$  (short) and  $I=0$  (open))

Step 2.  $R_{th}$  = equivalent  $R$  seen between the two desired nodes a-b.

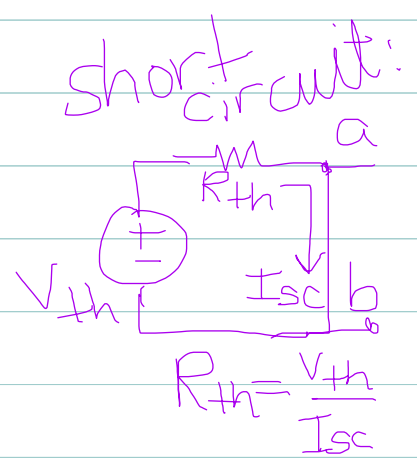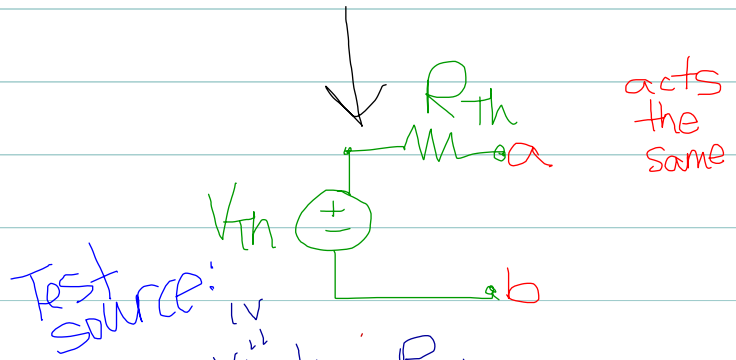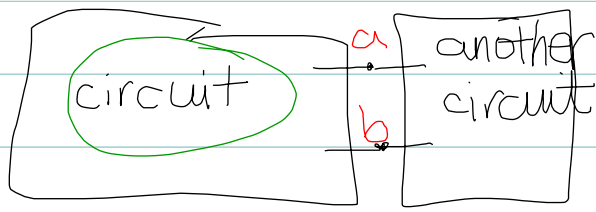Step 3.  $V_{th}$  = open circuit voltage between a-b.




Test source:

$$R_{th} = \frac{V_{test}}{I_{test}}$$

analyze circuit to find

independent src to zero

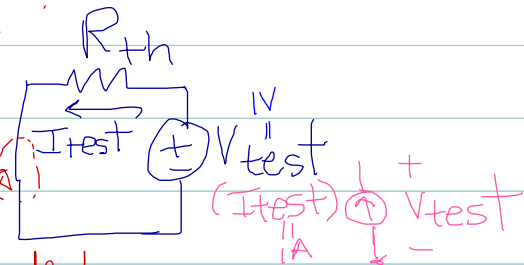

**CASE 2: Thevenin Equivalent (circuit with dependent sources)**

- Step 1. Calculate the open circuit voltage,  $V_{th}$ .
- Step 2. Calculate  $R_{th}$ . Use only one of the methods below:

Method 1: TEST SOURCE


- (a) Remove all independent sources.
- (b) Apply a voltage source  $V_{test}$  between  $a-b$  and determine the resulting current  $I_{test}$ . {OR apply a current source  $I_{test}$  between  $a-b$  and determine the resulting voltage  $V_{test}$ . Using 1V or 1A as the value of the applied test sources allow easy multiplication or division}
- (c)  $R_{th} = V_{test} / I_{test}$

Method 2: SHORT CIRCUIT


- (a) Short circuit between  $a-b$  and find  $I_{sc}$ , short circuit current.
- (b)  $R_{Th} = V_{th} / I_{sc}$

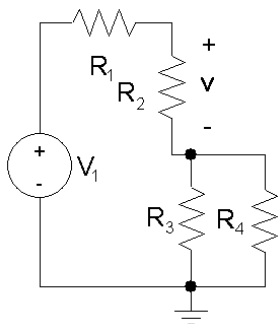**Example, Case 1: (independent sources) Find Thevenin across  $R_2$  (Removing  $R_2$  from the circuit).**

< [http://en.wikibooks.org/wiki/Electronics/Thevenin/Norton\\_Equivalents](http://en.wikibooks.org/wiki/Electronics/Thevenin/Norton_Equivalents) >



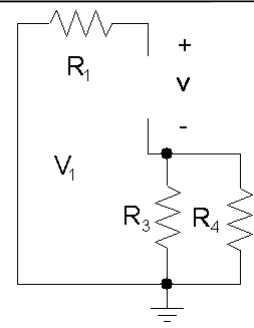independent sources. short) and  $I=0$  (open)  $R_{th}$ .




Step 2 and Step 3:

$$R_{th} = R_1 + R_3 || R_4$$

$$V_{th} = V_1$$

**Example Case 2:**

Find Thevenin between  $a-b$ .

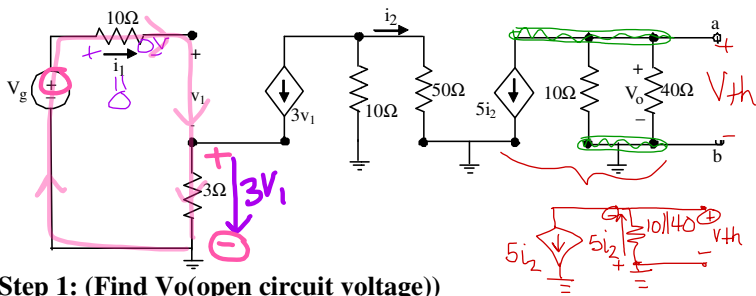

**Step 1: (Find  $V_o$  (open circuit voltage))**

$$V_o = -5i_2(10 || 40) = -5i_2(10)(40)/50 = -40i_2$$

$$i_2 = -3v_1(10)/60 = -1/2v_1$$

$$V_g - 10i_1 - v_1 - 3v_1(3) = 0 \quad (i_1 = 0) \Rightarrow 10v_1 = V_g$$

$$V_o = -40(-1/2)(V_g/10) = +2V_g = V_{th}$$

Dr. Rasmussen


Spring 2011

**Step 2:**

Method 1: TEST SOURCE

(a) Remove all independent sources.

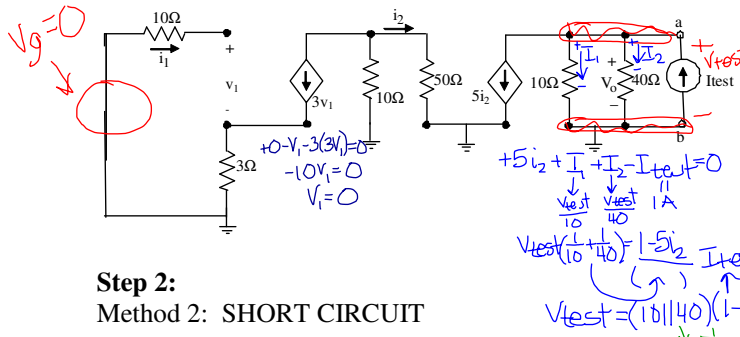(b) Apply a test source (I<sub>test</sub> in this case). Analyze circuit for V<sub>test</sub>=V<sub>o</sub> in this case.



$$V_o = V_{test} = (10 \parallel 40) \cdot (I_{test} - 5i_2)$$

$$i_1 = 0$$

$$v_1 = -3v_1(3) \Rightarrow v_1 + 9v_1 = 0 \Rightarrow v_1(10) = 0 \Rightarrow v_1 = 0$$


$$i_2 = 0$$

$$V_{test} = 8I_{test}$$

$$R_{th} = 8I_{test}/I_{test} = 8\text{ohm}$$

**Step 2:**

Method 2: SHORT CIRCUIT

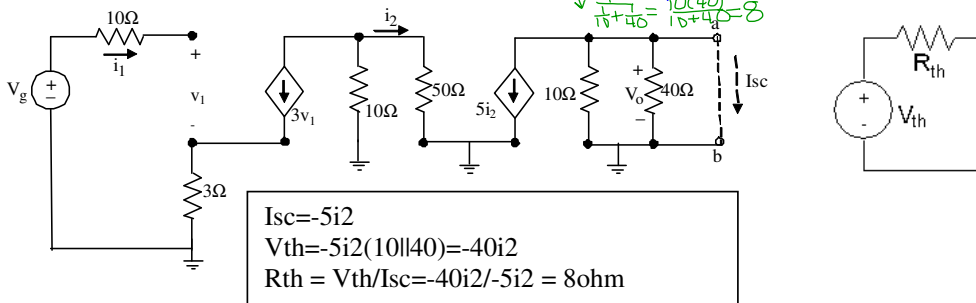

$$I_{sc} = -5i_2$$

$$V_{th} = -5i_2(10 \parallel 40) = -40i_2$$

$$R_{th} = V_{th}/I_{sc} = -40i_2/-5i_2 = 8\text{ohm}$$

**SAME**  
 Note: Use of the I<sub>sc</sub> is sometimes easier than the test source. Suggest trying that method first. Both method's can be used to "check" the other one.

**DC Review Notes** ECE 2100 A Stop 2/27/00

**Basic electrical quantities**

Charge, actually moves	Q	Coulomb (C)
Current, like fluid flow	$I = \frac{Q}{s}$	Amp (A, mA, μA, ...)
Voltage, like pressure	V	volt (V, mV, kV, ...)
Resistance	$R = \frac{V}{I}$	Ohm (Ω, kΩ, MΩ, ...)
Power energy/time	$P = \frac{W}{t}$	Watt (W, mW, kW, MW, ...)

**KCL, Kirchhoff's current law**  
 $I_{in} = I_{out}$  of any point, part, or section

**KVL, Kirchhoff's voltage law**  
 $V_{gain} = V_{drops}$  around any loop

**Node = all points connected by wire, all at same voltage (potential)**

**Ohm's law (resistors)**  
 $V = IR$   
 $V = IR \Rightarrow R = \frac{V}{I}$

**Power**  
 $P_{IN} = P_{OUT}$  for resistor circuits  
 contribute:  $P = VI = I^2R = \frac{V^2}{R}$   
 dissipate

**Schematic symbols**

- battery
- voltage sources
- current source
- ground,  $V=C$
- Volt (V)
- Amp (A)
- Ohm (Ω)
- variable resistors
- capacitor
- inductor or coil
- light bulb
- fuse
- speaker
- transformer
- diode
- LCD
- transistor
- switch
- up amp

**Resistors and Impedances**

**series:**  $R_{eq} = R_1 + R_2 + R_3 + \dots$  Exactly the same current through each resistor

**parallel:**  $R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots}$  Exactly the same voltage across each resistor

**Voltage divider:**  
 $V_{Rn} = V_{total} \frac{R_n}{R_1 + R_2 + R_3 + \dots}$

**current divider:**  
 $I_{Rn} = I_{total} \frac{1/R_n}{1/R_1 + 1/R_2 + 1/R_3 + \dots}$


**Multiple unknowns:**

- Combine resistors into equivalents where possible.
- Use superposition if there are multiple sources and you know all the resistors.
- Use KCL, KVL, & Ohm's laws to write multiple equations and solve.

**Non-linear elements:**  
 Assume a linear region and try to solve.

**Maximum power transfer:**  $R_L = Z_{Th}$   
 Load = Thevenin's

**Example #3**

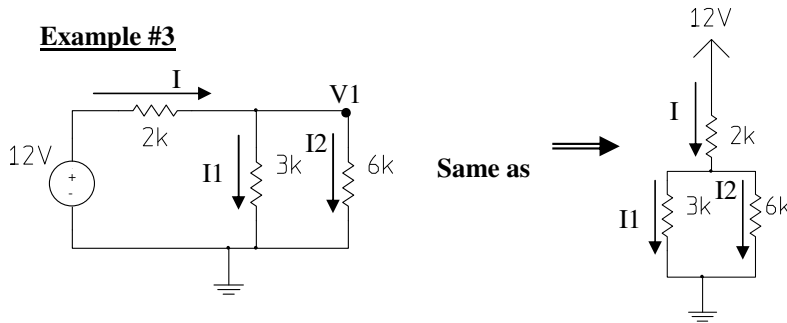


Solve for I, I1, I2, and V1: 
$$I = \frac{12V}{2k + 3k \parallel 6k} = \frac{12}{2k + \frac{3k(6k)}{3k+6k}} = \frac{12}{2k + 2k} = 3mA$$

$$I1 = \frac{V1}{3k}; I2 = \frac{V1}{6k}$$


$$I = I1 + I2 = V1 \left( \frac{1}{3k} + \frac{1}{6k} \right) = V1 \left( \frac{3k}{6k} \right) = V1 \left( \frac{1}{2k} \right) \Rightarrow V1 = I \cdot 2k = 3m(2k) = 6V$$
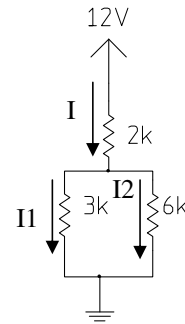
$$I1 = \frac{6}{3k} = 2mA; I2 = \frac{6}{6k} = 1mA$$



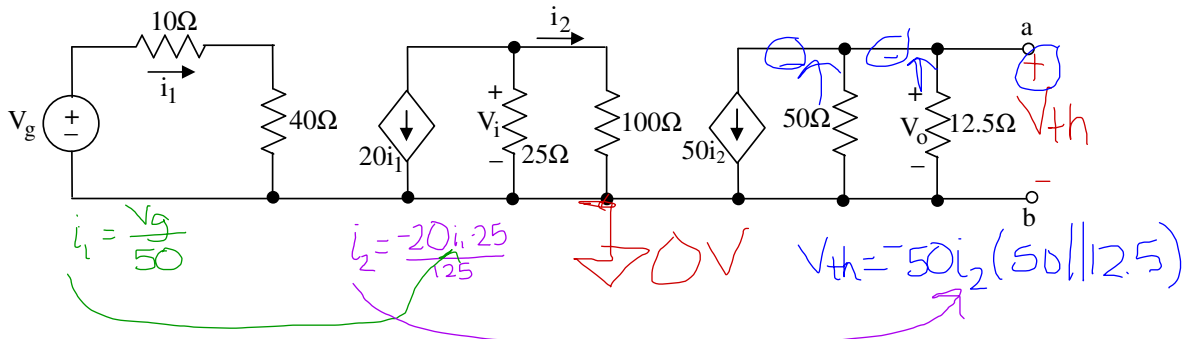**Example #4**

Given  $V_g = 6.25mV$ , find  $V_o$ . Find the Thevenin equivalent between terminals a-b.



$V_{th} = V_o \rightarrow$  Therefore find  $V_o$ :

$$V_o = (50\Omega \parallel 12.5\Omega) \cdot (-50i_2) = -500i_2$$

unknown -  
find eq.  
for  $i_2$

$$\frac{50 \cdot 12.5}{12.5 + 50} = 10\Omega$$

$$\Rightarrow i_2 = \frac{V_i}{100} = \frac{-20i_1 \cdot (25 \parallel 100)}{100} = \frac{-20i_1}{100} \cdot \frac{25 \cdot 100}{100 + 25} = -4i_1$$

unknown  
find  
new eq

$$\Rightarrow i_1 = \frac{V_g}{(10 + 40)} = \frac{6.25m}{50} = 0.125m$$


No unknowns  
plug into  
previous equations

$$i_2 = -4i_1 = -4(0.125m) = -0.5m$$

$$V_{th} = V_o = -500i_2 = +500(0.5) = 250V$$

$$R_{th} = \frac{V_{th}}{i_{sc}}$$

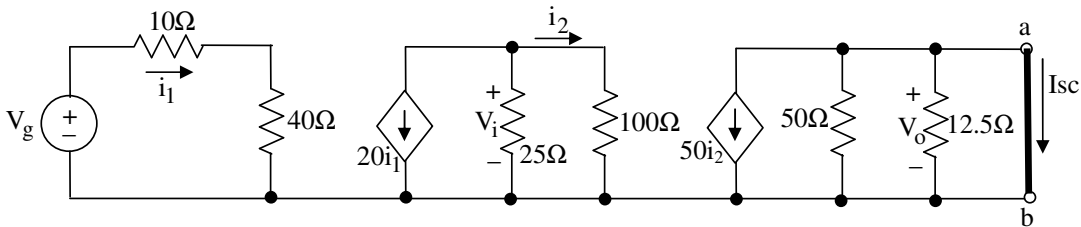where  $i_{sc}$  is the short circuited current  $\Rightarrow$




From the analysis for  $V_{th}$  (above).  $V_{th} = -500i_2$


$I_{sc} = -50i_2$  so

$$R_{th} = \frac{-500i_2}{-50i_2} = 10\Omega$$

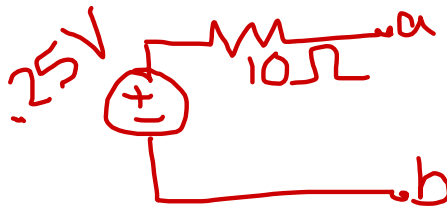(note that for this circuit configuration, it appears that the output R ( $R_{th}$ ) that the "top" of the dependent current source looks like an "open" so that the equivalent R is  $50 \parallel 12.5 = 10\Omega$ ).



3.

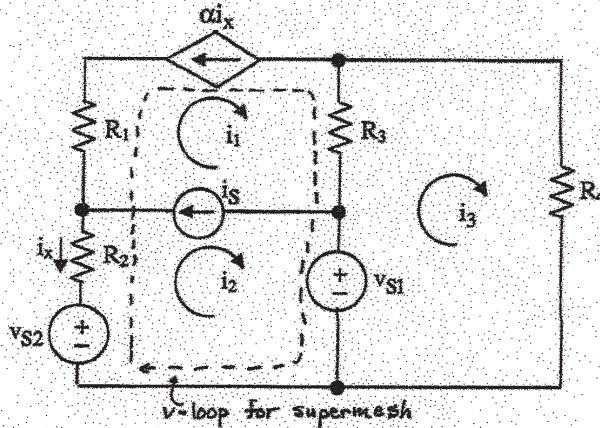

For the circuit shown, write three independent equations for the three mesh currents  $i_1$ ,  $i_2$ , and  $i_3$ . The quantity  $i_x$  must not appear in the equations.

sol'n: First, write  $i_x$  in terms of mesh currents.

$$i_x = -i_2 \quad (\text{Use mesh currents only})$$

Now do v-loops for mesh currents.

We have current source between loops for  $i_1$  and  $i_2$ .

$\therefore$  we have supermesh loop around outside of  $i_1$  and  $i_2$  loops (that avoids having to define  $v$  for  $i_3$ ).

supermesh v-loop:  $+v_{S2} - i_2 R_2 - i_1 R_1 -$  stop!   
*don't use  $i_x$  here!*   
*current src not allowed*

We must not need this v-loop. Indeed, we have a current src on the outside edge, giving us  $i_1 = -i_x(-i_2)$

we must also have a current eq'n for  $i_3$  source  $i_x$  to complete super mesh:

$$i_3 = i_1 - i_2$$

$\uparrow$  flows against  $i_3$  so  $i_x$  minus

Normal v-loop for  $i_3$ :

$$+v_{S1} - i_3 R_3 - i_3 R_4 = 0V$$


$$+ i_1 R_3$$

Question only requires 3 eq's we could solve, but we don't have to solve them.



84

1. c. (20 points)

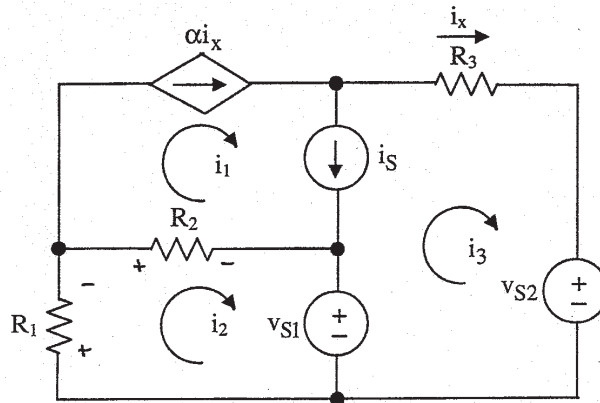

For the circuit shown, write three independent equations for the three mesh currents  $i_1$ ,  $i_2$ , and  $i_3$ . The quantity  $i_x$  must not appear in the equations.

sol'n:  $\alpha i_x$  dependent src in terms of  $i_1, i_2, i_3$ :

$$\alpha i_x = i_1, \quad i_x = i_3 \quad \neq 0 \quad \boxed{\alpha i_3 = i_1}$$

supermesh for  $i_1$  and  $i_3$  loops:

$$\boxed{i_3 = i_1 - i_2}$$

outer loop for  $i_1$  and  $i_3$ ? No, because of  $\alpha i_x$  src.

Mesh eq'n for  $i_2$ :


$$\boxed{-i_2 R_1 - i_2 R_2 - v_{S1} = 0V}$$

Homework #4 Examples

Sp 05

Dr. Neil Cotter
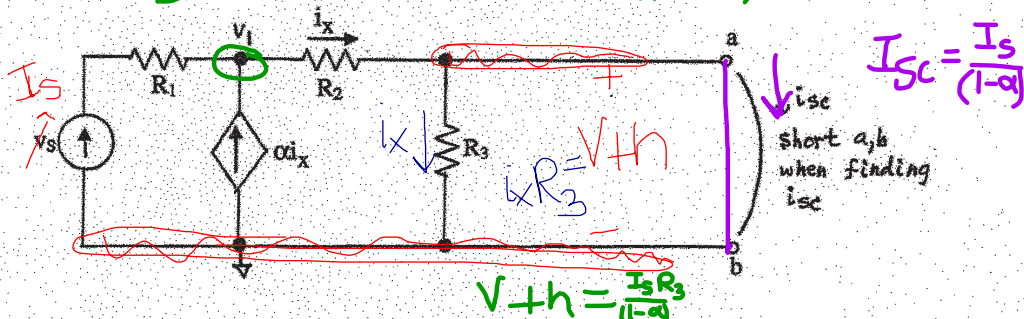
$$-I_s - \alpha i_x + i_x = 0 \rightarrow i_x = \frac{I_s}{(1-\alpha)}$$



Find the Thevenin's equivalent circuit at terminals a-b.  $i_x$  must not appear in your solution. Hint: Use the node voltage method. Note:  $\alpha > 0$ .

soln: Assuming  $V_s$  is current src:

$$R_{Th} = \frac{V_{Th}}{I_{s1}} = R_3$$

$$V_{Thev} = V_{a,b} \text{ open circuit}$$

Use node-voltage method to find  $V_1$ :

$$-\frac{I_s}{1-\alpha} - \alpha \frac{V_1}{R_2+R_3} + \frac{V_1}{R_2+R_3} = 0A$$


$$\text{or } V_1 \frac{1-\alpha}{R_2+R_3} = I_s$$

$$V_1 = I_s \frac{R_2+R_3}{1-\alpha}$$

$$V_{Thev} = V_1 \cdot \frac{R_3}{R_2+R_3} = V_s \frac{R_3}{1-\alpha} \quad \text{v-divider}$$

Now short a,b terminals and find  $I_{sc}$  flowing from a to b.

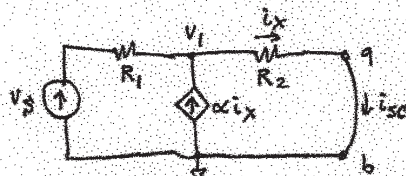Note that  $R_3$  will carry no current; it all flows thru the short.  $\therefore$  we may ignore  $R_3$ .



$$\text{Now, } I_{sc} = I_x = \frac{V_1}{R_2} = \frac{V_s}{1-\alpha}$$

$$R_{Thev} = V_{Thev} / I_{sc} = R_3$$

Use node voltage to find  $V_1$ .


$$-I_s - \alpha \frac{V_1}{R_2} + \frac{V_1}{R_2} = 0A$$

$$V_1 = I_s \frac{R_2}{1-\alpha}$$

Homework #4 Examples


Sp 05  
Dr. Neil Cotter

4. cont.

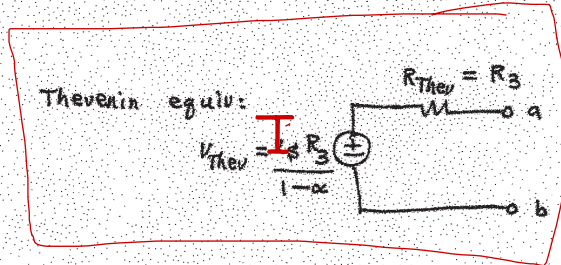

Assuming  $v_s$  is voltage src  $v_s$ :

$v_{Thev} = v_{a,b}$  open circuit

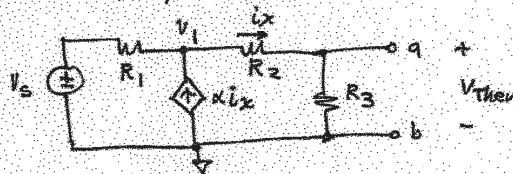

Use node-voltage method to find  $v_1$ :

$$\frac{v_1 - v_s}{R_1} - \alpha \frac{v_1}{R_2 + R_3} + \frac{v_1}{R_2 + R_3} = 0A$$

$= i_x$

$$v_1 \left( \frac{1}{R_1} + \frac{1 - \alpha}{R_2 + R_3} \right) = \frac{v_s}{R_1}$$

mult both sides by  $R_1$  and re-arrange:

$$v_1 = \frac{v_s}{1 + \frac{(1 - \alpha) R_1}{R_2 + R_3}}$$

$$v_{Thev} = v_1 \cdot \frac{R_3}{R_2 + R_3} = \frac{v_s R_3}{\left( 1 + \frac{(1 - \alpha) R_1}{R_2 + R_3} \right) (R_2 + R_3)}$$

$$v_{Thev} = \frac{v_s R_3}{R_2 + R_3 + (1 - \alpha) R_1}$$

Now short a,b terminals and find  $i_s$  flowing from a to b. Note that  $R_3$  will be bypassed. All current will flow thru short.


$\therefore$  we may ignore  $R_3$ .

Homework #4 Examples

Sp 05

Dr. Neil Cotter

4. cont.

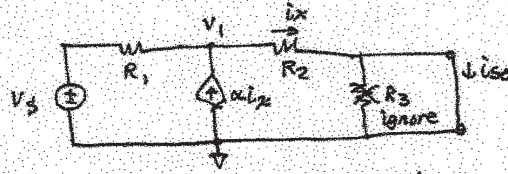

use node-voltage to find  $v_1$ :

$$\frac{v_1 - v_s}{R_1} - \alpha \frac{v_1}{R_2} + \frac{v_1}{R_2} = 0A$$

$= i_x$

$$v_1 \left( \frac{1}{R_1} + \frac{1-\alpha}{R_2} \right) = \frac{v_s}{R_1}$$

$$\text{or } v_1 = \frac{v_s}{1 + \frac{(1-\alpha)R_1}{R_2}}$$

$$i_{sc} = i_x = \frac{v_1}{R_2} = \frac{v_s}{R_2 + (1-\alpha)R_1}$$

$$R_{The} = \frac{v_{Thev}}{i_{sc}} = \frac{R_3}{R_2 + R_3 + (1-\alpha)R_1} \cdot R_2 + (1-\alpha)R_1$$

$$R_{Thev} = R_3 \parallel [R_2 + (1-\alpha)R_1]$$

Thevenin equiv:

