

ECE1270

**Introduction to Electrical and
Computer Engineering**
Professor Angela Rasmussen

Unit 1

UNITS

Current	Amps	A
Voltage	Volts	V
Resistance	Ohms	Ω
Capacitance	Farads	F
Inductance	Henrys	H
power	watts	W

Values

G	Giga	10^9
M	mega	10^6
K	kilo	10^3
m	milli	10^{-3}
μ	micro	10^{-6}
n	nano	10^{-9}
P	pico	10^{-12}
f	femto	10^{-15}

memorize

Independent Sources:

Voltage Source: (ex. Common battery) Able to supply or absorb any amount of current. Current value is set by EXTERNAL Circuit. Voltage is between + and - terminals.

Current Source: Supplies constant current in set "branch" of circuit. Voltage across current source is not zero for a nonideal current source.

Conversions:

$1F \equiv 1 \frac{C}{V}$
$1A \equiv 1 \frac{C}{sec}$
$1\Omega \equiv 1 \frac{V}{A}$
$1H \equiv 1 \frac{V \cdot s}{A}$

Dependent Sources:

"line"

Either current or voltage. Value is controlled by other variable (current or voltage). If value can be set, than it can be treated as independent source.

Circuit Elements:

time

independent

Voltage Source: Waterfall (height)

Current Source: pump

Resistance: pipe

Capacitor: storage tank


Inductor: paddle wheel

V increases over time

I increases over time

Passive Sign Convention:

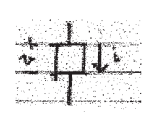Current arrow always pts from plus to negative (- at arrow)



same "line" even with bend


Ohms Law:

memorize

$V=IR$ or $I=V/R$

Linear device =>

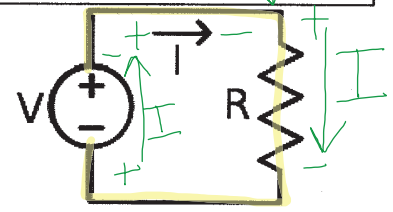$2x \text{ current} = 2x \text{ voltage}$



Kirchoff's Current Law (KCL):

- If you have water flowing into and out of a junction of several pipes, water flowing into the junction must equal water flowing out.
- The same applies to electric circuits

The algebraic sum of currents into a node at any instant is zero

node


$I_T - I_1 - I_2 = 0$ or

$-I_T + I_1 + I_2 = 0$

$I_T = I_1 + I_2$

Kirchoff's Voltage Law (KVL):

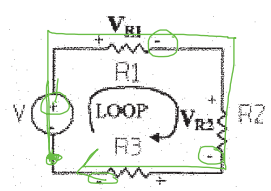
The algebraic sum of voltages around any closed path (loop) is zero



$-V + V_{R1} + V_{R2} + V_{R3} = 0$ or

$+V - V_{R1} - V_{R2} - V_{R3} = 0$ or

Voltage

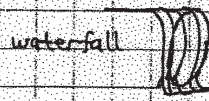

Voltage ↔ altitude
Volts 10V typ 1mV small
V


lift charge q change energy ΔW $V = \lim_{q \rightarrow 0} \frac{\Delta W}{\Delta q} = \frac{dW}{dq}$

V-source



± indicates polarity of measurement


dependent

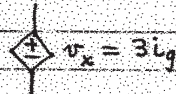

Current





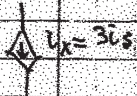Current ↔ flow rate
Amps 1A large 1mA typ
A



move charge q in time Δt $i = \lim_{\Delta t \rightarrow 0} \frac{\Delta q}{\Delta t} = \frac{dq}{dt}$

Power

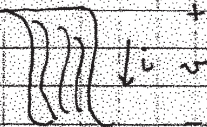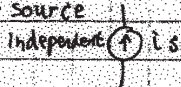

Power ↔ hydroelectric power
Watts 1W typ 100W med
W

change energy by ΔW in time Δt $p = \lim_{\Delta t \rightarrow 0} \frac{\Delta W}{\Delta t} = \frac{dW}{dt}$

chain rule $p = \frac{dW}{dq} \frac{dq}{dt}$ tot. pow. in circuit = 0