

7a

Procedure Summary to find I and V:
Note: Find equation for dependent variable.

1. a. Label every current through R's
- b. Label polarity with (-) at arrow side
2. Take a voltage loop for every possible path.

[NOTE!] → Do not take a loop across a current source

3. Write all node current summations.

[Note!] → Do not use a node with a branch having only a Vsrc in it.

4. Use Ohm's law for every R.

5. Reduce equation set to solve for unknown's (i.e. use a set with common unknown variables)

power summary:

$$P = I * V = I^2 R$$




[W] Watts

+ consuming
- generates

19

Ex:

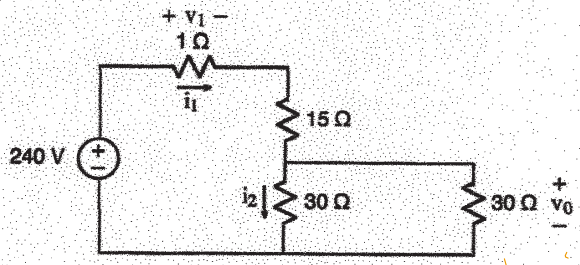

Calculate i_1 , i_2 , and v_0 .

$$0 = +i_2(30) - i_0(30)$$


sol'n: First, we label R's.

$$0 = +240 - i_1(1) - i_1(15) - i_2(30)$$

$$0 = +240 - i_1(1) - i_1(15) - i_0(30)$$

$$\sum I : -i_1 + i_2 + i_0 = 0$$

$$\vec{V} = \vec{I}R$$

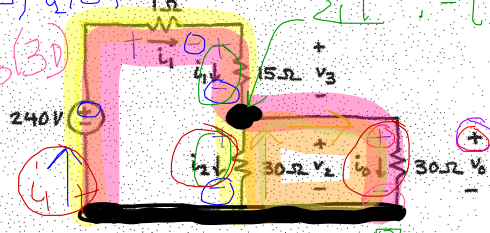

Second, we write v-loop eqns. We write eqns for both inner loops.

$$+240V - v_1 - v_3 - v_2 = 0V$$

$$+v_2 - v_0 = 0V$$

$$+i_1 - i_2 - i_0 = 0$$

Third, we write current-sum eqns for all but one node. For the node between R's on the right side we have

$$-i_1 + i_2 + i_0 = 0A$$

20

Fourth, we equate currents for components in series. We have already done this, however, by using i_1 for both the 1Ω and 15Ω R's.

Fifth, we write Ohm's law eqns for every R:

$$v_1 = i_1 \cdot 1\Omega$$

$$v_3 = i_1 \cdot 15\Omega$$

$$v_2 = i_2 \cdot 30\Omega$$

$$v_0 = i_0 \cdot 30\Omega$$

Now we use the Ohm's law eqns to substitute for v's:

$$+240V - i_1 \cdot 1\Omega - i_1 \cdot 15\Omega - i_2 \cdot 30\Omega = 0V$$

$$+ i_2 \cdot 30\Omega - i_0 \cdot 30\Omega = 0V$$

Our current sum eqn is unchanged:

$$-i_1 + i_2 + i_0 = 0A$$

From the 2nd of the above 3 eqns we have

$$i_0 = i_2$$

Using this in the 3rd eqn gives

(2)



$$i_1 = 2i_2$$

Using this in the 1st eq'n gives

$$+240V - 2i_2(1\Omega + 15\Omega) - i_2 \cdot 30\Omega = 0V$$

$$\text{or } i_2(2 \cdot 16\Omega + 30\Omega) = 240V$$

$$\text{or } i_2 = \frac{240V}{62\Omega} = \frac{120}{31} A \approx 3.87A$$

$$i_1 = 2i_2 = \frac{240}{31} A \approx 7.74A$$


$$v_o = i_o \cdot 30\Omega = i_2 \cdot 30\Omega = \frac{120(30)}{31} V$$

$$\text{or } v_o = \frac{3600}{31} V \approx 116V$$

23



Ex:

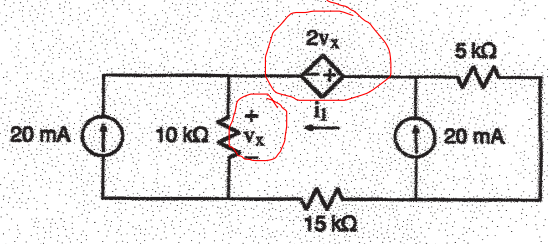


Find v_x , i_1 , and the power dissipated by the dependent source.

sol'n: We find i_1 , the current for the dependent V-src after we solve the circuit.

$$+i_x(10k) + 2v_x - i_2(5k) - i_3(15k) = 0$$

$$v_x = i_x(10k)$$

First, label i 's and v 's for R 's:

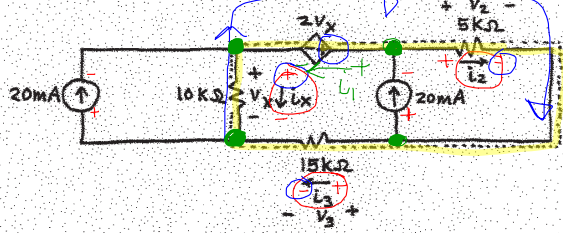

Second, write v-loop eqns for loops not containing current src's. There is only one such loop, indicated by the dotted line.

$$+v_x + 2v_x - v_2 - v_3 = 0V$$

Third, write current-sum eqns for nodes (unless nodes are connected only by v src's). We don't use the nodes on top since they are connected by only the $2v_x$ source.

25

$$20 \text{ mA} - i_x - (i_2 - 20 \text{ mA}) = 0 \text{ A}$$

$$i_x(10 \text{ k}\Omega + 20 \text{ k}\Omega) - i_2(5 \text{ k}\Omega) - (i_2 - 20 \text{ mA})15 \text{ k}\Omega = 0 \text{ V}$$

Solving the first of these eqns for i_2 gives

$$i_2 = 40 \text{ mA} - i_x$$

Using this in the second of the two eqns gives:

$$i_x(30 \text{ k}\Omega) - (40 \text{ mA} - i_x)(5 \text{ k}\Omega + 15 \text{ k}\Omega) = -20 \text{ mA} \cdot 15 \text{ k}\Omega$$

$$\text{or } i_x(30 \text{ k}\Omega + 20 \text{ k}\Omega) = 40 \text{ mA}(20 \text{ k}\Omega) - 20 \text{ mA} \cdot 15 \text{ k}\Omega$$

$$\text{or } i_x(50 \text{ k}\Omega) = 500 \text{ V}$$

$$\text{or } i_x = \frac{500 \text{ V}}{50 \text{ k}\Omega} = 10 \text{ mA}$$

Now we can find i_1 from a current sum at the node on top to the left of center:

$$-20 \text{ mA} + i_x - i_1 = 0 \text{ mA}$$



$$\text{or } i_1 = -20 \text{ mA} + i_x = -20 \text{ mA} + 10 \text{ mA} = -10 \text{ mA}$$

The power dissipated by the dependent source is

$$p = i_1 \cdot 2V_x = -10 \text{ mA} \cdot 2 \cdot \underbrace{10 \text{ mA} \cdot 10 \text{ k}\Omega}_{V_x \text{ from Ohm's Law}}$$

$$\text{or } p = -2 \text{ W}$$

Op-Amp Procedure: (Linear Operation)

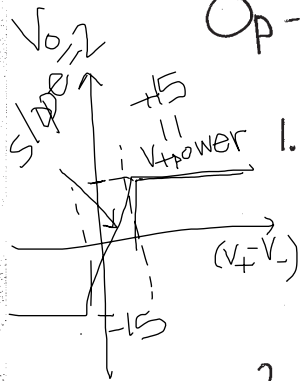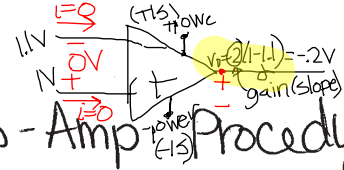

1. a. Replace Op-Amp with V_o source
- b. 0V across $+$, $-$ inputs
- c. $i=0$ into $+$, $-$ inputs

2. Follow procedure to solve for I & V (pg. 7a)

by using the V -loop that includes the 0V drop across $+$, $-$ inputs


- 2 different loops can be obtained
- make sure to use V_o in 1 loop

$$V_o = 2(V_+ - V_-)$$

36


Op Amp Example

sp 05
Dr. Colter

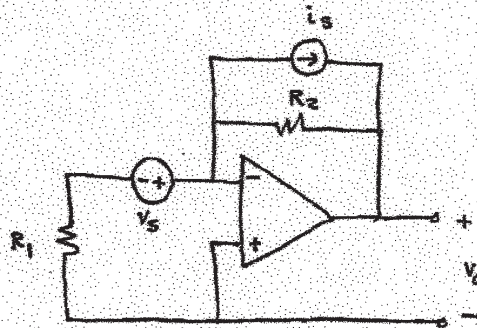

Derive expression for v_o in terms of not more than v_s , i_s , R_1 , and R_2 .

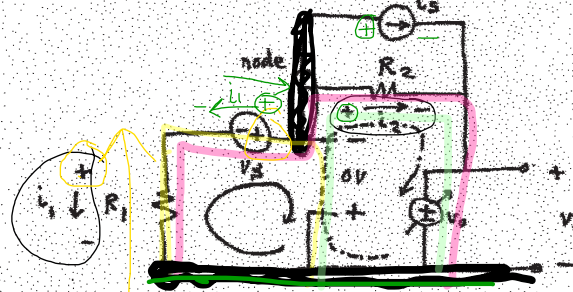sol'n: Replace op-amp with v_o source and assume 0V across $+,-$ inputs.



Use v-loop on left that includes 0V drop across $+,-$ inputs.

$$+i_1 R_1 + v_s + 0V = 0V$$

$$\text{or } i_1 = \frac{-v_s}{R_1}$$

Use v-loop on right that includes 0V drop across $+,-$ inputs.

$$-0V - i_2 R_2 - v_o = 0V$$

$$\text{or } v_o = -i_2 R_2$$

(37)

Sp 05
Dr. Colter

Op Amp sol'n: cont.

Use current sum at node next to - input.

$$i_1 + i_2 + i_3 = 0A$$

$$\text{or } i_2 = -(i_1 + i_3) = -\left(-\frac{v_s}{R_1} + i_s\right) = \frac{v_s}{R_1} - i_s$$

Use this in 2nd v-loop eq'n.

$$v_o = -i_2 R_2 = -\left(\frac{v_s}{R_1} - i_s\right) R_2$$

$$v_o = \left(i_s - \frac{v_s}{R_1}\right) R_2$$

Consistency check:

If $R_2 = 0$ then 2nd v-loop implies

$$v_o = 0V. \quad v_o = \left(i_s - \frac{v_s}{R_1}\right) \cdot 0 = 0V \quad \checkmark$$


If $i_s = 0A$ and $v_s = 0V$, we should

$$\text{get } v_o = 0V. \quad v_o = \left(0 - \frac{0}{R_1}\right) R_2 = 0V \quad \checkmark$$

38

Op Amp Examples

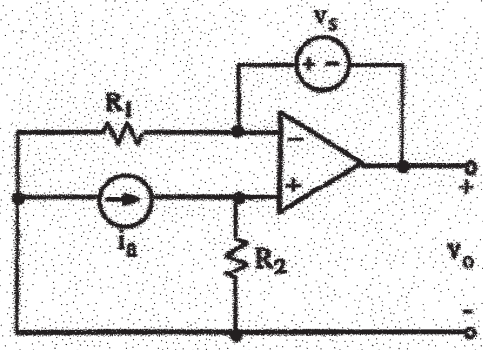
5. The op-amp operates in the linear mode. Using an appropriate model of the op amp, derive an expression for v_o in terms of not more than v_s , i_a , R_1 , and R_2 .



39



Ex:

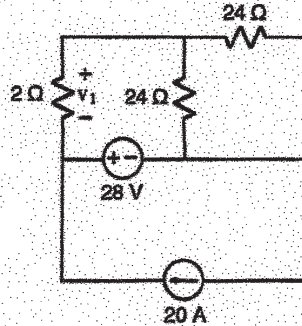

Calculate v_1 .

sol'n: We can use a voltage divider consisting of the 28V src, the 2Ω Resistor, and the two 24Ω resistors in parallel.

$$v_1 = -28V \cdot \frac{2\Omega}{2\Omega + 24\Omega \parallel 24\Omega}$$

$$= -28V \cdot \frac{2\Omega}{2\Omega + 24\Omega \cdot \frac{1}{1+1}}$$

$$\frac{1}{1+1} = \frac{1 \cdot 1}{1+1} = \frac{1}{2}$$

$$= -28V \cdot \frac{2\Omega}{2\Omega + 12\Omega}$$

$$v_1 = -4V$$

Note: We have a minus sign whenever the + sign of the resistor voltage measurement is on the side away from the + sign of the v src.