

Now that we have solved the circuit,  
we can find  $i_o$  from an i-sum eqn  
for the node on the right.

$$\text{or } i_o = -\frac{V_s}{R_1} - \frac{V_a + V_s}{R_2} + i_a$$

$$\text{or } i_o = i_1 + i_2 + i_a$$

$$-i_2 - i_1 - i_a + i_o = 0A$$

$$I_1 = \frac{V_a - V_b}{R_1} \text{ (same)}$$

$$V_a - I_1 R_1 - \frac{V_b}{R_2} (R_2) = 0$$

OR solving (1) with (3) plugged in

$$I_1 = \frac{V_a - V_b}{R_1}$$

Solving (2)  $\Rightarrow$

• Can not do current summation because of  $V_b$

$$(3) + I_2 R_2 - V_b = 0 \quad \leftarrow I_2 = \frac{V_b}{R_2}$$


$$(2) + V_a - I_1 R_1 - V_b = 0$$

Ohm's Law Ohm's Law  
for  $V_1$  for  $V_2$

$$(1) + V_a - I_1 R_1 - I_2 R_2 = 0$$

• Short circuit: (use Ohms law immediately in V-loops)

• Label all  $I_1$ 's &  $V_1$ 's

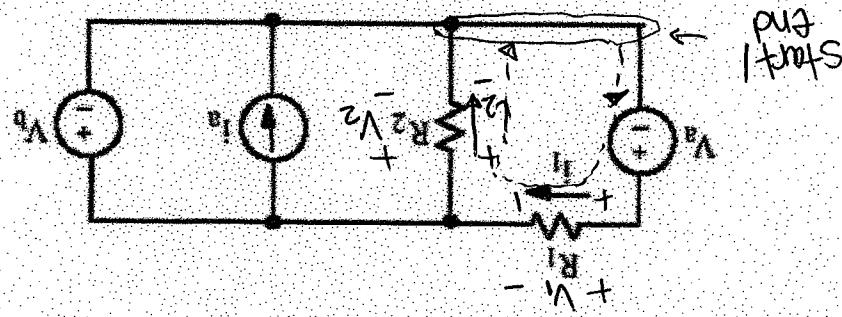


3. Derive an expression for  $I_1$ . The expression must not contain more than the circuit parameters  $V_a$ ,  $V_b$ ,  $I_2$ ,  $R_1$ , and  $R_2$ .

## HW #2 Examples

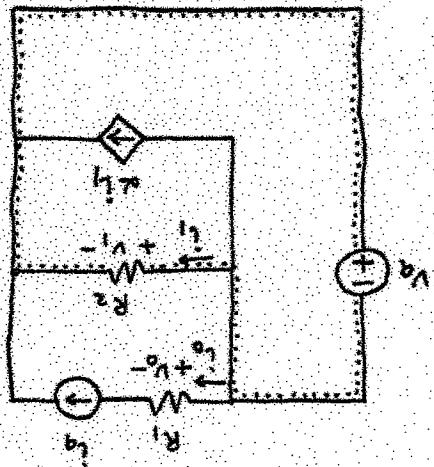
(47)

Only V-loop without current source is thru  
 $V_a$  and  $R_2$ , (dotted line).



soln: a) Label  $R_s$

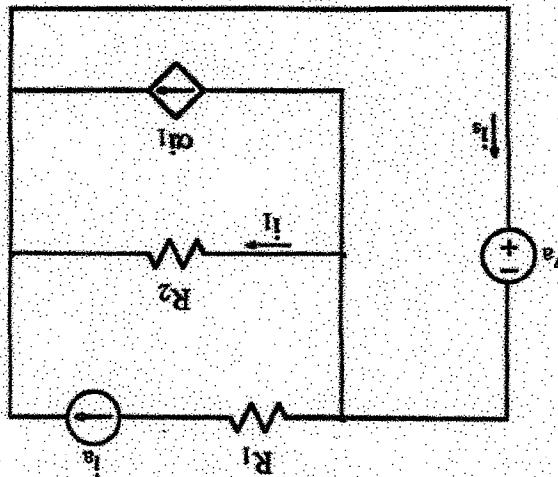- a) Derive an expression for  $I_s$ . The expression must not contain more than the circuit parameters  $\alpha$ ,  $V_a$ ,  $R_1$ , and  $R_2$ . (Make sure to eliminate  $I_1$  from the answer.)
- b) Make at least one consistency check (other than a units check) on your expression. Explain the consistency check clearly.



Ex:

Dr. Neil Cotter

Sp 06

ECE 1270

HOMEWORK #2 Example #4



48

Now we write i-sum eqn (for node consisting of wire on right side) to find  $i_3$ .

It follows that  $i_1 = -\frac{V_a}{R_2}$ .

$$\text{or } i_1 = -\frac{V_a}{R_2}$$

$$-V_a - i_1 R_2 = 0$$

Substituting for  $i_1$  in our v-loop eqn:

$$V_i = i_1 R_2$$

$$V_o = i_2 R_1 = i_3 R_1$$

From Ohm's law:

$$i_2 = i_3$$

We look for components in series carrying the same current.

Thus, we have no i-sum eqns.

We look for nodes where we can write i-sum eqns. Here, however, we really only have two nodes, and they are connected by only V-src  $V_a$ .

$$-V_a - V_i = 0$$



49


Then  $i_2 = i_a$ . Our eqn gives  $i_2 = i_a - (\alpha + 1) \cdot 0 = i_a$ .  
 Another example is to set  $V_a = 0V$ ,  $\alpha = 0$ .

$$i_2 = 0 - (\alpha + 1) \frac{V_a}{R_2} = -\frac{V_a}{R_2}$$

agrees:

Now we verify that our eqn from (a)
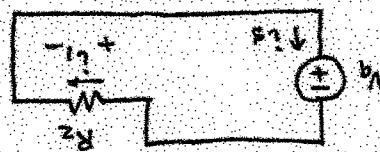
$$\text{We have } i_2 = i_1 = -\frac{V_a}{R_2}.$$



$$\text{Let } i_a = 0A \text{ and } \alpha = 0:$$

Sources:

One example is to eliminate current


we can solve it by inspection.  
 that make the circuit so simple that  
 the idea is to pick component values  
 Many constancy checks are possible.

$$\text{or } i_2 = i_a - (\alpha + 1) \frac{V_a}{R_2}$$

$$\text{or } i_2 = (\alpha + 1) \left( -\frac{V_a}{R_2} \right) + i_a$$

$$\text{or } i_2 = \alpha i_1 + i_1 + i_a$$


$$i_2 - \alpha i_1 - i_1 - i_a = 0A$$

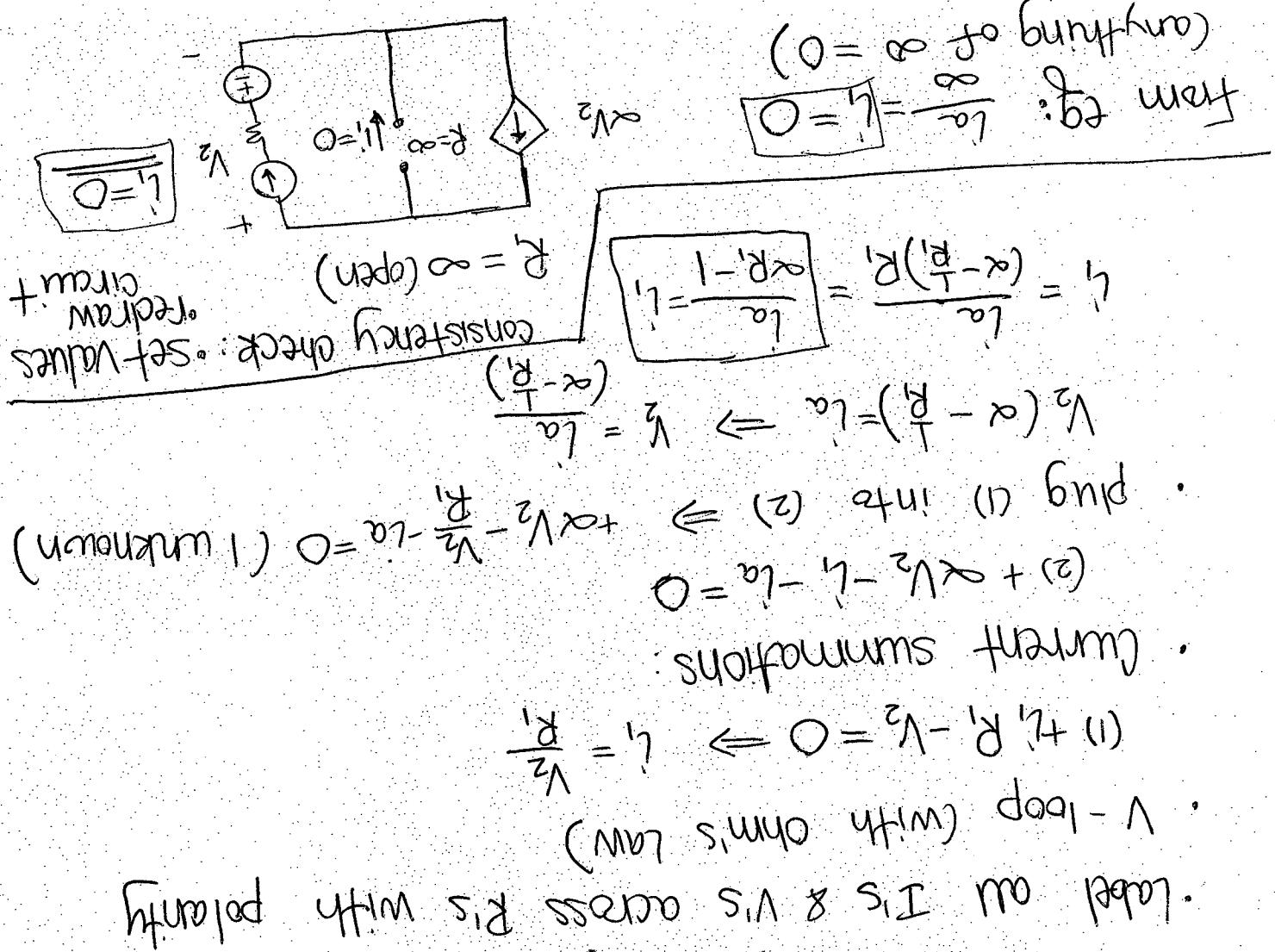

Make at least one consistency check (other than a units check) on your expression for

problem 4. Explain the consistency check (other than a units check) on your expression for

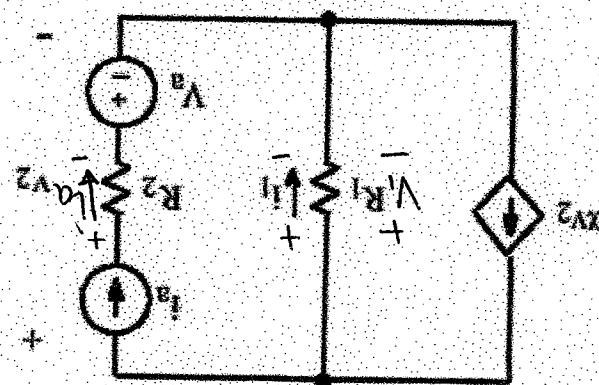
problem 4. Explain the consistency check (other than a units check) on your expression for



4. Define an expression for  $I_1$ . The expression must not contain more than the circuit parameters  $\alpha$ ,  $V_s$ ,  $i_a$ ,  $R_1$ , and  $R_2$ .


HW #2 Examples

51

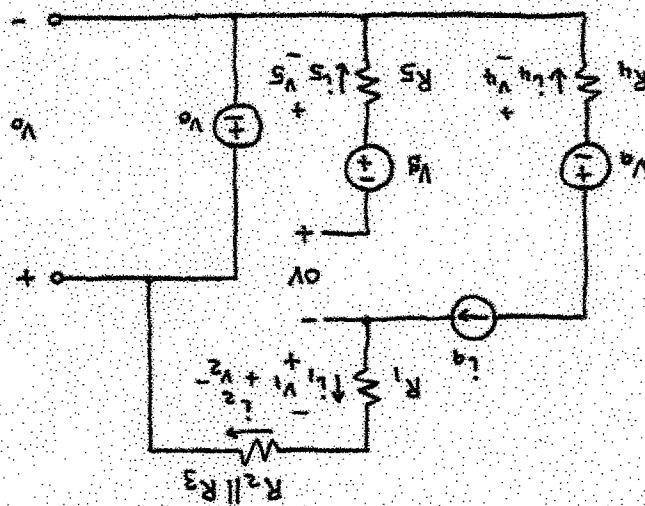

Soln: Replace op-amp with src called  $V_0$  and assume v-drop across  $R_2 +$  and  $-$  terminals is  $OV$ . We also combine  $R_2$  and  $R_3$ .

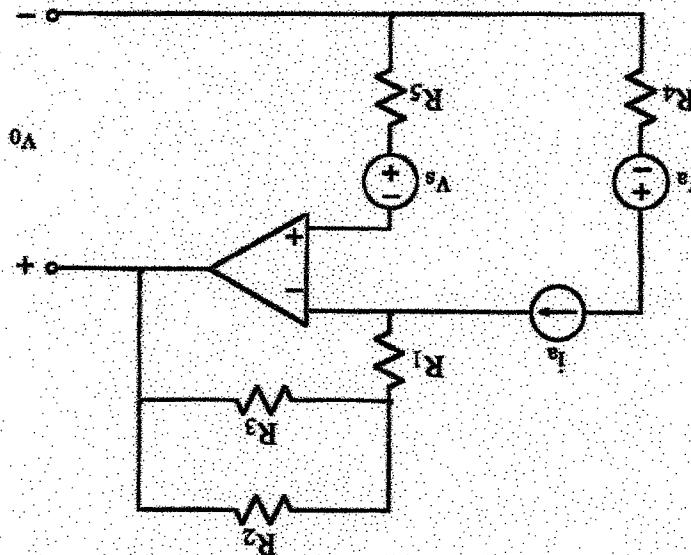The op-amp operates in the linear mode. Using an appropriate model of the op amp, derive an expression for  $V_0$  in terms of not more than  $V_s$ ,  $I_a$ ,  $R_1$ ,  $R_2$ ,  $R_3$ ,  $R_4$  and  $R_5$ .



Ex.

Write V-loops passing thru ou across  
+ and - terminals!  
+  $V_4 + V_4 + ?$  Don't use left-side V-loop

The only true node is on the bottom.  
Write current sums at nodes.

$$+V_5 - V_5 - \Omega V - V_1 - V_2 - V_6 = 0A$$

because of current src.

$$+V_4 + V_4 + ?$$

Look for components in series carrying  
the same current:

$$I_4 = -I_2$$

$$I_2 = I_1 = I_3$$

$$I_1 = I_3$$

$$I_4 = -I_2$$

We see that  $I_3$  flows all the way  
through the outer loop.

$I_3 = 0A$  (since it is in series with  
an open circuit)

$$V_1 = I_1 R_1 = I_3 R_1$$

each resistors:

V-loop using  $I_3$  and Ohm's law for  
we need only substitute for  $V_3$  in

$$V_o = -V_3 = i_a (R_1 + R_2 \parallel R_3)$$

Solving  $V_o$  gives the expression we seek:

$$\alpha V - V_3 - \alpha V = i_a R_1 - i_a R_2 \parallel R_3 - V_o = \alpha V$$

Our V-loop becomes:

$$V_5 = i_5 R_5 = \alpha \cdot R_5 = \alpha V$$

$$V_2 = i_2 \cdot R_2 \parallel R_3 = i_a \cdot R_2 \parallel R_3$$

$$(2) - I_s = I_3$$

because of  $V_o$  branch  
(no summation on right of  $I_s$ )

$$I_s + I_1 - I_2 - I_3 = 0$$

current summations:

$$0 = 0 - I_3 R_3 - V_o + (1)$$

$$0 = I_1 \Leftarrow (1) \quad I_1 = V_1 (R_1)$$

$$0 = I_2 \Leftarrow (2) \quad I_2 = V_2 (R_2)$$


$$V_2 = 0$$

$$-V_2 - 0 = 0$$


$V_{1bads}$ :

$$I_s R_3 = V_o +$$

plug (2) into (1)

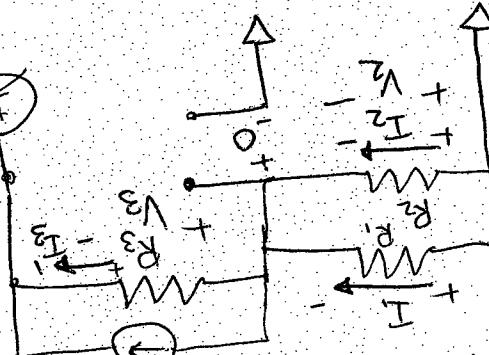

Redraw circuit.

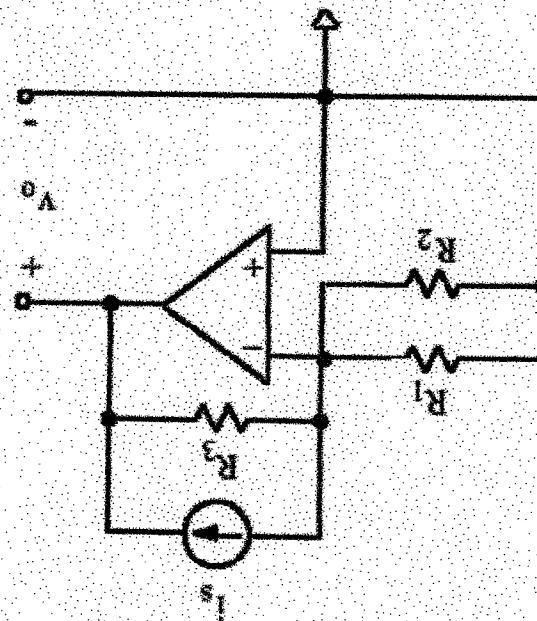

The op amp operates in the linear mode. Using an appropriate model of the op amp, derive an expression for  $V_o$  in terms of not more than  $I_s$ ,  $R_1$ ,  $R_2$ , and  $R_3$ .

## HW #2 Examples

65

expression must not contain more than the circuit

(30 points)

## Review Solution

1. a. (5 points)

Currents sum at top of bottom node of  $N_0$ , because we would have to define a current for source  $I_A$ .  
 Current at center node:  $I_B - I_C + I_E = 0$   
 No V-loop for other inner loops because we would have to define V-drop for  $I_A$ .  
 Now we have 3 loops in 3 unknowns, and we want to find  $I_A$ . We observe, however, that the three loops have only two unknowns, so we don't actually need the third one. This is due to fact that the three loops share only two unknowns.

**ANSWER**

$$V_1 = \frac{36.9 - 12.924244 + 10.0}{12.911244} = 1.69 \quad 8.75 / 18.0 = 0.472222222$$

**Sally:** The *Le Sourcier* across the wine may be ignored. Its current flows through the wife but produces no virtue without the wife but produces

A circuit diagram showing a series connection of three resistors (24Ω, 12Ω, and 10Ω) and a current source (6A). The current source is connected in series with the 24Ω resistor. The 12Ω resistor is connected in parallel with the 10Ω resistor.

56

(30 points)

a. Derive an expression for  $i_a$ . The expression must not contain more than three current parameters,  $C_1$ ,  $V_A$ ,  $R_1$ , and  $R_2$ .

b. Make at least one consistency check (other than a units check) on your expression. Explain the consistency check.

soln: a) Redraw circuit from (a) with these component values:

$i_a = -V_A / R_1 R_2 = -V_A / R_2 = -V_A \cdot \frac{1}{\frac{R_1}{R_2} + 1}$

We see that  $i_a$  is correct since  $R_1 \parallel R_2$  across  $V_A$ .

With  $R_1 \parallel R_2$  across  $V_A$ ,

$i_a = -V_A \cdot \frac{1}{\frac{R_1}{R_2} + 1} = -V_A \cdot \frac{1}{\frac{R_1}{R_2} + \frac{R_1}{R_1}} = -V_A \cdot \frac{1}{\frac{R_1 + R_2}{R_2}}$

Using formula from (a) with these component values:

$i_a = -12V \left( \frac{1}{\frac{1}{2}k\Omega} + \frac{1}{\frac{1}{2}k\Omega} \right) = -12V \cdot \frac{2}{k\Omega}$

for this example

No current sums at nodes because of  $V_A$ .

V-loop on left:  $V_A - i_a R_2 - V_A = 0 \Rightarrow i_a = \frac{V_A}{R_2}$

V-loop in middle:  $i_a R_2 + i_1 R_1 = 0 \Rightarrow i_1 = -\frac{i_a}{R_1}$

Now that we have found  $i_1$  and  $i_2$ , we use a different node to find  $i_a$ :

$i_a = -V_A \cdot \frac{1}{\frac{R_1}{R_2} + \frac{R_1}{R_1} + i_1}$  or  $i_a = -V_A \cdot \frac{1}{\frac{R_1 + R_2}{R_2} + \frac{R_1}{R_1}}$

58

$$V_o = V_s - i_a R_2 \quad \text{or} \quad i_a = \frac{V_s - V_o}{R_2}$$

Thus  $V_s - V_o = i_a R_2$

Now use  $i_s = \frac{i_f}{R_2}$ .

$$-V + V_s - i_f R_2 - V_o = 0 \quad \text{or} \quad i_f = \frac{V_s - V_o}{R_2}$$


$V$ -loop on right thru ov drop,  $V_s$ ,  $R_2$ , and  $V_o$ :

$$-i_a + i_i + i_s = 0 \quad \text{or} \quad i_s = i_a$$


Current sum at node above  $R_1$ :

$$i_i R_1 + \alpha V = 0 \quad \text{or} \quad i_i = 0$$

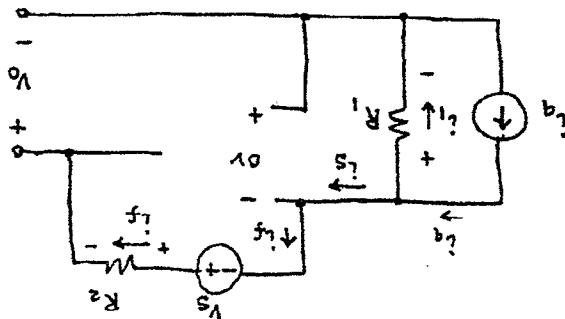$V$ -loop on left thru  $R_1$  and ov drop:



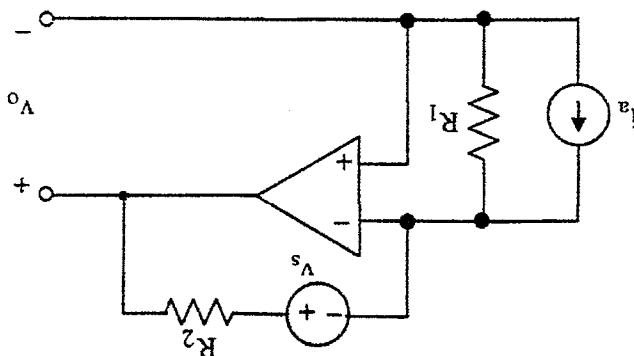Sol'n: Redraw without op-amp and ov drop across + and - inputs:



The op-amp operates in the linear mode. Using an appropriate model of the op amp, derive an expression for  $V_o$  in terms of not more than  $V_s$ ,  $i_a$ ,  $R_1$ , and  $R_2$ .

4. (30 points)

(59)

REVIEW (cont.)