

(175)

## Homework #8 Example

Dr. Neil Cotter

1.

Give numerical answers to each of the following questions:

pts

a. Rationalize  $\frac{3+j4}{7-j24}$ . Express your answer in rectangular form.

b. Find the rectangular form of  $\left[ \frac{1-\sqrt{2}e^{-j45^\circ}}{e^{j30^\circ}} \right]^*$ . Note the asterisk that means "conjugate".

c. Given  $\omega = 100\text{k rad/s}$ , find the following inverse phasor:  $P^{-1}[j30 \sin(-53^\circ)]$

d. Find the magnitude of  $(2e^{j30^\circ} - j) \left( \frac{5-j12}{e^{j17^\circ}} \right)$ .

e. Find the real part of  $e^{-j30^\circ}$ .

Soln: a)  $\frac{3+j4}{7-j24} \cdot \frac{7+j24}{7+j24} = \frac{z(1-4(24)) + j(3(24) + 4(7))}{7^2 + 24^2} = \frac{-75 + j100}{25^2} = \boxed{\frac{-3+j4}{25}}$

b)  $\left[ \frac{1-\sqrt{2}e^{-j45^\circ}}{e^{j30^\circ}} \right]^* = \frac{1-\sqrt{2}e^{j45^\circ}}{e^{-j30^\circ}} \cdot \frac{e^{j30^\circ}}{e^{j30^\circ}} = \left[ \frac{1-\sqrt{2}(1+j)}{\sqrt{2}} \right] \cdot e^{j30^\circ} = -j e^{j30^\circ}$   
 $= e^{-j10^\circ} e^{j30^\circ} = e^{-j60^\circ} = \boxed{+\frac{1}{2} - j \frac{\sqrt{3}}{2}}$

c)  $P^{-1}[j30 \sin(-53^\circ)] = P^{-1}[j30 j \cdot 1 \angle -53^\circ] = -30 \angle -53^\circ = 30 \angle 137^\circ$

" " =  $\boxed{30 \cos(100kt + 137^\circ) \text{ or } 30 \cos(100kt - 233^\circ)}$

d)  $\left| (2e^{j30^\circ} - j) \frac{5-j12}{e^{j17^\circ}} \right| = |2e^{j30^\circ} - j| \left| \frac{5-j12}{e^{j17^\circ}} \right| = |2\left(\frac{13}{2} + \frac{j}{2}\right)| \cdot \frac{13}{1} = \boxed{\sqrt{13} \cdot 13}$

e)  $\operatorname{Re} \left[ \frac{1}{e^{-j30^\circ}} \right] = \operatorname{Re} [e^{j30^\circ}] = \operatorname{Re} \left[ \frac{\sqrt{3}}{2} + j \frac{1}{2} \right] = \boxed{\frac{\sqrt{3}}{2}}$

## Homework #8 Examples

(176)

Give numerical answers to each of the following questions:


1. a. Rationalize  $\frac{23+j7}{15-j8}$ . Express your answer in rectangular form.
- b. Find the polar form of  $(2+j3)(3+j2) + [3+j16]^*$ . Note the asterisk that means "conjugate".
- c. Find the following phasor:  $P \left[ -5 \sin(100t - 30^\circ) \right]$ .
- d. Find the magnitude of  $\frac{100(3+j4)(4+j3)}{(7+j)(7-j)}$ .
- e. Find the imaginary part of  $(1+j)e^{-j45^\circ} (j2)$ .

(17)

## Homework #8 Example

Dr. Neil Cotter

2.

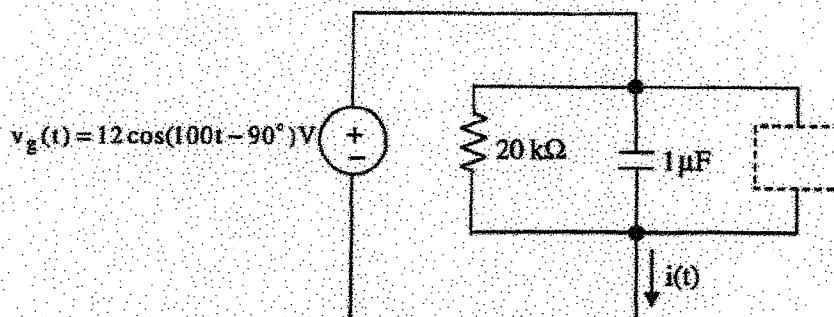pts

- a. Choose an R, an L, or a C to be placed in the dashed-line box to make

$$i(t) = I_0 \cos(100t - 45^\circ) \text{ A}$$

where  $I_0$  is a real constant. State the value of the component you choose.

- b. With your component from (a) in the circuit, calculate the resulting value of

$$I_0.$$

Soln: a) Use conductance:  $\mathbf{I} = I_0 \angle -45^\circ \text{ A} = V_g \cdot \underbrace{\left( \frac{1}{20k\Omega} + j\frac{100\mu\text{F}}{\Omega} + \frac{1}{z_{\text{box}}} \right)}_{G_{\text{tot}}}$   
(and phasors)

Note:  $\omega = 100$  from  $v_g(t)$  where  $V_g = 12 \angle -90^\circ \text{ V}$

We have  $\angle \mathbf{I} = \angle V_g + \angle G_{\text{tot}}$  from phasor multiplication

$$-45^\circ = -90^\circ + \angle G_{\text{tot}}$$

$$\therefore \angle G_{\text{tot}} = 45^\circ \text{ or } \text{Re}[G_{\text{tot}}] = \text{Im}[G_{\text{tot}}]$$

$$G_{\text{tot}} = \frac{50\mu\text{A}}{\Omega} + j\frac{100\mu\text{A}}{\Omega} + \frac{1}{z_{\text{box}}}$$

We can choose  $\frac{1}{z_{\text{box}}} = \frac{50\mu\text{A}}{\Omega} \Rightarrow z_{\text{box}} = 20k\Omega$  resistor

$$\text{or } \frac{1}{z_{\text{box}}} = -j\frac{50\mu\text{A}}{\Omega} = \frac{-j}{wL} = \frac{-j}{100 \cdot 2}$$

Note: Either answer accepted  $\Rightarrow z_{\text{box}} = 200 \text{ H inductor}$   
but  $20k\Omega$  R is more sensible.


$$\text{b) } I_0 = |\mathbf{I}| = |V_g| \cdot |G_{\text{tot}}| = 12 \cdot \sqrt{2 \cdot 100 \mu\text{A}} = \boxed{12 \cdot 12 \text{ mA for } 20k\Omega \text{ R}}$$

$\text{or } 12 \cdot \sqrt{2 \cdot 50 \mu\text{A}} = \boxed{12 \cdot 600 \mu\text{A for } 200 \text{ H L}}$

## Homework #8 Examples

(17B)

2.

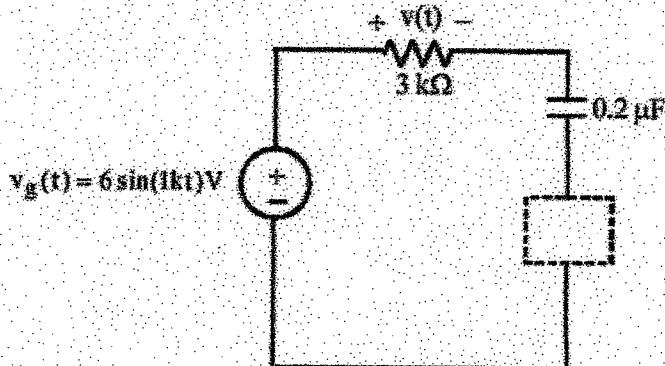

Choose an R, an L, or a C to be placed in the dashed-line box to make


$$v(t) = V_0 \cos(kt - 45^\circ)\text{V}$$

where  $V_0$  is a real constant. State the value of the component you choose.

## Homework #8 Example

Dr. Neil Cotter

3.

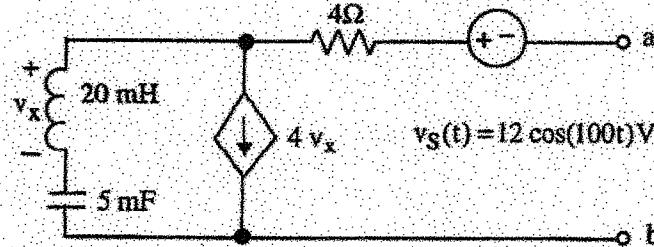


pts

- Draw a frequency-domain equivalent of the above circuit. Show a numerical phasor value for  $v_S(t)$ , and show numerical impedance values for R, L, and C. Label the dependent source appropriately.
- Find the Thevenin equivalent (in the frequency domain) for the above circuit. Give the numerical phasor value for  $V_{Th}$  and the numerical impedance value of  $Z_{Th}$ .

Sol'n: a)  $\omega = 100$  from  $v_S(t)$      $j\omega L = j100 \cdot 20 \text{ mH} = j2\Omega$

$$\frac{-j}{wC} = \frac{-j}{100 \cdot 5 \text{ m}} = \frac{-j}{500 \text{ m}} = -j2\Omega$$

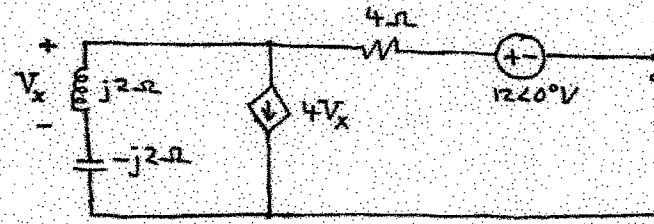phasor  $V_S \equiv P[12 \cos(100t)]V = 12 \angle 0^\circ V$



b)  $V_{Th} = V_{a,b}$  with no load.

We have  $z_L + z_C = 0\Omega$  so 0V across L & C together.

Also, no current in  $4\Omega \Rightarrow$  0V across  $4\Omega$ .

Add the  $-12V$  for v-source to get  $V_{Th} = -12V$


For  $Z_{Th}$ , short a,b and measure i out of a terminal.

Circuit model:

$4v_x$  irrelevant

$$i_{SC} = \frac{-12V}{4\Omega} = -3A$$

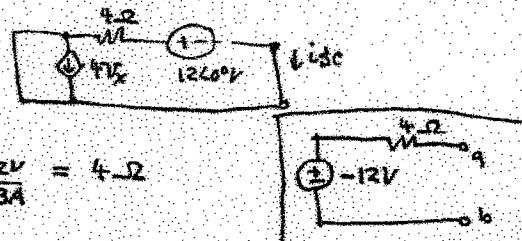
$$Z_{Th} = \frac{V_{Th}}{I_{SC}} = \frac{-12V}{-3A} = 4\Omega$$



180

## Homework #8 Examples

3.

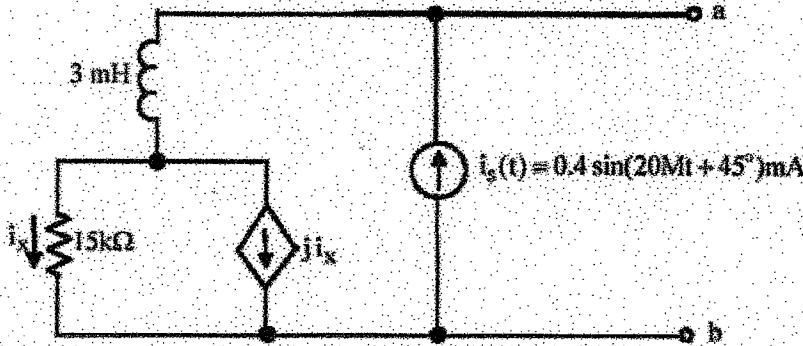

Find the Thevenin equivalent (in the frequency domain) for the above circuit. Give the numerical phasor value for  $V_{Th}$  and the numerical impedance value of  $Z_{Th}$ .

# Example

HOMEWORK #8:

ECE 1270  
Sp 06

Ex: Give numerical answers to each of the following questions:

a) Rationalize  $\frac{-25j}{3-4j}$ . Express your answer in rectangular form.

b) Find the rectangular form of  $\left[ \frac{(1+j)}{e^{j30^\circ}} \right] \left[ \frac{(1+j)}{e^{-j60^\circ}} \right]^*$ . (Note the asterisk that means "conjugate".)

c) Given  $\omega = 2\pi$  rad/s, find the following inverse phasor:  
 $P^{-1} [10(-0.866 - 0.5j)]$

d) Find the magnitude of  $\frac{(4e^{j30^\circ} - \frac{1}{2}j)(-1-j)}{\sqrt{2}e^{j10^\circ}}$ .

e) Find the real part of  $\frac{e^{-2}}{e^{j45^\circ}}$ .

Sol'n: a)  $\frac{-25j}{3-4j} \cdot \frac{3+4j}{3+4j}$  multiply top & bottom by complex conjugate of denominator

$$= \frac{(-25j)(4j) + (-25j)(3)}{3^2 + 4^2}$$

$$= \frac{100 - 75j}{25}$$

$$= 4 - 3j$$

b)  $\frac{1+j}{e^{j30^\circ}} \left[ \frac{1+j}{e^{-j60^\circ}} \right]^* = \frac{1+j}{e^{j30^\circ}} \cdot \frac{1-j}{e^{j60^\circ}} = \frac{1+j}{e^{j90^\circ}}$

But  $e^{j90^\circ} = j$  and  $1/j = -j$

∴ our answer is  $-j^2$

ECE 1270  
Sp 06

HOMEWORK #8:

UNIVERSITY  
OF TORONTO

c)  $P^{-1} [10(-0.866 - 0.5j)]$   
 $= P^{-1} \left[ 10 \sqrt{0.866^2 + 0.5^2} e^{j \tan^{-1} \left( \frac{-0.5}{0.866} \right)} \right]$   
 $= P^{-1} \left[ 10 \cdot 1 e^{j(-15^\circ)} \right]$   
 $= P^{-1} \left[ 10 e^{-j150^\circ} \right]$

$$= 10 \cos(\omega t - 150^\circ)$$

d) 
$$\left| \frac{(4e^{j30^\circ} - j\frac{1}{2})(-1-j)}{\sqrt{2}e^{j10^\circ}} \right| = \left| 4e^{j30^\circ} - j\frac{1}{2} \right| \left| -1-j \right| \over \left| \sqrt{2}e^{j10^\circ} \right|$$

Magnitude of product = product of magnitudes  
Now use  $|e^{jx}| = \sqrt{a^2 + b^2}$  for any real  $x$ , and  
 $|a+jb| = \sqrt{a^2 + b^2}$ .

$$\begin{aligned} &= \left| 4e^{j30^\circ} - j\frac{1}{2} \right| \\ &= \left| 4e^{j30^\circ} - \frac{j^2 + 1^2}{2} \right| \\ &= \left| 4e^{j30^\circ} - \frac{1^2 + 1^2}{2} \right| = \left| 4 \cos 30^\circ + j\frac{1}{2} \sin 30^\circ - j \right| \\ &= \left| 4 \cdot \frac{\sqrt{3}}{2} + j\frac{1}{2} - j \right| = \left| 2\sqrt{3} + j\frac{1}{2} \right| \\ &= \sqrt{(2\sqrt{3})^2 + (\frac{1}{2})^2} = \sqrt{4(3) + \frac{1}{4}} = \sqrt{14\frac{1}{4}} \text{ or } \sqrt{\frac{57}{4}} = \frac{\sqrt{57}}{4} \end{aligned}$$

(18)


ECE 1270  
Sp 06  
HOMEWORK #8 Solution Prob 1 (cont.)

ECE 1270  
Sp 06

UNIVERSITY OF TORONTO

$$\begin{aligned}
 e) \quad & \operatorname{Re} \left[ \frac{e^{-2}}{e^{-j45^\circ}} \right] = \operatorname{Re} \left[ \frac{e^{-2}}{e^{-j45^\circ}} \frac{e^{j45^\circ}}{e^{j45^\circ}} \right] \\
 & = \operatorname{Re} \left[ e^{-2} e^{j45^\circ} \right] \quad \text{since } e^{j0^\circ} = 1 \text{ in denominator} \\
 & = e^{-2} \operatorname{Re} [e^{j45^\circ}] \\
 & \approx e^{-2} \operatorname{Re} [\cos 45^\circ + j \sin 45^\circ] \\
 & = e^{-2} \cdot \frac{1}{\sqrt{2}} \quad \text{since } \operatorname{Re}[a+jb] = a
 \end{aligned}$$

Ex:

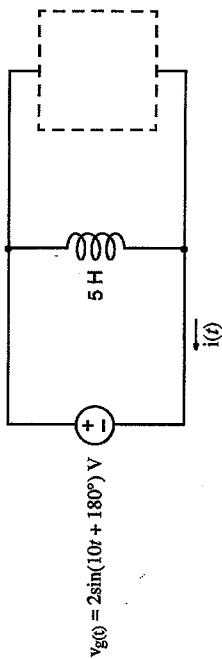

a) Choose an R, an L, or a C to be placed in the dashed-line box to make

$$i(t) = I_0 \cos(10t + 45^\circ) A$$

where  $I_0$  is a real constant. State the value of the component you choose.

b) With your component in the circuit, calculate the resulting value of  $I_0$ .


Soln: a) Transform to frequency domain.

$$V_g = -j2 e^{j180^\circ} V \quad \text{since } \operatorname{P}[\sin(\omega t)] = -j$$

$$V_g = +j2 V = 2 \angle 90^\circ V$$

$$Z_L = j\omega L = j \cdot 10 \text{ rad/s} \cdot 5 \Omega = j50 \Omega$$

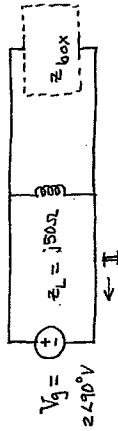Note:  $\omega = 10 \text{ rad/s}$  from  $v_g(t)$ .



$$\text{we have } \mathbb{I} = \frac{V_g}{Z_L \parallel Z_{box}}$$

182

In terms of angles:

$$\angle I = 45^\circ \text{ from } i(t) = I_0 \cos(\omega t + 45^\circ) \text{ A}$$

$$\angle V_L = 45^\circ = \angle V_g - \angle(z_L \parallel z_{box})$$

$$\text{or } 45^\circ = 90^\circ - \angle(z_L \parallel z_{box})$$

$$\text{Thus, } \angle(z_L \parallel z_{box}) = 45^\circ.$$

For parallel components, it is easier to use conductance =  $\frac{1}{Z} \equiv g$

$$g_L = \frac{1}{z_L} \quad g_{box} = \frac{1}{z_{box}} \\ \angle(z_L \parallel z_{box}) = -\angle\left(\frac{1}{z_L \parallel z_{box}}\right) = -\angle\left(\frac{1}{z_L} + \frac{1}{z_{box}}\right)$$


$$\text{or } \angle\left(\frac{1}{z_L} + \frac{1}{z_{box}}\right) = -\angle(z_L \parallel z_{box}) = -45^\circ$$

$$\angle(g_L + g_{box}) = -45^\circ$$

Now we use a plot:

$$g_L = \frac{1}{j50\Omega} = -j\frac{1}{50\Omega}$$

$$g_{box} = +j\frac{1}{50\Omega}$$

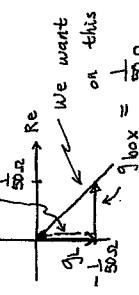

We want  $g_L + g_{box}$  on this line.

We have two possible solutions:

$$1) \quad g_{box} = j \frac{1}{50\Omega} \Rightarrow z_{box} = \frac{50\Omega}{j} = -j50\Omega$$

$$\text{Need capacitor: } z_C = \frac{-j}{\omega C} = \frac{-j}{10\cdot 50} = -j50\Omega$$

$$\Rightarrow C = \frac{1}{10 \cdot 50} F = 2 \text{ nF}$$

$$\text{or } 2) \quad g_{box} = \frac{1}{50\Omega} \Rightarrow z_{box} = 50\Omega \text{ resistor}$$

Either soln is technically correct, but solution (1) gives  $g_L + g_{box} = 0 \Rightarrow z = \infty$ .

Thus, no current flows for this soln.

b) Now use magnitude.

$$|I| = \left| \frac{V_g}{z_L \parallel z_{box}} \right| = \frac{|V_g|}{|z_L \parallel z_{box}|}$$


$$\text{or } I_o = |V_g| \cdot |g_L + g_{box}|$$

$$I_o = 2 \cdot |g_L + g_{box}|$$

From diagram used to find  $g_L + g_{box}$  on  $-45^\circ$  line, use magnitude of vector for  $g_L + g_{box}$ .

182a

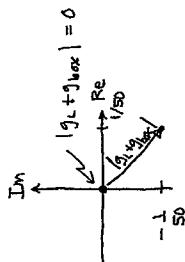ECE 1270  
Sp 06  
HOMEWORK #8 Solution Prob 2, 3 (cont.)




For sol'n (1),  $|g_L + jg_Bx| = 0 \Rightarrow I_o = 0 A$

$$\begin{aligned} \text{For sol'n (2), } |g_L + jg_Bx| &= \left| \frac{1}{50} - j \frac{1}{50} \right| \\ &= \left| \frac{1}{50} (1-j) \right| \\ &= \frac{1}{50} \sqrt{1^2 + 1^2} \\ &= \frac{\sqrt{2}}{50} \\ \Rightarrow I_o &= \frac{2 \cdot \sqrt{2} A}{50} = \frac{\sqrt{2}}{25} A \end{aligned}$$

ECE 1270  
Sp 06  
HOMEWORK #8 Solution Prob 4

Ex:

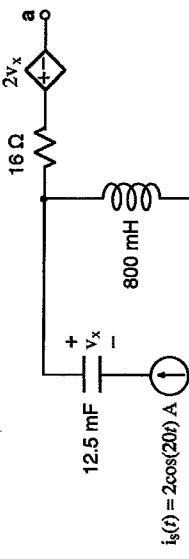


- a) Draw a frequency-domain equivalent of the above circuit. Show a numerical phasor value for  $i_s(t)$ , and show numerical impedance values for  $R$ ,  $L$ , and  $C$ . Label the dependent source appropriately.
- b) Find the Thevenin equivalent (in the frequency domain) for the above circuit. Give the numerical phasor value for  $V_{TH}$  and the numerical impedance value of  $z_{TH}$ .

Sol'n: a)  $\omega = 20 \text{ rad/s}$  from  $i_s(t)$

$I_s = 2 \angle 0^\circ A$

$$Z_C = -j \frac{1}{\omega C} = -j \frac{1}{20 \pi / 12.5 \text{ mF}} = -j \frac{1}{50 \text{ mF}} = -j 4 \Omega$$

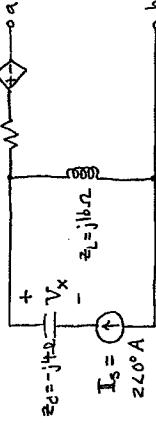
$Z_L = j \omega L = j 20 \pi / s \cdot 800 \text{ mH} = j 16 \text{ k} \omega \text{ mH} = j 16 \Omega$



183

b)  $V_{Th} = V_{ab}$  open circuit.

Use node voltage  $V_1$ :

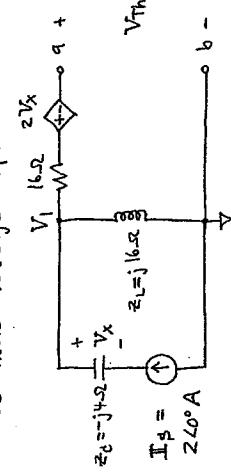

$$V_1 \text{ (from } I_s \cdot Z_L) = 2\angle 0^\circ A \cdot j 16\Omega = j 32V$$


We have 0V across  $16\Omega$  since no current flows.

$$\text{Thus, } V_{Th} = V_1 - 2V_x.$$

$$V_x = -I_s Z_c = -2\angle 0^\circ A \cdot (-j4\Omega) = j 8V$$

$$\text{So } V_{Th} = j 32V - 2(j 8V) = j 16V \text{ or } 16\angle -90^\circ V$$

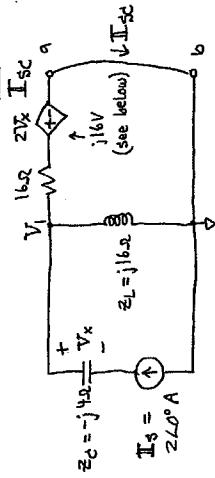To find  $Z_{Th}$ , use  $Z_{Th} = \frac{V_{Th}}{I_s}$




Since  $C$  is in series with current source, we have  $V_x = -I_s Z_c = j 8V$  as before.

Thus,  $2V_x = j 16V$ . We can now treat the dependent source as an independent source of  $j 16V$ .

Now we use superposition to find  $I_{sc}$ :

case 1:  $I_s$  on,  $2V_x$  off

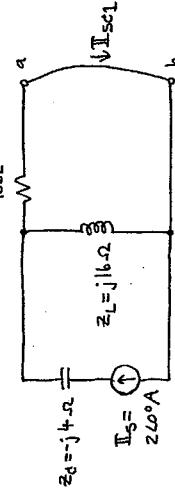


This is a current divider.

$$\begin{aligned} I_{sc1} &= I_s \cdot \frac{Z_L}{Z_d + Z_L} = j 16\Omega \frac{I_s}{j 16\Omega + 16\Omega} = \frac{j I_s}{1+j} \\ &= 2\angle 0^\circ A \cdot \frac{j}{1+j} = 2\angle 0^\circ A \frac{1+j}{1^2 + j^2} \\ I_{sc1} &= 1+j A \end{aligned}$$

183a

Case II:  $I_s$  off,  $2V_x$  on

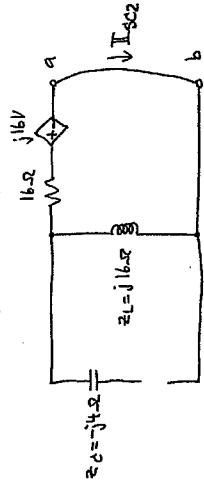

We have a V-loop on the right:

$$I_{sc2} = \frac{-j16V}{16\Omega + z_L} = \frac{-j16V}{16\Omega + j16\Omega} = \frac{-j}{1+j}$$

$$\text{or} = \frac{-j}{1+j} \frac{1-j}{1-j} A = \frac{-1-j}{1^2+1} = \frac{-1-j}{2}$$


Sum the results:  $I_{sc} = I_{sc1} + I_{sc2}$

$$= 1+j A + \frac{-1-j}{2} A$$

$$I_{sc} = \frac{1+j}{2} A \text{ or } \frac{1}{\sqrt{2}} \angle 45^\circ A$$

$$z_{Th} = \frac{V_{Th}}{I_{sc}} = \frac{j16V}{\frac{1+j}{2}} = \frac{16 \angle 90^\circ V}{\frac{1+j}{2}} = 16\sqrt{2} \angle 45^\circ \Omega$$

$$z_{Th} = 16 + j16 \Omega$$

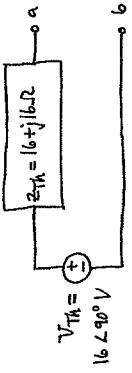

183b

Ex: Give numerical answers to each of the following questions:

a) Rationalize  $\frac{120 - j22}{-11 + j60}$ . Express your answer in rectangular form.

b) Find the polar form of  $j(1+j)*e^{j30^\circ}$ . (Note the asterisk that means "conjugate".)

c) Find the following phasor:  $\text{P}[-7\cos(49t + 135^\circ)]$ .

d) Find the magnitude of  $\left(\frac{24+j7}{3-j4}\right)\left(\frac{-1}{e^{j10^\circ}}\right)$ .

e) Find the imaginary part of  $\frac{e^{j45^\circ}}{e^{-j225^\circ}}$ .

$$\text{Solv: a)} \frac{120 - j22}{-11 + j60} \cdot \frac{-11 - j60}{-11 - j60} = \frac{2(60 - j11)(-1)(11 + j60)}{11^2 + 60^2}$$

$$= -2 \left[ \frac{60(11) + 11(60) + j3600 - j12}{61^2} \right]$$

$$= -\frac{1320 - j6958}{61^2}$$

$$= -\frac{1320}{3721} - \frac{j6958}{3721}$$

$$\approx -0.7 - j1.870$$

$$\text{b)} j(1+j)^* e^{j30^\circ} = j(-j) e^{j30^\circ}$$

$$= e^{j90^\circ} \sqrt{2} e^{-j45^\circ} e^{j30^\circ}$$

$$= \sqrt{2} e^{j75^\circ}$$

c)  $P[-7\cos(49t + 135^\circ)] = -7 \angle 135^\circ$

$$= 7 \angle 135^\circ \text{ or } 7 \angle -45^\circ$$

d) 
$$\left| \frac{24+j7}{3-j4} \right| \left| \frac{-1}{e^{j10^\circ}} \right| = \frac{|24+j7|}{|3-j4|} \left| \frac{-1}{e^{j10^\circ}} \right|$$

$$= \frac{\sqrt{24^2+7^2}}{\sqrt{3^2+4^2}} \cdot \frac{1}{1}$$

$$= \frac{25}{5} = 5$$

e)  $\text{Im} \left[ \frac{e^{j45^\circ}}{e^{-j225^\circ}} \right] = \text{Im} \left[ e^{j(45^\circ - 225^\circ)} \right]$


$$= \text{Im} [e^{j270^\circ}]$$

$$= \text{Im} [-j]$$

$$= -1$$

HW 8 Example

184

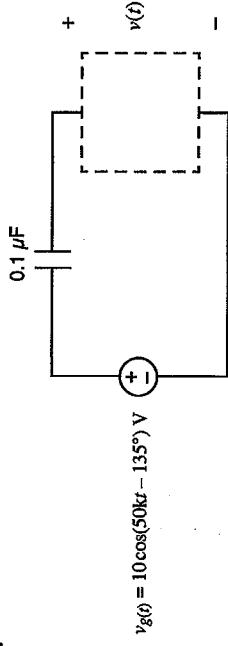


- a) Choose an R, an L, or a C to be placed in the dashed-line box to make  $v(t) = V_o \sin(50kt)$  where  $V_o$  is a positive real constant (with units of Volts). State the value of the component you choose.
- b) With your component from (a) in the circuit, calculate the resulting value of  $V_o$ .

Sol'n: a) We first transform the circuit to the frequency domain.

$$V_g = 10 \angle -135^\circ V \quad V = V_o \angle -90^\circ \text{ since } P[\sin(wt)] \\ = -j \text{ or } L \angle -90^\circ$$

$$Z_C = \frac{-j}{\omega C} = \frac{-j}{50 \cdot 0.1 \mu\text{F}} = -j 200 \Omega$$

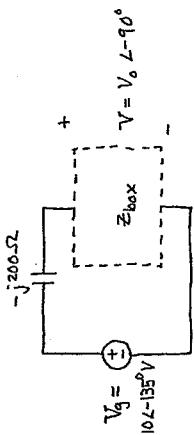Note:  $\omega = 50 \text{ rad/s}$  from  $v_g(t)$  and  $v(t)$ .



Now we consider phase relationships.

$$V = V_g \cdot \frac{Z_{box}}{Z_{box} - j 200 \Omega} \text{ from V-divider}$$

$$\angle V = \angle V_g + \angle Z_{box} - \angle (Z_{box} - j 200 \Omega) \\ \parallel \\ -90^\circ = -135^\circ + \angle Z_{box} - \angle (Z_{box} - j 200 \Omega)$$

$$\text{Thus, } \angle Z_{box} - \angle (Z_{box} - j 200 \Omega) = 45^\circ.$$

Consider possible contents of  $Z_{box}$ .

$$\text{If } Z_{box} = j\omega L \text{ or } -j \frac{1}{\omega C}, \text{ then all } Z \text{ values in the circuit are pure imaginary.}$$

$$\text{Thus, } \angle Z_{box} - \angle (Z_{box} - j 200 \Omega) \text{ would}$$


be some multiple of  $90^\circ$ . It follows that  $Z_{box}$  must be an R value.

$$\therefore \text{Let } Z_{box} = R. \quad \angle R = 0^\circ$$

$$\text{Then } \angle Z_{box} - \angle (Z_{box} - j 200 \Omega) = 45^\circ \\ = 0^\circ - \angle (R - j 200 \Omega)$$

$$\text{or } \angle (R - j 200 \Omega) = -45^\circ$$

Now we can find R graphically.

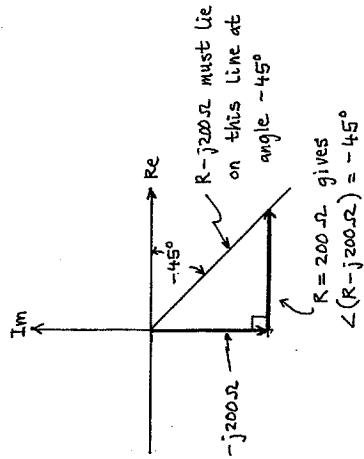


- b) To find  $V_o$ , we use magnitude.

$$\begin{aligned}
 V_o &= |V| = \left| V_g \cdot \frac{Z_{\text{box}}}{Z_{\text{box}} - j200\Omega} \right| \\
 &= \left| V_g \frac{R}{R - j200\Omega} \right| \\
 &= \left| V_g \frac{200\Omega}{200\Omega - j200\Omega} \right| \\
 &= |10| \left| \frac{200\Omega}{200\Omega - j200\Omega} \right|
 \end{aligned}$$

$$\begin{aligned}
 &= \frac{10V \cdot 200}{200 |1-j|} \\
 &= \frac{10V}{|1-j|} \\
 &= \frac{10V}{\sqrt{2}} \\
 V_o &= \frac{10}{\sqrt{2}} V
 \end{aligned}$$

(186)

## Solution Prob 3

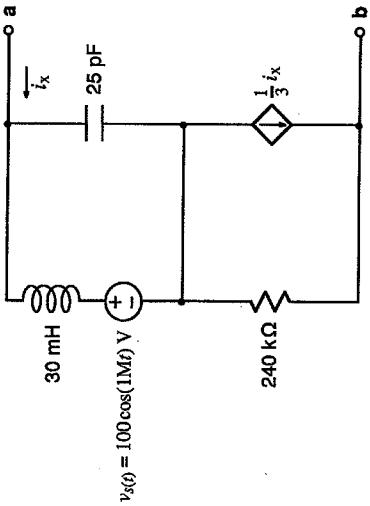

- a) Draw a frequency-domain equivalent of the above circuit. Show a numerical phasor value for  $v_s$ , and show numerical impedance values for  $R$ ,  $L$ , and  $C$ . Label the dependent source appropriately.
- b) Find the Thevenin equivalent (in the frequency domain) for the above circuit. Give the numerical phasor value for  $V_{Th}$  and the numerical impedance value of  $Z_{Th}$ .


Sol'n: a) First, we find phasors and  $\omega$  values.

$$V_s = 100 \angle 0^\circ V \quad \omega = 1M \text{ rad/s}$$

$$Z_L = j \omega L = j 1M \text{ rad/s} \cdot 30 \text{ mH} = j 30 \text{ k}\Omega$$


$$Z_C = \frac{-j}{\omega C} = \frac{-j}{1M \text{ rad/s} \cdot 25 \text{ pF}} = \frac{-j}{25 \mu} = -j 40 \text{ k}\Omega$$

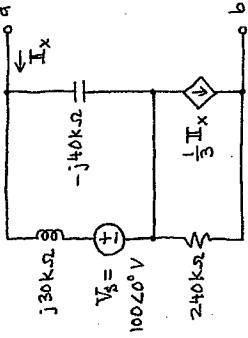Now we can draw the frequency domain model:



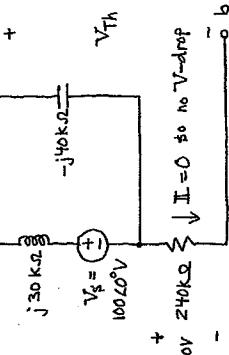- b) We first find  $V_{Th} = V_{ab}$  with no load connected across  $a, b$ .

In this case,  $I_x = 0 A$  since  $a, b$  = open.



We have a  $V$ -divider:

$$V_{Th} = V_s \frac{-j 40 \text{ k}\Omega}{-j 40 \text{ k}\Omega + j 30 \text{ k}\Omega} = V_s \frac{-j 40 \text{ k}\Omega}{-j 10 \text{ k}\Omega}$$

$$V_{Th} = 4V_s = 4(100 \angle 0^\circ V)$$


$$V_{Th} = 400 \angle 0^\circ V$$

(187)

To find  $Z_{Th}$ , we replace the dependent source with an equivalent impedance.

We observe that, regardless of what is connected between **a** and **b**,  $\mathbb{I}_x$  flows out of the **b** terminal, (and into the **a** terminal).

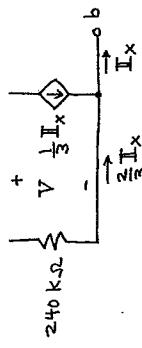Consider a current summation at the bottom node:



We have current  $\frac{2}{3}I_x$  through the  $240\text{k}\Omega$ .

The voltage across both the  $240\text{k}\Omega$  and the dependent source, by Ohm's law, will be  $V = \frac{2}{3}I_x \cdot 240\text{k}\Omega$ .

thus, the equivalent impedance for the dependent source is found by using Ohm's law:


$$\begin{aligned} Z_{eq} &= \frac{V}{\frac{1}{3}I_x} = \frac{\frac{2}{3}I_x \cdot 240\text{k}\Omega}{\frac{1}{3}I_x} \\ &= 2(240\text{k}\Omega) \\ &= 480\text{k}\Omega \end{aligned}$$

$$Z_{eq} = 480\text{k}\Omega$$

To find  $Z_{Th}$ , we replace the dependent source with an equivalent impedance.

$$\begin{aligned} R &= 240\text{k}\Omega \parallel 480\text{k}\Omega = 240\text{k}\Omega \cdot \frac{1}{2} \\ R &= 240\text{k}\Omega \cdot \frac{2}{3} = 160\text{k}\Omega \end{aligned}$$

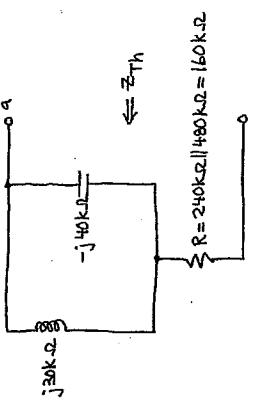Finally, we turn off the  $V_S$  source and look into the circuit from the **a**, **b** terminals to find  $Z_{Th}$ :



$$R = 240\text{k}\Omega \parallel 480\text{k}\Omega = 160\text{k}\Omega$$

$$Z_{Th} = j30\text{k}\Omega \parallel -j40\text{k}\Omega + 160\text{k}\Omega$$

$$= j10\text{k}\Omega \cdot 3 \parallel -4 + 160\text{k}\Omega$$

$$= j10\text{k}\Omega \cdot \frac{-12}{-1} + 160\text{k}\Omega$$

$$= j120\text{k}\Omega + 160\text{k}\Omega$$

$$\text{or } Z_{Th} = 160\text{k}\Omega + j120\text{k}\Omega$$


188

(18)

3. (b)

Different methodology:  $+V_1 + 100 - 30k_j (I_2) = 0$

$$I_2 = \frac{V_1 + 100}{30k_j}$$

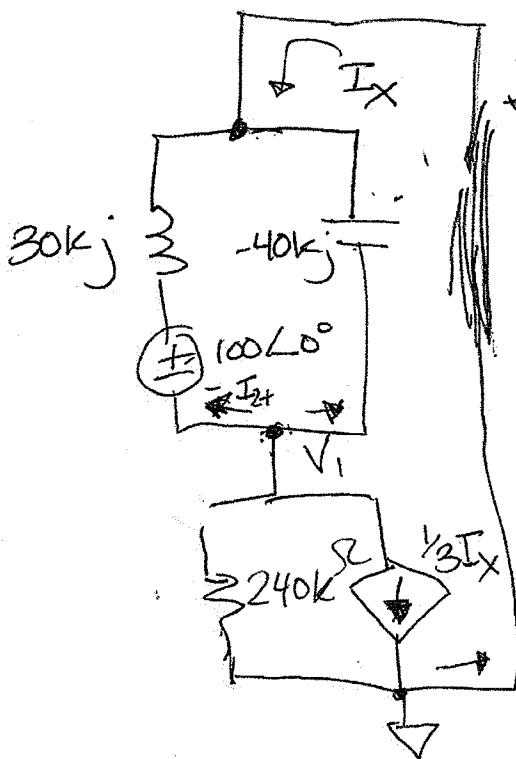

$$I_{SC} = -I_x$$

$$2m \angle 143^\circ = \frac{V_1}{2(80k)} = I_x = -I_{SC}$$

e.g.  $\frac{V_1}{240k} + \frac{1}{3}I_x - I_x = 0$  (current sum)

Node Voltage:

$$\frac{V_1}{240k} + \frac{1}{3}I_x + \frac{V_1}{-40k_j} + \frac{V_1 + 100}{30k_j} = 0$$

$$\frac{V_1}{240k} + \frac{1}{3} \left[ \frac{V_1}{2(80k)} \right] - \frac{V_1}{40k_j} + \frac{V_1}{30k_j} = -\frac{100}{300k}$$

$$V_1 \left( \frac{2}{240k} + \frac{1}{480k} + \frac{12j}{480k} + \frac{-16j}{480k} \right) = +\frac{j}{300}$$

$$V_1 \left( \frac{3-4j}{480k} \right) = \frac{j}{300} \frac{(480k)}{5} \angle 90^\circ + 53^\circ$$

$$V_1 = 320 \angle 143$$

$$V_{Th} = 400 \angle 0^\circ \Rightarrow Z_{Th} = \frac{V_{Th}}{I_{SC}} = \frac{400 \angle 0^\circ}{-2m \angle 143^\circ} = 200k \angle -143^\circ$$

$$Z_{Th} = (160k + 120k_j) \Omega$$