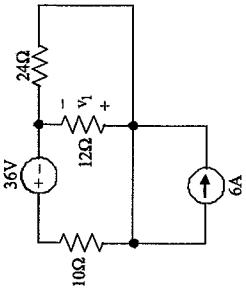



Problem Session #1 Problems:

1. Calculate v_1 .




Solution: $v_1 = 16V$

2. Calculate i_1 .

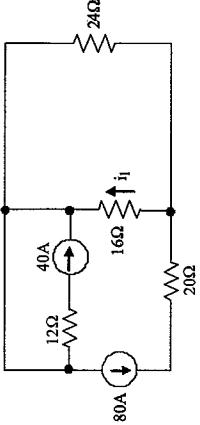


Solution: $i_1 = 48A$

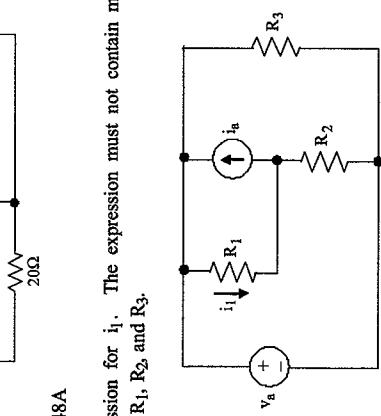3. Derive an expression for i_1 . The expression must not contain more than the circuit parameters v_a , i_a , R_1 , R_2 , and R_3 .



Solution: $i_1 = \frac{v_a + i_a R_2}{R_1 + R_2}$

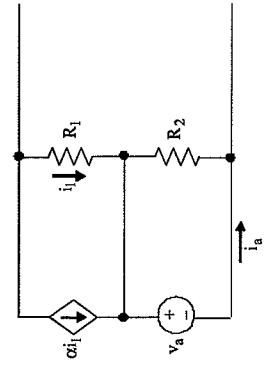
4. Derive an expression for i_a . The expression must not contain more than the circuit parameters α , v_a , R_1 , and R_2 .



Solution: $i_a = \frac{v_a}{R_2 \parallel \frac{R_1}{1+\alpha}}$

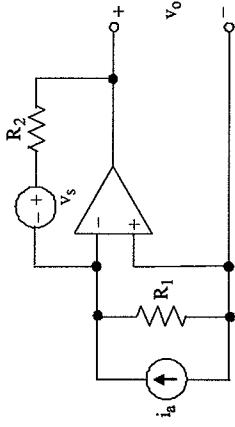
5. Make at least one consistency check (other than a units check) on your expression. Explain the consistency check clearly.

- The op-amp operates in the linear mode. Using an appropriate model of the op amp, derive an expression for v_o in terms of not more than v_s , i_a , R_1 , and R_2 .



Solution: $v_o = v_s - i_a R_2$

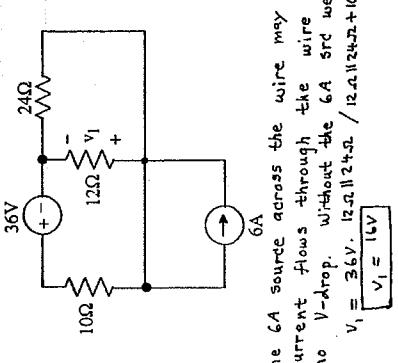
1. a. (5 points)
Calculate v_1 .
- b. (5 points)
Calculate i_1 .




soln: The 6A source across the wire may be ignored. Its current flows through the wire but produces no V-drop. without the 6A src we have a V-divider:

$$v_1 = \frac{36V}{12\Omega || 24\Omega} / (12\Omega || 24\Omega + 10\Omega) = 36V \cdot 8\Omega / 18\Omega = 16V$$

Calculate i_1 .

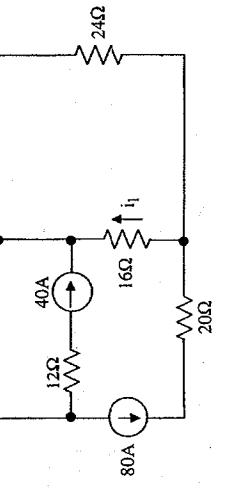


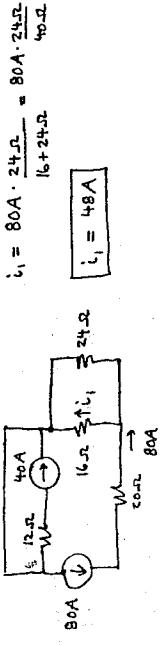soln: If we redraw the circuit, we see a current divider:



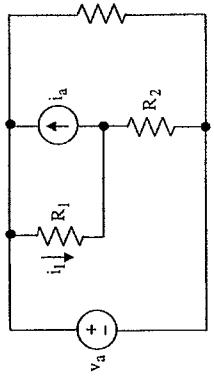
2. (30 points)

Derive an expression for i_1 . The expression must not contain more than the circuit parameters v_a , i_a , R_1 , R_2 , and R_3 .



soln:

Redraw with top as one node:

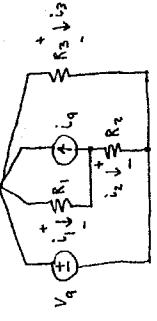

Current sum at top or bottom node? No, because we would have to define a current for source v_a .

Current at center node: $i_q - i_1 + i_2 = 0A$

V-loop around left inner loop: $v_a - i_1 R_1 - i_2 R_2 = 0V$


No V-loop for other inner loops because we would have to define V-drop for i_q .

Next larger loop is $R_1, R_2, R_3 : i_2 R_2 + i_1 R_1 - i_3 R_3 = 0V$
Now we have 3 eqns in 3 unknowns, and we want to find i_1 .

We observe, however, that the first two eqns have only two unknowns. So we don't actually need the 3rd eqn. Use 1st eqn to find $i_2 = i_1 - i_q$. Substitute into 2nd eqn: $v_a - i_1 R_1 - (i_1 - i_q) R_2 = 0V$
or $i_1 (-R_1 - R_2) = -v_a - i_q R_2$ or $i_1 = \frac{v_a + i_q R_2}{R_1 + R_2}$


3. (30 points)

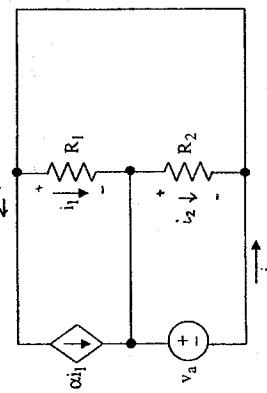- a. Derive an expression for i_a . The expression must not contain more than the circuit parameters α , v_a , R_1 , and R_2 .



- b. Make at least one consistency check (other than a units check) on your expression. Explain the consistency check clearly.

Soln: a) Redraw circuit

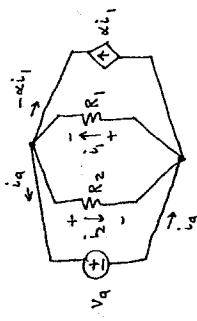

No current sums at nodes because of v_q .

$$\begin{aligned} V\text{-loop on left: } & v_q - i_2 R_2 = 0V \Rightarrow i_2 = \frac{v_q}{R_2} \\ V\text{-loop in middle: } & i_2 R_2 + i_1 R_1 = 0V \Rightarrow i_1 = -\frac{v_q}{R_1} \\ & \frac{v_q}{R_2} \end{aligned}$$

We could also just observe that v_q is across R_1 and R_2 .


Now that we have found i_1 and i_2 , we use a current at top node to find i_a :

$$\begin{aligned} i_a + i_2 - i_1 - \alpha i_1 &= 0A \quad \text{or } i_a + \frac{v_q}{R_2} + \frac{v_q}{R_1} + \alpha \frac{v_q}{R_1} = \\ \text{or } i_a &= -v_q \left(\frac{1}{R_2} + \frac{1}{R_1} + \alpha \right) \quad \text{or } i_a = -\frac{v_q}{R_1 \parallel \frac{R_2}{\alpha} \parallel R_2} \end{aligned}$$

Soln: 3.b)

Many possible answers.

Example: Suppose $\alpha = 0$.

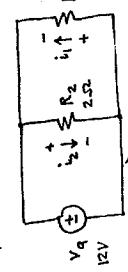

We see that i_q is current thru $R_1 \parallel R_2$ with $R_1 \parallel R_2$ across v_q .


$$\begin{aligned} R_1 \parallel R_2 &= 1 \parallel 2 \Omega = \frac{1 \cdot 2}{1+2} = \frac{2}{3} \Omega \\ \therefore i_q &= -v_q / R_1 R_2 = -12V \cdot \frac{2}{3} \Omega = -12V \cdot \frac{2}{3} \Omega = -18A \end{aligned}$$

Use formula from a) with these component values:


$$\begin{aligned} i_q &= -12V \left(\frac{1}{2\Omega} + \frac{1}{1\Omega} + \frac{2}{1+2} \right) = -12V \cdot \frac{3}{2} \\ i_q &= -18V \quad \checkmark \quad \text{agrees with obvious soln for this simple case} \end{aligned}$$

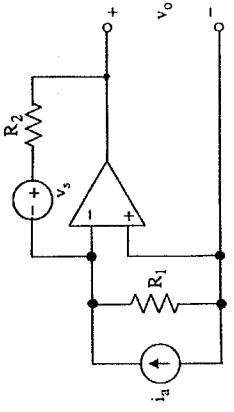4. (30 points)

The op-amp operates in the linear mode. Using an appropriate model of the op amp, derive an expression for v_o in terms of not more than v_s , i_a , R_1 , and R_2 .



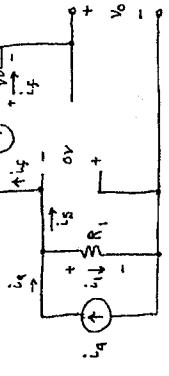Sol'n: Redraw without op-amp and ov drop across + and - inputs:



V-loop on left thru R_1 and ov drop:
 $i_A R_1 + \text{ov} = \text{ov}$ or $i_A = 0$

Current sum at node above R_1 :

$$-i_A + i_i + i_S = 0 \text{A} \quad \text{or} \quad i_S = i_A$$

V-loop on right thru ov drop, v_S , R_2 , and v_o :

$$-\text{ov} + v_S - i_S R_2 - v_o = \text{ov} \quad \text{or} \quad i_S = \frac{v_S - v_o}{R_2}$$

Now use $i_S = i_A$. Thus $v_S - v_o = i_A R_2$

$$i_A = \frac{v_S - v_o}{R_2} \quad \text{or} \quad v_o = v_S - i_A R_2$$