

2. (cont.)

$$3 \left[V_1 \left(\frac{12}{20} \right) - V_2 \left(\frac{3}{20} \right) = 56 \right]$$

$$12 \left[-V_1 \left(\frac{3}{20} \right) + V_2 \left(\frac{13}{20} \right) = 4 \right]$$

$$V_1 \left(\frac{3}{20} \right) - V_2 \left(\frac{9}{20} \right) = 108$$

$$+ V_1 \left(\frac{36}{20} \right) + V_2 \left(\frac{156}{20} \right) = 48$$

$$\underline{O} \quad + V_2 \left(\frac{147}{20} \right) = 216$$

$$\therefore V_2 = \frac{14820}{147} = \boxed{\frac{1440}{49} V}$$

$$\frac{1440}{49} \left(\frac{13}{20} \right) - V_1 \left(\frac{3}{20} \right) - 4 \Rightarrow V_1 = \frac{-3920 + 18720}{980} \left(\frac{20}{3} \right)$$


$$V_1 = \boxed{\frac{14800}{49(3)}}$$

$$i_{\text{through } 10} \Rightarrow +V_1 - i_1(10) + 40 - V_2 = 0$$

$$i_3 = V_1 - V_2 + 40 = \frac{14800}{49(3)} - \frac{3(1440)}{49(3)} + \frac{40(144)(3)}{49(3)} = \frac{1680}{49(3)}$$

$$\text{power} = i_3^2 \cdot (10) = \left[\frac{1680}{49(3)} \right]^2 (10) \approx \boxed{1238.6 \text{ W}}$$

3.

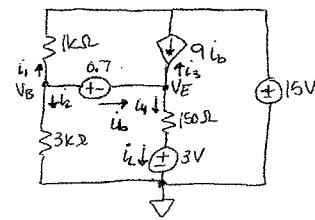

$$V_B - V_E = 0.7 \text{ V} \Rightarrow V_E = V_B - 0.7$$

$$\frac{V_B - 15}{1k} + \frac{V_B - 3}{3k} + i_b = 0$$

$$-9i_b - i_b + \frac{V_B - 3}{150} = 0 \Rightarrow 10i_b = \frac{V_B - 3}{150(10)}$$

$$\frac{V_B - 15}{1k} + \frac{V_B - 3}{3k} + \frac{(V_B - 0.7) - 3}{150(10)} = 0$$


$$V_B \left(\frac{1}{1k} + \frac{1}{3k} + \frac{1}{150(10)} \right) = \frac{15}{1k} + \frac{3.7}{150(10)} = \frac{45}{3k} + \frac{7.4}{150}$$

$$V_B \left(\frac{6}{3k} \right) = \frac{52.4}{3k} \Rightarrow V_B = \boxed{\frac{52.4}{6} V}$$

$$\therefore V_E = V_B - 0.7 = \boxed{\frac{48.2}{6} V}$$

$$i_e = \frac{V_E - 3}{150} = \frac{48.2}{6} - \frac{18}{6} = \boxed{\frac{30.2}{60(150)} A}$$

4.

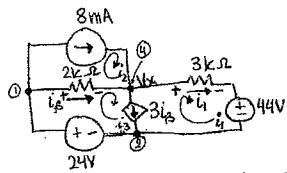

$$\textcircled{1} \quad i_p = i_3 - i_2 \quad \text{where } i_2 = 8 \text{ mA}$$

$$\textcircled{2} \quad 3i_p = i_3 - i_1$$

$$\textcircled{3} \quad +24 - i_p(2k) - i_1(3k) - 44 = 0$$

subtracting \textcircled{2} from \textcircled{1}
 or summation at node \textcircled{4}

$$2i_p = -i_1 + 8 \text{ mA}$$

plugging into \textcircled{3}

$$24 - (2k)(-i_1 + 8 \text{ mA}) - i_1(3k) - 44 = 0$$

$$-20 + i_1(1k) - 1k(8 \text{ mA}) - i_1(3k) = 0$$

$$i_1(-2k) = 20 + 8$$

$$\therefore i_1 = -14 \text{ mA}$$

Voltage V_x across $3i_p$:

$$+V_x - i_1(3k) - 44 = 0$$

$$V_x = -14 \text{ mA}(3k) + 44 = +2 \text{ V}$$

\therefore power absorbed \Rightarrow

$$V_x \cdot 3i_p = +2(3) \cdot -14 \text{ mA}$$

$$i_p = \frac{14 \text{ mA} + 8 \text{ mA}}{2} = 11 \text{ mA}$$

$$\therefore \text{power} = \boxed{+66 \text{ mW}}$$