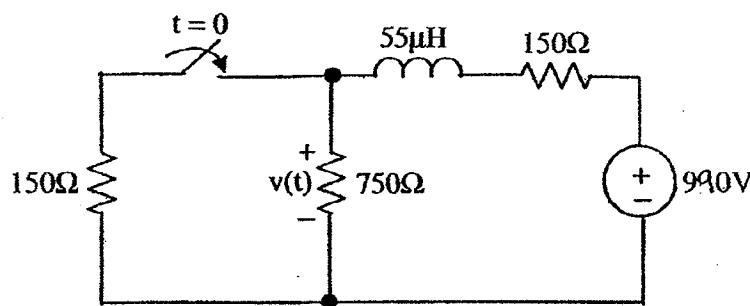


1.




After being open for a long time, the switch is closed at  $t = 0$ .

- Calculate the energy  $L$  stored on the inductor at  $t = 0$ .
- Write a numerical expression for  $v(t)$ ,  $t > 0$ .

Sol'n: a) Energy  $w = \frac{1}{2} L i_L^2$  so we find  $i_L(t \rightarrow \infty)$ .

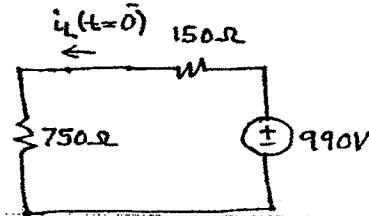$t = 0^-$ : L acts like wire. Switch is open.



$$R_{eq} = 150 + 750 \Omega$$

$$R_{eq} = 900 \Omega$$


$$i_L(t=0) = \frac{990V}{150\Omega + 750\Omega} = \frac{990V}{900 \Omega} = 1.1A$$

$$w(t=0) = \frac{1}{2} 55\mu H \cdot (1.1A)^2 = 33.275 \mu J$$

$w \doteq 33.3 \mu J$

Sol'n: 1.b) First, find  $i_L(0^-)$ .

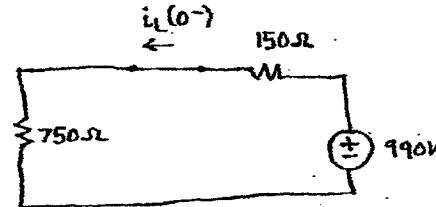$t=0^-$ : L acts like wire. Switch is open.




$$i_L(0^-) = \frac{990V}{150\Omega + 750\Omega} = \frac{990V}{900\Omega} = 1.1A$$

Now we find  $v(t=0^+)$ .

$t=0^+$ :  $i_L(0^+) = i_L(0^-) = 1.1A$  modeled as i src.

Switch closed.

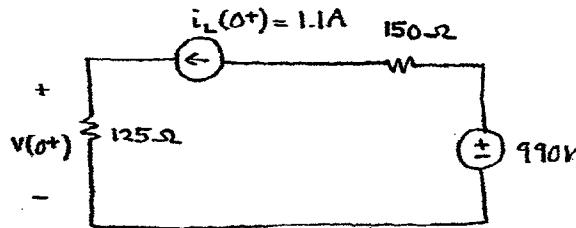$v(t)$  is across  $150\Omega \parallel 750\Omega = 125\Omega$



$$v(0+) = i_L(0+) \cdot 125\Omega = 1.1A \cdot 125\Omega = 137.5V$$


$t \rightarrow \infty$ :

We find  $v(t \rightarrow \infty)$  from  $L=\text{wire}$  and  $R_{\text{tot}} = 150\Omega + 125\Omega = 275\Omega$

$$v(t \rightarrow \infty) = \frac{990V}{R_{\text{tot}}} \cdot 125\Omega = \frac{990V}{275} \cdot 125\Omega = 450V$$

We find time constant  $\frac{L}{R_{\text{Th}}}$  from Thevenin

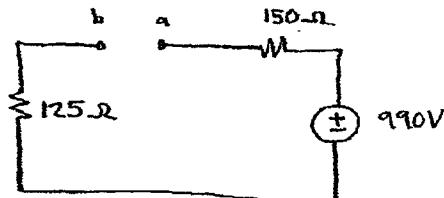equivalent of circuit where L is connected




# HW #6 cont.

Su 05

sol'n: 1.b) cont.

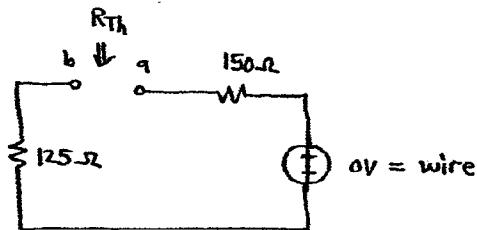We turn off the 990V src and look into the a,b terminals to find  $R_{Th}$ .



$$R_{Th} = 125\Omega + 150\Omega = 275\Omega$$

$$\frac{L}{R_{Th}} = \frac{55\mu H}{275\Omega} = 0.2\mu s = 200\text{ ns}$$


Now plug all values into general sol'n:

$$v(t>0) = v(t \rightarrow \infty) + [v(0^+) - v(t \rightarrow \infty)] e^{-t/L/R_{Th}}$$

$$v(t>0) = 450V + [137.5 - 450V] e^{-t/200\text{ ns}}$$

$$v(t>0) = 450V - 312.5V e^{-t/200\text{ ns}}$$

2.

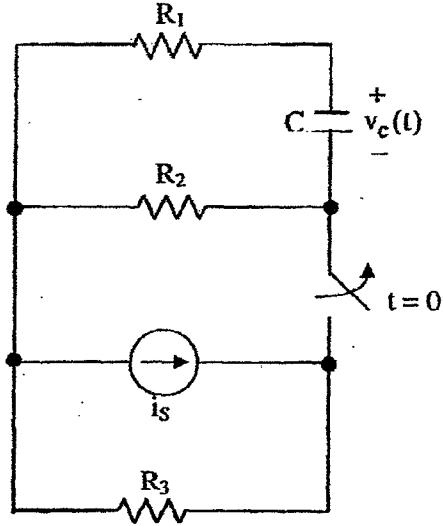


After being closed for a long time, the switch is opened at  $t = 0$ .

- Write an expression for  $v_c(t = 0^+)$ .
- Write an expression for  $v_c(t > 0)$ .

Sol'n: a)  $v_c(t = 0^+) = v_c(0^-)$

$\rightarrow t = 0^-$ :  $C$  acts like open circuit.

Switch is closed.

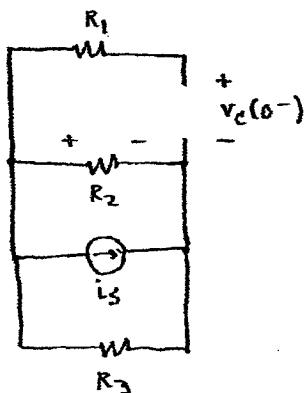

No current thru  $R_1$ ,  
 $\therefore$  no v-drop across  $R_1$

It follows that  $v_c(0^-)$   
>equals the v-drop  
>across  $R_2$ , measured  
>as shown.

Thus,  $v_c(0^-) = -i_S \cdot R_2 \parallel R_3$ .


$v_c(t = 0^+) = -i_S \cdot R_2 \parallel R_3$

sol'n: 2.b) We have  $v_c(0^+) = -i_s \cdot R_2 \parallel R_3$  from 2(a).

Find  $v_c(t \rightarrow \infty)$  and  $R_{Th} C$  to finish sol'n.

$t \rightarrow \infty$ : C acts like open circuit.

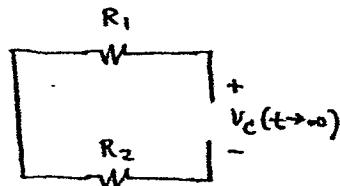
Switch is open.  $\therefore i_s$  and  $R_3$  not in circuit



C will discharge to 0V thru  $R_1$  and  $R_2$ .

Thus,  $v_c(t \rightarrow \infty) = 0V$

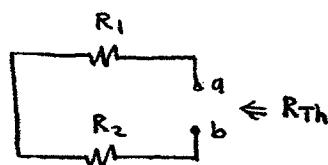We find  $R_{Th}$  from circuit where C connected.



We see  $R_{Th} = R_1 + R_2$ .


Plug values into general solution:

$$v_c(t > 0) = v_c(t \rightarrow \infty) + [v_c(0^+) - v_c(t \rightarrow \infty)] e^{-t/R_{Th}C}$$

$$v_c(t > 0) = 0V + [-i_s \cdot R_2 \parallel R_3 - 0V] e^{-t/(R_1+R_2)C}$$

$$v_c(t > 0) = -i_s \cdot R_2 \parallel R_3 e^{-t/(R_1+R_2)C}$$


3.

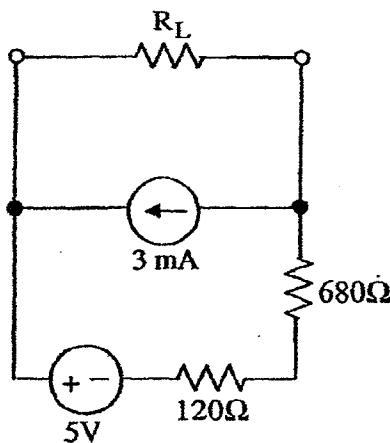

- Calculate the value of  $R_L$  that would absorb maximum power.
- Calculate that value of maximum power  $R_L$  could absorb.

Sol'n: a)  $R_L = R_{Th}$  for max pwr xfer

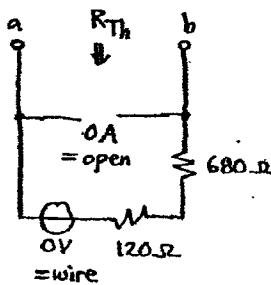Remove  $R_L$  and find  $R_{Th}$  by turning off independent src's and look into terminals where  $R_L$  connected.



$$R_{Th} = 680\Omega + 120\Omega$$

$$R_{Th} = 800\Omega$$

$R_L = 800\Omega$

HW #6 Conf.


Su 05

$$\text{sol'n: 3.b)} \quad \text{max pwr} = \frac{V_{Th}^2}{4R_{Th}}$$


Find  $V_{Th}$  as voltage where  $R_L$  connected when  $R_L$  is removed.

use superposition, (or node-voltage or etc.)

case I: 3 mA on, 5V off = wire

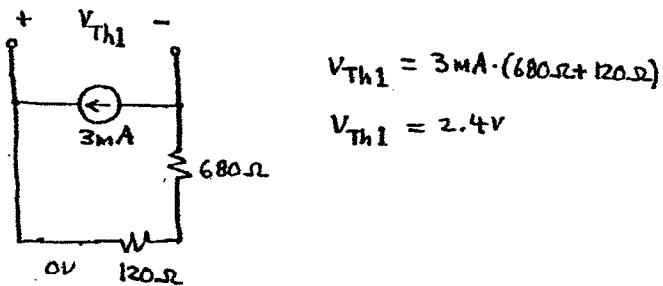

case II: 3 mA off, 5V on  
= open

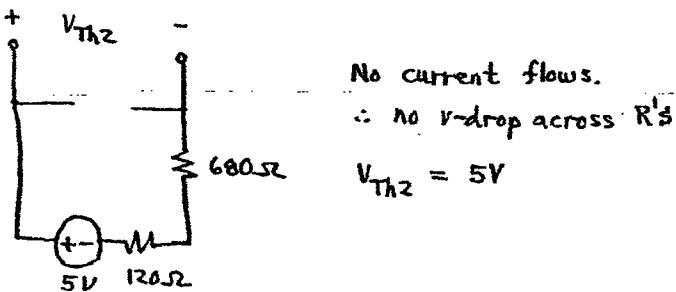


$$V_{Th} = V_{Th1} + V_{Th2} = 2.4V + 5V = 7.4V$$

$$\text{max pwr} = \frac{(7.4)^2}{4 \cdot 800\Omega} \doteq 17.1 \text{ mW}$$

$$\boxed{\text{max pwr} \doteq 17.1 \text{ mW}}$$

4.

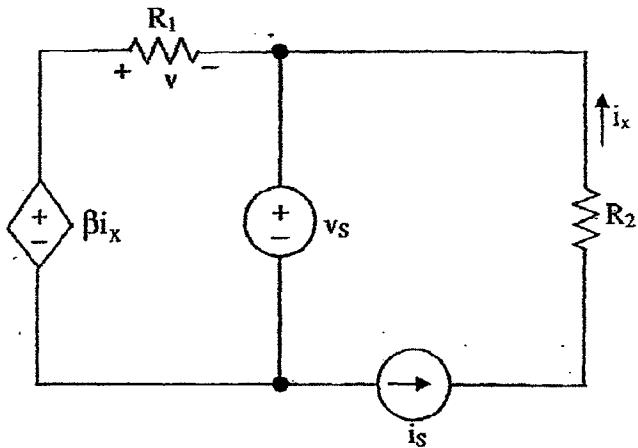


Using superposition, derive an expression for  $v$  that contains no circuit quantities other than  $i_s$ ,  $v_s$ ,  $R_1$ ,  $R_2$ , and  $\beta$ , where  $\beta > 0$ .

Sol'n: Turn on one independent src at a time.


(Keep dependent sources on at all times.)

case I:  $v_s$  on,  $i_s$  off = open

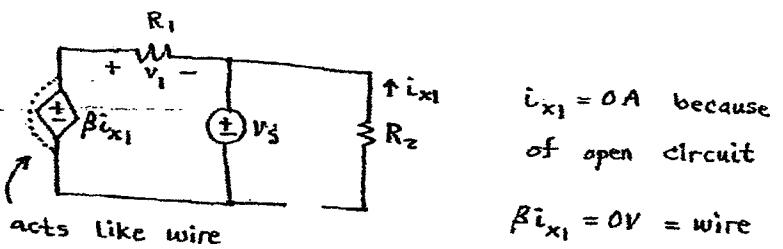

$$v_1 = -v_s \text{ from } v \text{ loop on left side}$$

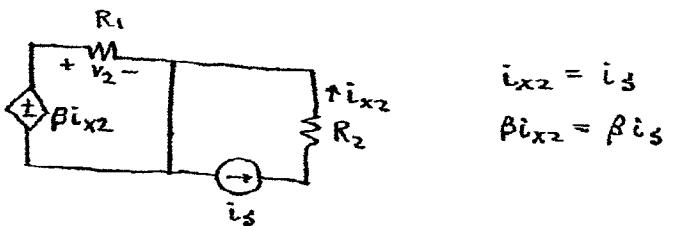case II:  $v_s$  off,  $i_s$  on  
= wire




$$v_2 = \beta i_{x2} = \beta i_s \text{ from } v \text{ loop on left side}$$

$$\boxed{v = v_1 + v_2 = -v_s + \beta i_s}$$

- 4.76** The variable resistor ( $R_L$ ) in the circuit in Fig. P4.76 is adjusted for maximum power transfer to  $R_L$ .

- P**
- Find the numerical value of  $R_L$ .
  - Find the maximum power transferred to  $R_L$ .

Figure P4.76

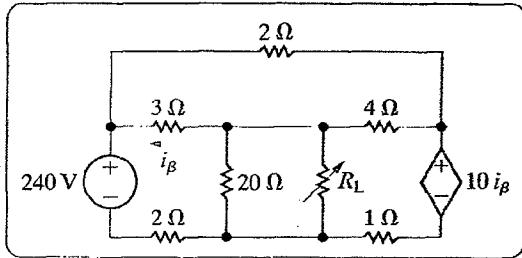
**4.77**

- The variable resistor in the circuit in Fig. P4.77 is adjusted for maximum power transfer to  $R_o$ .

**P**

- Find the value of  $R_o$ .
- Find the maximum power that can be delivered to  $R_o$ .

Figure P4.77

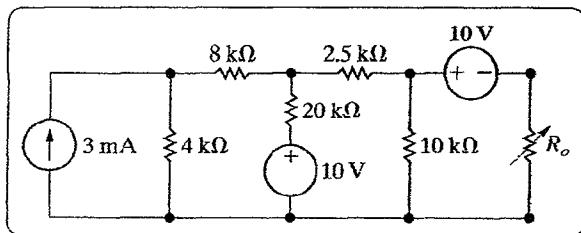**4.78**

- What percentage of the total power developed in the circuit in Fig. P4.77 is delivered to  $R_o$  when  $R_o$  is set for maximum power transfer?

**P**

- 4.79** A variable resistor  $R_o$  is connected across the terminals a,b in the circuit in Fig. P4.68. The variable resistor is adjusted until maximum power is transferred to  $R_o$ .

**P**

- Find the value of  $R_o$ .
- Find the maximum power delivered to  $R_o$ .
- Find the percentage of the total power developed in the circuit that is delivered to  $R_o$ .

**4.80**


- Calculate the power delivered for each value of  $R_o$  used in Problem 4.67.
- Plot the power delivered to  $R_o$  versus the resistance  $R_o$ .
- At what value of  $R_o$  is the power delivered to  $R_o$  a maximum?

**4.81**

- The variable resistor ( $R_o$ ) in the circuit in Fig. P4.81 is adjusted for maximum power transfer to  $R_o$ . What percentage of the total power developed in the circuit is delivered to  $R_o$ ?

**P**

Figure P4.81

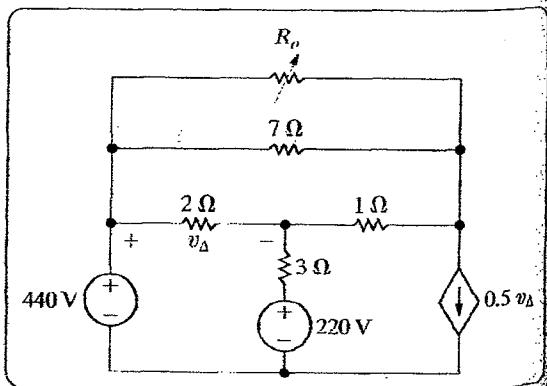

$$-240 + 3(i_1 - i_2) + 2i_1 = 0$$

$$2i_2 + 4(i_2 - i_3) + 3(i_2 - i_1) = 0$$

$$10i_\beta + 1i_3 + 4(i_3 - i_2) = 0$$

The dependent source constraint equation is:

$$i_\beta = i_2 - i_1$$

Place these equations in standard form:

$$i_1(3 + 2) + i_2(-3) + i_3(0) + i_\beta(0) = 240$$


$$i_1(-3) + i_2(2 + 4 + 3) + i_3(-4) + i_\beta(0) = 0$$

$$i_1(0) + i_2(-4) + i_3(4 + 1) + i_\beta(10) = 0$$

$$i_1(1) + i_2(-1) + i_3(0) + i_\beta(1) = 0$$

Solving,  $i_1 = 92 \text{ A}$ ;  $i_2 = 73.33 \text{ A}$ ;  $i_3 = 96 \text{ A}$ ;  $i_\beta = -18.67 \text{ A}$

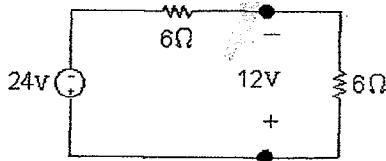
$$i_{sc} = i_1 - i_3 = -4 \text{ A}; \quad R_{Th} = \frac{V_{Th}}{i_{sc}} = \frac{-24}{-4} = 6 \Omega$$



$$R_L = R_{Th} = 6 \Omega$$

$$[b] \quad p_{max} = \frac{12^2}{6} = 24 \text{ W}$$

P 4.77 [a]

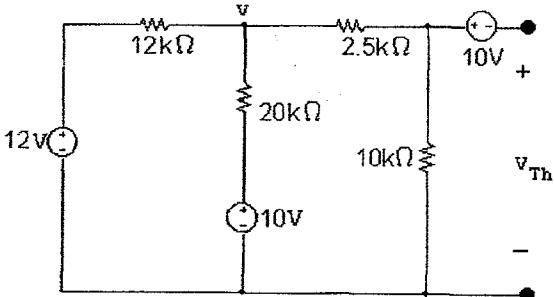


$$\frac{v - 12}{12,000} + \frac{v - 10}{20,000} + \frac{v}{12,500} = 0$$

$$\text{Solving, } v = 7.03125 \text{ V}$$

$$v_{10k} = \frac{10,000}{12,500} (7.03125) = 5.625 \text{ V}$$

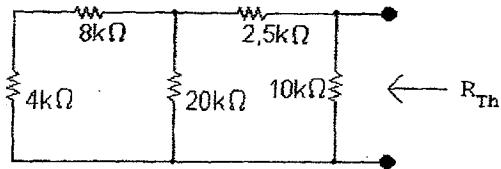
$$\therefore V_{Th} = v - 10 = -4.375 \text{ V}$$



$$R_{Th} = [(12,000 \parallel 20,000) + 2500] = 5 \text{ k}\Omega$$


$$R_o = R_{Th} = 5 \text{ k}\Omega$$

[b]

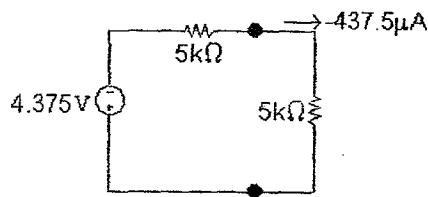

$$p_{max} = (-437.5 \times 10^{-6})^2 (5000) = 957.03 \mu \text{W}$$

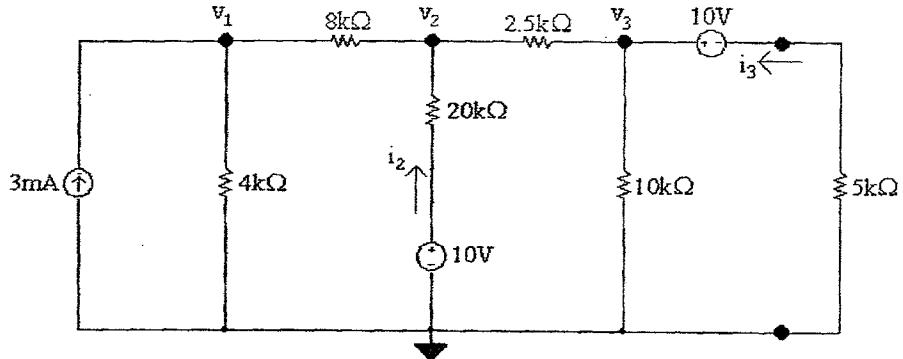P 4.78 Write KCL equations at each of the labeled nodes, place them in standard form, and solve:



$$\text{At } v_1: -3 \times 10^{-3} + \frac{v_1}{4000} + \frac{v_1 - v_2}{8000} = 0$$

$$\text{At } v_2: \frac{v_2 - v_1}{8000} + \frac{v_2 - 10}{20,000} + \frac{v_2 - v_3}{2500} = 0$$

$$\text{At } v_3: \frac{v_3 - v_2}{2500} + \frac{v_3}{10,000} + \frac{v_3 - 10}{5000} = 0$$