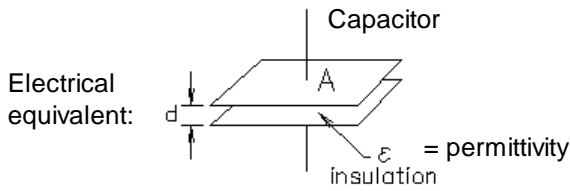


# ECE 2210 / 00 Capacitor Lecture Notes

A. Stolp  
2/17/03  
rev 9/16/09  
12/15 & 9/19

Now that we have voltages and currents which can be functions of time, it's time to introduce the capacitor and the inductor.



Electrical equivalent:

$$C = \epsilon \cdot \frac{A}{d} = \frac{Q}{V} = \frac{dq}{dv}$$


Units: farad =  $\frac{\text{coul}}{\text{volt}} = \frac{\text{amp}\cdot\text{sec}}{\text{volt}}$

$\mu\text{F} = 1 \cdot 10^{-6} \cdot \text{farad}$

$\text{pF} = 1 \cdot 10^{-12} \cdot \text{farad}$

For drawings of capacitors and info about tolerances, see Ch.3 of textbook.

Fluid Model:

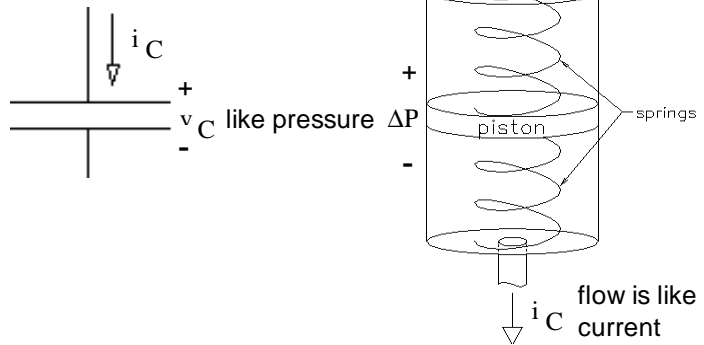

Basic equations you should know:

$$C = \frac{Q}{V}$$

$$i_C = C \cdot \frac{d}{dt} v_C$$

$$v_C = \frac{1}{C} \int_{-\infty}^t i_C dt$$

/ initial voltage

Or...

$$v_C = \frac{1}{C} \int_0^t i_C dt + v_C(0)$$


Or...

$$\Delta v_C = \frac{1}{C} \int_{t_1}^{t_2} i_C dt$$

Energy stored in electric field:  $W_C = \frac{1}{2} \cdot C \cdot V_C^2$


Capacitor voltage **cannot** change instantaneously

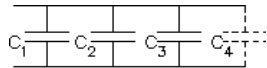**parallel:**  $C_{eq} = C_1 + C_2 + C_3 + \dots$



Capacitors are the only "backwards" components.

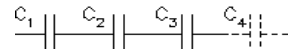**series:**  $C_{eq} = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots}$




## Sinusoids

$$i_C(t) = I_p \cdot \cos(\omega \cdot t)$$

$$v_C(t) = \frac{1}{C} \int i_C dt = \frac{1}{C} \cdot \frac{1}{\omega} \cdot I_p \cdot \sin(\omega \cdot t) = \frac{1}{C} \cdot \frac{1}{\omega} \cdot I_p \cdot \cos(\omega \cdot t - 90\text{-deg})$$

indefinite integral       $\underbrace{\quad}_{V_p}$        $\underbrace{\quad}_{V_p}$

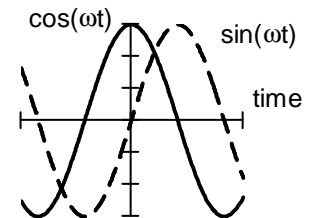Voltage "lags" current, makes sense, current has to flow in first to charge capacitor.




## Steady-state or Final conditions

If a circuit has been connected for "a long time", then it has reached a steady state condition. that means the currents and voltages are no longer changing.

$$\frac{d}{dt} v_C = 0 \quad i_C = C \cdot \frac{d}{dt} v_C = 0$$

no current means it looks like an open

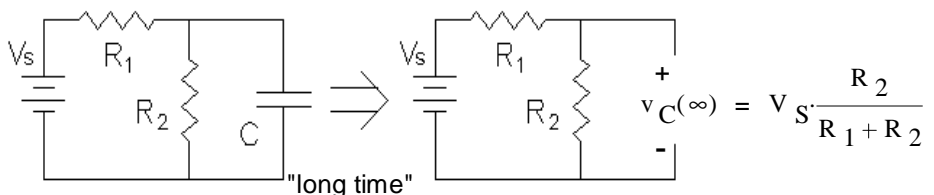


**Example**

The voltage across a  $0.5 \mu\text{F}$  capacitor is shown below. Make an accurate drawing of the capacitor current. Label the y-axis of your graph (I've already done the time-axis).

The accuracy of your plot at 0, 2, 6, and 8 ms is important, so calculate those values and plot or label them carefully. Between those points your plot must simply be the correct shape.

$C := 0.5 \mu\text{F}$

The curve is 2<sup>nd</sup> order

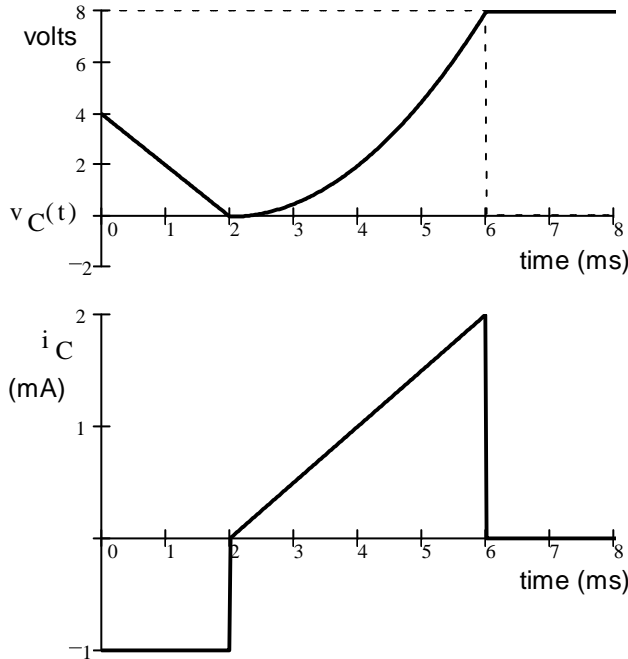

1 - 2ms:  $i_C = C \cdot \frac{\Delta V}{\Delta t} = 0.5 \mu\text{F} \cdot \frac{-4 \cdot \text{V}}{2 \cdot \text{ms}} = -1 \text{ mA}$

2ms - 6ms: Initial slope is zero and the final slope is positive, so the current must be a triangle that starts at zero and ends at some height.

$$\Delta v_C(t) = \frac{1}{C} \int_0^t i_C(t) dt$$


$$8 \cdot \text{V} = \frac{1}{C} \cdot \left( \frac{4 \cdot \text{ms} \cdot \text{height}}{2} \right)$$

$$\text{height} = 8 \cdot \text{V} \cdot \frac{C \cdot 2}{4 \cdot \text{ms}} = 2 \cdot \text{mA}$$

6ms - 8ms: Slope is zero, so the current must be zero.

**ECE 2210 / 00 Inductor Lecture Notes**

Fluid Model:

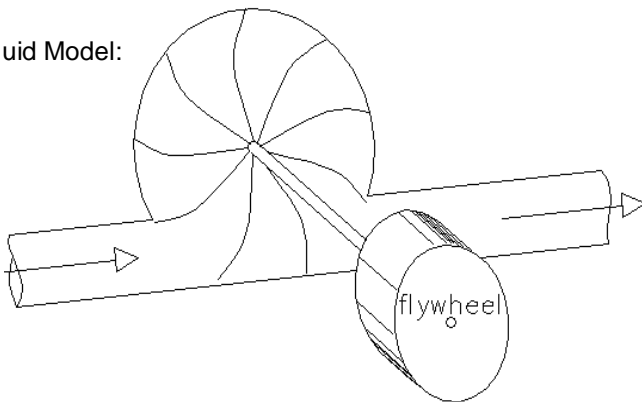

Basic equations you should know:

$$v_L = L \frac{d}{dt} i_L$$

Energy stored in electric field:  $W_L = \frac{1}{2} \cdot L \cdot I_L^2$


Inductor current **cannot** change instantaneously

Units: henry =  $\frac{\text{volt} \cdot \text{sec}}{\text{amp}}$

mH =  $10^{-3} \cdot \text{H}$

$\mu\text{H} = 10^{-6} \cdot \text{H}$

Electrical equivalent:

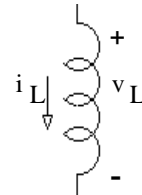

$$L = \mu_0 \cdot N^2 \cdot K$$

$\mu$  is the permeability of the inductor core

K is a constant which depends on the inductor geometry


N is the number of turns of wire

$$i_L = \frac{1}{L} \int_{-\infty}^t v_L dt$$


Or...  $i_L = \frac{1}{L} \int_0^t v_L dt + i_L(0)$  / initial current

Or...  $\Delta i_L = \frac{1}{L} \int_{t_1}^{t_2} v_L dt$

# ECE 2210 / 00 Capacitor / Inductor Lecture Notes p3
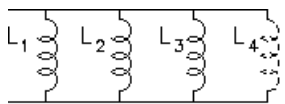
$$L_{eq} = \frac{1}{\frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} + \dots}$$

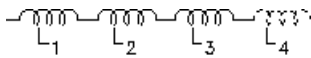
**series:**  $L_{eq} = L_1 + L_2 + L_3 + \dots$




**parallel:**

**Sinusoids**  $i_L(t) = I_p \cdot \cos(\omega \cdot t)$

$$v_L(t) = L \frac{d}{dt} i_L = L \cdot \omega \cdot (-I_p \cdot \sin(\omega \cdot t)) = L \cdot \omega \cdot I_p \cdot \cos(\omega \cdot t + 90\text{-deg})$$


$\underbrace{\quad}_{V_p}$

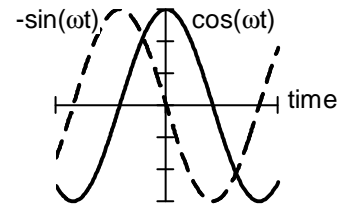Voltage "leads" current, makes sense, voltage has to present to make current change, so voltage comes first.




## Resonance

Series resonance

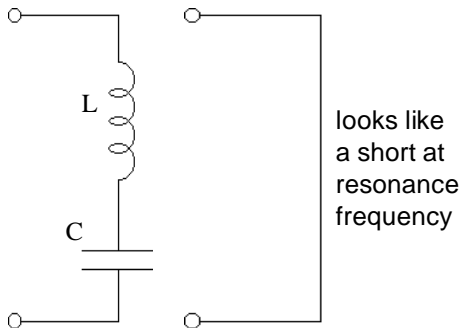

Parallel resonance

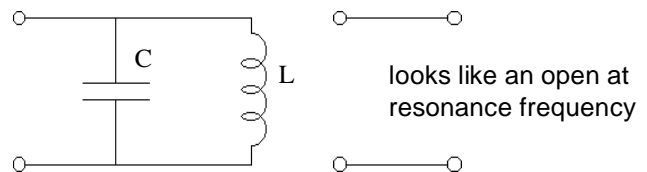

The resonance frequency is calculated the same way for either case:


$$\omega_o = \frac{1}{\sqrt{L \cdot C}} \left( \frac{\text{rad}}{\text{sec}} \right) \quad \text{OR..} \quad \omega_o = \frac{1}{\sqrt{L_{eq} \cdot C_{eq}}} \quad \text{If you have multiple capacitors or inductors which can be combined.} \quad f_o = \frac{\omega_o}{2 \cdot \pi} \text{ (Hz)}$$

## Steady-state of Final conditions

If a circuit has been connected for "a long time", then it has reached a steady state condition. that means the currents and voltages are no longer changing.

$$\frac{d}{dt} i_L = 0 \quad v_L = L \frac{d}{dt} i_L = 0$$


no voltage means it looks like a short

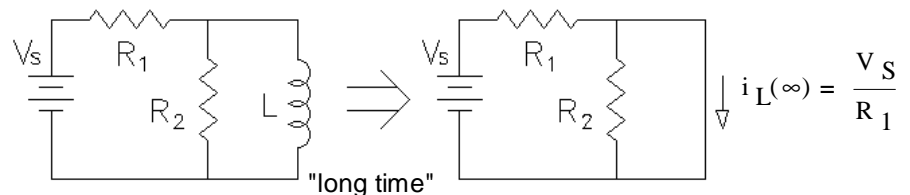

## Examples
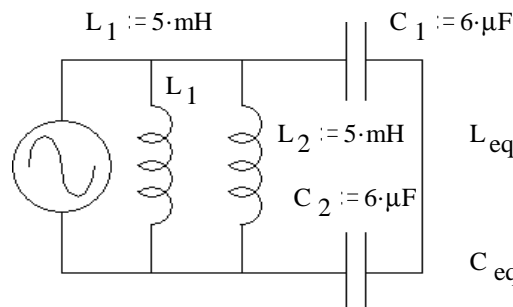
### Ex 1

Find the resonant frequency (or frequencies) of the circuit shown (in cycles/sec or Hz).



$$L_{eq} := \frac{1}{\frac{1}{L_1} + \frac{1}{L_2}} \quad L_{eq} = 2.5 \cdot \text{mH}$$

$$C_{eq} := \frac{1}{\frac{1}{C_1} + \frac{1}{C_2}} \quad C_{eq} = 3 \cdot \mu\text{F}$$


$$\omega_o := \frac{1}{\sqrt{L_{eq} \cdot C_{eq}}} \quad \omega_o = 11547 \cdot \frac{\text{rad}}{\text{sec}} \quad f_o = \frac{\omega_o}{2 \cdot \pi} = 1838 \cdot \text{Hz}$$

**Ex 2**

**ECE 2210 / 00 Capacitor / Inductor Lecture Notes p4**

The current through a 0.3mH inductor is shown below. Make an accurate drawing of the inductor voltage. Make reasonable assumptions where necessary. Label your graph.

$L := 0.3 \cdot \text{mH}$

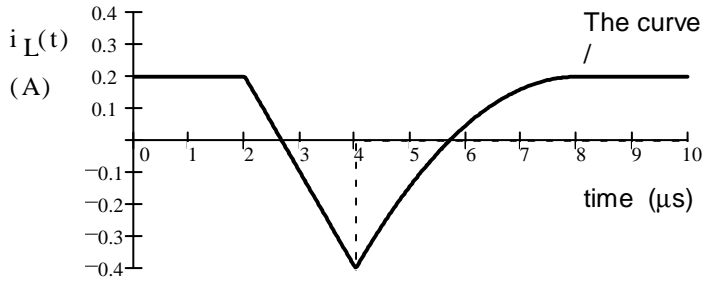


The curve is 2<sup>nd</sup> order and ends at 8μs

0 - 2μs: No change in current, so:  $v_L = 0$

$$2\mu\text{s} - 4\mu\text{s}: v_L = L \cdot \frac{\Delta I}{\Delta t} = 0.3 \cdot \text{mH} \cdot \frac{-0.6 \cdot \text{A}}{2 \cdot \mu\text{s}} = -90 \cdot \text{V}$$

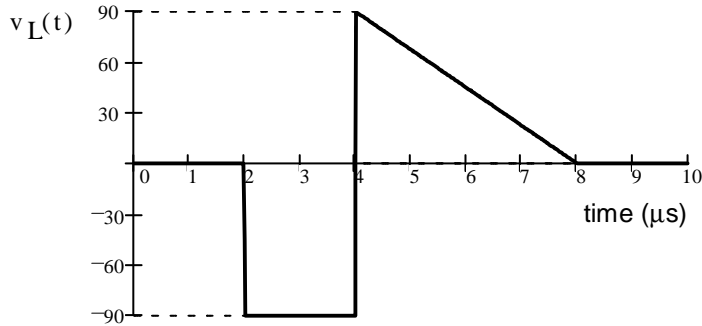4μs - 8μs: Initial slope is positive and the final slope is zero, so the voltage must be a triangle that starts at some height and ends at zero.



$$\Delta i_L(t) = \frac{1}{L} \int_0^t v_L(t) dt$$

$$0.6 \cdot \text{A} = \frac{1}{0.3 \cdot \text{mH}} \left( \frac{4 \cdot \mu\text{s} \cdot \text{height}}{2} \right)$$

$$\text{height} = 0.6 \cdot \text{A} \cdot \frac{0.3 \cdot \text{mH} \cdot 2}{4 \cdot \mu\text{s}} = 90 \cdot \text{V}$$

8μs - 10μs: No change in current, so:  $v_L = 0$


**Ex 3** Given a voltage, find the current,  $L := 4 \cdot \text{mH}$

$$\Delta i_L(t) = \frac{1}{L} \int_{1 \cdot \mu\text{s}}^{2 \cdot \mu\text{s}} 20 \cdot \text{V} dt = 5 \cdot \text{mA}$$


$$\frac{1}{L} \int_{4 \cdot \mu\text{s}}^{8 \cdot \mu\text{s}} -10 \cdot \text{V} dt + 5 \cdot \text{mA} = -5 \cdot \text{mA}$$

$$\frac{1}{L} \int_{8 \cdot \mu\text{s}}^{10 \cdot \mu\text{s}} V(t) dt + -5 \cdot \text{mA}$$

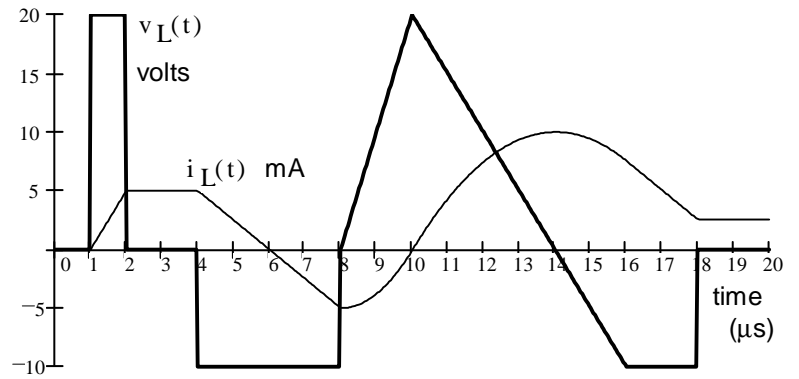
$$= \frac{1}{L} \cdot \frac{20 \cdot \text{V} \cdot 2 \cdot \mu\text{s}}{2} - 5 \cdot \text{mA} = 0 \cdot \text{mA} \quad \text{etc...}$$



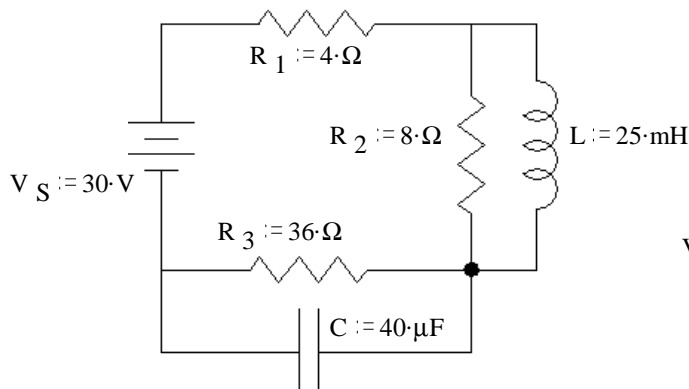**Ex 4** The following circuit has been connected as shown for a long time. Find the energy stored in the capacitor and the inductor.



Redraw:

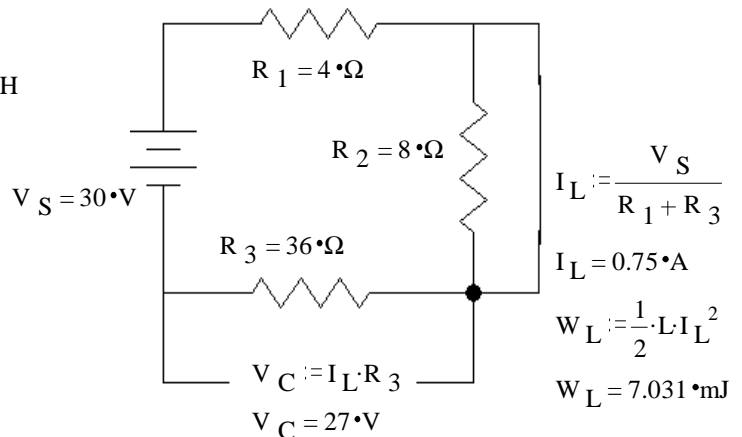

$$I_L := \frac{V_S}{R_1 + R_3}$$

$$I_L = 0.75 \cdot \text{A}$$

$$W_L := \frac{1}{2} \cdot L \cdot I_L^2$$

$$W_L = 7.031 \cdot \text{mJ}$$

$$V_C := I_L \cdot R_3$$

$$V_C = 27 \cdot \text{V}$$

**ECE 2210 / 00 Capacitor / Inductor Lecture Notes p4**

$$W_C := \frac{1}{2} \cdot C \cdot V_C^2$$

$$W_C = 14.58 \cdot \text{mJ}$$

# Capacitor, Inductor Notes

ECE 2210 / 00


A.Stolp  
2/27/00,  
9/13/05

## Capacitors


$$C = \frac{Q}{V} \quad \text{farad} = \frac{\text{coul}}{\text{volt}} = \frac{\text{amp}\cdot\text{sec}}{\text{volt}} \quad v_C = \frac{1}{C} \int_{-\infty}^t i_C dt + v_C(0) \quad \text{initial voltage} \quad i_C = C \frac{d}{dt} v_C$$

Energy stored in electric field:  $W_C = \frac{1}{2} C \cdot V_C^2$  Capacitor voltage **cannot** change instantaneously

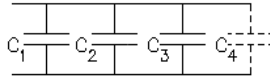parallel:  $C_{eq} = C_1 + C_2 + C_3 + \dots$



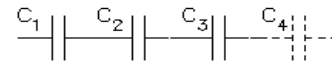series:  $C_{eq} = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots}$



Steady-state sinusoids:


Impedance:  $Z_C = \frac{1}{j \cdot \omega \cdot C} = \frac{-j}{\omega \cdot C}$  Current leads voltage by 90 deg

## Inductors


$$\text{henry} = \frac{\text{volt}\cdot\text{sec}}{\text{amp}} \quad i_L = \frac{1}{L} \int_{-\infty}^t v_L dt + i_L(0) \quad \text{initial current} \quad v_L = L \frac{d}{dt} i_L$$

Energy stored in magnetic field:  $W_L = \frac{1}{2} L \cdot I_L^2$  Inductor current **cannot** change instantaneously

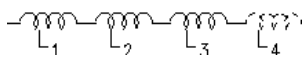series:  $L_{eq} = L_1 + L_2 + L_3 + \dots$



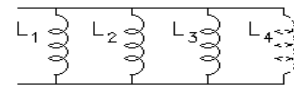parallel:  $L_{eq} = \frac{1}{\frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} + \dots}$



Steady-state sinusoids:

Impedance:  $Z_L = j \cdot \omega \cdot L$  Current lags voltage by 90 deg

## RC and RL first-order transient circuits

For all first order transients:  $v_X(t) = v_X(\infty) + (v_X(0) - v_X(\infty)) \cdot e^{-\frac{t}{\tau}}$   $i_X(t) = i_X(\infty) + (i_X(0) - i_X(\infty)) \cdot e^{-\frac{t}{\tau}}$




**Find initial Conditions** ( $v_C$  and/or  $i_L$ )

Find conditions just before time  $t = 0$ ,  $v_C(0^-)$  and  $i_L(0^-)$ . These will be the same just after time  $t = 0$ ,  $v_C(0^+)$  and  $i_L(0^+)$  and will be your initial conditions. (If initial conditions are zero: Capacitors are shorts, Inductors are opens.) Use normal circuit analysis to find your desired variable:  $v_X(0)$  or  $i_X(0)$




**Find final conditions** ("steady-state" or "forced" solution)

Inductors are shorts Capacitors are opens Solve by DC analysis  $v_X(\infty)$  or  $i_X(\infty)$

RC Time constant  $= \tau = RC$

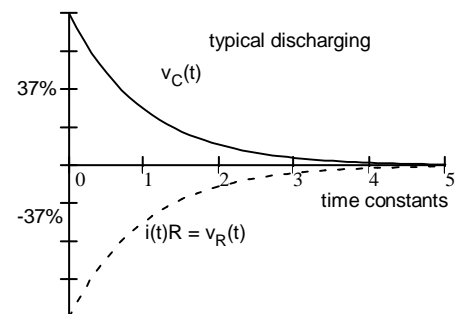
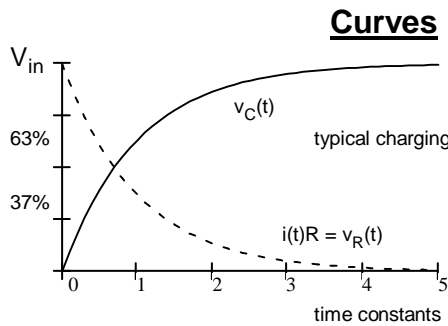
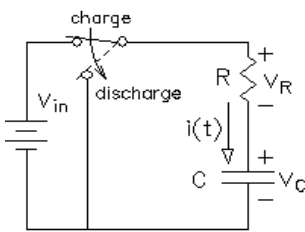


RL Time constant  $= \tau = \frac{L}{R}$

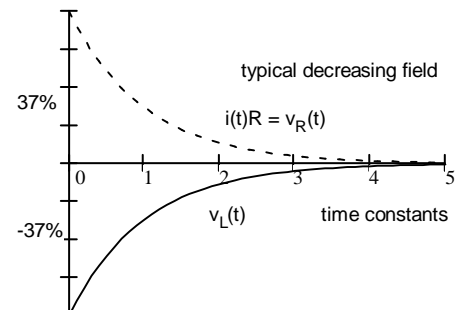
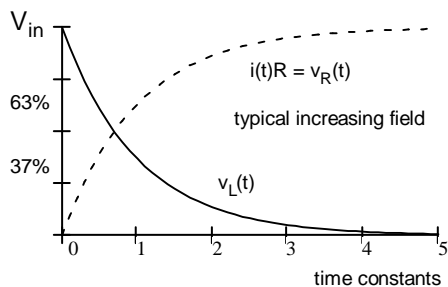
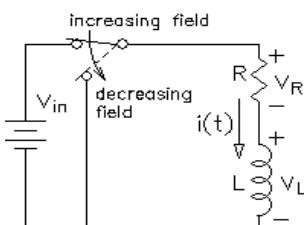




1) Find  $C_{eq}$  in each case

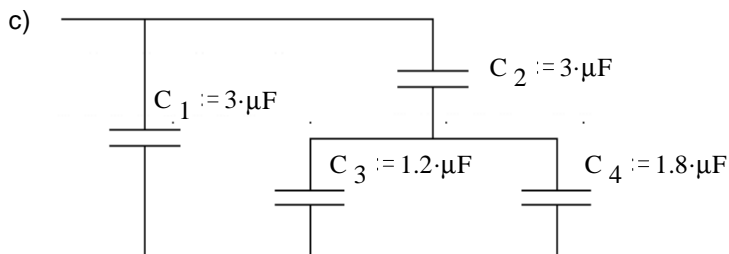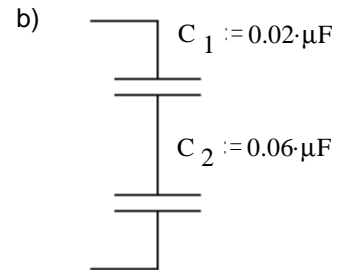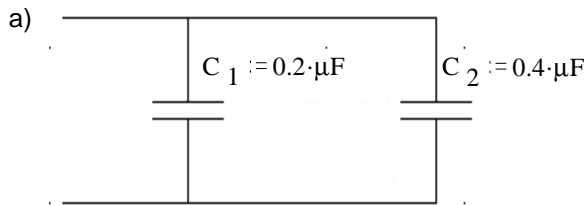

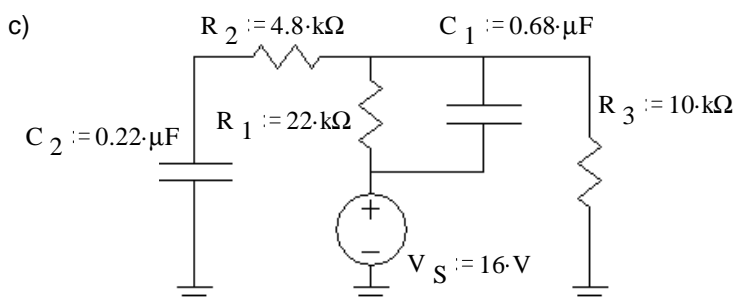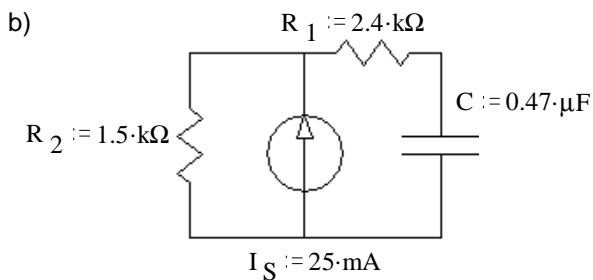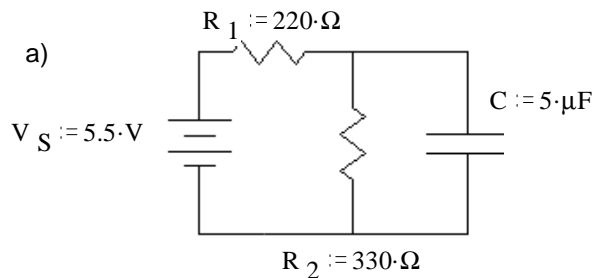
2. Each of the following circuits have been connected as shown for a long time. Find the voltage across each capacitor and the energy stored in each.




## ECE 2210 / 00 homework # 8

Name: \_\_\_\_\_ You may want to hand in this page with answers to problems 3 & 4.

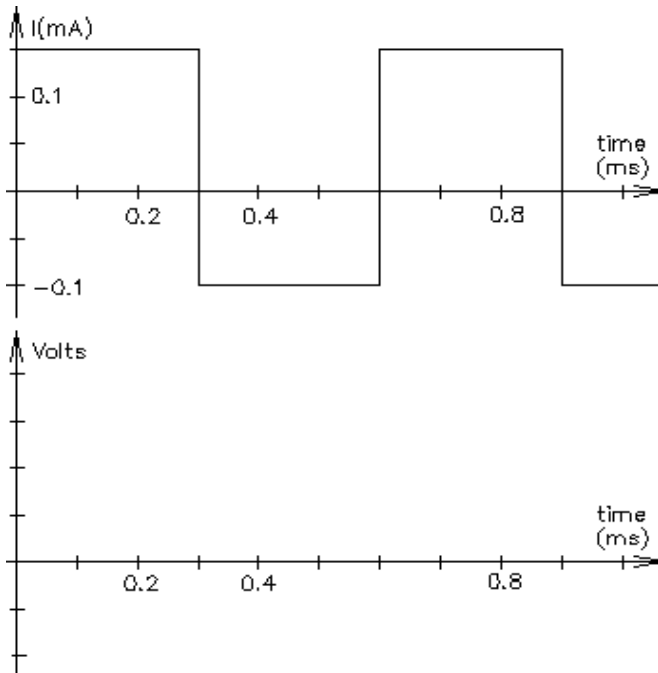3. The current waveform shown below flows through a  $0.025 \mu\text{F}$  capacitor. Make an accurate drawing of the voltage across it. Label your graph. Assume the initial voltage across the capacitor is  $0 \text{ V}$ .



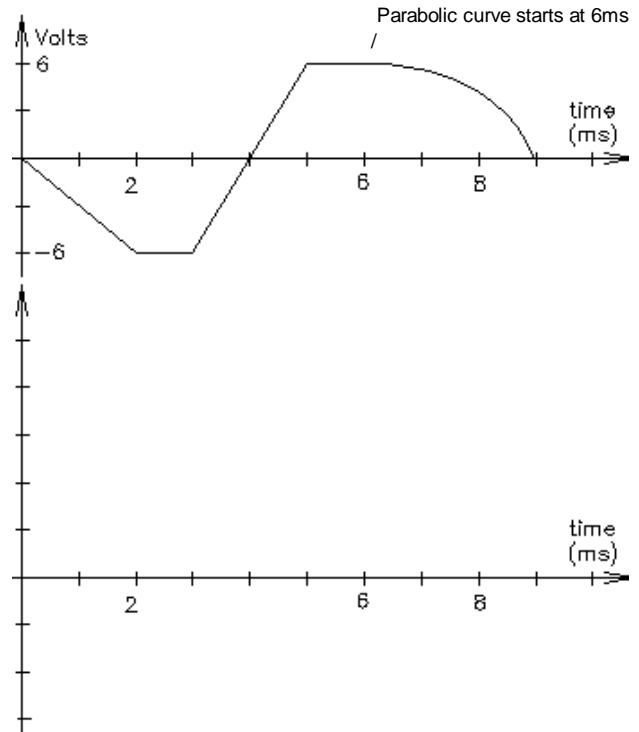
4. The voltage across a  $2 \mu\text{F}$  capacitor is shown below. Make an accurate drawing of the capacitor current. Label your graph.



5. The voltage across a  $0.68 \mu\text{F}$  capacitor is  $v_c = 6 \cdot \text{V} \cdot \cos\left(200 \cdot t + \frac{\pi}{2}\right)$  find  $i_c$ .

6. The current through a  $0.0047 \mu\text{F}$  capacitor is  $i_c = 18 \cdot \mu\text{A} \cdot \cos\left(628 \cdot t - \frac{\pi}{4}\right)$  find  $v_c$ .

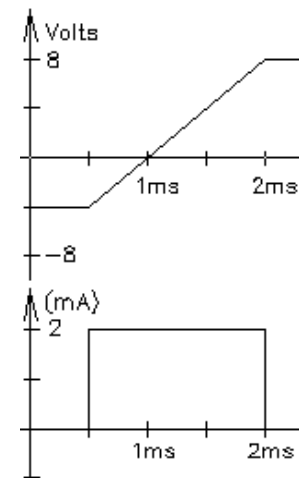7. A capacitor voltage and current are shown at right. What value is the capacitor?



### Answers

1. a)  $0.6 \mu\text{F}$     b)  $0.015 \mu\text{F}$     c)  $4.5 \mu\text{F}$   
 2. a)  $3.3 \text{ V}$   $0.027 \text{ mJ}$     b)  $37.5 \text{ V}$   $0.33 \text{ mJ}$     c)  $11 \text{ V}$   $0.0411 \text{ mJ}$      $5 \text{ V}$      $2.75 \mu\text{J}$   
 3.  $1.8 \text{ V}$   $0.6 \text{ V}$   $2.4 \text{ V}$     4.  $-6 \text{ mA}$   $12 \text{ mA}$     ramp to  $-8 \text{ mA}$   
 5.  $i_c = 0.816 \text{ mA} \cdot \cos(200 \cdot t + \pi)$     6.  $v_c = 6.1 \cdot \text{V} \cdot \cos\left(628 \cdot t - \frac{3 \cdot \pi}{4}\right)$     7.  $0.25 \mu\text{F}$





Name: \_\_\_\_\_

Due: Fri, 2/18/22



ECE 2210 / 00 hw # 9

You will need another paper for your calculations, but you may want to hand this sheet in with your drawings.



1. Find  $L_{eq}$  in each case

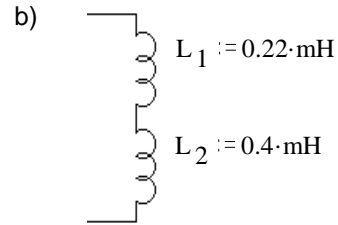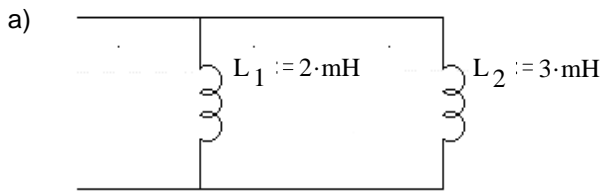

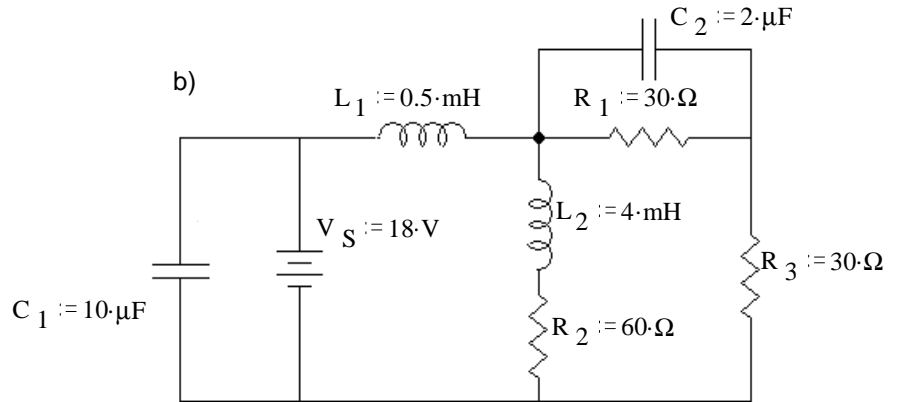
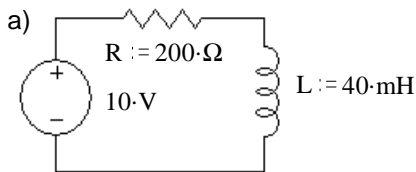
2. Find the stored energy in each capacitor and/or inductor under steady-state conditions. Note: Treat caps as opens and inductors as shorts to find DC voltages and currents.



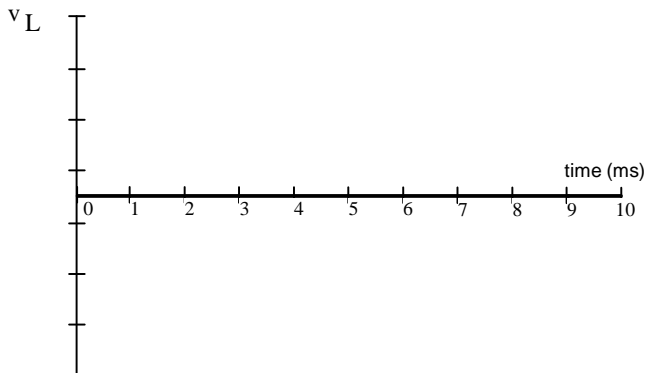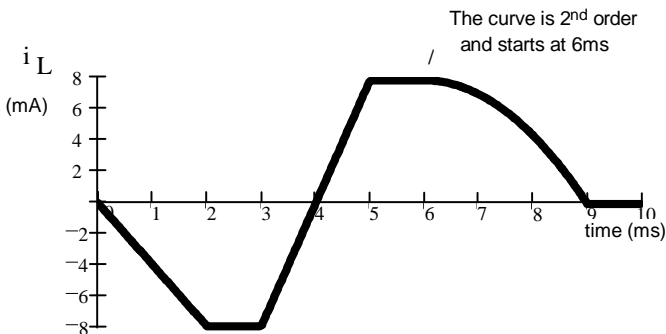3. The current waveform shown below flows through a 2 mH inductor. Make an accurate drawing of the voltage across it. Label your graph.



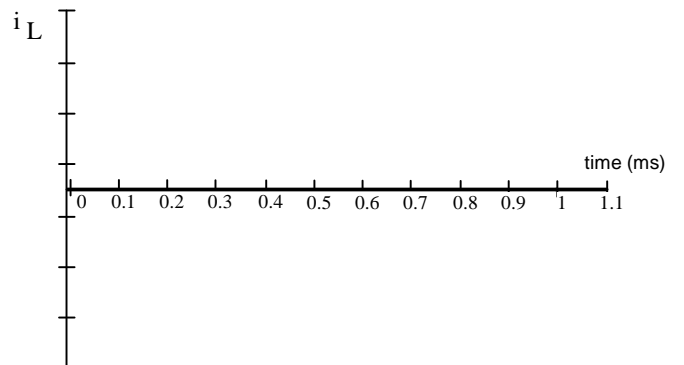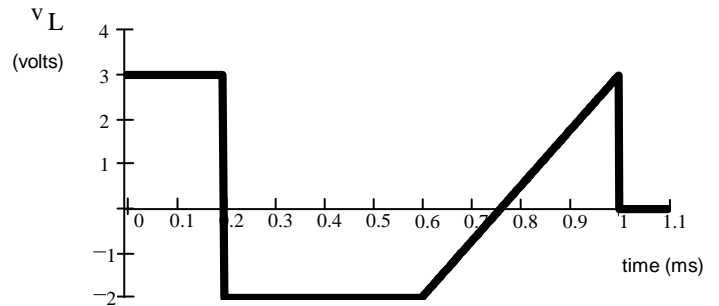4. The voltage across a 0.5 mH inductor is shown below. Make an accurate drawing of the inductor current. Label your graph. Assume the initial current is 0 mA.



## ECE 2210 / 00 homework # 9


5. The voltage across a 1.2 mH inductor is  $v_L = 4 \cdot \text{mV} \cdot \cos(300 \cdot t)$  find  $i_L$ .

6. The current through a 0.08 mH inductor is  $i_L = 20 \cdot \text{mA} \cdot \cos\left(628 \cdot t - \frac{\pi}{4}\right)$  find  $v_L$ .


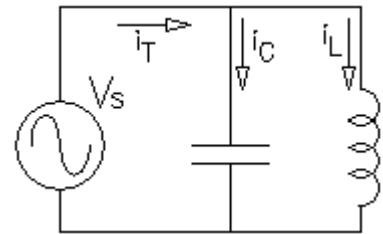
7. Refer to the circuit shown. Assume that  $V_s$  is a sinusoidal input voltage whose frequency can be adjusted. At some frequency of  $V_s$  this circuit can resonate. At that frequency  $i_C(t) = -i_L(t)$ . ( $i_C(t)$  is 180 degrees out-of-phase with  $i_L(t)$ ).

Show that resonance occurs at this frequency:

$$\omega_o = \frac{1}{\sqrt{L \cdot C}}, \quad f_o = \frac{1}{2 \cdot \pi \cdot \sqrt{L \cdot C}}$$



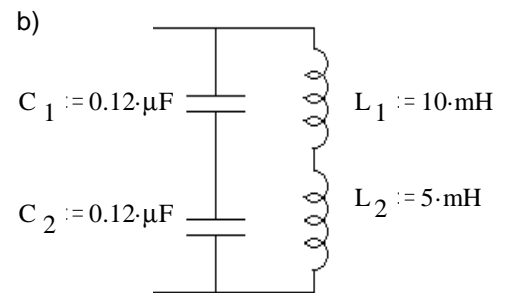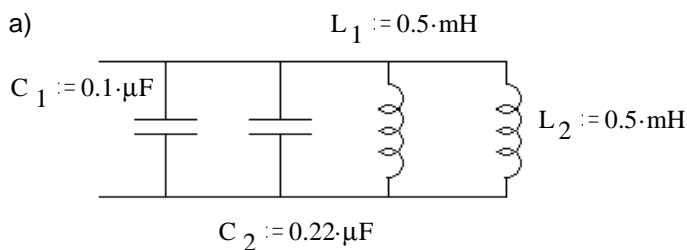8. Find the resonant frequency,  $f_o$  in each case.



### Answers

1. 1.2·mH    0.62·mH                      2. a) 0.05·mJ            b) 1.62·mJ    0.081·mJ    0.09·mJ    0.18·mJ

3. Straight lines between the following points: (0ms,-8mV), (2ms,-8mV), (2ms,0mV), (3ms,0mV), (3ms,16mV), (5ms,16mV), (5ms,0mV), (6ms,0mV), (9ms,-10.67mV), (9ms,0mV), (10ms,0mV)

4. Straight lines between the following points: (0ms,0A), (0.2ms,1.2A), (0.6ms,-0.4A), curves until it's flat at (0.76ms, -0.72A), continues to curve up to (1ms, 0A), (1.1ms,0A)

5.  $i_L = 11.1 \cdot \text{mA} \cdot \cos(300 \cdot t - 90\text{-deg})$                       6.  $v_L = 1 \cdot \text{mV} \cdot \cos\left(628 \cdot t + \frac{1}{4} \cdot \pi\right)$

7. Assume a sinusoidal voltage, find  $i_C$  and  $i_L$  by integration and differentiation, and show that they are equal and opposite at the resonant frequency.

8. a) 17.79·kHz            b) 5305·Hz