
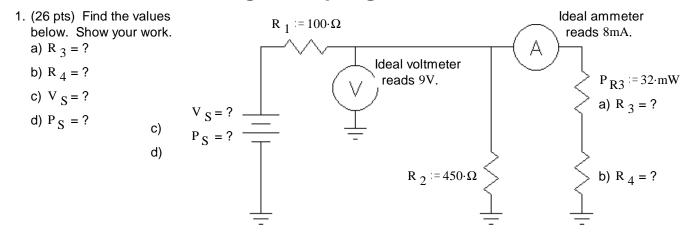
ECE 2210/00 Exam 1 given: Spring 13 (The space between problems has been removed.)




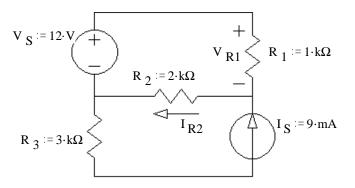2. (25 pts) Use the method of superposition to find I_{R2} and $V_{R1}.$

Be sure to redraw the circuit as needed and to clearly show and **circle** your intermediate results.




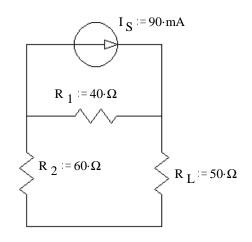
- 3. (20 pts) a) Find and draw the Thévenin equivalent of the circuit shown. The load resistor is $R_{\rm L}$.
 - b) Find and draw the Norton equivalent of the same circuit.




ECE 2210/00 Exam 1 Spring 13 p2

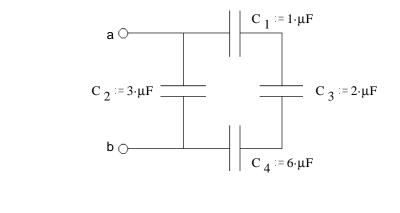4. (7 pts) Find C_{eq} between terminals a and b.



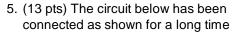

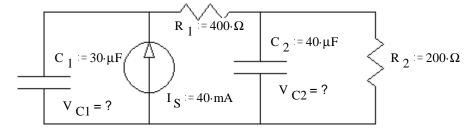- a) Find the voltage across each capacitor.
- b) How much energy is stored in capacitor C_2 .



The questions below are similar to what you might see on the FE exam. They expect you to average about 2 minutes per question.

6. (5 pts)

In the circuit shown, the power loss in R_2 is 0.6 W and the power loss in R_3 is 0.3 W. What is the value of the resistor, R_3 ?

a) 100 Ω b) 141 Ω c) 283 Ω d) 400 Ω

7. (4 pts)

In the circuit above, what is output power of the battery? a) 0.6 W b) 0.9 W c) 1.2 W d) 1.5 W

c) 11 8.V


d) 0.33.W

<u>Answers</u>

1. a) 500-32	0) 025.32	C) 11.0 V	u) 0.55 W
2. 7·mA	- 2·V		
3. a)	100· Ω	b)	c) 1.2·V
3.6·V		36·mA	ο
4. 3.6·µF	5. a) 24.	V 8.V	b) 1.28·mJ
6 a) 7. d)			

h) 625.0

ECE 2210/00 Exam 1 Spring 13 p2

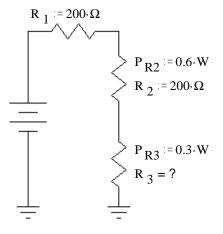

Folder Number _

ECE 2210 / 00	Midterm #1 Arn Stolp		
Name Scores:			
Prob 1	of a possible 26 pts		
Prob 2	of a possible 25 pts		
Prob 3	of a possible 20 pts		
Probs 4&5	of a possible 20 pts		
	of a possible 9 pts of a possible 100 pts		