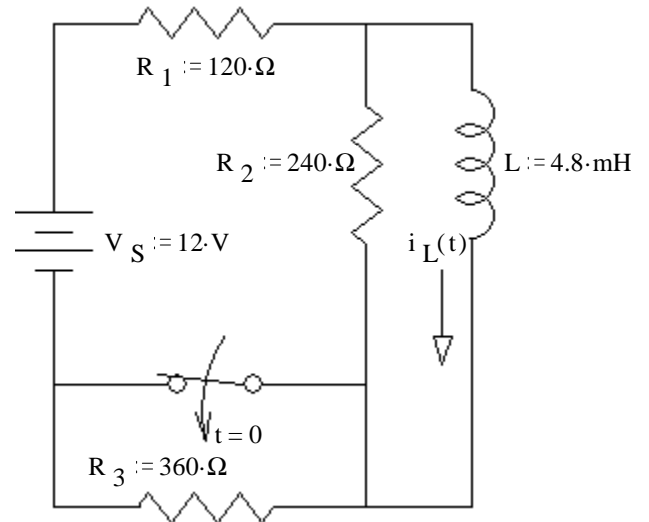


ECE 2210/00 Exam 2 given: Fall 20

(Some space between problems has been removed.)

1. (33 pts) The switch has been open for a long time and is closed (as shown) at time $t = 0$.

a) Find the complete expression for $i_L(t)$.




b) Find i_L at time $t = 1.2\tau$. $i_L(1.2\tau) = ?$

c) At time $t = 1.2\tau$ the switch is opened again. Find the complete expression for $i_L(t')$, where t' starts at $t = 1.2\tau$. Be sure to clearly show the time constant.

ECE 2210/00 Exam 2 Fall 20 p2

Problems are out-of-order

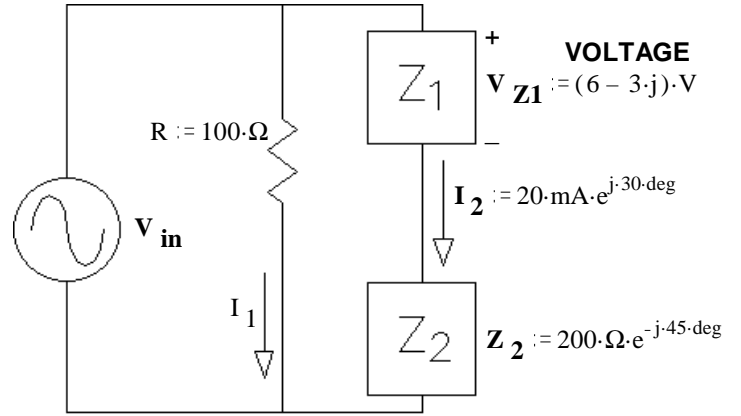
3. (30 pts) For partial credit, you must show work and/or intermediate results.
 a) Find Z_1



- b) Find V_s

- c) Find I_1 in polar form.

- Answers**
- | | |
|--|---|
| 1. a) $100 \cdot \text{mA} - 75 \cdot \text{mA} \cdot e^{\frac{-t}{60 \cdot \mu\text{s}}}$ | c) $25 \cdot \text{mA} + 52.4 \cdot \text{mA} \cdot e^{\frac{-t'}{30 \cdot \mu\text{s}}}$ |
| b) $77.4 \cdot \text{mA}$ | |
| 2. $1300 \Omega \angle -67.38^\circ$ | 3. a) $184.8 - 279.9 \cdot j \Omega = 335.4 \angle -56.6^\circ \Omega$ |
| | b) $3.864 - 1.035 \cdot j \text{ V} = 4 \text{ V} \angle -15^\circ \text{ V}$ |
| ECE 2210/00 Exam 2 Fall 20 p2 | c) $106.6 \angle -22.25^\circ \text{ mA}$ |

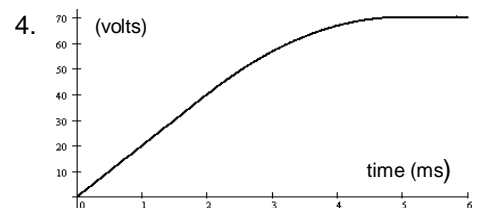


ECE 2210/00 Exam 2 Fall 20 p3

2. (20 pts) Z_{eq} is the total impedance between the two terminals.

Find Z_{eq} in simple **polar form** (give me numbers).

For partial credit, you must show work and/or intermediate results.

$f := 3183.1 \cdot \text{Hz}$

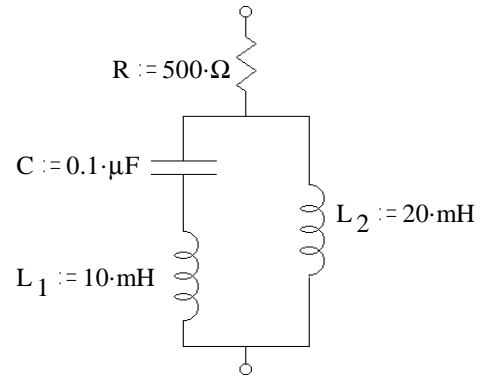


4. (17 pts) The graph below shows the current through a $20 \mu\text{F}$ capacitor. Make an accurate drawing of the capacitor voltage. Make reasonable assumptions where necessary. $v_c(0) = 0$. Label your graph (numbers).

Note: You will be graded on the accuracy of your plot at 0, 2, 5, and 6 ms, so calculate those values and plot them carefully. Between those points your plot must simply be the correct shape.

You **MUST SHOW** how you calculate your values starting from the original relationships between voltage and current.

That is: **Start** with the **interger** and/or **differential** equations for the capacitor!

capacitor current (A)

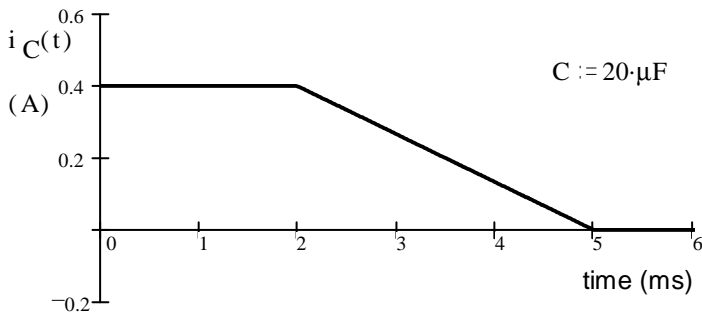

capacitor voltage (volts)

