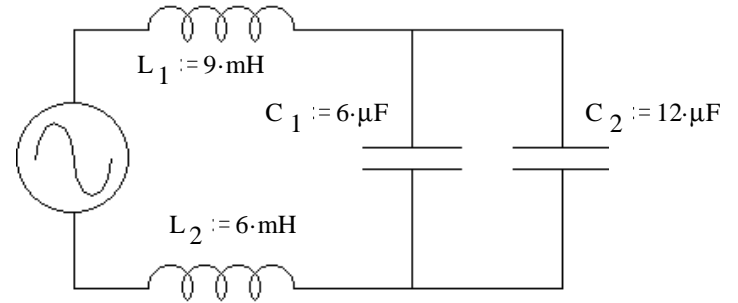



# ECE 2210/00 Exam 2 given: Fall 21

1. (9 pts) Find the resonant frequency (or frequencies) of the circuit shown (in cycles/sec or Hz).



2. (28 pts) The switch has been open (not making contact) for a long time and is switched closed (as shown) at time  $t = 0$ .

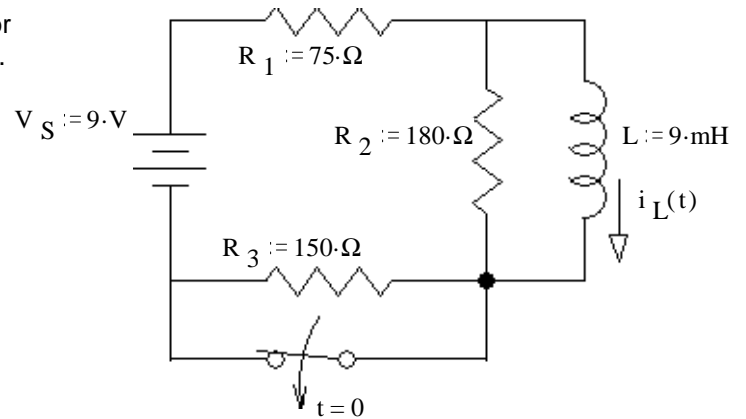- a) Find the complete expression for  $i_L(t)$ .




- b) Find  $i_L$  at time  $t = 1.2\tau$ .  $i_L(1.2\tau) = ?$

- c) At time  $t = 1.2\tau$  the switch is opened again. Will the time constant be different now? If yes, find the new time constant.


**ECE 2210/00 Exam 2 Fall 21 p2**

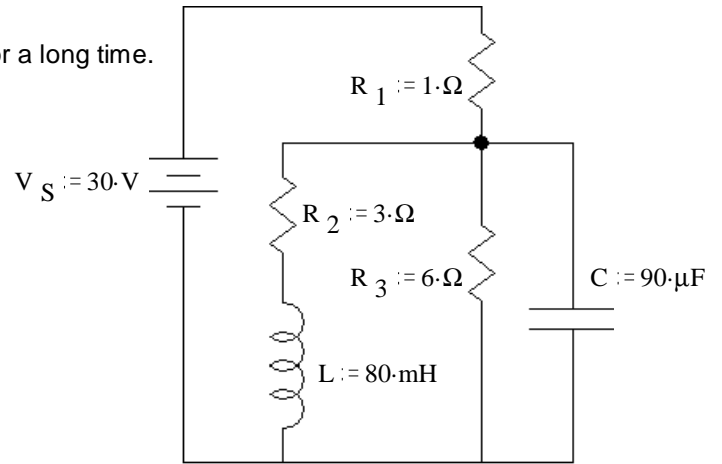3. (15 pts) The following circuit has been connected as shown for a long time.  
 Find the energy stored in the capacitor and the inductor.  
 Also show the values of the voltage(s) and current(s) necessary to answer this question.



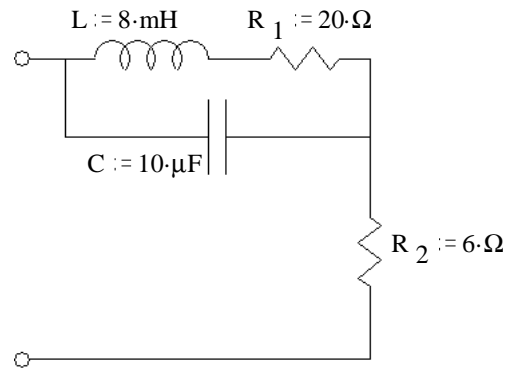
4. (20 pts)  $Z_{eq}$  is the total impedance between the two terminals.  
 Find  $Z_{eq}$  in polar form (give me numbers).  
 You must show work and/or intermediate results.

$f := 795.78 \cdot \text{Hz}$        $Z_{eq} = ?$



5. (28 pts) Find  $I_{Z1}$ ,  $I_{Z2}$  &  $Z_2$ .

a) Find  $I_{Z1}$  in any form.

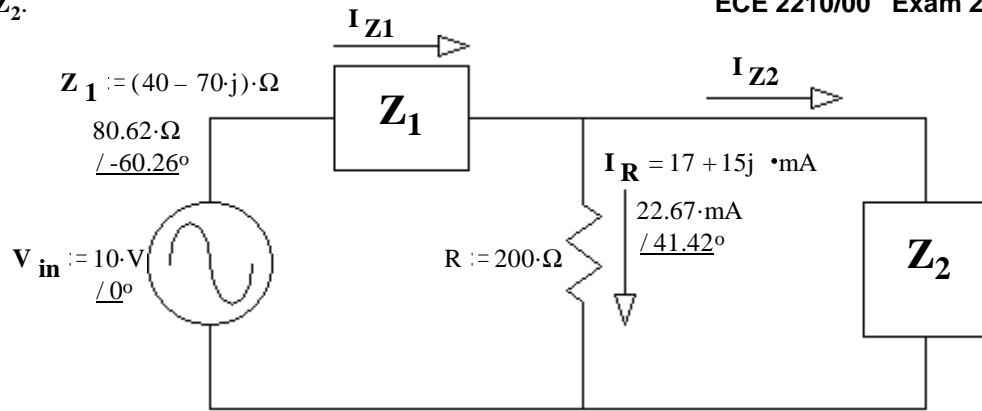

b) Find  $I_{Z2}$  in any form.

c) Find  $Z_2$  in polar form.

### Answers

1. 306·Hz      2. a)  $120 \cdot mA - 80 \cdot mA \cdot e^{-\frac{t}{0.17 \cdot ms}}$       b) 95.9·mA      c) 90·μs

3. 18·mJ    1.78·J    4.  $34 \Omega \underline{-61.9^\circ}$   
 5. a)  $(72.92 + 52.62j) \cdot mA$     b)  $(55.92 + 37.62j) \cdot mA = 67.4mA \underline{33.93^\circ}$     c)  $67.3 \cdot \Omega \underline{7.49^\circ}$     **ECE 2210/00 E2 F21 p3**