

ECE 2210 / 00

Exam 2

Useful Information

$$C = \frac{Q}{V}$$

$$\text{farad} = \frac{\text{coul}}{\text{volt}} = \frac{\text{amp}\cdot\text{sec}}{\text{volt}}$$

$$v_C = \frac{1}{C} \int_{-\infty}^t i_C dt = \frac{1}{C} \int_0^t i_C dt + v_C(0)^{\text{initial voltage}}$$

$$\Delta v_C = \frac{1}{C} \int_{t_1}^{t_2} i_C dt$$

parallel: $C_{\text{eq}} = C_1 + C_2 + C_3 + \dots$

series: $C_{\text{eq}} = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots}$

$$W_C = \frac{1}{2} \cdot C \cdot V_C^2$$

Capacitor voltage **cannot** change instantaneously

$$\text{henry} = \frac{\text{volt}\cdot\text{sec}}{\text{amp}}$$

$$i_L = \frac{1}{L} \int_{-\infty}^t v_L dt = \frac{1}{L} \int_0^t v_L dt + i_L(0)^{\text{initial current}}$$


$$\Delta i_L = \frac{1}{L} \int_{t_1}^{t_2} v_L dt$$

$$W_L = \frac{1}{2} \cdot L \cdot I_L^2$$


$$v_L = L \frac{d}{dt} i_L$$

Inductor current **cannot** change instantaneously

Final Conditions:

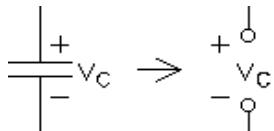

Replace capacitors with opens

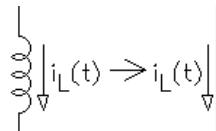

Replace inductors with wires

For all first order transients: $x(t) = x(\infty) + (x(0) - x(\infty)) \cdot e^{-\frac{t}{\tau}}$

$$\tau = R_{\text{Th}} C$$

OR $\frac{L}{R_{\text{Th}}}$

Resonance: $\omega_0 = \frac{1}{\sqrt{L_{\text{eq}} \cdot C_{\text{eq}}}}$

Steady-state sinusoidal AC Impedances: $Z_C = \frac{1}{j \cdot \omega \cdot C} = \frac{-j}{\omega \cdot C}$ $Z_L = j \cdot \omega \cdot L$ $\omega = 2 \cdot \pi \cdot f$

$$A = |A| = \sqrt{a^2 + b^2}$$

$$\theta = \arg(A) = \arctan\left(\frac{b}{a}\right)$$

$$a = A \cdot \cos(\theta)$$

$$b = A \cdot \sin(\theta)$$