

ECE 2210/00 Exam 2 given: Spring 11 (The space between problems has been removed.)

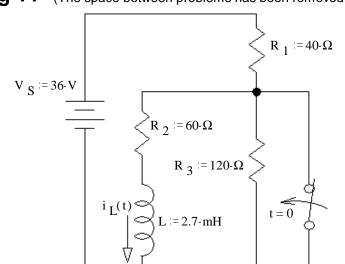- 1. (35 pts) The switch has been open for a long time and is closed (as shown) at time t = 0.
 - a) Find the complete expression for $i_{I}(t)$.
 - b) Find i_L at time $t = 1.2\tau$. $i_L(1.2\cdot\tau) = ?$
 - c) At time $t = 1.2\tau$ the switch is opened again. Find the complete expression for $i_{L}(t')$, where t' starts at $t = 1.2\tau$. Be sure to clearly show the time constant.



- $I_2 = 40 \cdot \text{mA} \cdot e^{-j \cdot 20 \cdot \text{deg}}$ 2. (25 pts) For partial credit, you must I_T show work and/or intermediate results. a) Find V_s in polar form. $R := 30 \cdot \Omega$ $I_1 = (30 - 20 \cdot j) \cdot mA$ b) Find I_T v_s = 36.06mA / -33.7° $\mathbf{Z}_{2} := (50 + 100 \cdot \mathbf{j}) \cdot \Omega$ Z2 *L*1 c) Find Z₁
 - d) Circle 1: i) I_1 lags I_2 ii) I_1 leads I_2
 - e) By how much? I.E. what is the phase angle between I_1 and I_2 ?
- 3. (21 pts) Find \mathbf{Z}_{eq} in simple polar form (give me numbers & units). f = 318.31 · Hz

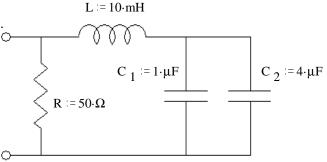

ECE 2210/00 Exam 2 Spring 11 p2

4. 19 pts) The voltage across a capacitor is shown below. Make an accurate drawing of the capacitor current. Make reasonable assumptions where necessary. Label your graph.

Note: You will be graded on the accuracy of your plot at 0, 0.05, 0.06 and 0.08 sec, so calculate those values and plot or label them carefully. Between those points your plot must simply be the correct shape.

You **MUST SHOW** how you calculate your values starting from the original relationships between voltage and current.

That is: Start with the interger and/or differential equations for the capacitor!

