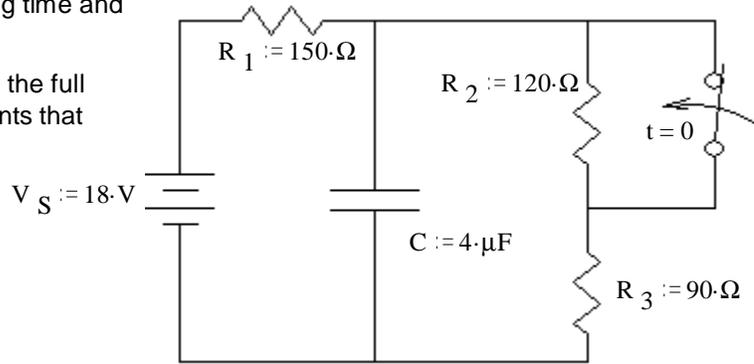


ECE 2210/00 Exam 2 given: Fall 12

(The space between problems has been removed.)

1. (32 pts) a) The switch has been open for a long time and is closed (as shown) at time $t = 0$.

a) Find the initial and final conditions and write the full expression for $v_C(t)$, including all the constants that you find.




b) What is v_C when $t = 1.2\tau$? $v_C(1.2\tau) = ?$

c) At time $t = 1.2\tau$ the switch is opened again. Find the complete expression for $v_C(t')$, where t' starts when the switch opens. Be sure to clearly show the time constant.

2. (20 pts) Find Z_{eq} in simple polar form (give me numbers).


For partial credit, you must show work and/or intermediate results.

$$f = 159.155 \cdot \text{Hz}$$

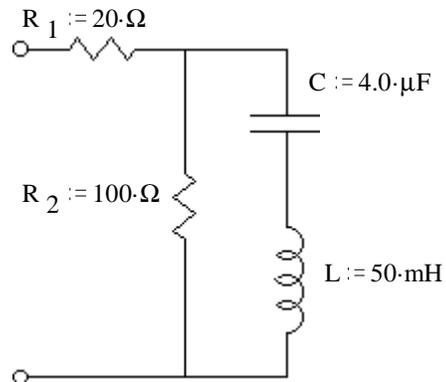

3. (28 pts)

a) Find V_{in} in polar form.

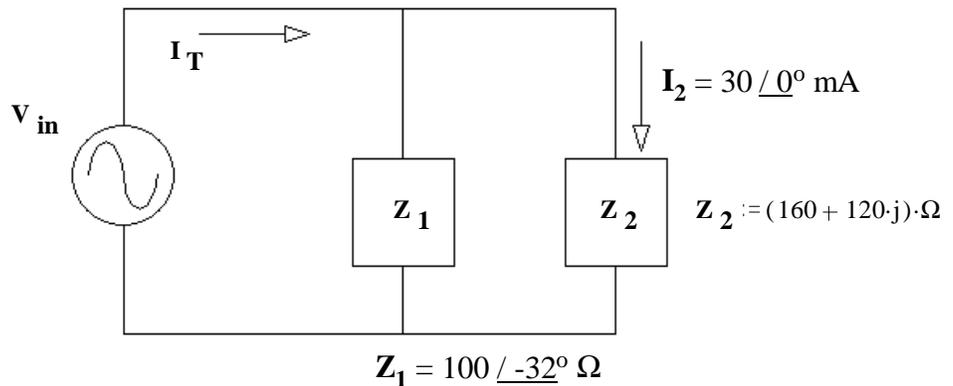

b) Find I_T .



c) Circle 1: i) The source current leads the source voltage ii) The source voltage leads the source current

d) By how much? I.E. what is the phase angle between the voltage and current? **ECE 2210/00 Exam 2 Fall 12 p1**

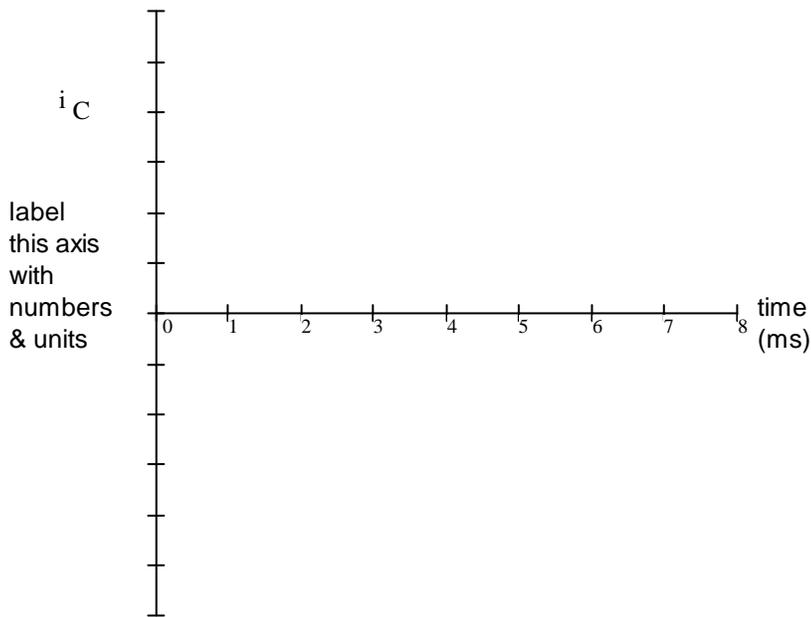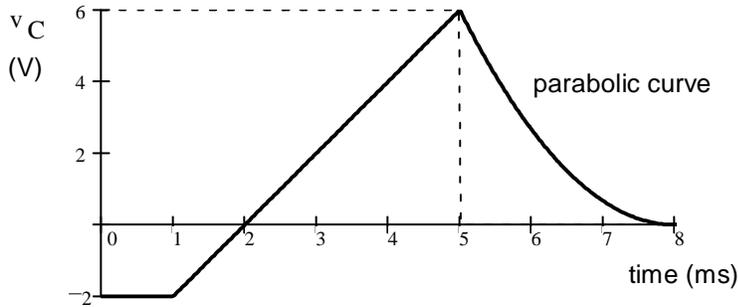4. 20 pts) The voltage across a capacitor is shown below. Make an accurate drawing of the capacitor current. Make reasonable assumptions where necessary. Label your graph.

Note: You will be graded on the accuracy of your plot at 0, 1, 5 and 8 ms, so calculate those values and plot or label them carefully. Between those points your plot must simply be the correct shape.

You **MUST SHOW** how you calculate your values starting from the original relationships between voltage and current. That is: **Start with the interger and/or differential equations for the capacitor!**



Answers

1. a) $6.75 \cdot V + 3.75 \cdot V \cdot e^{-\frac{t}{225 \cdot \mu s}}$ b) 7.88 · V

c) $10.5 \cdot V - 2.62 \cdot V \cdot e^{-\frac{t'}{350 \cdot \mu s}}$

2. $108 \Omega / -21.8^\circ$

3. a) $6 V / 36.9^\circ$ b) $76.1 \text{mA} / 47.3^\circ$

c) i) d) 10.4 · deg

