

ECE 2210 Exam 3 given: Fall 21


1. (26 pts) a) Draw the asymptotic Bode plot (the straight-line approximation) of the transfer function below.

Accurately draw it on the graph provided.

You **must** show and use the method from the class notes to get the Bode plot. That is, show things like the corner frequency(ies), the approximations of the transfer function in each frequency region, calculations of dB, etc..

$$H(f) := \frac{10 \cdot (10 \cdot \text{Hz} + j \cdot f)}{(400 \cdot \text{Hz} + j \cdot f) \cdot \left(1 + \frac{0.00002}{\text{Hz}} \cdot j \cdot f\right)}$$

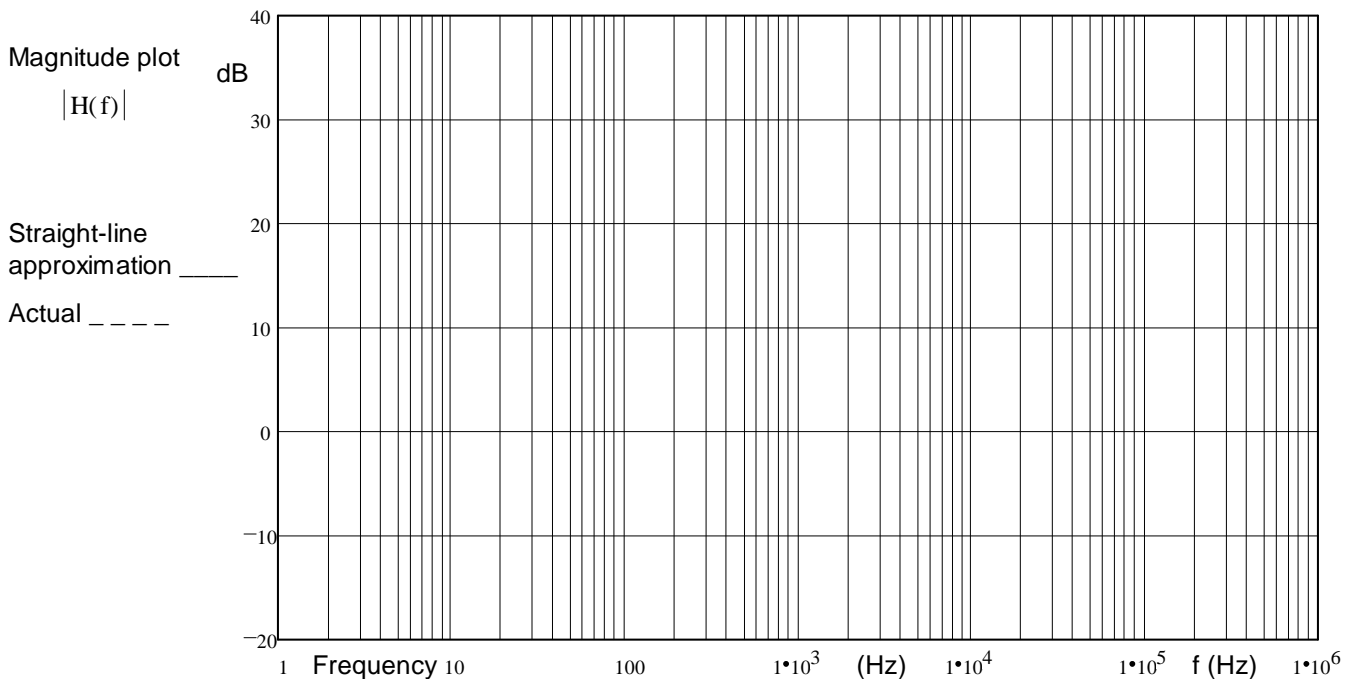
Indicate which corner frequency(ies) are **poles** and/or **zeroes**.



b) The asymptotic Bode plot is not exact. Using a dotted line, sketch the actual magnitude of the transfer function $|H(f)|$ on the plot above. Indicate the point(s) where the difference between the two lines is the biggest (draw arrow(s)) and write down the actual magnitude(s) at that (those) point(s).

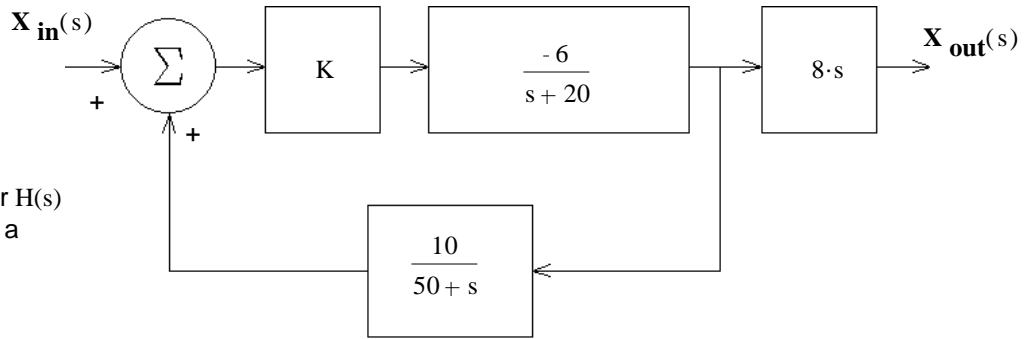2. (20 pts) a) A feedback system is shown in the figure. What is the transfer function of the whole system, with feedback.

$$H(s) = \frac{X_{out}(s)}{X_{in}(s)} = ?$$



Simplify your expression for H(s) so that the denominator is a simple polynomial.

b) Find the value of K to make the transfer function critically damped.

c) If K is **less** than this value the system will be: underdamped or overdamped Circle one


d) Does the transfer function have a zero? Answer no or find the s value(s) of the zero(s).

Answers


2. a) $8 \cdot s \cdot \frac{-6 \cdot K \cdot (s + 50)}{s^2 + 70 \cdot s + 60 \cdot K + 1000}$ b) 3.75 c) overdamped d) 0 - 50

3. a) $4.8 \cdot V$ $400 \cdot mA$ b) $240 \cdot mA$ $960 \cdot \frac{A}{sec}$ c) $4.8 \cdot V$ $-40000 \cdot \frac{V}{sec}$

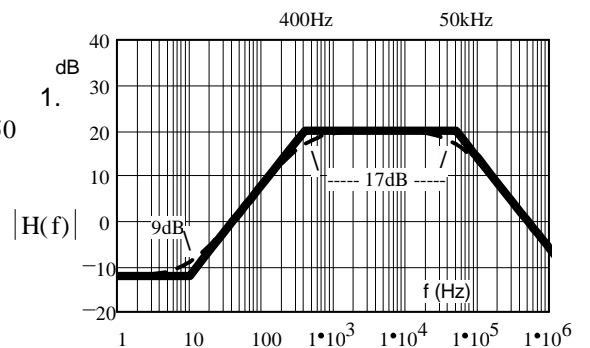4. a) $80 \cdot mA$ $-44 \cdot mA$ $124 \cdot mA$ $-0.94 \cdot V$ b) yes $124 \cdot mA > 0$
 c) no $-44 \cdot mA < 0$ d) yes $-0.94 \cdot V < 0.7V$



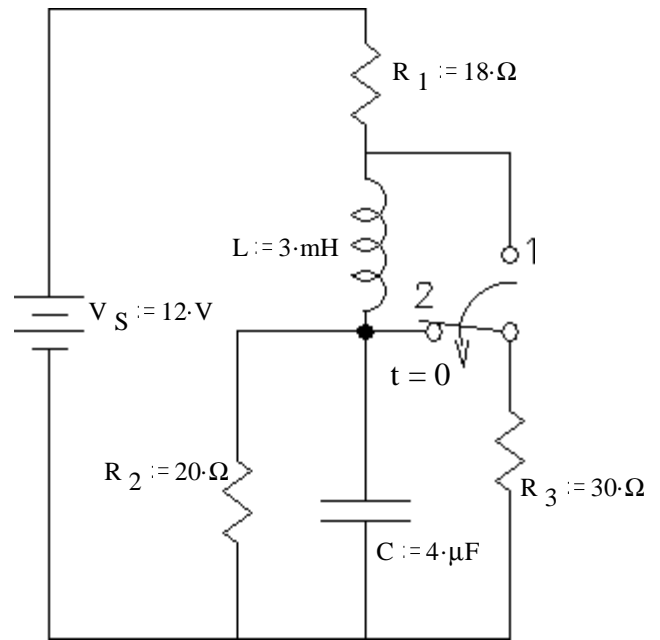3. (32 pts) The switch has been up in position 1 for a long time and is switched down to position 2 (as shown) at time $t = 0$. SHOW YOUR WORK, no credit for guesses!
- a) What are the final conditions of i_L and the v_C ?
- $i_L(\infty) = ?$ $v_C(\infty) = ?$



- b) Find the initial condition and initial slope of i_L that you would need to have in order to find all the constants in $i_L(t)$. Don't find $i_L(t)$ or it's constants, just the initial conditions.

- c) Find the initial condition and initial slope of v_C that you would need to have in order to find all the constants in $v_C(t)$. Don't find $v_C(t)$ or it's constants, just the initial conditions.

4. (22 pts) Assume that diodes D_1 and D_2 **DO** conduct.

Assume that diode D_3 does **NOT** conduct.


a) Find I_{R2} , I_{D2} , I_{D1} , & V_{D3} based on these assumptions.
Stick with these assumptions even if your answers come out absurd.

$I_{R2} =$ _____

$I_{D2} =$ _____

$I_{D1} =$ _____

$V_{D3} =$ _____

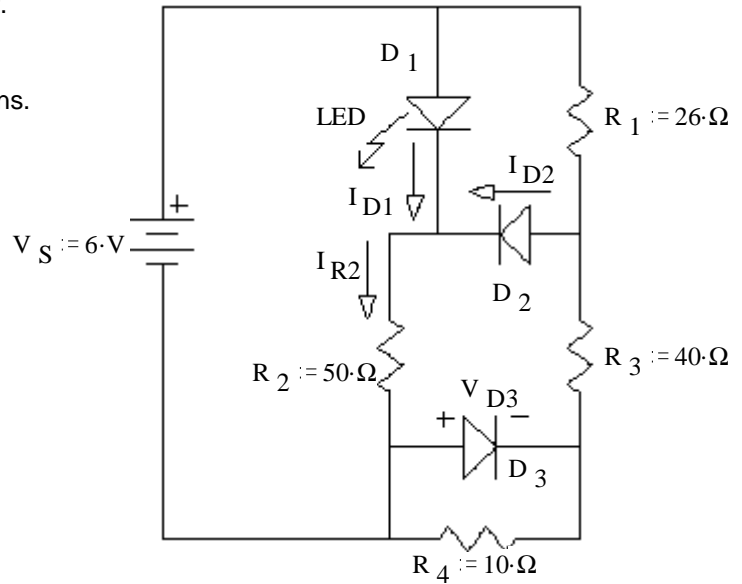

b) Based on the numbers above, was the assumption about D_1 correct? yes no (circle one)
How do you know? (Specifically show a value which is or is not within a correct range.)

c) Was the assumption about D_2 correct? yes no
How do you know? (Show a value & range.) (circle one)

d) Was the assumption about D_3 correct? yes no
How do you know? (Show a value & range.) (circle one)