

Note: In the following problems, you may assume voltages and currents are RMS unless stated otherwise or given as a function of time.

1. Read the AC power notes and examples. More in your text, section 2.27.3, ~p.175 and 2.28. Actually, start reading about 1.5 pages earlier, at "Series Impedance (RL circuit)".

2. Compute the power factor for an inductive load consisting of $L := 20\text{-mH}$ and $R := 6\text{-}\Omega$ in series. $\omega := 377\frac{\text{rad}}{\text{s}}$

3. The complex power consumed by a load is $620 \angle 29^\circ$ VA. Find:

a) Apparent power (as always, give the correct units).


b) Real power.

c) Reactive power.

d) Power factor.

e) Is the power factor leading or lagging?

f) Draw a phasor diagram.

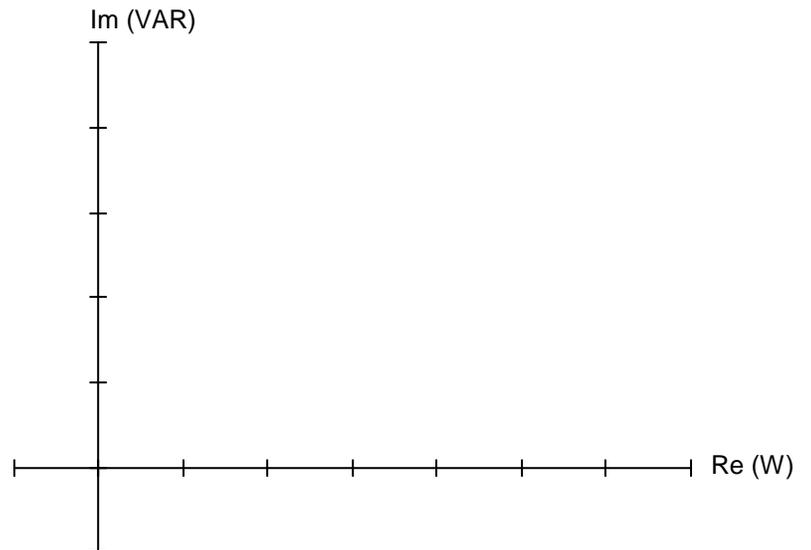

ECE 2210 homework PA1 p2

4. In the circuit shown, the voltmeter measures 120V, the ammeter measures 6.3A and the wattmeter measures 560W. The load consists of a resistor and an inductor. The frequency is 60Hz. Find the following:

a) Power factor



b) Leading or lagging?

c) Real power.

d) Apparent power.

e) Reactive power.

f) Draw a phasor diagram.

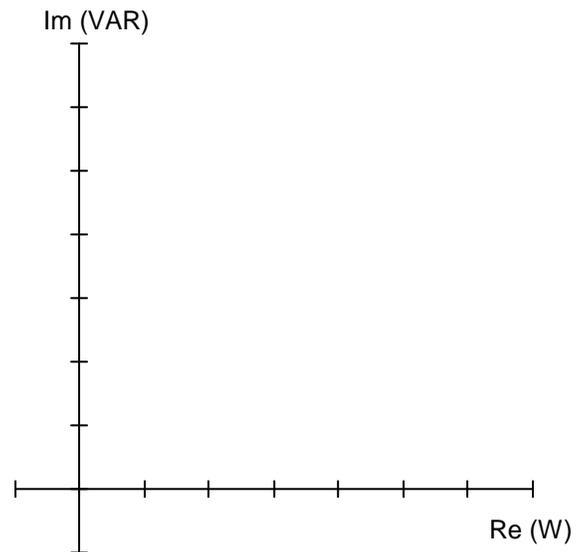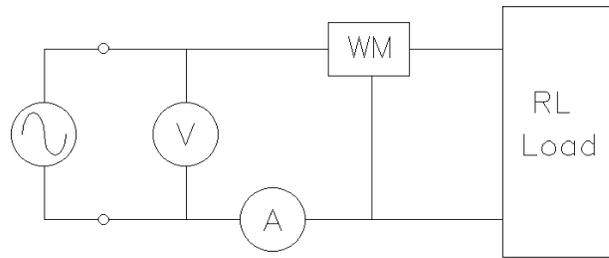


g) The load is in a box which cannot be opened. Add another component to the circuit above to correct the power factor (make $pf = 1$). Draw the correct component in the correct place and find its value. This component should not affect the real power consumption of the load.

ECE 2210 homework PA1 p3

5. For the circuit shown, find the following:
(as always, give the correct units)

a) The complex power.

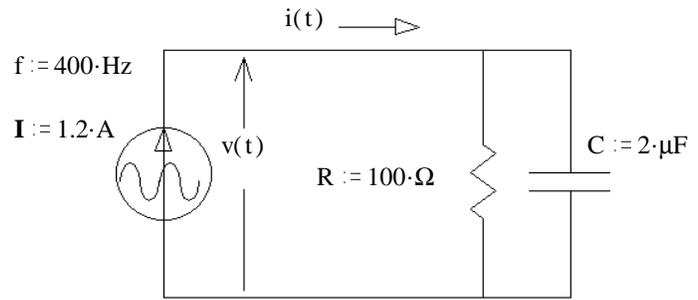


b) Real power.

c) Reactive power.

d) Apparent power.


e) Draw a power phasor diagram.

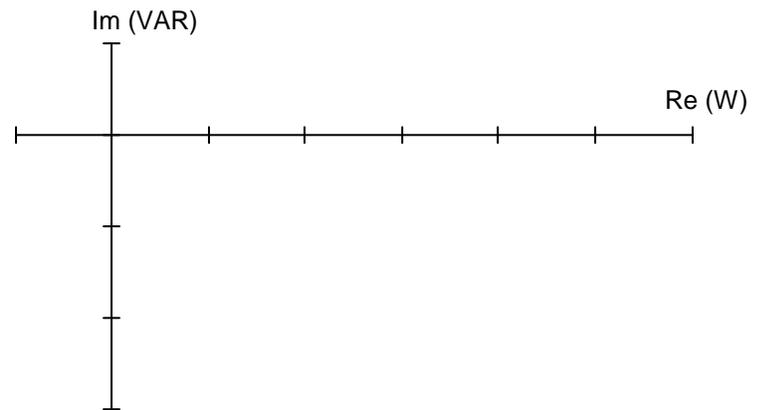

6. Consider the circuit at right.

The resistor and capacitor together make up the load.

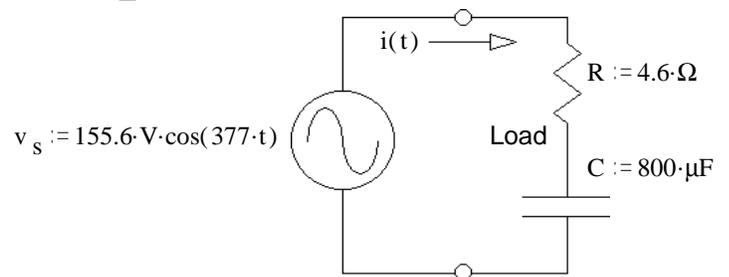a) Find the load impedance of the circuit.




b) Compute the average power dissipated by the load.

7. A load draws 12kVA at 0.8 pf, lagging when hooked to 480V.

A capacitance is hooked in parallel with the load and the power factor is corrected to 0.9, lagging.

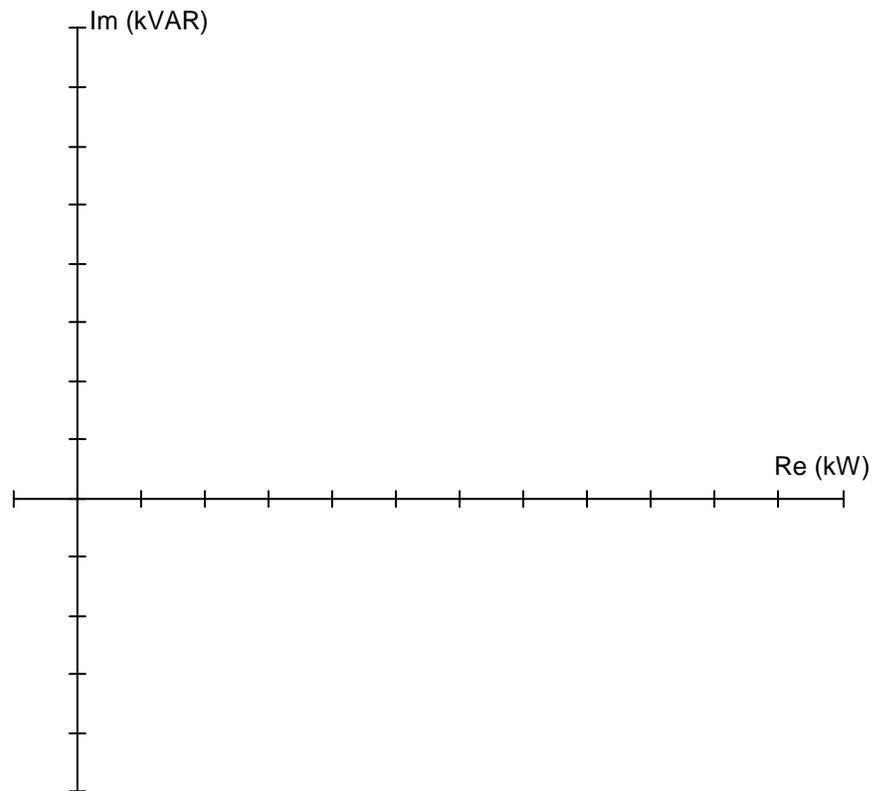
a) Find the reactive power (VAR) of the capacitor. Draw a phasor diagram as part of the solution.



b) Find the value of the capacitor assuming $f = 60\text{Hz}$.


ECE 2210 homework PA1 p5

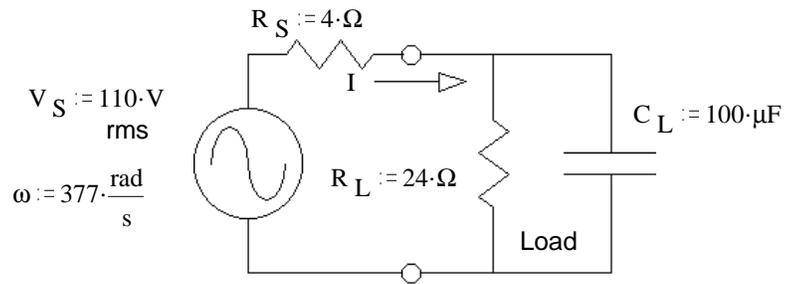8. a) Compute the average power dissipated by the load (R_L and C_L taken together).
 b) Compute the power dissipated by the internal source resistance (R_S) in this circuit.




Answers

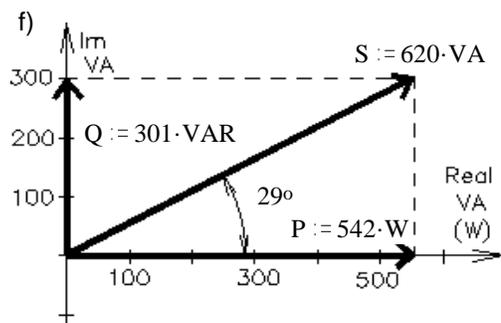2. $pf := 0.623$
 3. a) $620 \cdot VA$
 b) $542 \cdot W$
 c) $301 \cdot VAR$
 d) 0.875
 e) lagging
 ----->




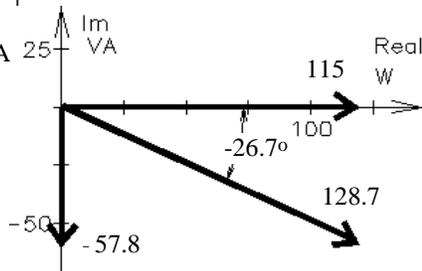5. a) $(115 - 57.8j) \cdot VA$
 b) $115 \cdot W$
 c) $-57.8 \cdot VAR$
 d) $128.7 \cdot VA$
 e) ----->




6. a) $Z := 5.67 \cdot \Omega \cdot e^{-j35.8 \cdot deg}$ b) $P_{av} := 1.73 \cdot kW$
 8. a) $P_{av} := 364 \cdot W$ b) $110 \cdot W$

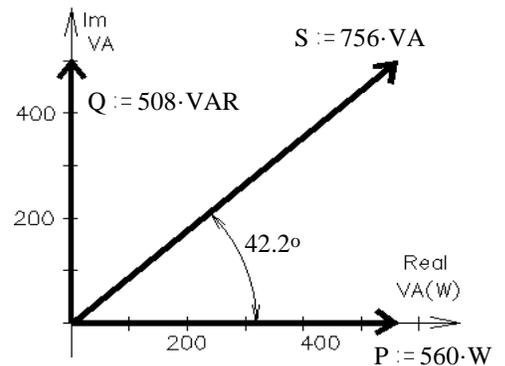4. a) 0.741
 b) lagging
 c) $560 \cdot W$
 d) $756 \cdot VA$
 e) $508 \cdot VAR$
 f) ----->
 g) $93.6 \cdot \mu F$ capacitor in parallel with load



7.

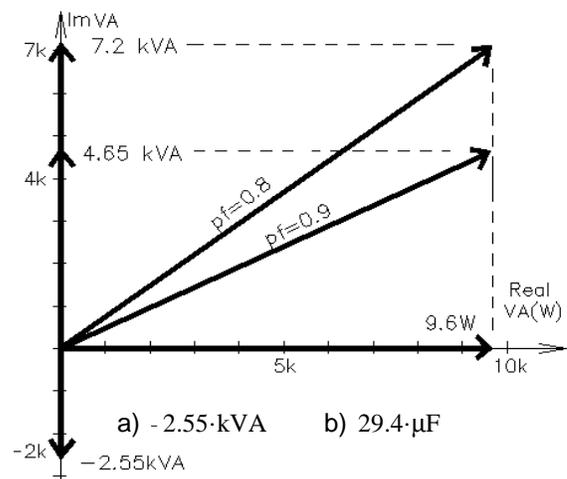

ECE 2210 homework PA1 p5