
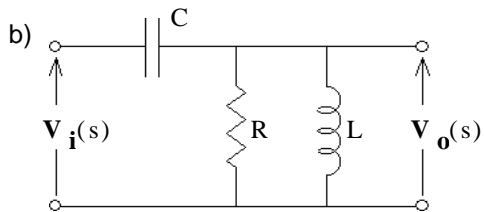


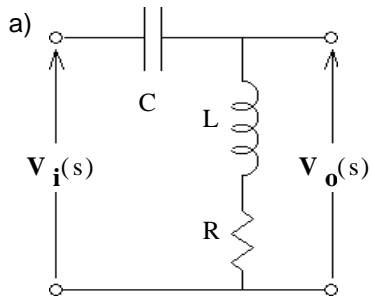1. Find the transfer function $H(s) = \frac{V_o(s)}{V_i(s)}$ for these circuits.

Write $H(s)$ in the normal form: $H(s) = K \cdot \frac{s^n + k_1 \cdot s^{n-1} + \dots + k_{n-1}}{s^m + c_1 \cdot s^{m-1} + \dots + c_{m-1}}$



2. Write the characteristic equation for each of the circuits in problem 2.

a)


b)

ECE 2210 homework 2ndTr1 p2

3. a) Find the s-type transfer function of the circuit shown. I_{in} is the input and V_{out} is the "output".

You MUST show work to get credit. Simplify your expression for $H(s)$ so that it is a ratio of simple polynomials just like my examples.

a) $H(s) = ?$

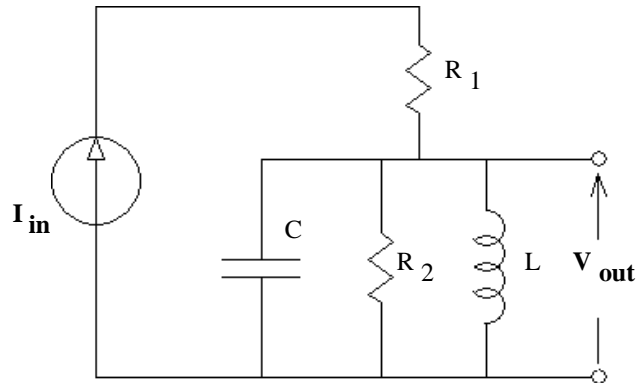

b) Find the solutions to the characteristic equation and express them in terms of the circuit parts.

Answers

1.a) $H(s) = \frac{s^2 + \frac{R}{L} \cdot s}{s^2 + \frac{R}{L} \cdot s + \frac{1}{L \cdot C}}$ b) $H(s) = \frac{s^2}{s^2 + \frac{1}{C \cdot R} \cdot s + \frac{1}{L \cdot C}}$

3.b) $-\frac{1}{2 \cdot C \cdot R_2} \pm \frac{1}{2} \cdot \sqrt{\left(\frac{1}{C \cdot R_2}\right)^2 - 4 \cdot \frac{1}{C \cdot L}}$

4.a) $\frac{240 \cdot \Omega \cdot s^2 + 2 \cdot 10^5 \cdot \frac{\Omega}{\text{sec}} \cdot s + 1.2 \cdot 10^{10} \cdot \frac{\Omega}{\text{sec}^2}}{s^2 + 5 \cdot 10^7 \cdot \frac{1}{\text{sec}^2}}$

- b) 240·Ω
- c) 240·Ω
- e) underdamped
- f) R 0.1·A L 0·A C 0.1·A
- g) R 0.1·A L 0.1·A C 0·A

More on next page ==>


2.a) $0 = s^2 + \frac{R}{L} \cdot s + \frac{1}{L \cdot C}$ b) $0 = s^2 + \frac{1}{C \cdot R} \cdot s + \frac{1}{L \cdot C}$

3.a) $\frac{\frac{1}{C} \cdot s}{s^2 + \frac{1}{C \cdot R_2} \cdot s + \frac{1}{C \cdot L}}$

d) $\frac{\frac{1}{240 \cdot \Omega} \cdot s^2 + 2.083 \cdot 10^5 \cdot \frac{1}{\Omega \cdot \text{sec}^2}}{s^2 + 833.333 \cdot \frac{1}{\text{sec}} \cdot s + 5 \cdot 10^7 \cdot \frac{1}{\text{sec}^2}}$ solutions to char. eq.
 -417 + 7059·j 1/sec
 -417 - 7059·j 1/sec

ECE 2210 homework 2ndTr1 p3

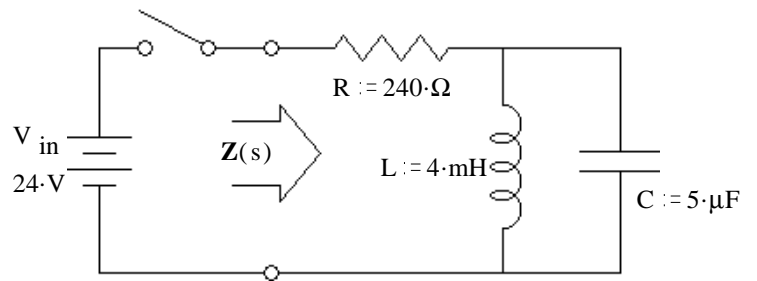4. For the circuit shown, with a disconnected source:
a) Find the generalized impedance of the circuit, $Z(s)$.
(This is just the equivalent impedance of R, L & C.)



b) What is the impedance at $s = 0$? (DC)

c) What is the impedance at $s = \infty$? (infinite frequency)

ECE 2210 homework 2ndTr1 p4

d) When the switch is closed, current will begin to flow. The voltage source is the input and the current through R can be considered the "output" (i.e. caused by the input). Find the transfer function of the circuit and the s-solutions to the characteristic equation.

e) What is the character of the response? i) undamped **ii) underdamped** iii) critically damped iv) overdamped

f) Find the initial values of all three currents.

g) Find the final values of all three currents