

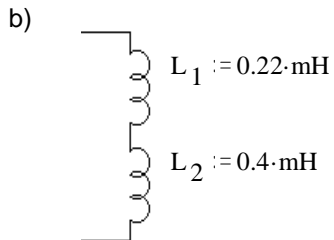
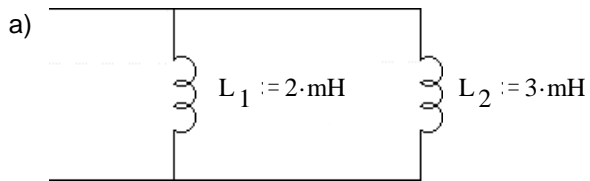


1. Find L_{eq} in each case

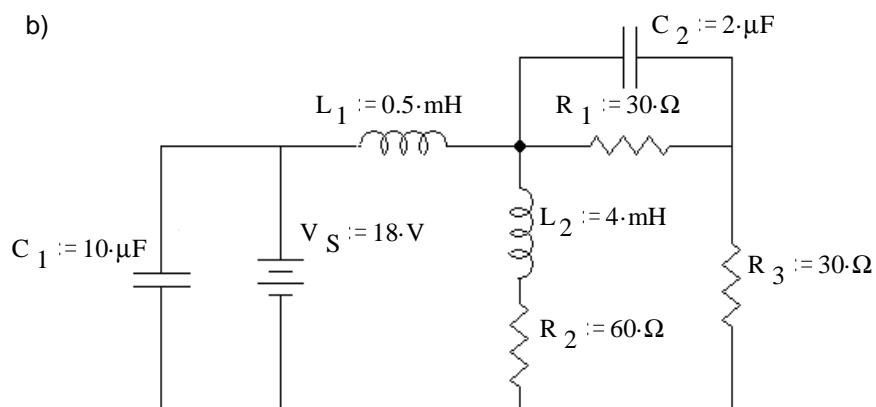


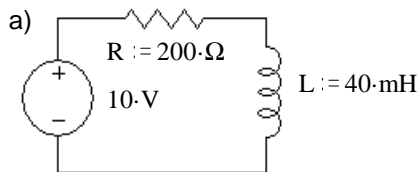
2. Find the stored energy in each capacitor and/or inductor under steady-state conditions. Note: Treat caps as opens and inductors as shorts to find DC voltages and currents.



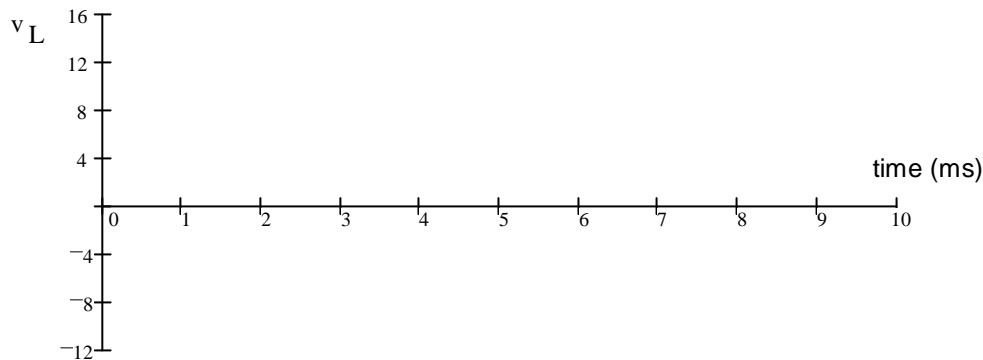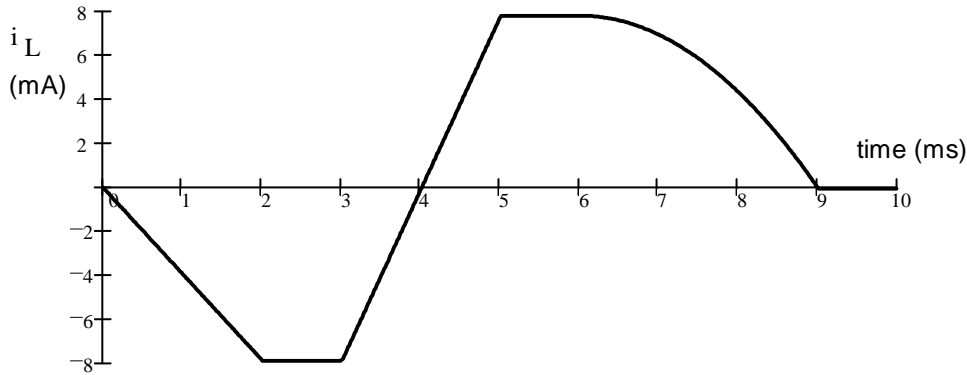3. The current waveform shown below flows through a 2 mH inductor. Make an accurate drawing of the voltage across it. Label your graph.

$L := 2\text{-mH}$

The curve is 2nd order / and starts at 6ms




GO TO Next Page

Answers

1. 1.2·mH 0.62·mH 2. a) 0.05·mJ b) 1.62·mJ 0.081·mJ 0.09·mJ 0.18·mJ
3. Straight lines between the following points: (0ms,-8mV), (2ms,-8mV), (2ms,0mV), (3ms,0mV), (3ms,16mV), (5ms,16mV), (5ms,0mV), (6ms,0mV), (9ms,-10.67mV), (9ms,0mV), (10ms,0mV)
4. Straight lines between the following points: (0ms,0A), (0.2ms,1.2A), (0.6ms,-0.4A), curves until it's flat at (0.76ms, -0.72A), continues to curve up to (1ms, 0A), (1.1ms,0A)
5. $i_L = 11.1\text{-mA}\cdot\cos(300\cdot t - 90\text{-deg})$ 6. $v_L = 1\text{-mV}\cdot\cos\left(628\cdot t + \frac{1}{4}\cdot\pi\right)$ 7. Assume a sinusoidal voltage, find i_C and i_L by integration and differentiation, and show that they are equal and opposite at the resonant frequency.
8. a) 17.79·kHz b) 5305·Hz

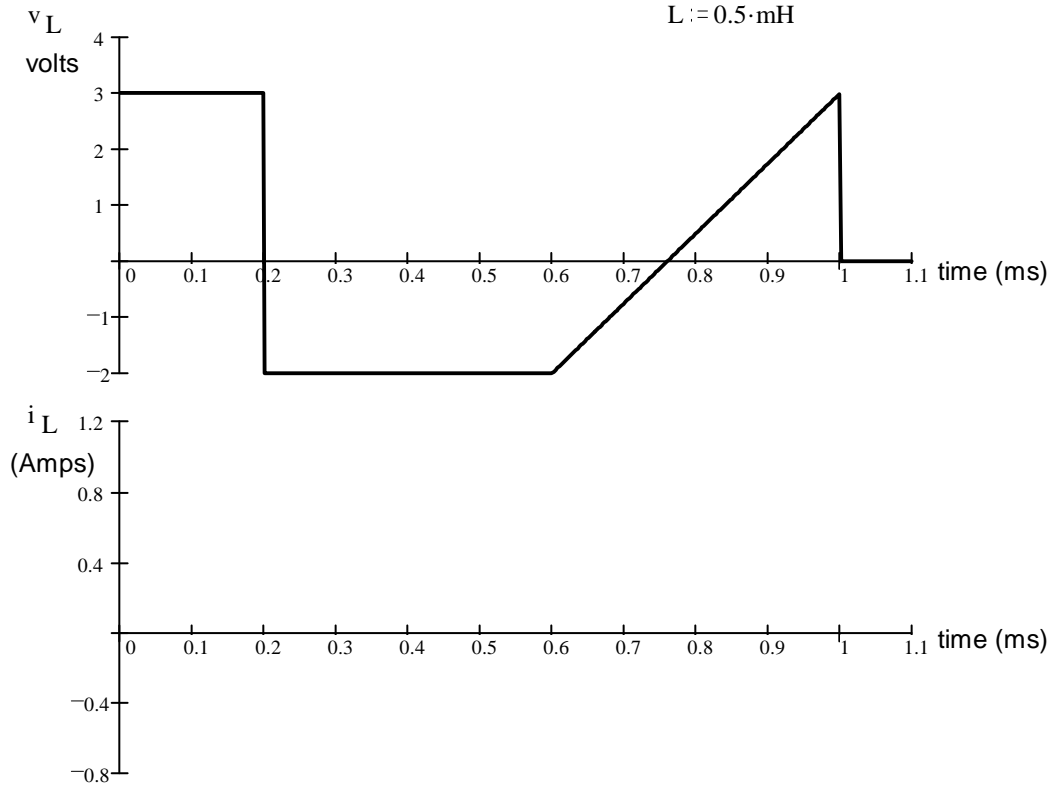4. The voltage across a 0.5 mH inductor is shown below. Make an accurate drawing of the inductor current. Label your graph. Assume the initial current is 0 mA.




5. The voltage across a 1.2 mH inductor is $v_L = 4 \cdot \text{mV} \cdot \cos(300 \cdot t)$ find i_L .

ECE 2210 / 00 homework Ind p4

6. The current through a 0.08 mH inductor is $i_L = 20 \cdot \text{mA} \cdot \cos\left(628 \cdot t - \frac{\pi}{4}\right)$ find v_L .

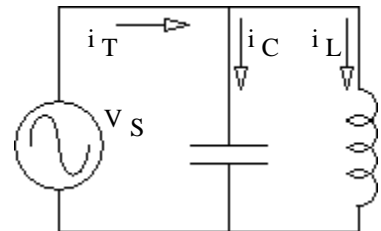7. Refer to the circuit shown. Assume that V_s is a sinusoidal input voltage whose frequency can be adjusted. At some frequency of V_s this circuit can resonate. At that frequency $i_C(t) = -i_L(t)$. ($i_C(t)$ is 180 degrees out-of-phase with $i_L(t)$).

Show that resonance occurs at this frequency: $\omega_o = \frac{1}{\sqrt{L \cdot C}}$, $f_o = \frac{1}{2 \cdot \pi \cdot \sqrt{L \cdot C}}$



8. Find the resonant frequency, f_o in each case.

