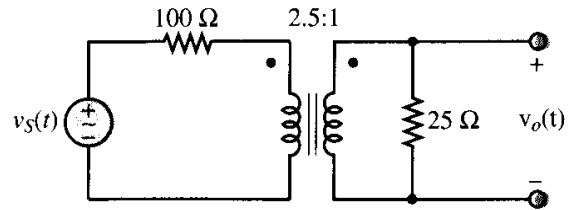


Note: In the following problems, you may assume voltages and currents are RMS unless stated otherwise or given as a function of time. Transformers are ideal unless stated otherwise.

1. Read sections 2.28, & 3.8 in your textbook. Note: His secondary windings and currents are backwards.
2. An ideal transformer has 330 turns on the primary winding and 36 turns on the secondary. If the primary is connected across a 110 V (rms) generator, what is the rms output voltage?
3. A transformer has  $N_1 = 320$  turns and  $N_2 = 1000$  turns. If the input voltage is  $v(t) = (255 \text{ V})\cos(\omega t)$ , what rms voltage is developed across the secondary coil?
4. A step-up transformer is designed to have an output voltage of 2200 V (rms) when the primary is connected across a 240 V (rms) source.
  - a) If there are 150 turns on the primary winding, how many turns are required on the secondary?
  - b) If a load resistor across the secondary draws a current of 1.2 A, what is the current in the primary, assuming ideal conditions?
5. The primary current of an ideal transformer is 8.5 A and the primary voltage is 80 V. 1.0 A is delivered to a load resistor connected to the secondary. Calculate the voltage across the secondary.
6. An ideal transformer has a turns ratio ( $N = N_1/N_2$ ) of 1.5 . It is desired to operate a  $200 \Omega$  resistive load at 150 V (rms).
  - a) Find the secondary and primary currents.
  - b) Find the source voltage ( $V_1$ ).
  - c) Find the power dissipated in the load resistor and the power delivered to the primary from the source.
  - d) Find the impedance the source sees looking into the primary winding by calculating  $Z_{eq} = N^2 Z_L$  and again by calculating  $V_1 / I_1$ .


**ECE 2210 homework PA2 p2**

7. For the ideal transformer shown in the figure, find  $v_o(t)$  if  $v_s(t)$  is  $320V\cos(377t)$ .



8. The transformer shown in the circuit below is ideal. It is rated at 120/30 V, 80 VA, 60 Hz  
Find the following:

a)  $I_1 = ?$

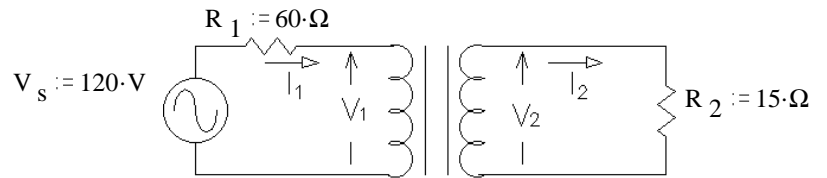

b)  $V_2 = ?$


### ECE 2210 homework PA2 p3

9. A transformer is rated at 13,800/480 V, 60 kVA, 60 Hz.  
(Note: kVA stands for kilo-Volt-Amp, in this case it is the transformer's voltage rating times its current rating.) Find the allowable primary and secondary currents at a supply voltage of 12,000 V at 100% power factor. Repeat for a power factor of 50%.
10. An ideal transformer has a rating of 500/125 V, 10 kVA, 60 Hz. It is loaded with an impedance of  $5\Omega$  at 80% pf (0.80). The source voltage applied to the primary winding is 440 V (rms). Find:
- a) the load voltage
  - b) the load current
  - c) the kVA delivered to load
  - d) the power delivered to load
  - e) the primary current
  - f) the power factor of primary
  - g) the impedance the source sees looking into primary.
11. An ideal transformer is rated to deliver 400 kVA at 460 V to a customer.
- a) How much current can the transformer supply to the customer?
  - b) If the customer's load is purely resistive (i.e. if the pf = 1), what is the maximum power the customer can receive?
  - c) If the customer's power factor is 0.8 (lagging), what is the maximum usable power the customer can receive?
  - d) What is the maximum power if the power factor is 0.7 (lagging)?
  - e) If the customer requires 300 kW to operate, what is the minimum allowable power factor given the rating of this transformer?

## ECE 2210 homework PA2 p4

12. The transformer shown in the circuit is ideal. It is rated at 240/80 V, 100 VA, 60 Hz, Find:

a) The primary current (magnitude).  $|\mathbf{I}_1|$

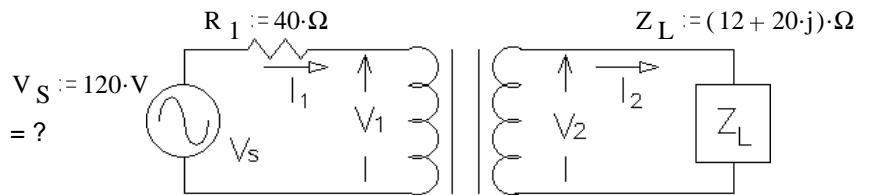

b) The primary voltage (magnitude).  $|\mathbf{V}_1|$

c) The secondary voltage (magnitude).  $|\mathbf{V}_2|$

d) The power supplied by the source ( $V_s$ ).  $P_S$

e) The power factor as seen by the source ( $V_s$ ).  $\text{pf} = ?$   
leading or lagging?

f) Is this transformer operating within its ratings? Show your evidence.

### Answers

2. 12 V    3. 563 V    4. a) 1375 turns    5. 680 V    b) 11 A    6. a) 0.75 A, 0.50 A    b) 225 V  
c) 112.5 W    d) 450  $\Omega$
7.  $78V\cos(377t)$     8. a) 0.4 A    b) 24V
9. 4.35 A, 125 A any pf, (Using the transformer at a lower voltage does not increase its current rating.)
10. a) 110 V    b) 22 A    c) 2.42 kVA    d) 1.94 kW    e) 5.5 A    f) 0.80    g)  $80\Omega \angle 36.9^\circ \Omega$
11. a) 870 A    b) 400 kW    c) 320 kW    d) 280 kW    e) 0.75
12. a) 0.515 A    b) 108 V    c) 36 V    d) 39.25 W    e) 0.635 lagging
- f) NO,  $I_{1\max} = \frac{100 \cdot \text{VA}}{240 \cdot \text{V}} = 0.417 \cdot \text{A} < 0.515 \cdot \text{A}$