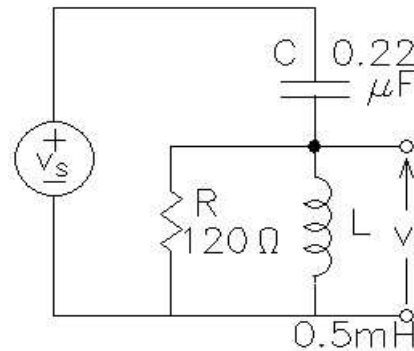


Ex. 1 For the circuit shown:a) Find the transfer function v_L .

$$\mathbf{V}_L(s) = \frac{\frac{1}{\frac{1}{Ls} + \frac{1}{R}}}{\frac{1}{\frac{1}{Ls} + \frac{1}{R}} + \frac{1}{Cs}} \cdot \mathbf{V}_S(s)$$



$$= \frac{1}{1 + \frac{1}{Cs} \cdot \left(\frac{1}{Ls} + \frac{1}{R} \right)} \cdot \mathbf{V}_S(s) = \frac{1}{1 + \frac{1}{Cs} \cdot \frac{1}{Ls} + \frac{1}{Cs} \cdot \frac{1}{R}} \cdot \mathbf{V}_S(s) = \frac{s^2}{s^2 + \frac{1}{C \cdot R} \cdot s + \frac{1}{L \cdot C}} \cdot \mathbf{V}_S(s)$$

$$\mathbf{H}(s) = \frac{\mathbf{V}_L(s)}{\mathbf{V}_S(s)} = \frac{s^2}{s^2 + \frac{1}{C \cdot R} \cdot s + \frac{1}{L \cdot C}}$$

$$= \frac{s^2}{s^2 + \frac{3.788 \cdot 10^4}{\text{sec}} \cdot s + \frac{9.091 \cdot 10^9}{\text{sec}^2}}$$

$$R := 120 \cdot \Omega \quad C := 0.22 \cdot \mu\text{F} \quad L := 0.5 \cdot \text{mH}$$

$$\frac{1}{C \cdot R} = 3.788 \cdot 10^4 \cdot \frac{1}{\text{sec}} \quad \frac{1}{L \cdot C} = 9.091 \cdot 10^9 \cdot \frac{1}{\text{sec}^2}$$

b) Find the characteristic equation for this circuit.

$$0 = s^2 + \frac{1}{C \cdot R} \cdot s + \frac{1}{L \cdot C} = s^2 + \frac{3.788 \cdot 10^4}{\text{sec}} \cdot s + \frac{9.091 \cdot 10^9}{\text{sec}^2}$$

Just the denominator set to zero. The solutions of the characteristic equation are the "poles" of the transfer function.

c) Find the differential equation for v_L .

Cross-multiply the transfer function

$$s^2 \cdot \mathbf{V}_S(s) = \left(s^2 + \frac{1}{C \cdot R} \cdot s + \frac{1}{L \cdot C} \right) \cdot \mathbf{V}_L(s)$$

$$s^2 \cdot \mathbf{V}_S(s) = s^2 \cdot \mathbf{V}_L(s) + \frac{1}{C \cdot R} \cdot s \cdot \mathbf{V}_L(s) + \frac{1}{L \cdot C} \cdot \mathbf{V}_L(s)$$

$$\frac{d^2}{dt^2} v_S(t) = \frac{d^2}{dt^2} v_L(t) + \frac{1}{C \cdot R} \cdot \frac{d}{dt} v_L(t) + \frac{1}{L \cdot C} \cdot v_L(t)$$

$$\frac{d^2}{dt^2} v_S(t) = \frac{d^2}{dt^2} v_L(t) + \frac{3.788 \cdot 10^4}{\text{sec}} \cdot \frac{d}{dt} v_L(t) + \frac{9.091 \cdot 10^9}{\text{sec}^2} \cdot v_L(t)$$

d) What are the solutions to the characteristic equation?

$$s_1 = \frac{-3.788 \cdot 10^4}{2} + \frac{1}{2} \cdot \sqrt{(3.788 \cdot 10^4)^2 - 4 \cdot (9.091 \cdot 10^9)} = -1.894 \cdot 10^4 + 9.345 \cdot 10^4 j$$

$$s_2 = \frac{-3.788 \cdot 10^4}{2} - \frac{1}{2} \cdot \sqrt{(3.788 \cdot 10^4)^2 - 4 \cdot (9.091 \cdot 10^9)} = -1.894 \cdot 10^4 - 9.345 \cdot 10^4 j$$


e) What type of response do you expect from this circuit?

The solutions to the characteristic equation are complex so the response will be **underdamped**.

ECE 2210 Lecture 18 notes p2

Ex. 2 Analysis of the circuit shown yields the characteristic equation below.

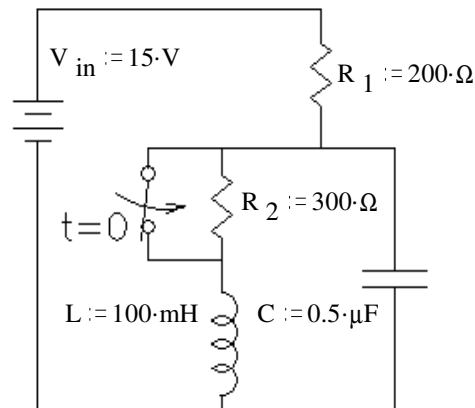The switch has been in the open position for a long time and is closed (as shown) at time $t = 0$. Find the initial and final conditions and write the full expression for $i_L(t)$, including all the constants that you find.



$$s^2 + \left(\frac{1}{C \cdot R_1}\right) \cdot s + \left(\frac{1}{L \cdot C}\right) = 0$$

$$\left(\frac{1}{C \cdot R_1}\right) = 1 \cdot 10^4 \cdot \frac{1}{\text{sec}} \quad \left(\frac{1}{L \cdot C}\right) = 2 \cdot 10^7 \cdot \frac{1}{\text{sec}^2}$$

$$s^2 + 10000 \cdot \frac{1}{\text{sec}} \cdot s + 2 \cdot 10^7 \cdot \frac{1}{\text{sec}^2} = 0$$

$$s_1 := \left[\frac{-10000}{2} + \frac{1}{2} \cdot \sqrt{(10000)^2 - 4 \cdot (2 \cdot 10^7)} \right] \cdot \text{sec}^{-1}$$

$$s_2 := \left[\frac{-10000}{2} - \frac{1}{2} \cdot \sqrt{(10000)^2 - 4 \cdot (2 \cdot 10^7)} \right] \cdot \text{sec}^{-1}$$

$$s_1 = -2764 \cdot \text{sec}^{-1}$$


$$s_2 = -7236 \cdot \text{sec}^{-1}$$

s_1 and s_2 are both real and distinct, overdamped

Find the initial conditions:

Before the switch closed, the inductor current was: $\frac{15\text{V}}{R_1 + R_2} = 30\text{mA} = i_L(0)$

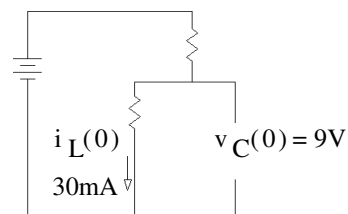Before the switch closed, the capacitor voltage was: $\frac{R_2}{R_1 + R_2} \cdot (15\text{V}) = 9\text{V} = v_C(0)$




When the switch is closed, the inductor is suddenly in parallel with the capacitor, and:

$$v_L(0) = v_C(0)$$


$$\frac{d}{dt} i_L(0) = \frac{1}{L} \cdot v_L(0) =$$
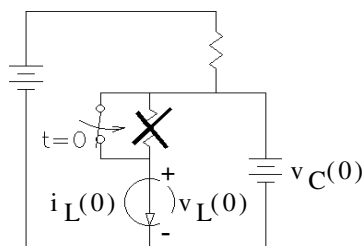
$$\frac{1}{L} \cdot 9\text{V} = 90 \cdot \frac{\text{A}}{\text{sec}}$$



Find the final condition:
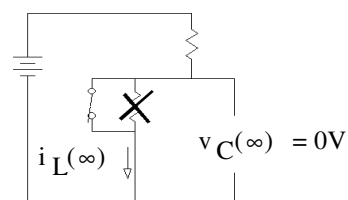
$$i_L(\infty) = \frac{15\text{V}}{R_1} = 75\text{mA}$$



General solution for the overdamped condition: $i_L(t) = i_L(\infty) + B \cdot e^{s_1 t} + D \cdot e^{s_2 t}$

Initial conditions: $i_L(0) = \frac{15\text{V}}{R_1 + R_2} = i_L(\infty) + B + D$, so $B = i_L(0) - i_L(\infty) - D = 30\text{mA} - 75\text{mA} - D = -45\text{mA} - D$

$$\frac{d}{dt} i_L(0) = 90 \cdot \frac{\text{A}}{\text{sec}} = s_1 \cdot B + s_2 \cdot D = s_1 \cdot (-45\text{mA} - D) + s_2 \cdot D = s_1 \cdot (-45\text{mA}) - s_1 \cdot D + s_2 \cdot D$$


solve for D & B: $D := \frac{90 \cdot \frac{\text{A}}{\text{sec}} - s_1 \cdot (-45\text{mA})}{-s_1 + s_2}$

$$D = 7.69\text{mA}$$

$$B := -45\text{mA} - D$$

$$B = -52.7\text{mA}$$

Plug numbers back in: $i_L(t) := 75\text{mA} - 52.7\text{mA} \cdot e^{-2764t} + 7.69\text{mA} \cdot e^{-7236t}$

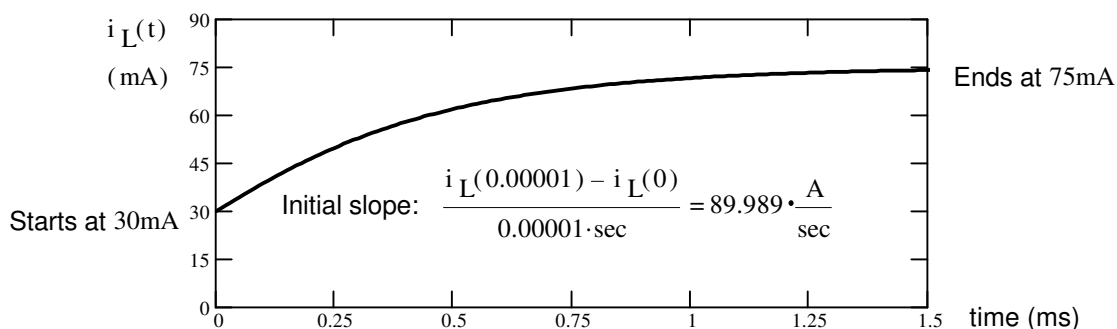


Ex. 3

Analysis of the circuit shown yields the characteristic equation and s values below. The switch has been in the closed position for a long time and is opened (as shown) at time $t = 0$. Find the initial and final conditions and write the full expression for $v_C(t)$, including all the constants.


$$0 = s^2 + \frac{R_1}{L} \cdot s + \frac{1}{LC}$$

$$s_1 := (-250 + 10^4 \cdot j) \cdot \frac{1}{\text{sec}}, \quad s_2 := (-250 - 10^4 \cdot j) \cdot \frac{1}{\text{sec}}$$

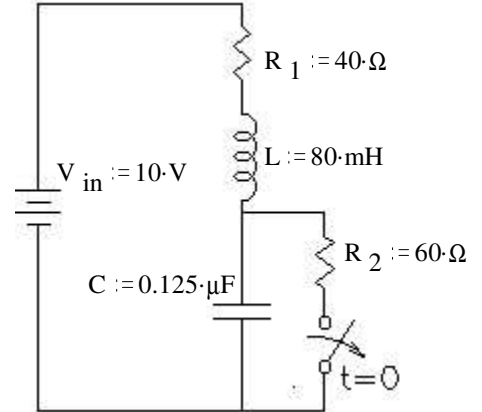
Solution: $\alpha := -250 \cdot \frac{1}{\text{sec}}$ $\omega := 10000 \cdot \frac{\text{rad}}{\text{sec}}$




Initial conditions:

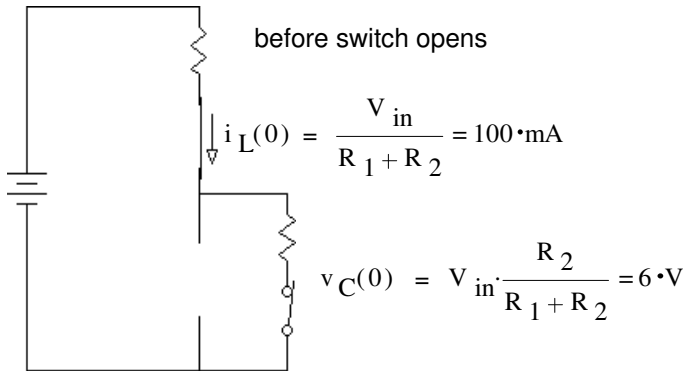

just after the switch opens

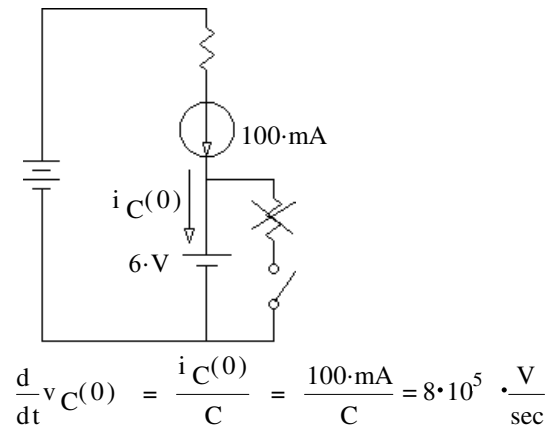

Find final condition:

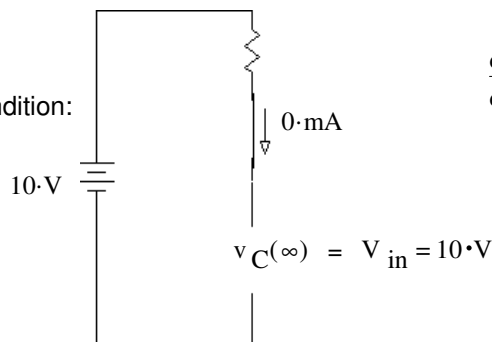

Find constants: $v_C(0) = v_C(\infty) + B$ $B = v_C(0) - v_C(\infty)$ $B := 6 \cdot \text{V} - 10 \cdot \text{V}$ $B = -4 \cdot \text{V}$

$$\frac{d}{dt} v_C(0) = \alpha \cdot B + D \cdot \omega$$

$$D := \frac{8 \cdot 10^5 \cdot \frac{\text{V}}{\text{sec}} - \alpha \cdot B}{\omega}$$

$$D = 79.9 \cdot \text{V}$$


Write the full expression for $v_C(t)$, including all the constants that you find.

$$v_C(t) = e^{\alpha t} \cdot (B \cdot \cos(\omega t) + D \cdot \sin(\omega t)) + v_C(\infty)$$

$$v_C(t) := e^{-250t} \cdot (-4 \cdot \text{V} \cdot \cos(10^4 \cdot t) + 79.9 \cdot \text{V} \cdot \sin(10^4 \cdot t)) + 10 \cdot \text{V}$$

$$\sqrt{D^2 + B^2} = 80 \cdot \text{V}$$

$v_C(t)$
(volts)

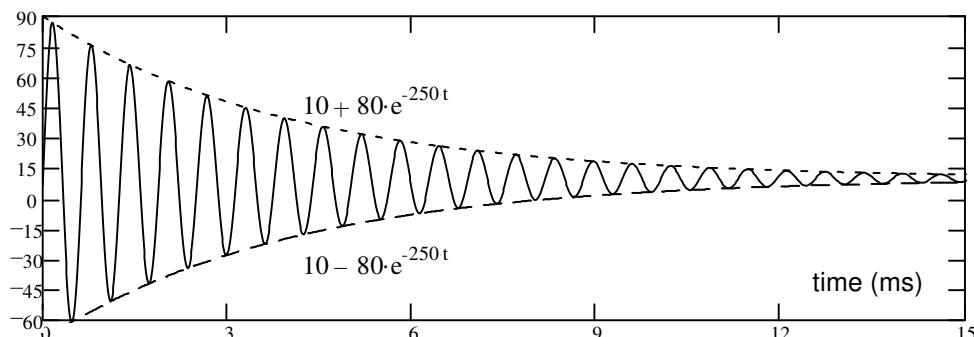



ECE 2210 Lecture 18 notes p4

Ex. 4 Ex.3 Backwards, switch closes at $t = 0$


Characteristic eq.: $0 = s^2 + \left(\frac{1}{C \cdot R_2} + \frac{R_1}{L}\right) \cdot s + \left(1 + \frac{R_1}{R_2}\right) \cdot \frac{1}{L \cdot C}$

$s_1 := -1.257 \cdot 10^3 \cdot \frac{1}{\text{sec}}$ $s_2 := -1.326 \cdot 10^5 \cdot \frac{1}{\text{sec}}$


Initial conditions, same as Ex.3 final:

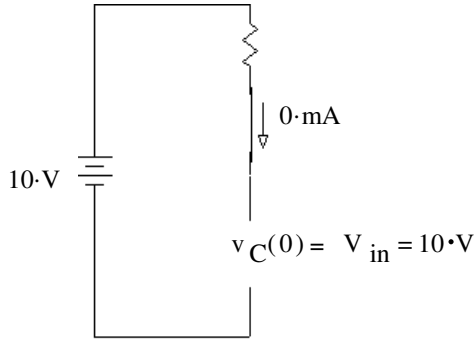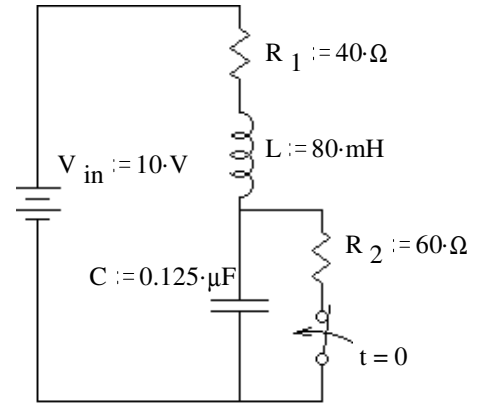

just after the switch opens

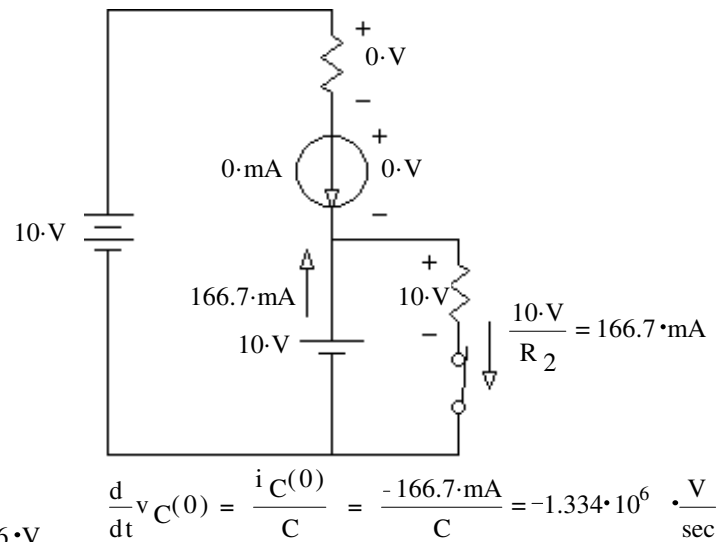

Find final condition:

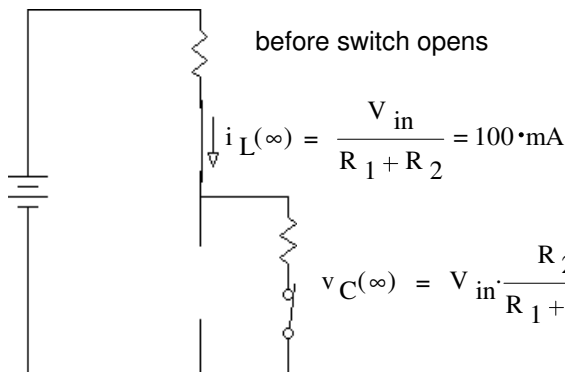

before switch opens

$i_L(\infty) = \frac{V_{in}}{R_1 + R_2} = 100 \cdot \text{mA}$

$v_C(\infty) = V_{in} \cdot \frac{R_2}{R_1 + R_2} = 6 \cdot \text{V}$

$\frac{d}{dt} v_C(0) = \frac{i_C(0)}{C} = \frac{-166.7 \cdot \text{mA}}{C} = -1.334 \cdot 10^6 \cdot \frac{\text{V}}{\text{sec}}$

Find constants: $v_C(0) = v_C(\infty) + B + D$, so $B = v_C(0) - v_C(\infty) - D = 10 \cdot \text{V} - 6 \cdot \text{V} - D = 4 \cdot \text{V} - D$

$\frac{d}{dt} v_C(0) = -1.334 \cdot 10^6 \cdot \frac{\text{V}}{\text{sec}} = s_1 \cdot B + s_2 \cdot D = s_1 \cdot (4 \cdot \text{V} - D) + s_2 \cdot D = s_1 \cdot (4 \cdot \text{V}) - s_1 \cdot D + s_2 \cdot D$


$D := \frac{-1.334 \cdot 10^6 \cdot \frac{\text{V}}{\text{sec}} - s_1 \cdot (4 \cdot \text{V})}{-s_1 + s_2}$

$D = 10.12 \cdot \text{V}$

$B = 4 \cdot \text{V} - D$

$B = -6.12 \cdot \text{V}$

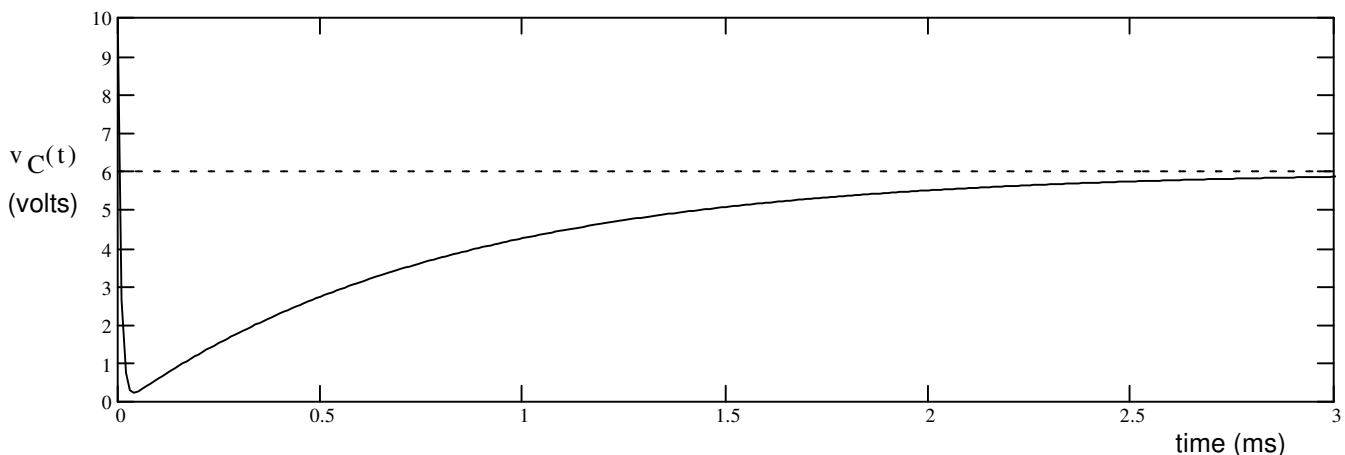$v_C(t) := 6 \cdot \text{V} - 6.12 \cdot \text{V} \cdot e^{-1257t} + 10.12 \cdot \text{V} \cdot e^{-132600t}$



Ex. 5 Analysis of a circuit (not pictured) yields the characteristic equation below.

$$0 = s^2 + 400 \cdot s + 400000$$

$$R := 80 \cdot \Omega$$

$$L := 20 \cdot \text{mH}$$

$$C := 2 \cdot \mu\text{F}$$

Further analysis yields the following initial and final conditions:

$$i_L(0) = 120 \cdot \text{mA}$$

$$v_L(0) = -3 \cdot \text{V}$$

$$v_C(0) = 7 \cdot \text{V}$$

$$i_C(0) = -80 \cdot \text{mA}$$

$$i_L(\infty) = 800 \cdot \text{mA}$$

$$v_L(\infty) = 0 \cdot \text{V}$$

$$v_C(\infty) = 12 \cdot \text{V}$$

$$i_C(\infty) = 0 \cdot \text{mA}$$

Write the full expression for $i_L(t)$, including all the constants that you find.

$$i_L(t) = ?$$

Solution:

$$\frac{400}{2} = 200 \quad \frac{\sqrt{400^2 - 4 \cdot 400000}}{2} = 600j$$

$$s_1 := (-200 + 600j) \cdot \frac{1}{\text{sec}} \quad \text{and} \quad s_2 := (-200 - 600j) \cdot \frac{1}{\text{sec}}$$

$$\alpha := \text{Re}(s_1)$$

$$\alpha = -200 \cdot \text{sec}^{-1}$$

$$\omega := \text{Im}(s_1)$$

$$\omega = 600 \cdot \text{sec}^{-1}$$

$$\text{Initial slope:} \quad \frac{d}{dt} i_L(0) = \frac{v_L(0)}{L} = \frac{-3 \cdot \text{V}}{L} = -150 \cdot \frac{\text{A}}{\text{sec}}$$

General solution for the underdamped condition: $i_L(t) = i_L(\infty) + e^{\alpha t} \cdot (B \cdot \cos(\omega \cdot t) + D \cdot \sin(\omega \cdot t))$

$$\text{Find constants:} \quad i_L(0) = i_L(\infty) + B$$

$$B = i_L(0) - i_L(\infty)$$

$$B := 120 \cdot \text{mA} - 800 \cdot \text{mA}$$

$$B = -680 \cdot \text{mA}$$


$$\frac{d}{dt} i_L(0) = \alpha \cdot B + D \cdot \omega$$

$$D := \frac{-150 \cdot \frac{\text{A}}{\text{sec}} - \alpha \cdot B}{\omega}$$

$$D = -476.667 \cdot \text{mA}$$

Write the full expression for $i_L(t)$, including all the constants that you find.

$$i_L(t) := 800 \cdot \text{mA} + e^{-200t} \cdot (-680 \cdot \text{mA} \cdot \cos(600 \cdot t) - 477 \cdot \text{mA} \cdot \sin(600 \cdot t))$$

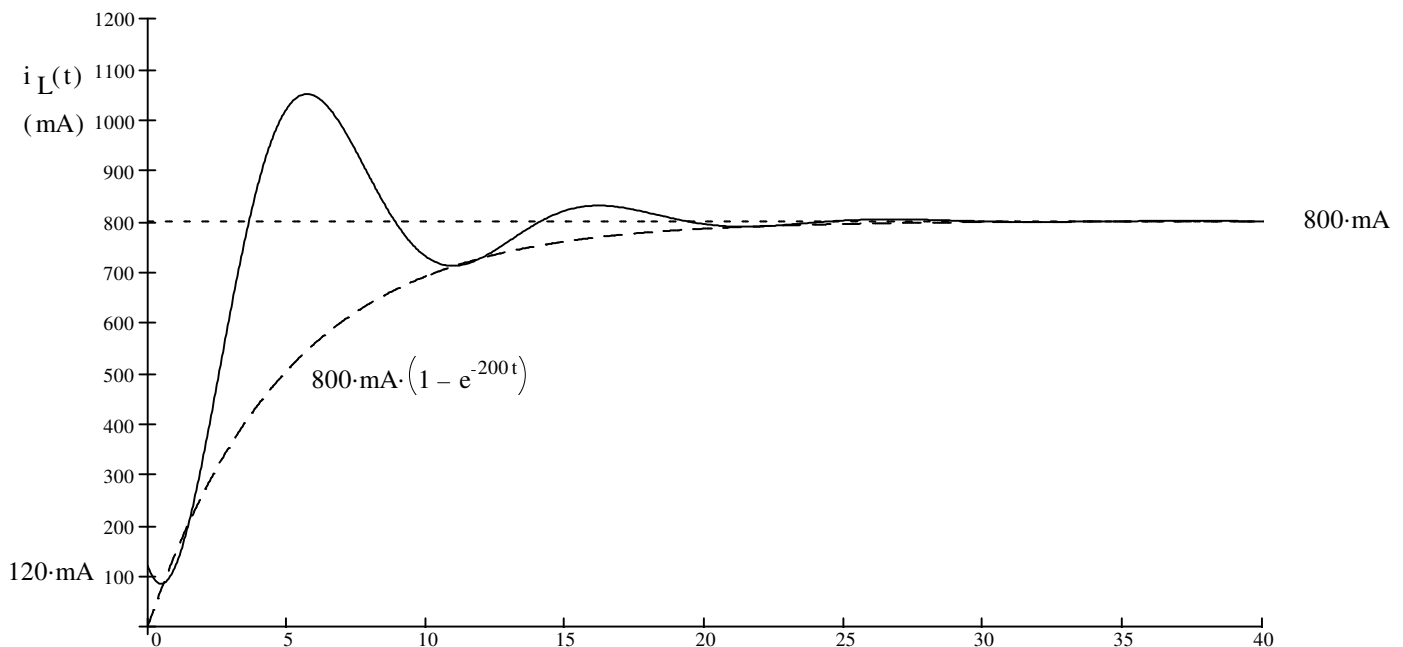

Ex. 6

Analysis of a circuit (not pictured) yields the characteristic equation below.

$$0 = s^2 + 800 \cdot s + 160000$$

$$R := 60 \cdot \Omega$$

$$L := 350 \cdot \text{mH}$$

$$C := 20 \cdot \mu\text{F}$$

$$V_{in} := 12 \cdot \text{V}$$

Further analysis yields the following initial and final conditions:

$$i_L(0) = 30 \cdot \text{mA}$$

$$v_L(0) = -7 \cdot \text{V}$$

$$v_C(0) = 5 \cdot \text{V}$$

$$i_C(0) = 70 \cdot \text{mA}$$

$$i_L(\infty) = 90 \cdot \text{mA}$$

$$v_L(\infty) = 0 \cdot \text{V}$$

$$v_C(\infty) = 12 \cdot \text{V}$$

$$i_C(\infty) = 0 \cdot \text{mA}$$

Write the full expression for $i_L(t)$, including all the constants that you find. $i_L(t) = ?$

Include **units** in your answer

Solution:

$$\frac{-800 \pm \sqrt{800^2 - 4 \cdot 160000}}{2} = -400$$

$$s_1 := -400 \cdot \frac{1}{\text{sec}}$$

$$s_2 := -400 \cdot \frac{1}{\text{sec}}$$

s_1 and s_2 are the same, **critically damped**

Initial slope: $\frac{d}{dt}i_L(0) = \frac{v_L(0)}{L} = \frac{-7 \cdot \text{V}}{L} = -20 \cdot \frac{\text{A}}{\text{sec}}$

General solution for the critically damped condition: $i_L(t) = i_L(\infty) + B \cdot e^{s_1 t} + D \cdot t \cdot e^{s_2 t}$

Find constants: $i_L(0) = i_L(\infty) + B$

$$B = i_L(0) - i_L(\infty)$$

$$B := 30 \cdot \text{mA} - 90 \cdot \text{mA}$$

$$B = -60 \cdot \text{mA}$$

$$\frac{d}{dt}i_L(0) = B \cdot s_1 + D$$

$$D := -20 \cdot \frac{\text{A}}{\text{sec}} - B \cdot s_1$$

$$D = -44 \cdot \frac{\text{A}}{\text{sec}}$$

Write the full expression for $i_L(t)$, including all the constants that you find.

$$i_L(t) := 90 \cdot \text{mA} - 60 \cdot \text{mA} \cdot e^{-\frac{400}{\text{sec}} t} - 44 \cdot \frac{\text{A}}{\text{sec}} \cdot t \cdot e^{-\frac{400}{\text{sec}} t}$$

