

Ex 1. For the circuit shown:

a) Find the transfer function v_L .

$$\mathbf{V_L(s)} = \frac{\frac{1}{\frac{1}{Ls} + \frac{1}{R}}}{\frac{1}{\frac{1}{Ls} + \frac{1}{R}} + \frac{1}{Cs}} \cdot \mathbf{V_S(s)}$$

$$= \frac{1}{1 + \frac{1}{Cs} \cdot \left(\frac{1}{Ls} + \frac{1}{R} \right)} \cdot \mathbf{V_S(s)} = \frac{1}{1 + \frac{1}{Cs} \cdot \frac{1}{Ls} + \frac{1}{Cs} \cdot \frac{1}{R}} \cdot \mathbf{V_S(s)} = \frac{s^2}{s^2 + \frac{1}{C \cdot R} \cdot s + \frac{1}{L \cdot C}} \cdot \mathbf{V_S(s)}$$

$$\mathbf{H(s)} = \frac{\mathbf{V_L(s)}}{\mathbf{V_S(s)}} = \frac{s^2}{s^2 + \frac{1}{C \cdot R} \cdot s + \frac{1}{L \cdot C}}$$

$$= \frac{s^2}{s^2 + \frac{3.788 \cdot 10^4}{\text{sec}} \cdot s + \frac{9.091 \cdot 10^9}{\text{sec}^2}}$$


$$R := 120 \cdot \Omega$$

$$C := 0.22 \cdot \mu\text{F}$$

$$L := 0.5 \cdot \text{mH}$$

$$\frac{1}{C \cdot R} = 3.788 \cdot 10^4 \cdot \frac{1}{\text{sec}}$$
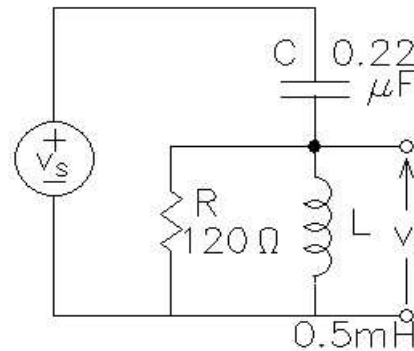
$$\frac{1}{L \cdot C} = 9.091 \cdot 10^9 \cdot \frac{1}{\text{sec}^2}$$



b) Find the characteristic equation for this circuit.

$$0 = s^2 + \frac{1}{C \cdot R} \cdot s + \frac{1}{L \cdot C} = s^2 + \frac{3.788 \cdot 10^4}{\text{sec}} \cdot s + \frac{9.091 \cdot 10^9}{\text{sec}^2}$$

Just the denominator set to zero. The solutions of the characteristic equation are the "poles" of the transfer function.

c) Find the differential equation for v_L .

Cross-multiply the transfer function

$$s^2 \cdot \mathbf{V_S(s)} = \left(s^2 + \frac{1}{C \cdot R} \cdot s + \frac{1}{L \cdot C} \right) \cdot \mathbf{V_L(s)}$$

$$s^2 \cdot \mathbf{V_S(s)} = s^2 \cdot \mathbf{V_L(s)} + \frac{1}{C \cdot R} \cdot s \cdot \mathbf{V_L(s)} + \frac{1}{L \cdot C} \cdot \mathbf{V_L(s)}$$

$$\frac{d^2}{dt^2} v_S(t) = \frac{d^2}{dt^2} v_L(t) + \frac{1}{C \cdot R} \cdot \frac{d}{dt} v_L(t) + \frac{1}{L \cdot C} \cdot v_L(t)$$

$$\frac{d^2}{dt^2} v_S(t) = \frac{d^2}{dt^2} v_L(t) + \frac{3.788 \cdot 10^4}{\text{sec}} \cdot \frac{d}{dt} v_L(t) + \frac{9.091 \cdot 10^9}{\text{sec}^2} \cdot v_L(t)$$

d) What are the solutions to the characteristic equation?

$$s_1 = \frac{-3.788 \cdot 10^4}{2} + \frac{1}{2} \cdot \sqrt{(3.788 \cdot 10^4)^2 - 4 \cdot (9.091 \cdot 10^9)} = -1.894 \cdot 10^4 + 9.345 \cdot 10^4 j$$

$$s_2 = \frac{-3.788 \cdot 10^4}{2} - \frac{1}{2} \cdot \sqrt{(3.788 \cdot 10^4)^2 - 4 \cdot (9.091 \cdot 10^9)} = -1.894 \cdot 10^4 - 9.345 \cdot 10^4 j$$

e) What type of response do you expect from this circuit?

The solutions to the characteristic equation are complex so the response will be **underdamped**.

ECE 2210 Lecture 18 notes p2

2. Analysis of the circuit shown yields the characteristic equation below. The switch has been in the open position for a long time and is closed (as shown) at time $t = 0$. Find the initial and final conditions and write the full expression for $i_L(t)$, including all the constants that you find. Don't let the odd position of the switch throw you, just use it to find your initial conditions.

Clearly show important numbers (like initial and final conditions) to get partial credit. If you can't find some of these, guess so that you can move on.

$$s^2 + \left(\frac{1}{C \cdot R_1}\right) \cdot s + \left(\frac{1}{L \cdot C}\right) = 0$$

$$\left(\frac{1}{C \cdot R_1}\right) = 1 \cdot 10^4 \cdot \text{sec}^{-1} \quad \left(\frac{1}{L \cdot C}\right) = 4 \cdot 10^9 \cdot \text{sec}^{-2}$$

$$s^2 + 10000 \cdot \frac{1}{\text{sec}} \cdot s + 2 \cdot 10^7 \cdot \frac{1}{\text{sec}^2} = 0$$

$$s_1 := \left[\frac{-10000}{2} + \frac{1}{2} \cdot \sqrt{(10000)^2 - 4 \cdot (2 \cdot 10^7)} \right] \cdot \text{sec}^{-1}$$

$$s_1 = -2764 \cdot \text{sec}^{-1}$$

$$s_2 := \left[\frac{-10000}{2} - \frac{1}{2} \cdot \sqrt{(10000)^2 - 4 \cdot (2 \cdot 10^7)} \right] \cdot \text{sec}^{-1}$$

$$s_2 = -7236 \cdot \text{sec}^{-1}$$

s_1 and s_2 are both real and distinct, overdamped

Find the initial conditions:


Before the switch closed, the inductor current was: $\frac{15 \cdot \text{V}}{R_1 + R_2} = 30 \cdot \text{mA} = i_L(0)$

Before the switch closed, the capacitor voltage was: $v_C(0) = \frac{R_2}{R_1 + R_2} \cdot (15 \cdot \text{V}) = 9 \cdot \text{V}$ so: $v_{C0} := 9 \cdot \text{V}$

When the switch is opened, the new voltage across the inductor is: $v_{L0} := v_{C0}$


$$\frac{d}{dt} i_L(0) = \frac{1}{L} \cdot v_{L0} =$$
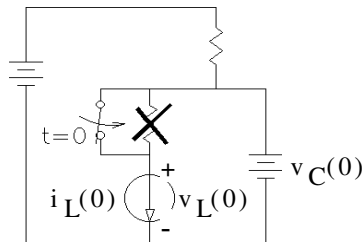
$$\frac{1}{L} \cdot v_{C0} = 90 \cdot \frac{\text{A}}{\text{sec}}$$



Find the final condition:
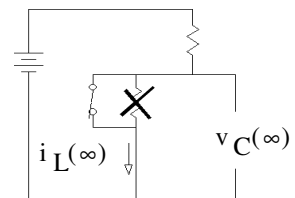
$$i_L(\infty) = \frac{15 \cdot \text{V}}{R_1} = 75 \cdot \text{mA}$$



General solution for the overdamped condition: $i_L(t) = i_L(\infty) + B \cdot e^{s_1 t} + D \cdot e^{s_2 t}$

Initial conditions: $i_{L0} := \frac{15 \cdot \text{V}}{R_1 + R_2} = i_L(\infty) + B + D$, so $B = i_{L0} - i_L(\infty) - D = 30 \cdot \text{mA} - 75 \cdot \text{mA} - D = -45 \cdot \text{mA} - D$

$$\frac{d}{dt} i_L(0) = 90 \cdot \frac{\text{A}}{\text{sec}} = s_1 \cdot B + s_2 \cdot D = s_1 \cdot (-45 \cdot \text{mA} - D) + s_2 \cdot D = s_1 \cdot (-45 \cdot \text{mA}) - s_1 \cdot D + s_2 \cdot D$$


$$\text{solve for D \& B: } D := \frac{90 \cdot \frac{\text{A}}{\text{sec}} - s_1 \cdot (-45 \cdot \text{mA})}{-s_1 + s_2}$$

$$D = 7.69 \cdot \text{mA}$$

$$B := -45 \cdot \text{mA} - D$$

$$B = -52.7 \cdot \text{mA}$$

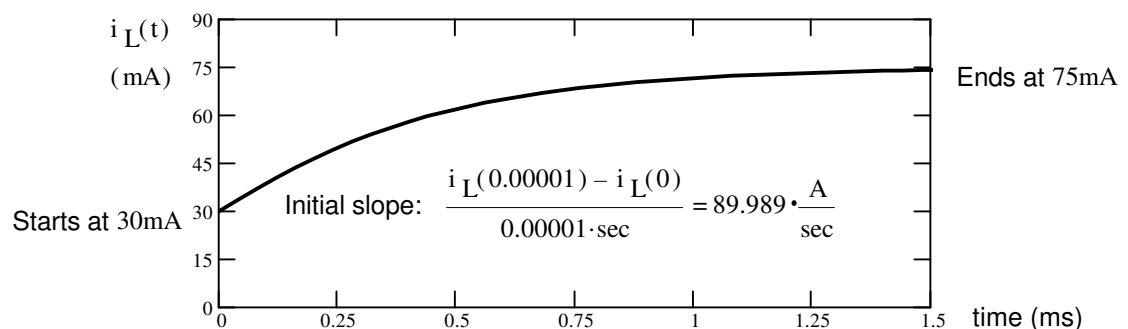Plug numbers back in: $i_L(t) := 75 \cdot \text{mA} - 52.7 \cdot \text{mA} \cdot e^{-2764 t} + 7.69 \cdot \text{mA} \cdot e^{-7236 t}$




ECE 2210 Lecture 18 notes p3

3. Analysis of the circuit shown yields the characteristic equation and s values below. The switch has been in the closed position for a long time and is opened (as shown) at time $t = 0$. Find the initial and final conditions and write the full expression for $v_C(t)$, including all the constants.


$$0 = s^2 + \frac{R_1}{L} \cdot s + \frac{1}{L \cdot C}$$

$$s_1 := (-250 + 10^4 \cdot j) \cdot \frac{1}{\text{sec}}, \quad s_2 := (-250 - 10^4 \cdot j) \cdot \frac{1}{\text{sec}}$$

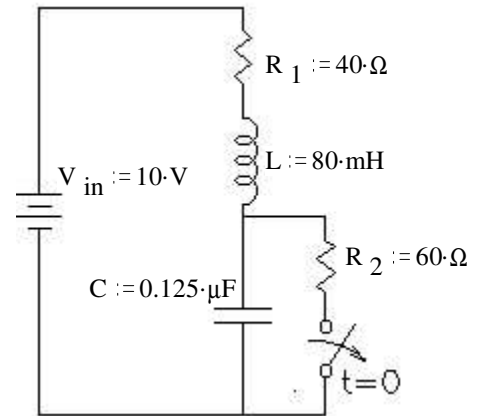
Solution: $\alpha := -250 \cdot \frac{1}{\text{sec}} \quad \omega := 10000 \cdot \frac{\text{rad}}{\text{sec}}$




Initial conditions:

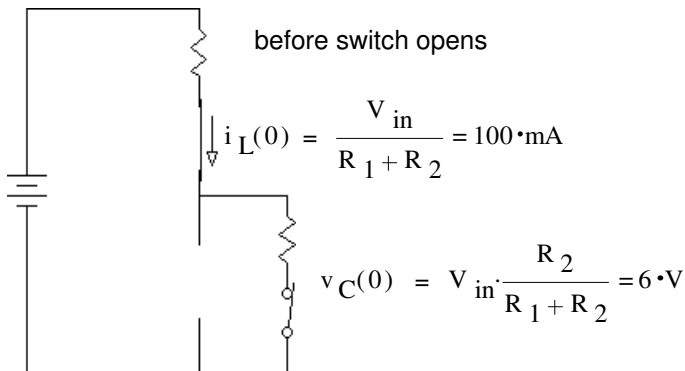

just after the switch opens

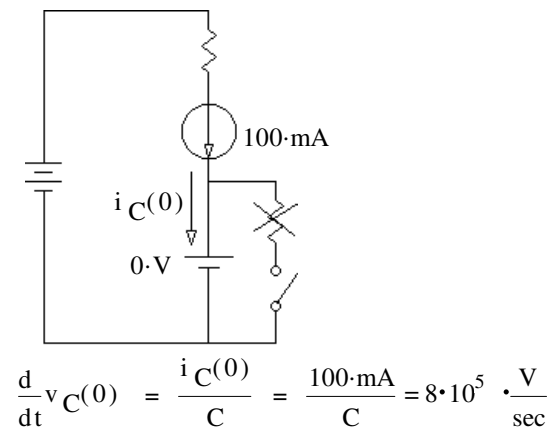

Find final condition:

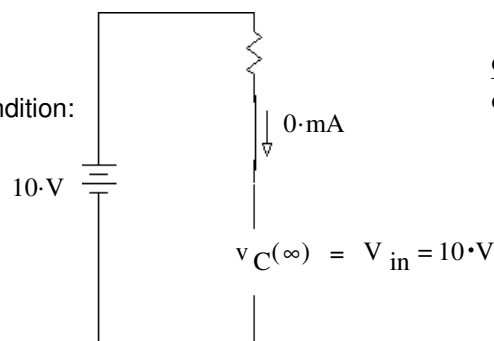

Find constants: $v_C(0) = v_C(\infty) + B \quad B = v_C(0) - v_C(\infty) \quad B := 6 \cdot \text{V} - 10 \cdot \text{V} \quad B = -4 \cdot \text{V}$

$$\frac{d}{dt} v_C(0) = \alpha \cdot B + D \cdot \omega \quad D := \frac{8 \cdot 10^5 \cdot \frac{\text{V}}{\text{sec}} - \alpha \cdot B}{\omega} \quad D = 79.9 \cdot \text{V}$$


Write the full expression for $v_C(t)$, including all the constants that you find.

$$v_C(t) = e^{\alpha t} \cdot (B \cdot \cos(\omega \cdot t) + D \cdot \sin(\omega \cdot t)) + v_C(\infty)$$

$$v_C(t) := e^{-250t} \cdot (-4 \cdot \text{V} \cdot \cos(10^4 \cdot t) + 79.9 \cdot \text{V} \cdot \sin(10^4 \cdot t)) + 10 \cdot \text{V}$$

$$\sqrt{D^2 + B^2} = 80 \cdot \text{V}$$

$v_C(t)$
(volts)

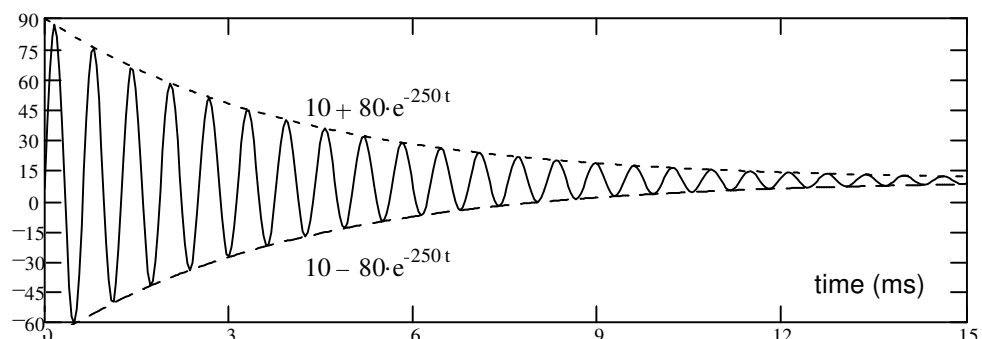

ECE 2210 Lecture 18 notes p4

4. Analysis of a circuit (not pictured) yields the characteristic equation below.

$$0 = s^2 + 400 \cdot s + 400000$$

$$R := 80 \cdot \Omega$$

$$L := 20 \cdot \text{mH}$$

$$C := 2 \cdot \mu\text{F}$$

Further analysis yields the following initial and final conditions:

$$i_L(0) = 120 \cdot \text{mA}$$

$$v_L(0) = -3 \cdot \text{V}$$

$$v_C(0) = 7 \cdot \text{V}$$

$$i_C(0) = -80 \cdot \text{mA}$$

$$i_L(\infty) = 800 \cdot \text{mA}$$

$$v_L(\infty) = 0 \cdot \text{V}$$

$$v_C(\infty) = 12 \cdot \text{V}$$

$$i_C(\infty) = 0 \cdot \text{mA}$$

Write the full expression for $i_L(t)$, including all the constants that you find.

$$i_L(t) = ?$$

Solution: $\frac{400}{2} = 200$ $\frac{\sqrt{400^2 - 4 \cdot 400000}}{2} = 600j$

$$s_1 := (-200 + 600j) \cdot \frac{1}{\text{sec}} \quad \text{and} \quad s_2 := (-200 - 600j) \cdot \frac{1}{\text{sec}}$$

$$\alpha := \text{Re}(s_1)$$

$$\alpha = -200 \cdot \text{sec}^{-1}$$

$$\omega := \text{Im}(s_1)$$

$$\omega = 600 \cdot \text{sec}^{-1}$$

Initial slope: $\frac{d}{dt} i_L(0) = \frac{v_L(0)}{L} = \frac{-3 \cdot \text{V}}{L} = -150 \cdot \frac{\text{A}}{\text{sec}}$

General solution for the underdamped condition: $i_L(t) = i_L(\infty) + e^{\alpha t} \cdot (B \cdot \cos(\omega \cdot t) + D \cdot \sin(\omega \cdot t))$

Find constants: $i_L(0) = i_L(\infty) + B$

$$B = i_L(0) - i_L(\infty)$$

$$B := 120 \cdot \text{mA} - 800 \cdot \text{mA}$$

$$B = -680 \cdot \text{mA}$$

$$\frac{d}{dt} i_L(0) = \alpha \cdot B + D \cdot \omega$$

$$D := \frac{-150 \cdot \frac{\text{A}}{\text{sec}} - \alpha \cdot B}{\omega}$$

$$D = -476.667 \cdot \text{mA}$$

Write the full expression for $i_L(t)$, including all the constants that you find.

$$i_L(t) := 800 \cdot \text{mA} + e^{-200t} \cdot (-680 \cdot \text{mA} \cdot \cos(600 \cdot t) - 477 \cdot \text{mA} \cdot \sin(600 \cdot t))$$

