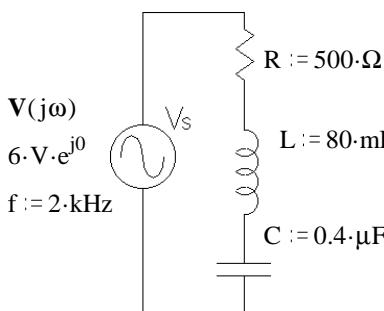


ECE 2210 / 00 Phasor Examples

Ex 1. Find \mathbf{V}_R , \mathbf{V}_L , and \mathbf{V}_C in polar phasor form. $f := 2\text{ kHz}$



$$\mathbf{V}(j\omega)$$

$$6 \cdot V \cdot e^{j0}$$

$$f := 2\text{ kHz}$$

$$\omega := 2 \cdot \pi \cdot f$$

$$\omega = 1.257 \cdot 10^4 \frac{\text{rad}}{\text{sec}}$$

$$\mathbf{Z}_L := j \cdot \omega \cdot L$$

$$\mathbf{Z}_L = 1.005j \cdot k\Omega$$

$$\mathbf{Z}_C := \frac{1}{j \cdot \omega \cdot C}$$

$$\mathbf{Z}_C = -0.199j \cdot k\Omega$$

$$\mathbf{Z}_{\text{eq}} := R + j \cdot \omega \cdot L + \frac{1}{j \cdot \omega \cdot C}$$

$$\mathbf{Z}_{\text{eq}} = 500 + 806.366j \cdot \Omega$$

$$\sqrt{500^2 + 806^2} = 948.491$$

$$\text{atan}\left(\frac{806}{500}\right) = 58.187^\circ$$

$$\mathbf{Z}_{\text{eq}} = 948.5 \Omega \angle 58.2^\circ$$

$$\text{find the current: } \mathbf{I} := \frac{6 \cdot V \cdot e^{j0}}{\mathbf{Z}_{\text{eq}}}$$

$$\text{magnitude: } \frac{6 \cdot V}{948.5 \cdot \Omega} = 6.326 \cdot \text{mA}$$

$$\text{angle: } 0^\circ - 58.2^\circ = -58.2^\circ$$

$$\mathbf{I} = 6.326 \text{mA} \angle -58.2^\circ$$

find the magnitude

find the angle

$$\mathbf{V}_R := \mathbf{I} \cdot R$$

$$6.326 \cdot \text{mA} \cdot 500 \cdot \Omega = 3.163 \cdot \text{V}$$

$$-58.2^\circ + 0^\circ = -58.2^\circ$$

$$\mathbf{V}_R = 3.163 \text{V} \angle -58.2^\circ$$

$$\mathbf{V}_L := \mathbf{I} \cdot \mathbf{Z}_L$$

$$6.326 \cdot \text{mA} \cdot 1005 \cdot \Omega = 6.358 \cdot \text{V}$$

$$-58.2^\circ + 90^\circ = 31.8^\circ$$

$$\mathbf{V}_L = 6.358 \text{V} \angle 31.8^\circ$$

$$\mathbf{V}_C := \mathbf{I} \cdot \mathbf{Z}_C$$

$$6.326 \cdot \text{mA} \cdot (-199) \cdot \Omega = -1.259 \cdot \text{V}$$

$$-58.2^\circ + (90^\circ) = 31.8^\circ$$

$$\mathbf{V}_C = -1.259 \text{V} \angle 31.8^\circ$$

$$\text{OR: } 6.326 \cdot \text{mA} \cdot (199) \cdot \Omega = 1.259 \cdot \text{V}$$

$$-58.2^\circ + (-90^\circ) = -148.2^\circ$$

$$\mathbf{V}_C = 1.259 \text{V} \angle -148.2^\circ$$

OR, you can also find these voltages directly, using a voltage divider. I.E. to find \mathbf{V}_C directly:

$$\mathbf{V}_C := \frac{\frac{1}{j \cdot \omega \cdot C}}{R + j \cdot \omega \cdot L + \frac{1}{j \cdot \omega \cdot C}} \cdot 6 \cdot V = \frac{1}{R \cdot (j \cdot \omega \cdot C) + j \cdot \omega \cdot L \cdot (j \cdot \omega \cdot C) + 1} \cdot 6 \cdot V = \frac{1}{R \cdot (j \cdot \omega \cdot C) - \omega^2 \cdot L \cdot C + 1} \cdot 6 \cdot V$$

$$= \frac{1}{(1 - \omega^2 \cdot L \cdot C) + j \cdot \omega \cdot R \cdot C} \cdot 6 \cdot V \quad (1 - \omega^2 \cdot L \cdot C) = -4.053 \quad j \cdot \omega \cdot R \cdot C = 2.513j$$

$$= \frac{6 \cdot V}{-4.053 + 2.513j} \cdot \frac{(-4.053 - 2.513j)}{(-4.053 - 2.513j)} = \frac{6 \cdot V \cdot (-4.053 - 2.513j)}{(-4.053)^2 + 2.513^2}$$

$$6 \cdot V \cdot (-4.053 - 2.513j) = -24.318 - 15.078j \text{ V}$$

$$(-4.053)^2 + 2.513^2 = 22.742$$

$$= \left(\frac{-24.318}{22.742} - \frac{15.078j}{22.742} \right) \cdot V = -1.069 - 0.663j \text{ V}$$



$$\text{magnitude: } \sqrt{1.069^2 + 0.663^2} = 1.258$$

$$\text{angle: } \text{atan}\left(\frac{-0.663}{-1.069}\right) = 31.81^\circ$$

but this is actually in the third quadrant,
so modify your calculator's results:

$$31.81^\circ \cdot \text{deg} - 180^\circ \cdot \text{deg} = -148.19^\circ$$


$$= 1.258 \text{V} \angle -148.2^\circ$$

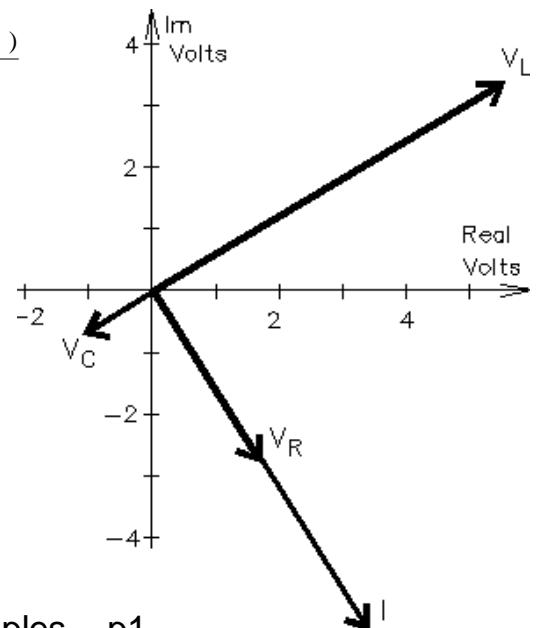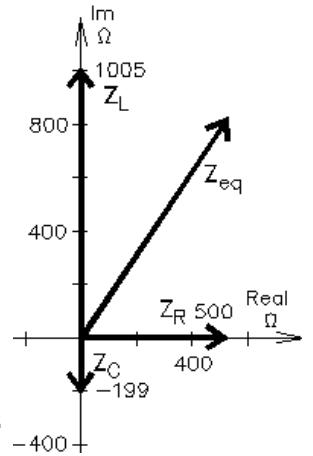

ECE 2210 / 00 Phasor Examples p2

Ex 2. a) Find Z_{eq} . $f := 2.5 \cdot kHz$ $\omega := 2 \cdot \pi \cdot f$ $\omega = 1.571 \cdot 10^4 \frac{\text{rad}}{\text{sec}}$
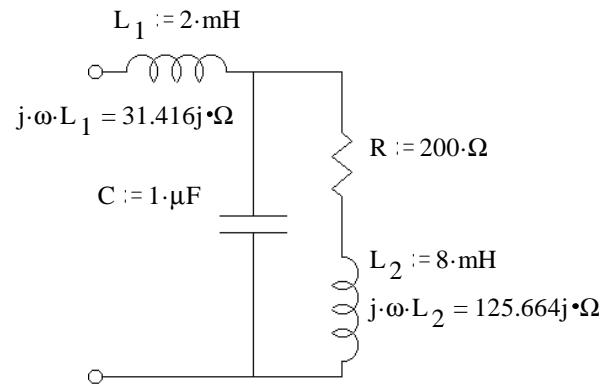
$$Z_{eq} = j \cdot \omega \cdot L_1 + \frac{1}{\frac{1}{j \cdot \omega \cdot C} + \frac{1}{R + j \cdot \omega \cdot L_2}}$$



But it's easier to split the problem up

Left branch

$$Z_I := \frac{1}{j \cdot \omega \cdot C} \quad Z_I = -63.662j \cdot \Omega$$

$$\frac{1}{\left(\frac{1}{j \cdot \omega \cdot C}\right)} = j \cdot \omega \cdot C = 0.01571i \cdot \frac{1}{\Omega}$$

Right branch

$$Z_r := j \cdot \omega \cdot L_2 + R \quad Z_r = 200 + 125.664j \cdot \Omega$$

$$\frac{1}{200 + 125.664j} = 3.585 \cdot 10^{-3} - 2.252 \cdot 10^{-3}j$$

$$\text{denominator: } j \cdot \omega \cdot C + \frac{1}{R + j \cdot \omega \cdot L_2} = 0.01571 \cdot j + (3.585 \cdot 10^{-3} - 2.252 \cdot 10^{-3}j) = 3.585 \cdot 10^{-3} + 1.346 \cdot 10^{-2}i \quad \frac{1}{\Omega}$$

rectangular division:

$$\frac{1}{(3.585 \cdot 10^{-3} + 1.346 \cdot 10^{-2}i)} \cdot \frac{(3.585 \cdot 10^{-3} - 1.346 \cdot 10^{-2}i)}{(3.585 \cdot 10^{-3} - 1.346 \cdot 10^{-2}i)} = \frac{3.585 \cdot 10^{-3} - 1.346 \cdot 10^{-2}i}{1.94 \cdot 10^{-4}} = 18.479 - 69.381j \quad \Omega$$

$$(3.585 \cdot 10^{-3})^2 + (1.346 \cdot 10^{-2})^2 = 1.94 \cdot 10^{-4}$$

$$\text{add: } j \cdot \omega \cdot L_1 = 31.416j \cdot \Omega \quad 31.416j + (18.479 - 69.381j) = 18.479 - 37.965j \quad \Omega$$

$$\text{convert to polar (if needed): } \sqrt{18.48^2 + 37.97^2} = 42.228 \quad \text{atan}\left(\frac{-37.97}{18.48}\right) = -64.048 \cdot \text{deg} \quad Z_{eq} = 42.23 \Omega \angle -64.05^\circ$$

Another Way

Sometimes you might simplify a little before putting in numbers.

$$Z_{eq} := j \cdot \omega \cdot L_1 + \frac{1}{\frac{1}{R + j \cdot \omega \cdot L_2} + \frac{1}{j \cdot \omega \cdot C}} = j \cdot \omega \cdot L_1 + \frac{1}{\frac{1}{R + j \cdot \omega \cdot L_2} + j \cdot \omega \cdot C} = j \cdot \omega \cdot L_1 + \frac{R + j \cdot \omega \cdot L_2}{1 + j \cdot \omega \cdot C \cdot (R + j \cdot \omega \cdot L_2)}$$

$$= j \cdot \omega \cdot L_1 + \frac{R + j \cdot \omega \cdot L_2}{1 - \omega^2 \cdot C \cdot L_2 + j \cdot \omega \cdot C \cdot R}$$

$$Z_{eq} = 31.416 \cdot j \cdot \Omega + \frac{(200 + 125.664 \cdot j) \cdot \Omega}{-0.974 + 3.142 \cdot j} \cdot \frac{(-0.974 - 3.142 \cdot j)}{(-0.974 - 3.142 \cdot j)} = 31.416 \cdot j \cdot \Omega + \frac{(200 + 125.664 \cdot j) \cdot (-0.974 - 3.142 \cdot j)}{0.974^2 + 3.142^2}$$

$$= 31.416 \cdot j \cdot \Omega + \frac{((200 \cdot -0.974) - 125.664 \cdot (-3.142)) + (125.664 \cdot -0.974) - 200 \cdot 3.142 \cdot j) \cdot \Omega}{0.974^2 + 3.142^2}$$

$$= 31.416 \cdot j \cdot \Omega + \frac{(200.036288 - 750.796736 \cdot j) \cdot \Omega}{10.82084} = 31.416 \cdot j \cdot \Omega + 18.486 \cdot \Omega - 69.384 \cdot j \cdot \Omega = 18.486 - 37.968j \cdot \Omega$$

$$\sqrt{18.49^2 + 37.97^2} = 42.233 \quad \text{atan}\left(\frac{-37.97}{18.49}\right) = -64.036 \cdot \text{deg} \quad Z_{eq} = 42.23 \Omega \angle -64.04^\circ$$

b) $V_{in} := 12 \cdot V \cdot e^{j \cdot 20^\circ \text{deg}}$ Find I_{L1} , V_C $I_{L1} := \frac{V_{in}}{Z_{eq}}$ $\frac{12 \cdot V}{42.23 \cdot \Omega} = 284.16 \cdot \text{mA}$ $20^\circ \text{deg} - (-64.04)^\circ \text{deg} = 84.04^\circ \text{deg}$
 $I_{L1} = 284 \text{mA} / 84.04^\circ$

$$V_C := I_{L1} \cdot (18.479 - 69.381 \cdot j) \cdot \Omega \quad 284 \cdot \text{mA} \cdot \sqrt{18.479^2 + 69.381^2} \cdot \Omega = 20.391 \cdot V$$

$$84.04^\circ \text{deg} + \text{atan}\left(\frac{-69.381}{18.479}\right) = 8.954^\circ \text{deg} \quad V_C = 20.4V / 8.95^\circ$$

convert to rectangular (if needed): $20.391 \cdot V \cdot \cos(8.954^\circ \text{deg}) = 20.143 \cdot V$
 $20.391 \cdot V \cdot \sin(8.954^\circ \text{deg}) = 3.174 \cdot V$

$$V_C = 20.14 + 3.174 \cdot j \cdot V$$

Another Way

To find V_C directly:

$$V_C := \frac{\frac{1}{R + j \cdot \omega \cdot L_2}}{\frac{1}{j \cdot \omega \cdot L_1} + \frac{1}{R + j \cdot \omega \cdot C}} \cdot V_{in}$$

--> math --> $V_C = 20.153 + 3.178j \cdot V$ Same but for a little roundoff difference

c) Let's find I_{L2} . $Z_r = 200 + 125.664j \cdot \Omega \quad \sqrt{200^2 + 125.664^2} = 236.202 \quad \text{atan}\left(\frac{125.664}{200}\right) = 32.142^\circ \text{deg}$

$$I_{L2} := \frac{V_C}{Z_r} = \frac{20.4 \cdot V \cdot e^{j \cdot 8.95^\circ \text{deg}}}{236.202 \cdot \Omega \cdot e^{j \cdot 32.142^\circ \text{deg}}} = \frac{20.4 \cdot V}{236.202 \cdot \Omega} / 8.95 - 32.142^\circ = 86.4 \text{mA} / -23.19$$

Another Way

Directly by Current divider: $I_{L2} := \frac{\frac{1}{R + j \cdot \omega \cdot L_2}}{\frac{1}{j \cdot \omega \cdot C} + \frac{1}{R + j \cdot \omega \cdot L_2}} \cdot I_{L1} = \frac{1}{j \cdot \omega \cdot C \cdot (R + j \cdot \omega \cdot L_2) + 1} \cdot I_{L1} = \frac{I_{L1}}{1 - \omega^2 \cdot C \cdot L_2 + j \cdot \omega \cdot C \cdot R}$

denominator: $\sqrt{(1 - \omega^2 \cdot C \cdot L_2)^2 + (\omega \cdot C \cdot R)^2} = 3.289 \quad \text{atan}\left(\frac{\omega \cdot C \cdot R}{1 - \omega^2 \cdot C \cdot L_2}\right) + 180^\circ \text{deg} = 107.224^\circ \text{deg}$

$$I_{L2} = \frac{284 \cdot \text{mA} \cdot e^{j \cdot 84.04^\circ \text{deg}}}{3.289 \cdot e^{j \cdot 107.224^\circ \text{deg}}} = \frac{284 \cdot \text{mA}}{3.289} / 84.04 - 107.224^\circ = 86.4 \text{mA} / -23.18^\circ$$

d) How about I_C ? $I_C := \frac{V_C}{\left(\frac{1}{j \cdot \omega \cdot C}\right)} = V_C \cdot j \cdot \omega \cdot C = 20.4V / 8.95^\circ \cdot 0.015708 / 90^\circ \cdot \frac{1}{\Omega} = 320 \text{mA} / 98.95^\circ$

Another Way Could also be found directly by current divider: $I_C := \frac{j \cdot \omega \cdot C}{j \cdot \omega \cdot C + \frac{1}{R + j \cdot \omega \cdot L_2}} \cdot I_{L1} = 320 \text{mA} / 98.95^\circ$

Something Weird

I_C is greater than the input current (I_{L1}). What's going on?

The angle between I_C & I_{L2} is big enough that they somewhat cancel each other out (partially resonate). ?

Check Kirchoff's Current Law: $I_C + I_{L2} = 29.485 + 282.569j \cdot \text{mA} = I_{L1} = 29.485 + 282.569j \cdot \text{mA}$
yes

ECE 2210 / 00 Phasor Examples p4

Ex 3. a) Find Z_2 .


$$I := 25 \cdot \text{mA} \cdot e^{j \cdot 10^\circ}$$

$$V_{\text{in}} := 10 \cdot \text{V} \cdot e^{-j \cdot 20^\circ}$$

$$Z_T := \frac{V_{\text{in}}}{I} = \frac{10 \cdot \text{V}}{25 \cdot \text{mA}} \underline{-20 - 10^\circ} = 400 \Omega \underline{-30^\circ}$$

$$Z_T = 346.41 - 200j \cdot \Omega$$
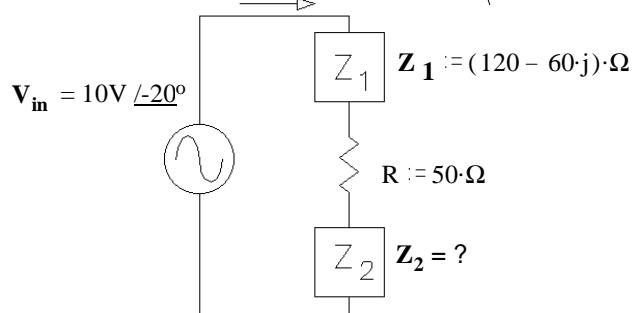
$$i(t) = 25 \cdot \text{mA} \cdot \cos \left(377 \cdot \frac{\text{rad}}{\text{sec}} \cdot t + 10^\circ \right)$$



$$Z_2 := Z_T - R - Z_1 = (346.41 - 200j) \cdot \Omega - 50 \cdot \Omega - (120 - 60j) \cdot \Omega = 176.41 - 140j \cdot \Omega$$

- b) Circle 1: i) The source current leads the source voltage
ii) The source voltage leads the source current

<--- answer, because $10^\circ > -20^\circ$.

Ex 4. a) Find V_{in} in polar form.

$$I_Z := 100 \cdot \text{mA}$$

$$Z := (80 - 60j) \cdot \Omega$$


$$\omega := 1000 \cdot \frac{\text{rad}}{\text{sec}}$$

$$V_{\text{in}} := I_Z \cdot Z$$

$$V_{\text{in}} = 8 - 6j \cdot \text{V}$$

$$\sqrt{8^2 + 6^2} = 10 \quad \text{atan}\left(\frac{-6}{8}\right) = -36.87^\circ$$
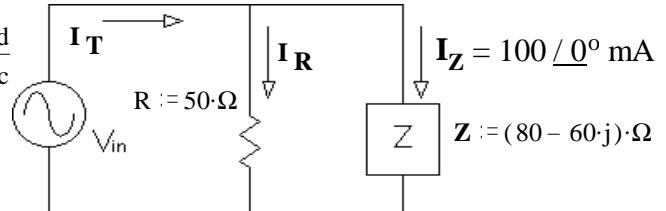
$$V_{\text{in}} = 10 \text{V} \underline{-36.9^\circ}$$



- b) Find I_T in polar form. $I_R := \frac{V_{\text{in}}}{R} = \frac{10 \cdot \text{V}}{50 \cdot \Omega} \underline{-36.9^\circ} = \frac{10 \cdot \text{V}}{50 \cdot \Omega} \cdot \cos(-36.9^\circ) + j \cdot \frac{10 \cdot \text{V}}{50 \cdot \Omega} \cdot \sin(-36.9^\circ) = 160 - 120j \cdot \text{mA}$

$$I_T := I_R + I_Z = (160 - 120j) \cdot \text{mA} + 100 \cdot \text{mA} = 260 - 120j \cdot \text{mA}$$

$$\sqrt{260^2 + 120^2} = 286.356 \quad \text{atan}\left(\frac{-120}{260}\right) = -24.78^\circ \quad I_T = 286 \text{mA} \underline{-24.8^\circ}$$

- c) Circle 1: i) The source current leads the source voltage
ii) The source voltage leads the source current

answer i), $-24.8^\circ > -36.9^\circ$


d) The impedance Z (above) is made of two components in series. What are they and what are their values?

$$Z = 80 - 60j \cdot \Omega$$

Must have a resistor because there is a real part.

$$R := \text{Re}(Z)$$


$$R = 80 \cdot \Omega$$

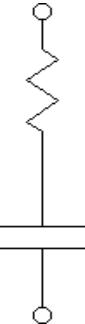

Must have a capacitor because the imaginary part is negative.

$$\text{Im}(Z) = -60 \cdot \Omega = \frac{-1}{\omega \cdot C} \quad C := \frac{-1}{\omega \cdot \text{Im}(Z)}$$

$$C = 16.667 \cdot \mu\text{F}$$

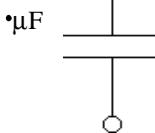

ECE 2210 / 00 Phasor Examples p5

Ex 5. The impedance $Z = 80 - 60j \Omega$ is made of two components in parallel. What are they and what are their values?

Must have a resistor because there is a real part.

Must have an capacitor because the imaginary part is negative.

$$Z = \frac{1}{\frac{1}{R} + j \cdot \omega \cdot C}$$

$$\frac{1}{Z} = \frac{1}{(80 - 60j) \cdot \Omega} \cdot \left(\frac{80 + 60j}{80 + 60j} \right) = \frac{80 + 60j}{80^2 + 60^2} = \frac{80 + 60j}{10,000} \frac{1}{\Omega}$$

$$\frac{1}{Z} = 0.008 + 0.006i \cdot \Omega^{-1} = \frac{1}{R} + j \cdot \omega \cdot C$$

$$\frac{1}{R} = .008 \cdot \frac{1}{\Omega}$$


$$R := \frac{1}{.008 \cdot \Omega^{-1}}$$

$$R = 125 \Omega$$

$$\omega \cdot C = .006 \cdot \frac{1}{\Omega}$$

$$C := \frac{.006 \cdot \Omega^{-1}}{\omega}$$

$$C = 6 \mu F$$

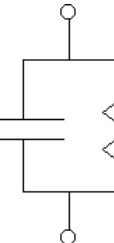

$$R = 125 \Omega$$

Positive imaginary parts would require inductors


Ex 6. a) Find I_1

$$\omega := 20000 \frac{\text{rad}}{\text{sec}}$$

$$V_{in} := 20 \cdot V \cdot e^{j \cdot 30\text{-deg}}$$

$$I_1 := \frac{V_{in}}{R} = \frac{20 \cdot V}{250 \cdot \Omega} \cdot e^{j \cdot 30\text{-deg}} = 80 \cdot \text{mA} \cdot e^{j \cdot 30\text{-deg}}$$

polar division

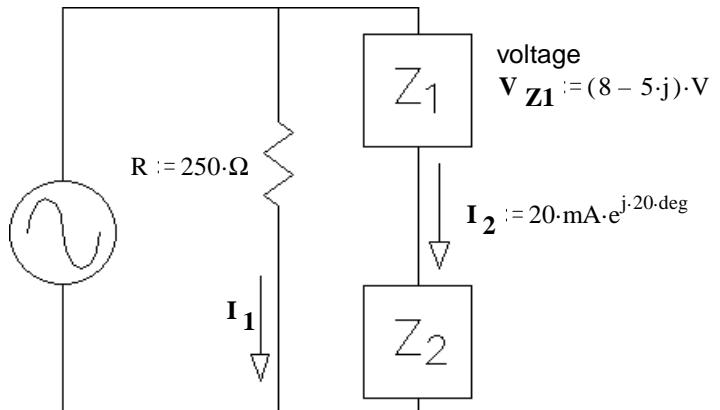

b) Circle 1:

i) V_{in} leads I_2

ii) V_{in} lags I_2

Why? Show numbers: 30 > 20

 <

c) Find Z_2 in polar form

Convert V_{in} to rectangular coordinates

$$20 \cdot V \cdot \cos(30\text{-deg}) = 17.321 \cdot V$$

$$20 \cdot V \cdot \sin(30\text{-deg}) = 10 \cdot V$$

pol to rect

$$V_{in} = 17.321 + 10j \cdot V$$

$$V_{Z2} := V_{in} - V_{Z1}$$

$$V_{Z2} = 9.321 + 15j \cdot V$$

subtract

$$\text{rect to pol} \quad \sqrt{9.321^2 + 15^2} = |V_{Z2}| = 17.66 \cdot V$$

$$\tan\left(\frac{15}{9.321}\right) = \arg(V_{Z2}) = 58.145 \cdot \text{deg}$$

$$\text{div } Z_2 := \frac{V_{Z2}}{I_2} = \frac{17.66 \cdot V}{20 \cdot \text{mA}} = 883 \cdot \Omega \quad / \quad 58.145 \cdot \text{deg} - 20 \cdot \text{deg} = 38.145 \cdot \text{deg} \quad Z_2 = 883 \angle 38.145^\circ \Omega$$

$$Z_2 = 694.436 + 545.379j \cdot \Omega$$


Ex 7. You need to design a circuit in which the "output" voltage leads the input voltage ($v_S(t)$) by 40° of phase.

a) What should go in the box: R, L, C?

$$V_o = \frac{Z_{\text{box}}}{R + Z_{\text{box}}} \cdot V_S$$

$$\text{angle of } \frac{Z_{\text{box}}}{R + Z_{\text{box}}} \text{ is } 40^\circ.$$

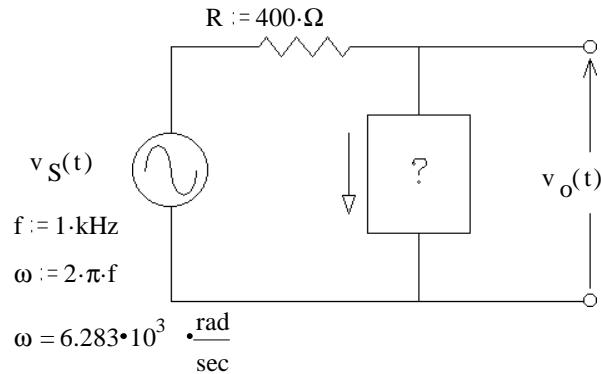This can only happen if the angle of Z_{box} is positive, so Z_{box} is a inductor



b) Find its value. $V_o = \frac{j \cdot \omega \cdot L}{R + j \cdot \omega \cdot L} \cdot V_S$ angle $\frac{j \cdot \omega \cdot L}{R + j \cdot \omega \cdot L}$ is $90 - \tan^{-1}\left(\frac{\omega \cdot L}{R}\right) = 40^\circ$.

$$\text{So: } \tan^{-1}\left(\frac{\omega \cdot L}{R}\right) = 50^\circ \quad \frac{\omega \cdot L}{R} = \tan(50 \cdot \text{deg}) = 1.192 \quad L = \frac{R \cdot 1.192}{\omega} = 75.9 \cdot \mu\text{H}$$

c) Repeat if the "output" voltage should lag the input voltage ($v_S(t)$) by 20° of phase.


$$\text{angle of } \frac{Z_{\text{box}}}{R + Z_{\text{box}}} \text{ is } -20^\circ. \quad \text{This can only happen if the angle of } Z_{\text{box}} \text{ is negative, so } Z_{\text{box}} \text{ is a capacitor}$$

$$V_o = \frac{\frac{1}{j \cdot \omega \cdot C}}{R + \frac{1}{j \cdot \omega \cdot C}} \cdot V_S \quad \text{angle } \frac{\frac{1}{j \cdot \omega \cdot C}}{R + \frac{1}{j \cdot \omega \cdot C}} \text{ is } -90 - \tan^{-1}\left(-\frac{1}{\omega \cdot C \cdot R}\right) = -90 - \tan^{-1}\left(-\frac{1}{\omega \cdot C \cdot R}\right)$$

$$\tan^{-1}\left(-\frac{1}{\omega \cdot C \cdot R}\right) = -70^\circ. \quad -\frac{1}{\omega \cdot C \cdot R} = \tan(-70 \cdot \text{deg}) = -2.747 \quad C = \frac{1}{\omega \cdot R \cdot 2.747} = 0.145 \cdot \mu\text{F}$$

Ex 8. Find V_o in the circuit shown. Express it as a magnitude and phase angle (polar).
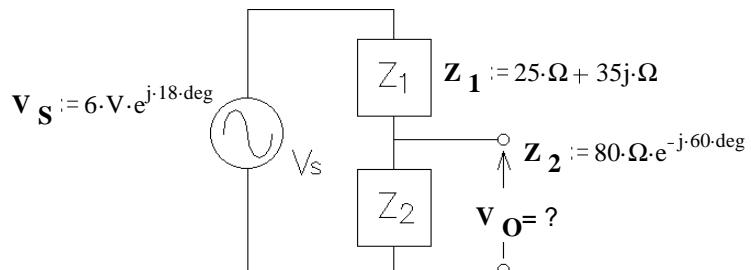
$$V_o = \frac{Z_2}{Z_1 + Z_2} \cdot V_S \quad \text{Simple voltage divider}$$



$$|Z_2| \cdot \cos(-60^\circ) = 40 \cdot \Omega$$

$$|Z_2| \cdot \sin(-60^\circ) = -69.282 \cdot \Omega$$

$$Z_2 = 40 - 69.282j \cdot \Omega$$

$$Z_1 + Z_2 = 25 \cdot \Omega + 35j \cdot \Omega + 40 \cdot \Omega - 69.282 \cdot j \cdot \Omega = 65 - 34.282j \cdot \Omega = 73.486 \cdot \Omega \cdot e^{-j27.81^\circ}$$

$$V_o = \frac{Z_2}{Z_1 + Z_2} \cdot V_S = \frac{80 \cdot \Omega \cdot e^{-j60^\circ}}{73.486 \cdot \Omega \cdot e^{-j27.81^\circ}} \cdot (6 \cdot V \cdot e^{j18^\circ}) = \frac{80 \cdot \Omega}{73.486 \cdot \Omega} \cdot 6 \cdot V \cdot e^{j(-60 - (-27.81) + 18)^\circ} = 6.53 \cdot V \cdot e^{-j14.2^\circ}$$