

The 2nd exam will include this material

Read about phasors in your book (chapter 4 in the textbook).

1. For the complex numbers $z_1 := -4 + 5j$ and $z_2 := 2 + 4j$ Determine the following

a) Does $|z_1 \cdot z_2|$ equal $|z_1| \cdot |z_2|$?

b) Does $\frac{|z_1|}{|z_2|}$ equal $\frac{z_1}{z_2}$?

c) Does $|z_1 + z_2|$ equal $|z_1| + |z_2|$?

2. a) Find the phasor for $v(t) = 8.4 \cdot \cos(100t - 90\text{-deg})$ Express in both forms, polar and rectangular.

- b) The phasor representation of a current is $I := (5 + j \cdot 12) \cdot \mu\text{A}$ Find the time-domain representation, $i(t)$. $f := 600 \cdot \text{Hz}$

3. Add or subtract the sinusoidal voltages using phasors. Draw a phasor diagram which shows all 3 phasors, and give your final answer in time domain form.

a) $v_1(t) = 1.5 \cdot V \cdot \cos(\omega t + 10\text{-deg})$ $v_2(t) = 3.2 \cdot V \cdot \cos(\omega t + 25\text{-deg})$ Find $v_3(t) = v_1(t) + v_2(t)$

b) $v_1(t) = 1.5 \cdot V \cdot \cos(\omega t + 10\text{-deg})$ $v_2(t) = 3.2 \cdot V \cdot \cos(\omega t + 25\text{-deg})$ Find $v_4(t) = v_1(t) - v_2(t)$

you may add V_4 to the phasor diagram you've already drawn for part a).

c) $v_1(t) = 50 \cdot V \cdot \cos(\omega t - 60\text{-deg})$ $v_2(t) = 24 \cdot V \cdot \cos(\omega t + 15\text{-deg})$ Find $v_3(t) = v_1(t) + v_2(t)$

d) $v_1(t) = 0.9 \cdot V \cdot \cos(\omega t + 72\text{-deg})$ $v_2(t) = 1.2 \cdot V \cdot \cos(\omega t - 20\text{-deg})$ Find $v_3(t) = v_1(t) + v_2(t)$

e) $v_1(t) = 0.9 \cdot V \cdot \cos(\omega t + 72\text{-deg})$ $v_2(t) = 1.2 \cdot V \cdot \cos(\omega t - 20\text{-deg})$ Find $v_4(t) = v_2(t) - v_1(t)$

you may add V_4 to the phasor diagram you've already drawn for part d).

4. Express the impedance of a 5.2mH inductor at 60 Hz in polar form?





5. a) A capacitor impedance has a magnitude of 240Ω at a frequency of 1.8kHz. What is the value of capacitor?

- b) What value inductor has the same impedance magnitude at the same frequency?

- c) Find the reactance (magnitude of the impedance with + or - sign) of this capacitor and this inductor at 3.6kHz?

- d) What would be the total impedance of this inductance and this capacitance connected in series at 2.7kHz?

6. Find Z_{eq} in each case.

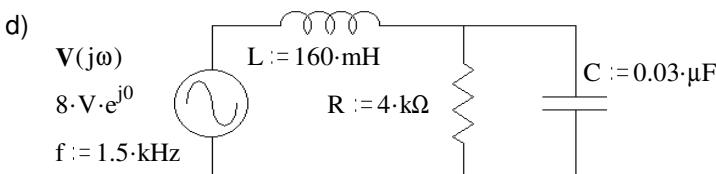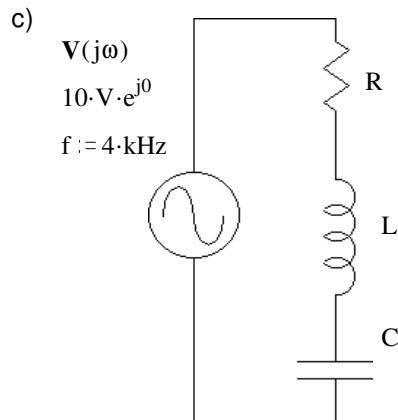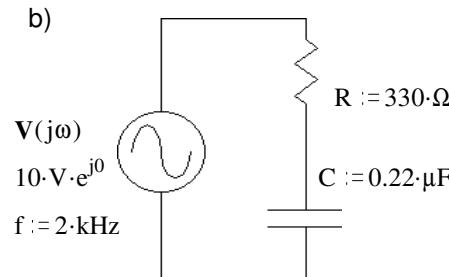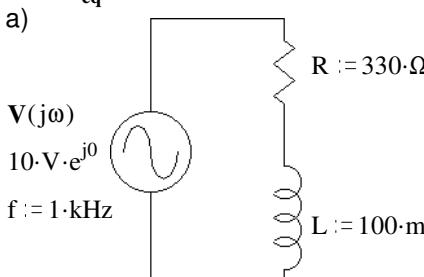


7. Find the current $I(j\omega)$ in each case above.

8. a) Find Z . Hint: Find the total impedance ($R+Z$) first.

b) Which leads, current or voltage?

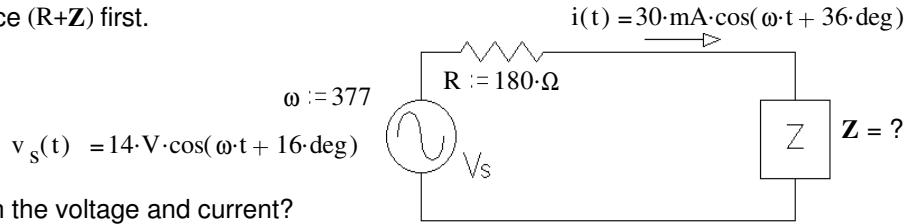c) By how much?
I.E. what is the phase angle between the voltage and current?




9. a) A resistor and a capacitor are connected in series to create an impedance of $Z := 50 \cdot \Omega \cdot e^{-j66\text{deg}} = 50\Omega/-66^\circ$ at a frequency $f := 3\text{-kHz}$ Find R and C .

b) A resistor and a capacitor are connected in parallel to create an impedance of $Z := 50 \cdot \Omega \cdot e^{-j66\text{deg}} = 50\Omega/-66^\circ$ at a frequency $f := 3\text{-kHz}$ Find R and C .


$$\text{Hint: invert } Z_{\text{eq}}, \text{ Instead of solving this: } 50/-66\text{deg} = \frac{1}{\frac{1}{R} + j\omega C} \quad \text{solve this: } \frac{1}{Z_{\text{eq}}} = 0.02/66\text{deg} = \frac{1}{R} + j\omega C$$

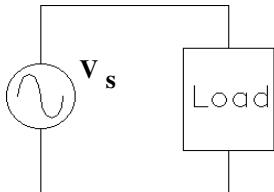10. The phasor diagram at right shows the voltage and current in the circuit below



Assume the load consists of a resistor in series with a reactive component and the frequency is 60 Hz.

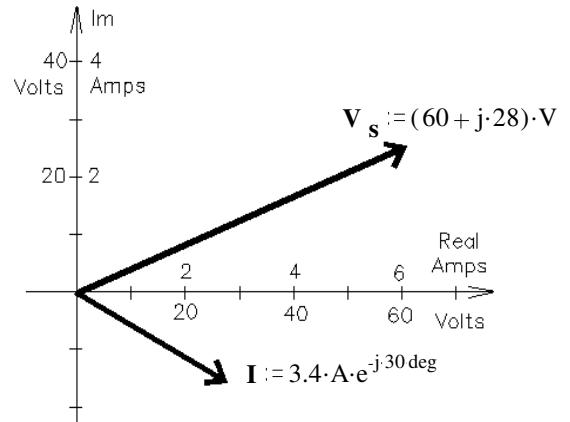- a) What is the magnitude of the impedance?
b) What is the value of the resistor?
c) What is the reactive component (type and value)?



11. For the circuit shown, draw a phasor diagram showing \mathbf{V}_s , \mathbf{I} , \mathbf{V}_R , and \mathbf{V}_C . Draw the voltages to scale so that you can show that they obey KVL.

Answers

1. a) $28.636 = 28.636$ Yes b) $1.432 = 1.432$ Yes
c) $9.22 \text{ not} = 10.875$ No

2. a) $8.4/-90^\circ = 8.4 \cdot e^{-j90\text{deg}} = -8.4j$ b) $13 \cdot \mu\text{A} \cdot \cos(3770 \cdot t + 67.4 \cdot \text{deg})$

3. a) $v_1(t) + v_2(t) = 4.67 \cdot \cos(\omega \cdot t + 20.2 \cdot \text{deg}) \cdot \text{V}$
b) $v_1(t) - v_2(t) = 1.794 \cdot \cos(\omega \cdot t - 142.5 \cdot \text{deg}) \cdot \text{V}$
d) $v_1(t) + v_2(t) = 1.48 \cdot \cos(\omega \cdot t + 17.6 \cdot \text{deg}) \cdot \text{V}$
c) $v_1(t) - v_2(t) = 60.8 \cdot \cos(\omega \cdot t - 37.6 \cdot \text{deg}) \cdot \text{V}$
e) $v_2(t) - v_1(t) = 1.525 \cdot \cos(\omega \cdot t - 56.15 \cdot \text{deg}) \cdot \text{V}$

4. $1.96 \Omega/90^\circ$ 5. a) $0.368 \cdot \mu\text{F}$ b) $21.2 \cdot \text{mH}$ c) $-120 \cdot \Omega$ d) $480 \cdot \Omega$ d) $200 \cdot j \cdot \Omega$


6. a) $(330 + 628.3 \cdot j) \cdot \Omega = 709.7 \Omega/62.29^\circ$
b) $(330 - 361.7 \cdot j) \cdot \Omega = 489.6 \Omega/-47.63^\circ$

7. a) $(6.6 - 12.5 \cdot j) \cdot \text{mA} = 14.1 \text{mA}/-62.29^\circ$
b) $(13.8 + 15.1 \cdot j) \cdot \text{mA} = 20.4 \text{mA}/47.63^\circ$
d) $4.4 \text{mA}/15.2^\circ$

8. a) $259 - 160 \cdot j$ b) The current leads the voltage c) 20°

9. a) $20.34 \cdot \Omega$ b) $1.16 \cdot \mu\text{F}$ b) $123 \cdot \Omega$ 0.969 $\cdot \mu\text{F}$

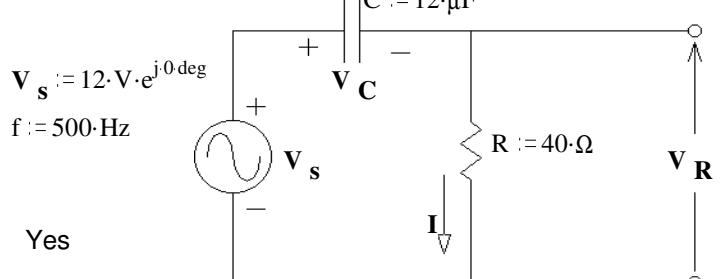10. a) $19.5 \cdot \Omega$ b) $11.2 \cdot \Omega$ c) inductor 42.3 $\cdot \text{mH}$



$$\text{c)} \quad \frac{10 \cdot \text{V}}{\sqrt{R^2 + \left(\omega \cdot L - \frac{1}{\omega \cdot C}\right)^2}}$$

$$\text{angle: } -\text{atan}\left(\frac{\omega \cdot L - \frac{1}{\omega \cdot C}}{R}\right)$$

