


## ECE 2210 Homework #20

c

Note: In the following problems, you may assume voltages and currents are RMS unless stated otherwise or given as a function of time.


- Read the section on AC power in your book (section 6.2, p 288 in the textbook).
- Compute the power factor for an inductive load consisting of  $L := 20\text{ mH}$  and  $R := 6\text{ }\Omega$  in series.  $\omega := 377\frac{\text{rad}}{\text{s}}$
- The complex power consumed by a load is  $620\angle 29^\circ\text{ VA}$ . Find:
  - Apparent power (as always, give the correct units).
  - Real power.
  - Reactive power.
  - Power factor.
  - Is the power factor leading or lagging?
  - Draw a phasor diagram.
- In the circuit shown, the voltmeter measures 120V, the ammeter measures 6.3A and the wattmeter measures 560W. The load consists of a resistor and an inductor. The frequency is 60Hz. Find the following:
  - Power factor
  - Leading or lagging?
  - Real power.
  - Apparent power.
  - Reactive power.
  - Draw a phasor diagram.

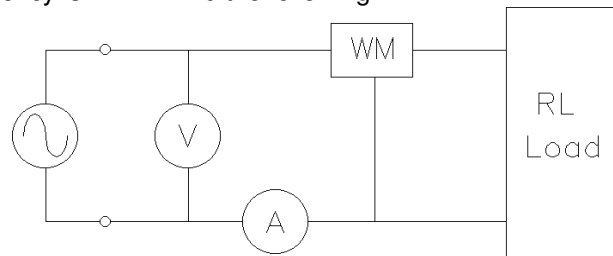g) The load is in a box which cannot be opened. Add another component to the circuit above to correct the power factor (make  $\text{pf} = 1$ ). Draw the correct component in the correct place and find its value. This component should not affect the real power consumption of the load.



- For the circuit shown, find the following: (as always, give the correct units)

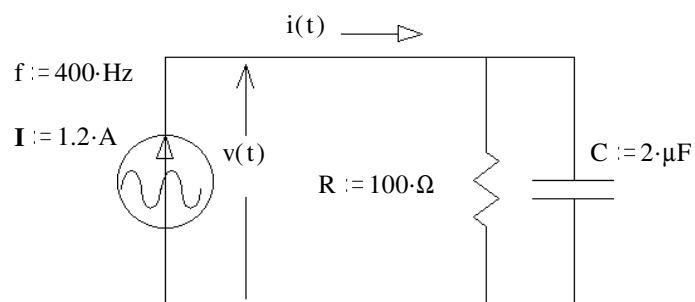
- The complex power.
- Real power.
- Reactive power.
- Apparent power.
- Draw a power phasor diagram.



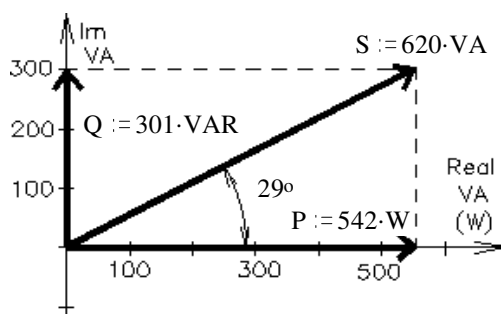
### Answers

- $\text{pf} := 0.623$


- $620\text{ VA}$
  - $542\text{ W}$
  - $301\text{ VAR}$
  - $0.875$
  - lagging
  - >



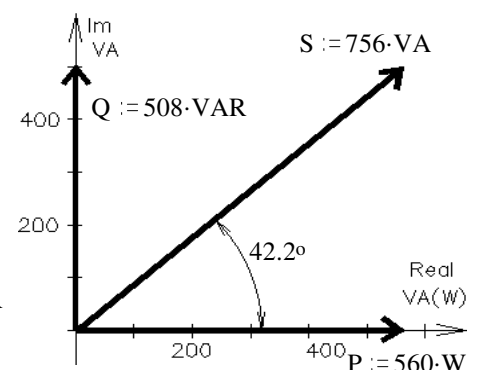- $0.741$
  - lagging
  - $560\text{ W}$
  - $756\text{ VA}$
  - $508\text{ VAR}$
  - >



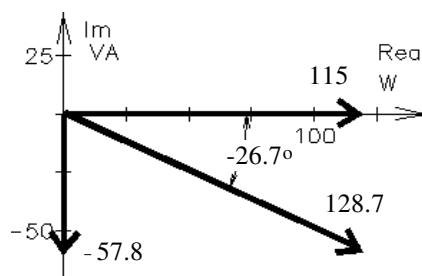- $(115 - 57.8j)\text{ VA}$
  - $115\text{ W}$
  - $-57.8\text{ VAR}$
  - $128.7\text{ VA}$
  - >



- $93.6\text{ }\mu\text{F}$  capacitor in parallel with load

