

3rd exam will include this material


Note: In the following problems, you may assume voltages and currents are RMS unless stated otherwise or given as a function of time. Transformers are ideal unless stated otherwise.

1. A load draws 12kVA at 0.8 pf, lagging when hooked to 480V. A capacitance is hooked in parallel with the load and the power factor is corrected to 0.9, lagging.


- Find the reactive power (VAR) of the capacitor. Draw a phasor diagram as part of the solution.
- Find the value of the capacitor assuming $f = 60\text{Hz}$.

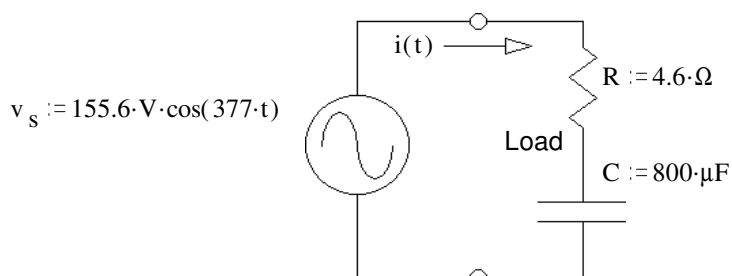2. Consider the circuit at right.
The resistor and capacitor together make up the load.

- Find the load impedance of the circuit.
- Compute the average power dissipated by the load.




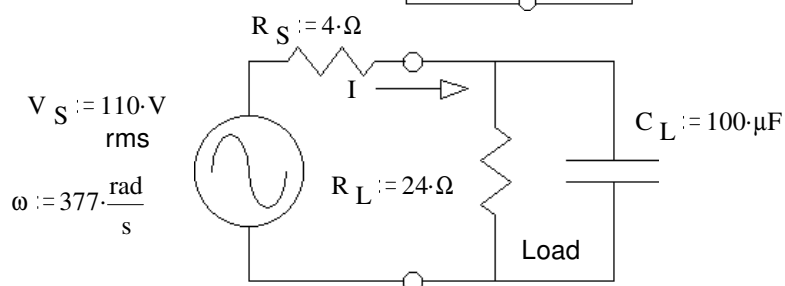- Compute the average power dissipated by the load (R_L and C_L taken together).
- Compute the power dissipated by the internal source resistance (R_S) in this circuit.



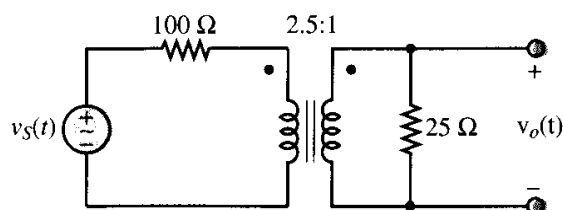4. Read section 6.3, p 301 in your textbook.


- An ideal transformer has 330 turns on the primary winding and 36 turns on the secondary. If the primary is connected across a 110 V (rms) generator, what is the rms output voltage?
- A transformer has $N_1 = 320$ turns and $N_2 = 1000$ turns. If the input voltage is $v(t) = (255 \text{ V})\cos(\omega t)$, what rms voltage is developed across the secondary coil?
- A step-up transformer is designed to have an output voltage of 2200 V (rms) when the primary is connected across a 240 V (rms) source.
 - If there are 150 turns on the primary winding, how many turns are required on the secondary?
 - If a load resistor across the secondary draws a current of 1.2 A, what is the current in the primary, assuming ideal conditions?
- The primary current of an ideal transformer is 8.5 A and the primary voltage is 80 V. 1.0 A is delivered to a load resistor connected to the secondary. Calculate the voltage across the secondary.
- An ideal transformer has a turns ratio ($N = N_1/N_2$) of 1.5. It is desired to operate a 200Ω resistive load at 150 V (rms).
 - Find the secondary and primary currents.
 - Find the source voltage (V_1).
 - Find the power dissipated in the load resistor and the power delivered to the primary from the source.
 - Find the impedance the source sees looking into the primary winding by calculating $Z_{eq} = N^2 Z_L$ and again by calculating V_1 / I_1 .
- For the ideal transformer shown in the figure, find $v_o(t)$ if $v_s(t)$ is $320\text{V}\cos(377t)$.



ECE 2210 Homework #21 p2


11. The transformer shown in the circuit below is ideal. It is rated at 120/30 V, 80 VA, 60 Hz
Find the following:

- a) $I_1 = ?$
b) $V_2 = ?$

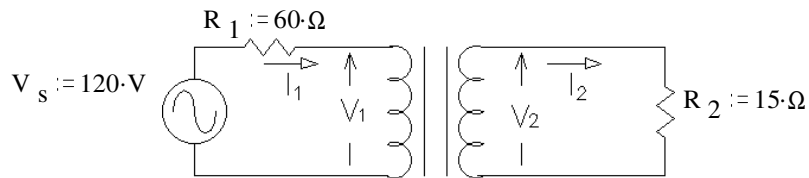

12. A transformer is rated at 13,800/480 V, 60 kVA, 60 Hz. (Note: kVA stands for kilo-Volt-Amp, in this case it is the transformer's voltage rating times its current rating.) Find the allowable primary and secondary currents at a supply voltage of 12,000 V at 100% power factor. Repeat for a power factor of 50%.
13. An ideal transformer has a rating of 500/125 V, 10 kVA, 60 Hz. It is loaded with an impedance of 5Ω at 80% pf (0.80). The source voltage applied to the primary winding is 440 V (rms). Find:
- the load voltage
 - the load current
 - the kVA delivered to load
 - the power delivered to load
 - the primary current
 - the power factor of primary
 - the impedance the source sees looking into primary.
14. An ideal transformer is rated to deliver 400 kVA at 460 V to a customer.
- How much current can the transformer supply to the customer?
 - If the customer's load is purely resistive (i.e. if the pf = 1), what is the maximum power the customer can receive?
 - If the customer's power factor is 0.8 (lagging), what is the maximum usable power the customer can receive?
 - What is the maximum power if the power factor is 0.7 (lagging)?
 - If the customer requires 300 kW to operate, what is the minimum allowable power factor given the rating of this transformer?

Answers

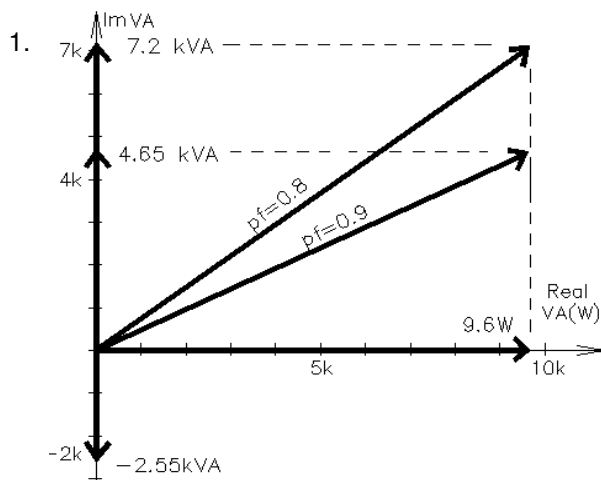

a) $-2.55 \cdot \text{kVA}$

b) $29.4 \cdot \mu\text{F}$

2. a) $Z := 5.67 \cdot \Omega \cdot e^{-j35.8 \cdot \text{deg}}$

b) $P_{av} := 1.73 \cdot \text{kW}$

3. a) $P_{av} := 364 \cdot \text{W}$

b) $110 \cdot \text{W}$

5. $12 \cdot \text{V}$

6. $563 \cdot \text{V}$

7. a) $1375 \cdot \text{turns}$

b) $11 \cdot \text{A}$

8. $680 \cdot \text{V}$

9. a) $0.75 \cdot \text{A}$, $0.50 \cdot \text{A}$ b) $225 \cdot \text{V}$ c) $112.5 \cdot \text{W}$ d) $450 \cdot \Omega$

10. $78\text{V}\cos(377t)$

11. a) $0.4 \cdot \text{A}$

b) 24V

12. $4.35 \cdot \text{A}$, $125 \cdot \text{A}$ any pf, (Using the transformer at a lower voltage does not increase its current rating.)

13. a) $110 \cdot \text{V}$ b) $22 \cdot \text{A}$ c) $2.42 \cdot \text{kVA}$ d) $1.94 \cdot \text{kW}$ e) $5.5 \cdot \text{A}$ f) 0.80 g) $80\Omega \angle 36.9^\circ \cdot \Omega$

14. a) $870 \cdot \text{A}$ b) $400 \cdot \text{kW}$ c) $320 \cdot \text{kW}$ d) $280 \cdot \text{kW}$ e) 0.75