
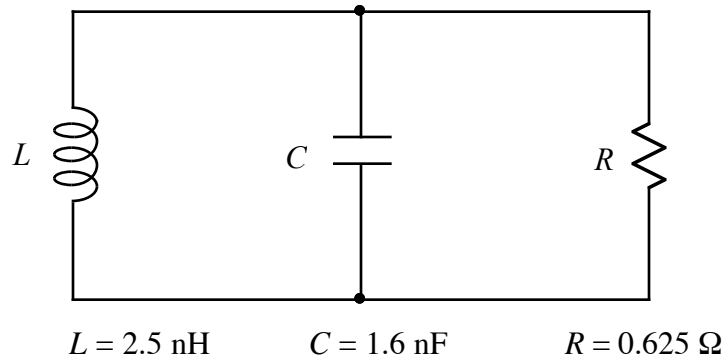


1.

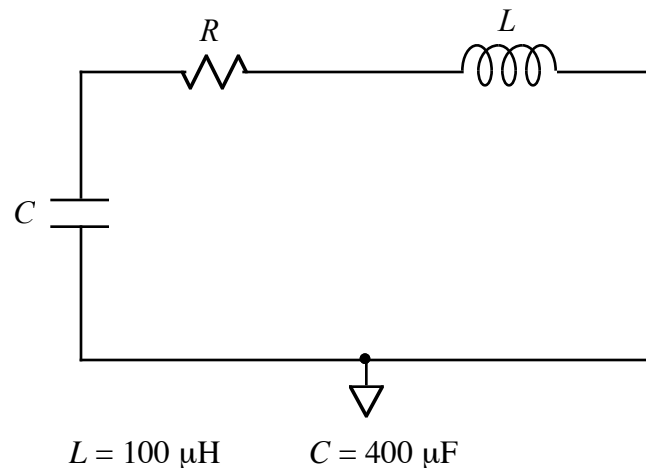

- a) Find the characteristic roots, s_1 and s_2 , for the above circuit.
- b) Is the circuit over-damped, critically-damped, or under-damped? Explain your answer.
- c) If the L and C values in the circuit are increased by a factor of 10, (and R remains the same), will the circuit be over-damped, critically-damped, or under-damped? Justify your answer with calculations.


2.



The above circuit may be used to generate a note for an electronic synthesizer.

- a) Find the value of R that will make the circuit oscillate at 440 Hz, (corresponding to an 'A' note). Remember to convert Hz to rad/s.
- b) Find the value of the damping factor, α , for your circuit.

3.

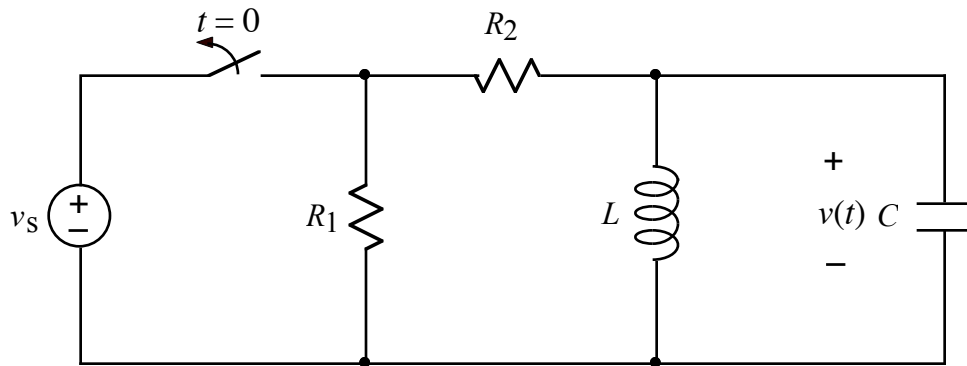


After being closed for a long time, the switch opens at $t = 0$.

$$L = 10 \text{ nH} \quad C = 250 \text{ nF} \quad R_1 = 0.1 \text{ } \Omega \quad R_2 = 0.025 \text{ } \Omega$$

If $v_s = 10 \text{ V}$, find $v(t)$ for $t > 0$.

4.

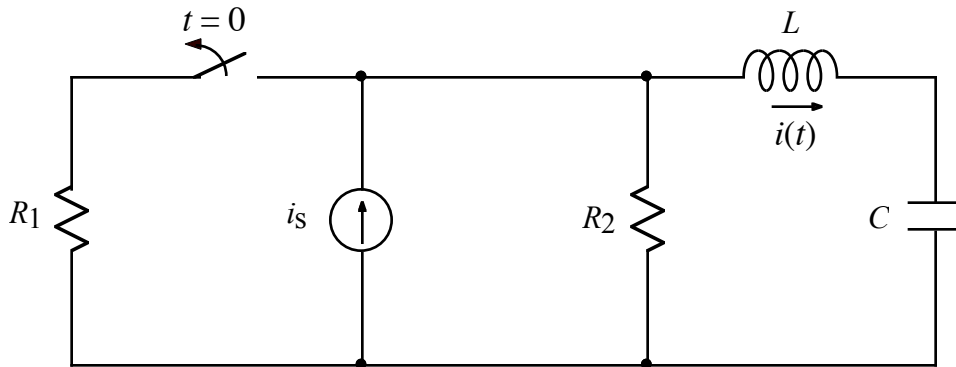


After being closed for a long time, the switch opens at $t = 0$.

$$L = 1 \text{ } \mu\text{H} \quad C = 16 \text{ } \mu\text{F} \quad R_1 = 0.15 \text{ } \Omega \quad R_2 = 0.1 \text{ } \Omega$$

If $i_s = 30 \text{ mA}$, find $i(t)$ for $t > 0$.

5.

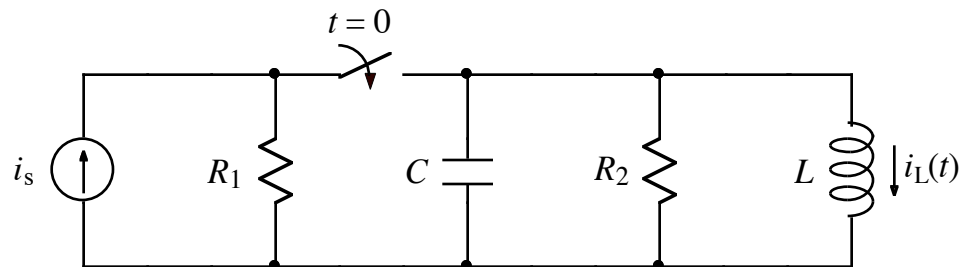

After being open for a long time, the switch closes at $t = 0$.

$$i_s = 4 \text{ mA} \quad C = 2 \text{ } \mu\text{F} \quad R_1 = 200 \text{ } \Omega \quad R_2 = 200 \text{ } \Omega$$

- If $L = 125 \text{ mH}$, find the characteristic roots, s_1 and s_2 , for the above circuit.
- If $L = 11.834 \text{ mH}$, find the damping frequency, ω_d .
- Find the value of L that makes the circuit critically-damped, and find $i_L(t)$ for that value of L .