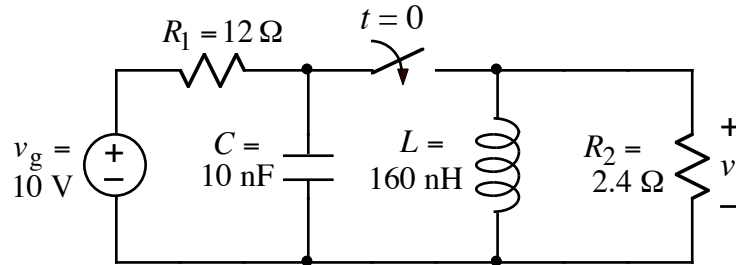


Ex:



After being open for a long time, the switch closes at $t = 0$.

- State whether $v(t)$ is under-damped, over-damped, or critically-damped.
- Write a numerical time-domain expression for $v(t)$, $t > 0$, the voltage across R_2 in problem 4. This expression must not contain any complex numbers.

SOL'N: a) After $t=0$, we have a parallel RLC with $R = R_1 \parallel R_2$. (We could use a Norton equivalent for v_g and R_1 to see that we have $R = R_1 \parallel R_2$.)

For parallel RLC, we have

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}, \quad \alpha = \frac{1}{2RC}, \quad \omega_0^2 = \frac{1}{LC}$$

$$\text{where } R = R_1 \parallel R_2 = 12\Omega \parallel 2.4\Omega$$

$$= 2.4\Omega \cdot 5 \parallel 1 = 2\Omega$$

$$\alpha = \frac{1}{2 \cdot 2\Omega \cdot 10\text{nF}} = \frac{1\text{G/s}}{40} = 25\text{ M r/s}$$

$$\omega_0^2 = \frac{1}{160\text{nH} \cdot 10\text{nF}} = \left(\frac{1\text{G}}{40}\right)^2 (\text{r/s})^2 = (25\text{ M})^2 (\text{r/s})^2$$

Since $\alpha^2 = \omega_0^2$, the circuit is critically-damped.


b) For critically-damped circuit, we use

$$v(t) = A_1 e^{-\alpha t} + A_2 t e^{-\alpha t} + A_3$$

where $\alpha = 25 \text{ M r/s}$

$$A_3 = v(t \rightarrow \infty).$$

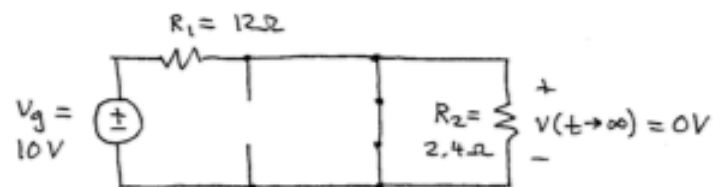$t \rightarrow \infty$ model: $L = \text{wire}$, $C = \text{open}$, switch closed



Since R_2 is shorted by L , we have

$$A_3 = v(t \rightarrow \infty) = 0V$$

Now we match the symbolic and circuit values of $v(0^+)$ and $\frac{dv}{dt} \Big|_{t=0^+}$.

$$\text{symbolic } v(0^+) = A_1 e^{-\alpha \cdot 0^+} + A_2 \cdot 0^+ \cdot e^{-\alpha \cdot 0^+}$$

or

$$v(0^+) = A_1$$

\uparrow makes 2nd term = 0

$$\text{symbolic } \frac{dv}{dt} \Big|_{t=0^+} = -\alpha A_1 e^{-\alpha t} + A_2 e^{-\alpha t} - \alpha A_2 t e^{-\alpha t} \Big|_{t=0^+}$$


or

$$\frac{dv}{dt} \Big|_{t=0^+} = -\alpha A_1 + A_2$$

For the circuit, we start with $t=0^-$, $L = \text{wire}$, $C = \text{open}$, switch open, and we find i_L and V_C .

We have two separate circuits at $t=0^-$:

$t=0^-$ model:

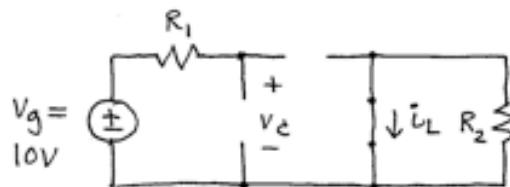


On the left, v_C charges to 10V.
(There is no current in R_1 , and no v -drop across R_1 .)

On the right, the current in L must be zero. (L discharges thru R_2 .)

$$v_C(0^-) = 10V \quad i_L(0^-) = 0A$$

$t=0^+$ model: Use sources for v_C and i_L
 $v_C(0^+) = v_C(0^-) = 10V$
 $i_L(0^+) = i_L(0^-) = 0A$ (open)

$R_1 = 12\Omega$ switch closed

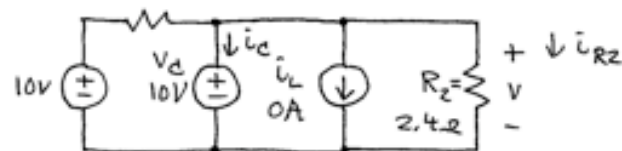

Since R_2 is across C , $v(0^+) = v_C(0^+) = 10V$

$$v(0^+) = A_1 = 10V$$

For $\left. \frac{dv}{dt} \right|_{t=0^+}$, we have $\frac{dv(t)}{dt} = \frac{dv_C}{dt} = \frac{i_C}{C}$
(v is across C).

So we want to find $i_C(0^+)$.

Using a current summation for the top node, we have

$$\frac{10V - 10V}{R_1} + i_C(0^+) + i_L(0^+) + \frac{10V}{R_2} = 0A$$

$\begin{matrix} \text{0A} & & \text{0A} \end{matrix}$

or

$$i_C(0^+) = -\frac{10V}{R_2} \quad (\text{Current flows up out of C and down thru } R_2)$$

$$\text{Thus } \left. \frac{dv}{dt} \right|_{0^+} = \frac{-10V}{R_2} = \frac{-10V}{2.4\Omega \cdot 10nF} = -\frac{1}{2.4} \text{GV/s}$$

$$= -\alpha A_1 + A_2 = -25 \text{M/s} \cdot 10V + A_2$$

$$\text{We have } A_2 = -\frac{1}{2.4} \text{GV/s} + 250 \text{MV/s}$$

$$A_2 \doteq -416.7 \text{M} + 250 \text{MV/s}$$

$$A_2 \doteq -166.7 \text{MV/s}$$

so

$$v(t) \doteq 10 e^{-25 \text{M}t} - 167 \text{M/s} \cdot t e^{-2 \text{M}t} \text{ V}$$