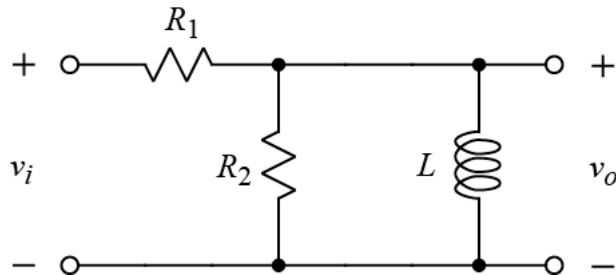


Ex:



$$R_1 = 1.5 \text{ k}\Omega \quad R_2 = 3 \text{ k}\Omega \quad L = 40 \text{ }\mu\text{H}$$

- Determine the transfer function V_o/V_i . **Hint:** use a Thevenin equivalent on the left side.
- Plot $|V_o/V_i|$ versus ω .
- Find the cutoff frequency, ω_c .


SOL'N: a) We use a Thevenin equivalent, as suggested in the problem, consisting of the input source, v_i , R_1 , and R_2 . The Thevenin voltage source is obtained by removing the L from the circuit and measuring the voltage across R_2 . This leaves a voltage divider:

$$v_{\text{Th}} = v_i \frac{R_2}{R_1 + R_2}$$

To find R_{Th} , we turn off the v_i source, which becomes a wire, and look in from the output terminals of the Thevenin circuit, (i.e., across R_2), and we see resistance $R_1 \parallel R_2$.

$$R_{\text{Th}} = R_1 \parallel R_2$$

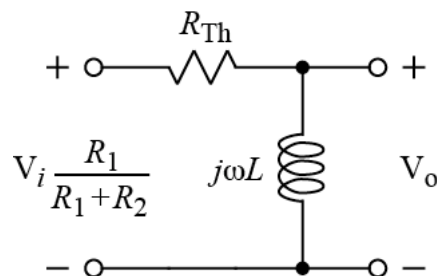Our new circuit, converted to the frequency domain, is shown below:



The voltage-divider formula gives the transfer function, starting with the formula for V_o :

$$V_o = V_i \frac{R_2}{R_1 + R_2} \frac{j\omega L}{R_{Th} + j\omega L}$$

Dividing by V_i gives the transfer function. (Note that we do *not* replace V_i with V_{Th} .)

$$H(j\omega) = \frac{V_o}{V_i} = \frac{R_2}{R_1 + R_2} \frac{j\omega L}{R_{Th} + j\omega L}$$

A better form is obtained by dividing top and bottom by $j\omega L$:


$$\begin{aligned} H(j\omega) &= \frac{R_2}{R_1 + R_2} \frac{1}{1 + \frac{R_{Th}}{j\omega L}} = \frac{R_2}{R_1 + R_2} \frac{1}{1 - j \frac{R_{Th}}{\omega L}} \\ &= \frac{R_2}{R_1 + R_2} \frac{1}{1 - j \frac{1k}{\omega 40\mu}} = \frac{R_2}{R_1 + R_2} \frac{1}{1 - j \frac{25M}{\omega}} \end{aligned}$$

b) The plot is generated with the following Matlab® code.

```
% ECE2260F10_HW3p3soln.m
% Plot of transfer function of RL high-pass filter.

R1 = 1.5e3; % Ohms
R2 = 3e3; % Ohms
R_Th = R1 * R2 / (R1 + R2); % Ohms
L = 40e-6; % Henry's

omega = 1e6:1e6:100e6;
H = R2/(R1 + R2) * 1 ./ (1 - j*R_Th ./ (omega*L));
plot(omega,abs(H))
xlabel('omega')
ylabel('|H|')
```

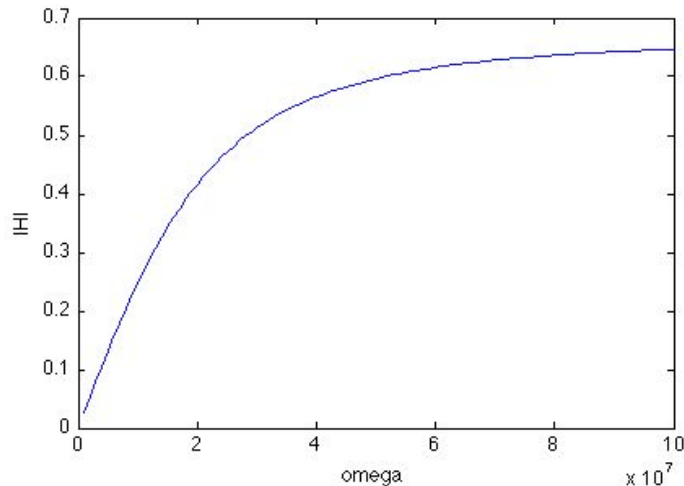

c) We find the cutoff frequency by setting the magnitude of the transfer function equal to $1/\sqrt{2}$ times the max value of $|H|$. Here the max value of $|H|$ will be $R_2/(R_1 + R_2) = 2/3$.

$$|H(j\omega_c)| = \frac{1}{\sqrt{2}} \max_{\omega} |H(j\omega)| = \frac{1}{\sqrt{2}} \left(\frac{2}{3} \right)$$

The factor of $2/3$, however, is also present in the magnitude of H , and we may cancel it out. This leaves us with the following equation:

$$|H(j\omega)| = \left| \frac{1}{1 + \frac{R_{Th}}{j\omega L}} \right| = \frac{1}{\sqrt{2}}$$

We observe that $\sqrt{2} = |1 \pm j|$ meaning we can solve for ω_c by setting $R_{Th}/\omega L$ equal to one:

$$\frac{R_{Th}}{\omega_c L} = 1$$

or

$$\omega_c = \frac{R_{Th}}{L} = \frac{1\text{k}}{40\mu} \text{r/s} = 25\text{Mr/s}$$