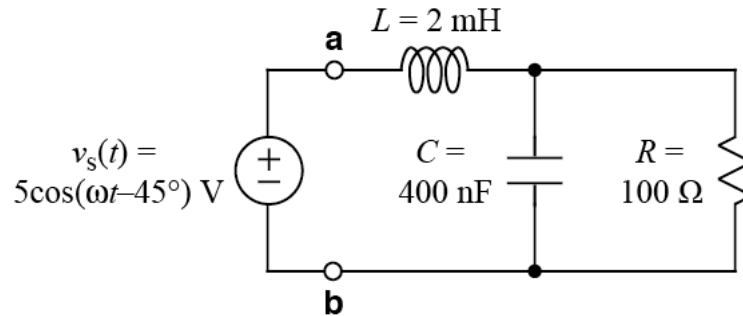


1.




Note: $\omega = 25 \text{ k r/s}$.

Do the following for the impedance to the right of the a, b terminals:


- Calculate complex power $S = P + jQ$.
- Calculate average (or DC) power.
- Calculate maximum instantaneous power.
- Sketch the power waveform, $p(t)$.

2.

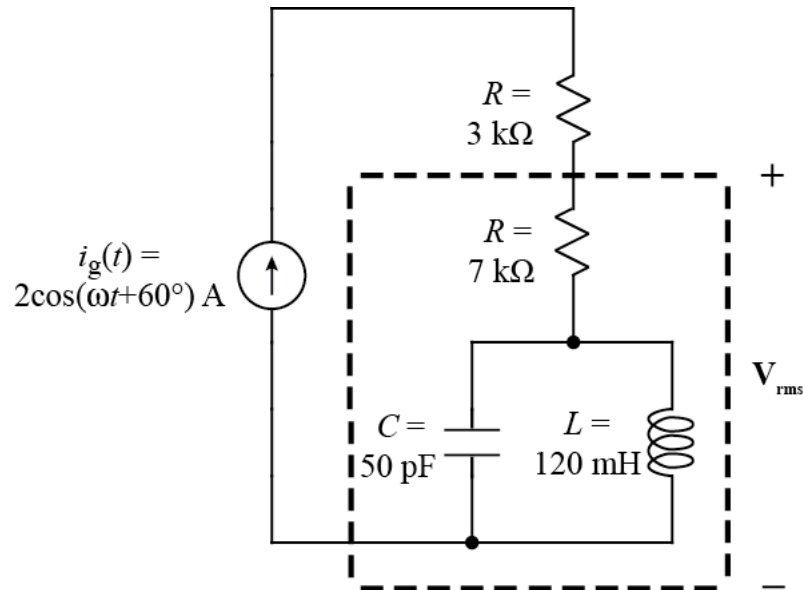

- Calculate V_{rms} . Note: $\omega = 1 \text{ Mr/s}$.
- Calculate the complex power, S , for the components inside the box.


3.

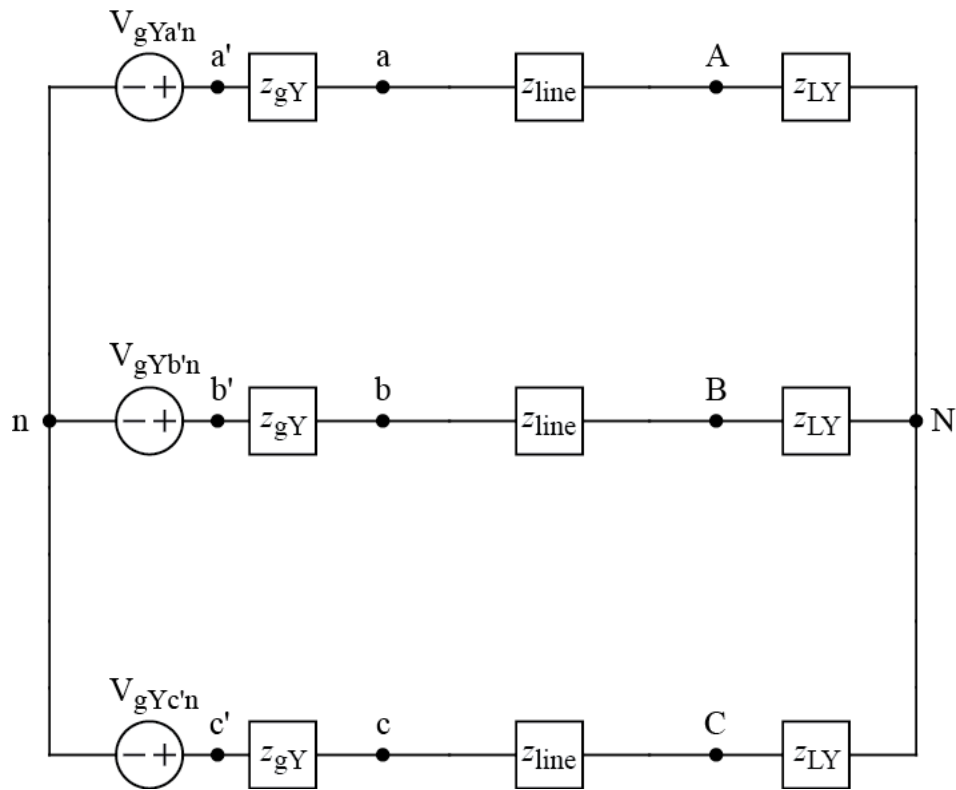

$$\begin{aligned}
 V_{gYa'n} &= 120\angle 0^\circ \text{ V} & z_{gY} &= j0.3 \ \Omega \\
 V_{gYb'n} &= 120\angle +120^\circ \text{ V} & z_{\text{line}} &= j0.6 \ \Omega \\
 V_{gYc'n} &= 120\angle -120^\circ \text{ V} & z_{LY} &= 3 - j0.1 \ \Omega
 \end{aligned}$$

- a) Draw the single-phase equivalent circuit.
- b) Calculate V_{aA} .

4.

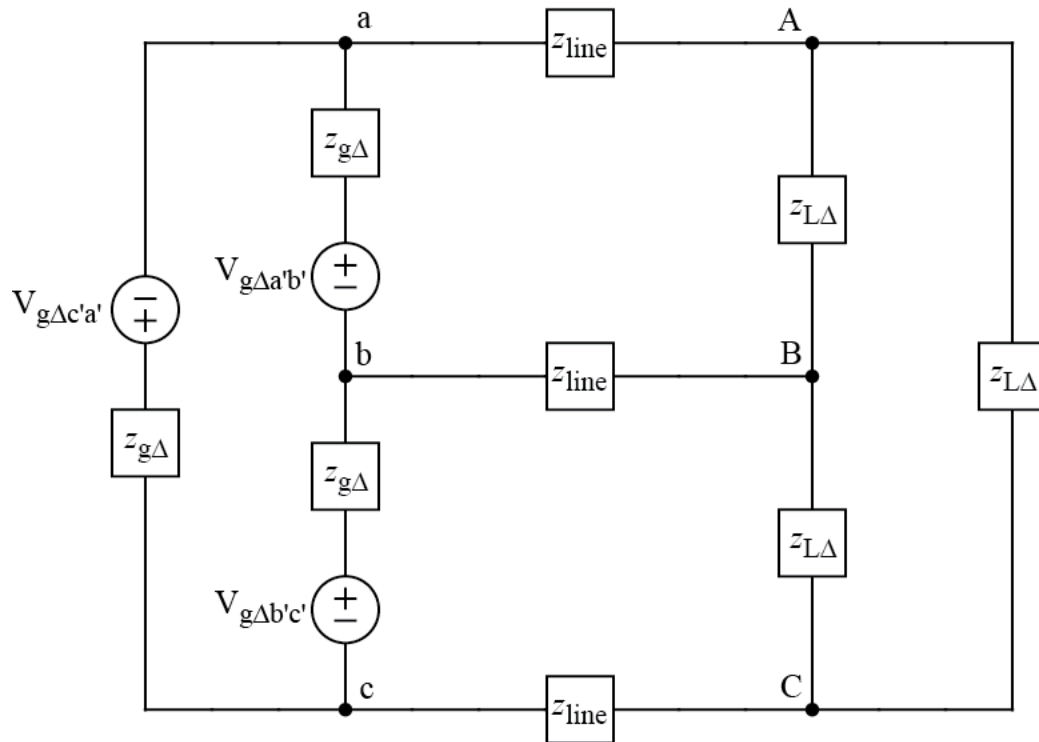

$$\begin{aligned}
 V_{g\Delta a'b'} &= 265\angle 0^\circ \text{ V} & z_{g\Delta} &= 8.3\Omega \text{ resistor in series with } 5/6\mu\text{F capacitor} \\
 V_{g\Delta b'c'} &= 265\angle -120^\circ \text{ V} & z_{\text{line}} &= 1\Omega \text{ resistor in series with } 700 \text{ nH inductor} \\
 V_{g\Delta c'a'} &= 265\angle +120^\circ \text{ V} & z_{L\Delta} &= 4\Omega \text{ resistor in series with } 10/9\mu\text{F capacitor}
 \end{aligned}$$

- a) Draw the single-phase equivalent circuit. Note: $\omega = 1 \text{ Mr/s}$.
 - b) Calculate \mathbf{I}_{bB} .
- 5.
- a) Calculate \mathbf{V}_{AB} .
 - b) Write a numerical time-domain expression for $v_{AB}(t)$.